

A fast LED driver prototype for HCAL calibration

**EUDET annual meeting at Ecole
Polytechnique, Palaiseau**

Proposal for calibration system

- New LED driver with reduced crosstalk
- A tunable calibration light in the range 0 to 100MIP
- Simplification of the optical system: one LED -> one side emitting fibre, one row of scintillator tiles
- PIN photo diode, do we need them?

LED driver strategy for SiPM calibration

- At AHCAL prototype (uses SiPM), we used CMB, calibration system with UV-LED 400nm driven by very fast rectangular pulses (1ns rise/fall time).
- Steep Rectangular waveform satisfied the needs to vary pulse-width, BUT creates lots of harmonics → electromagnetic **crosstalk!**
- We have found **fixed** pulse-width to about 6ns, we can go to use narrow band ->smooth waveform ≈ **less RF interference = Quasi Resonant LED driver (single pulse)**

Quasi-Resonant LED driver

LC circuit, heavily damped

- **Simulation**


- ~ 5ns puls width (slightly depends on the amplitude)
- 33nH PCB inductance, no ferromagnetic core

- **Prototyping**

- Used my lovely single side copper foil PCB
- We need more work on components optimization


Simulation at 1.5V amplitude

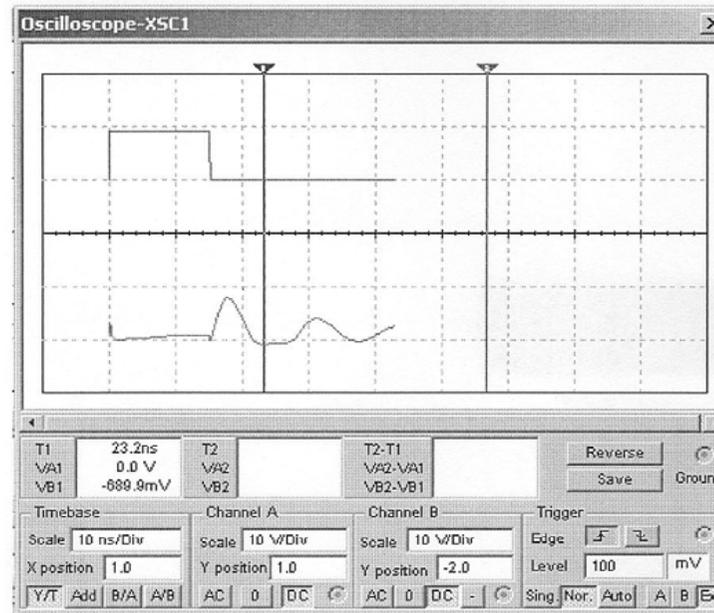- XSC1:
- Upper trace - sync pulse
- Lower trace – voltage at LED hot end




$$V_A = 1,5V$$

- XSC2: Lower trace LED current

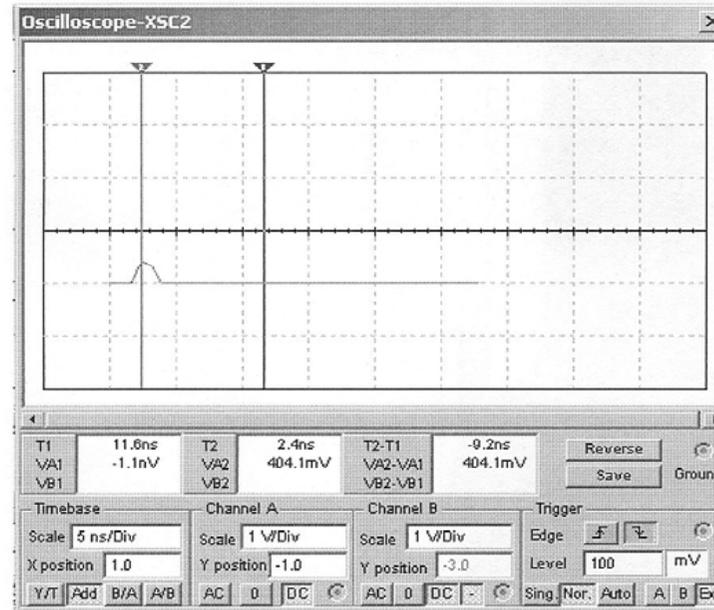


Simulation at 3V

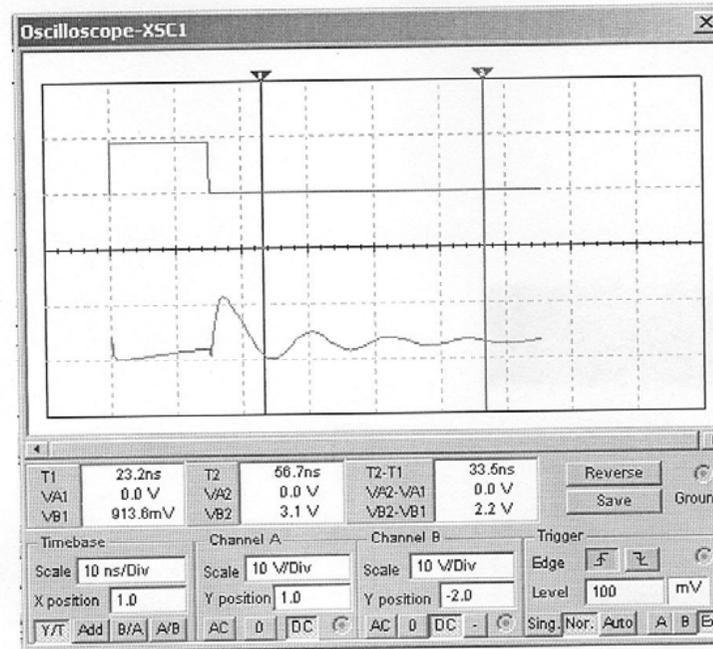- XSC1:
- Upper trace - sync pulse
- Lower trace – voltage at LED hot end




$$V_1 = 3V$$

- XSC2: Lower trace LED current

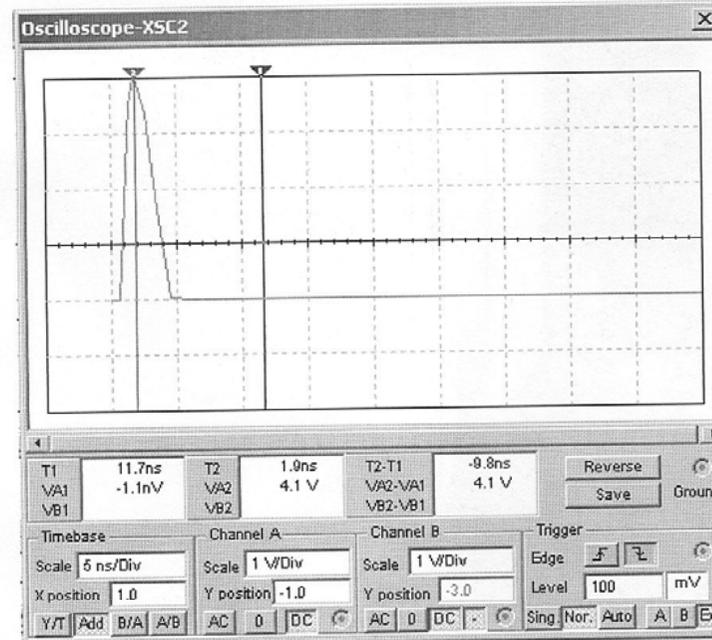

Prototype of QR LED driver

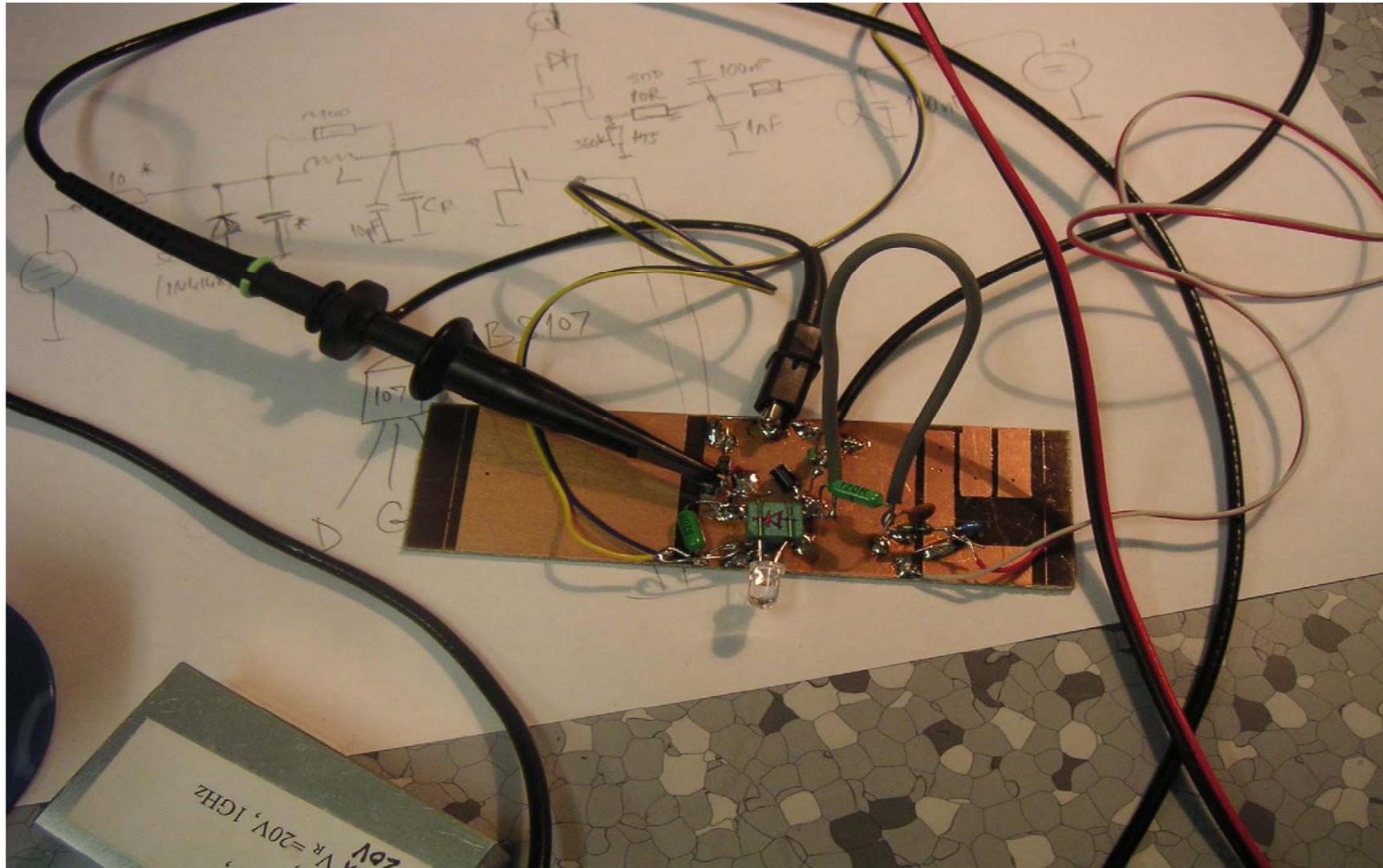


EUDET, OCT8 - 10,
2007


Ivo Polak, IoP Prague

8

LED current waveform (GRN) a=2

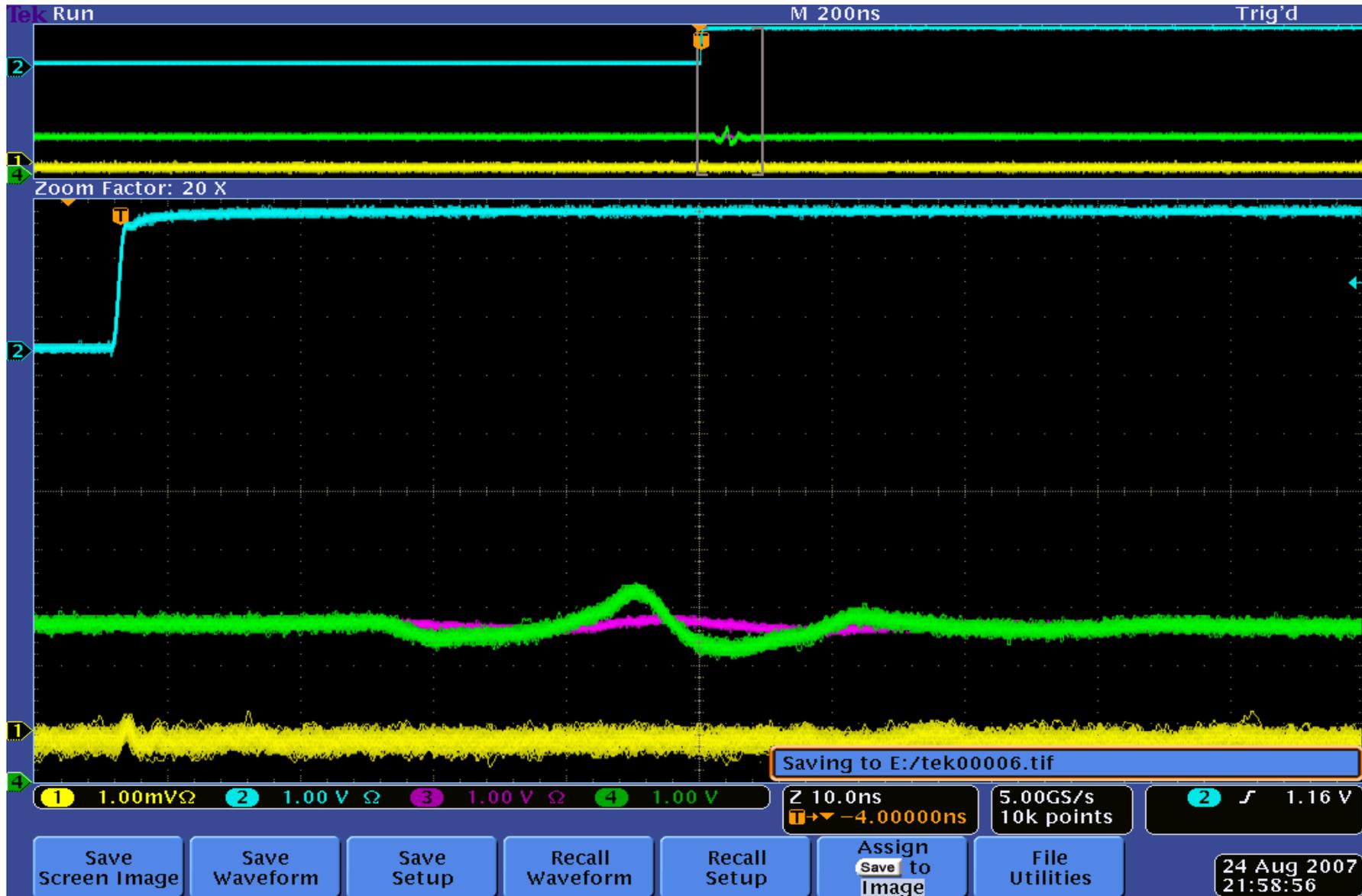

LED current waveform (GRN) a=1

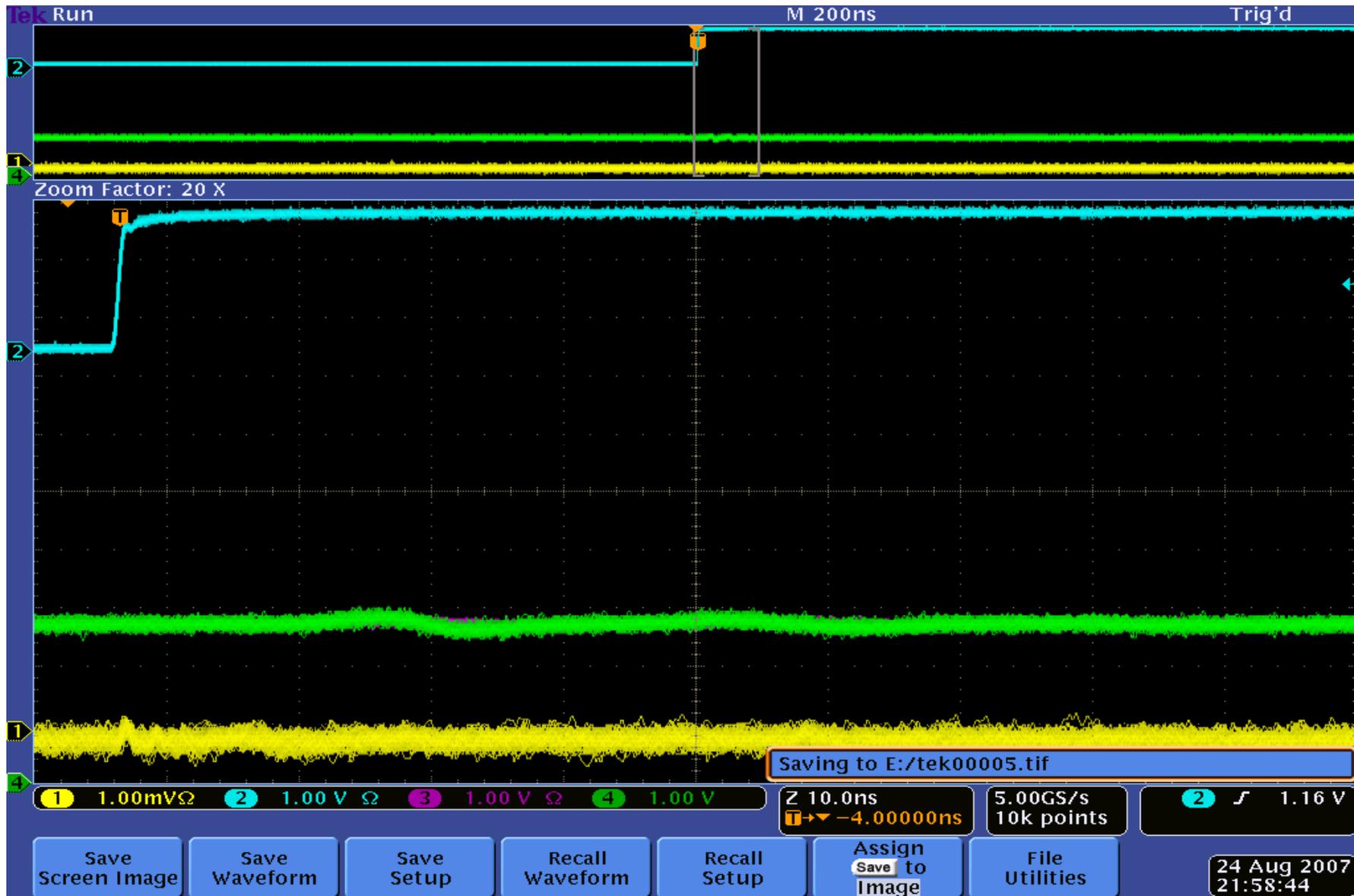


Last tests, more power on LED


- We see response of PIN photodiode at oscilloscope
- Amplitude up to 2mV_{peak} @ 50 Ω

Response to low amplitude

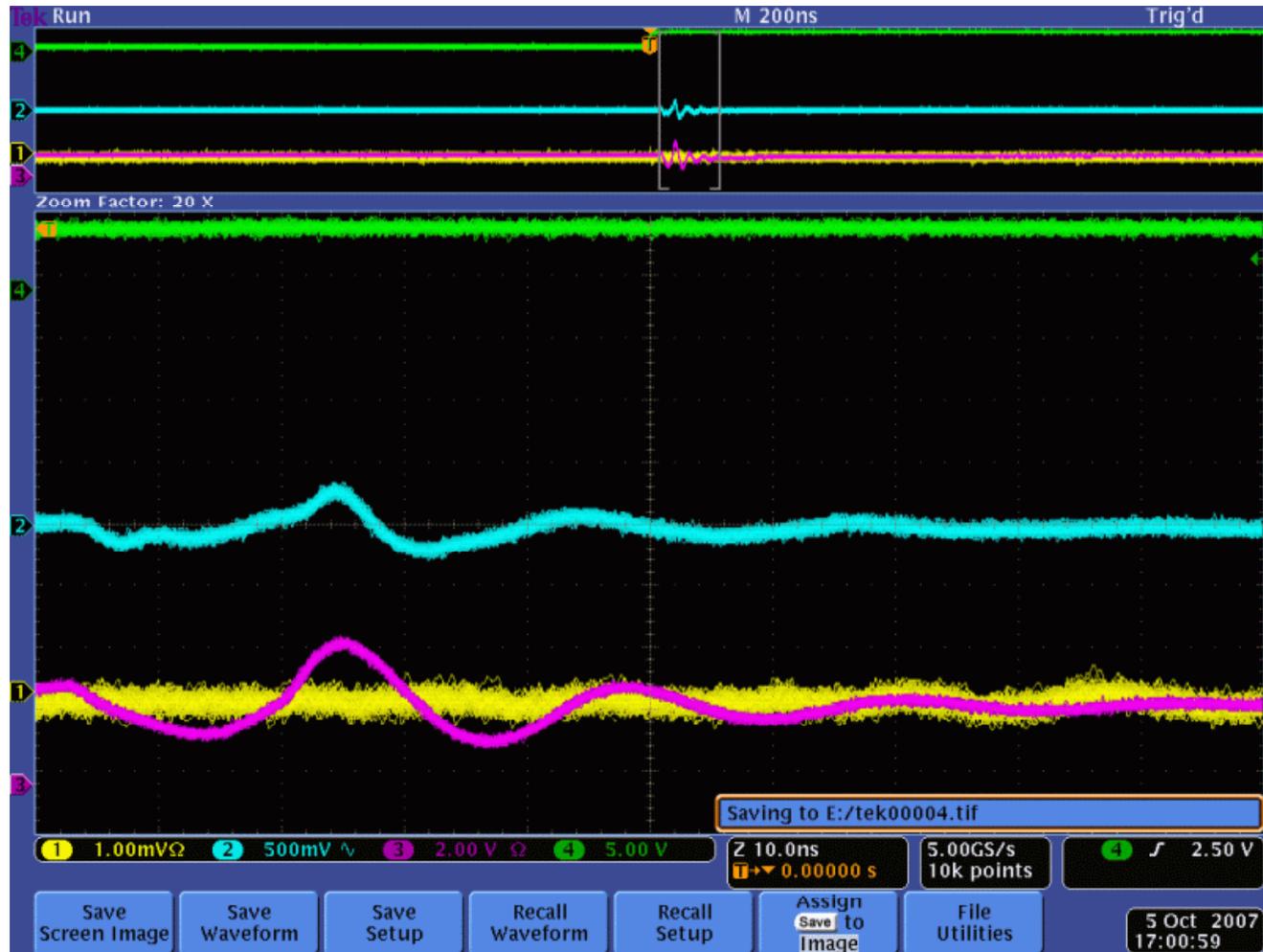- LED current (cyan)
(voltage @ 100hm)
- PIN response (yellow)
- LED anode (violet)




Response to middle amplitude

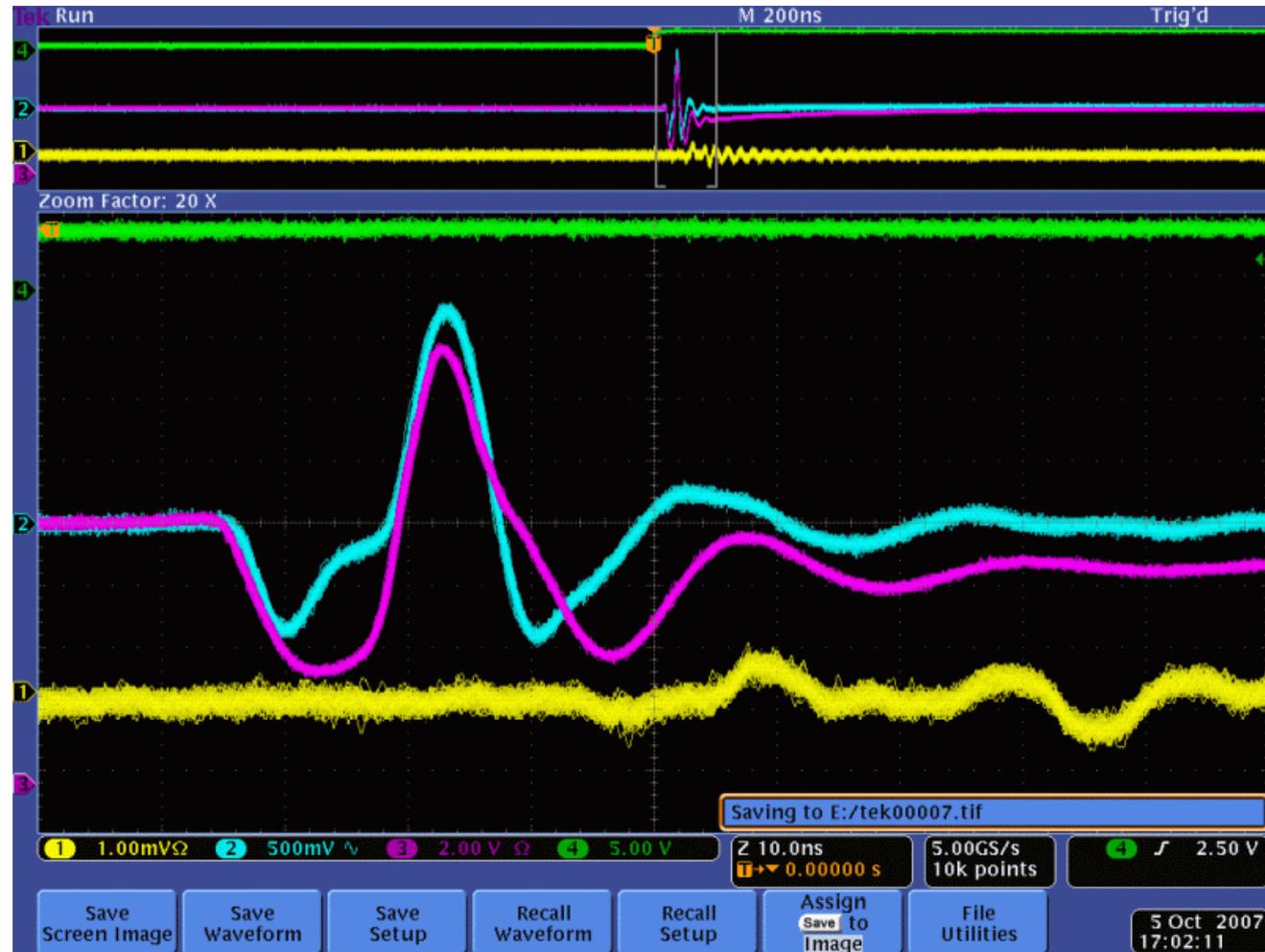


Response to high amplitude

- **200mA**
current at
LED

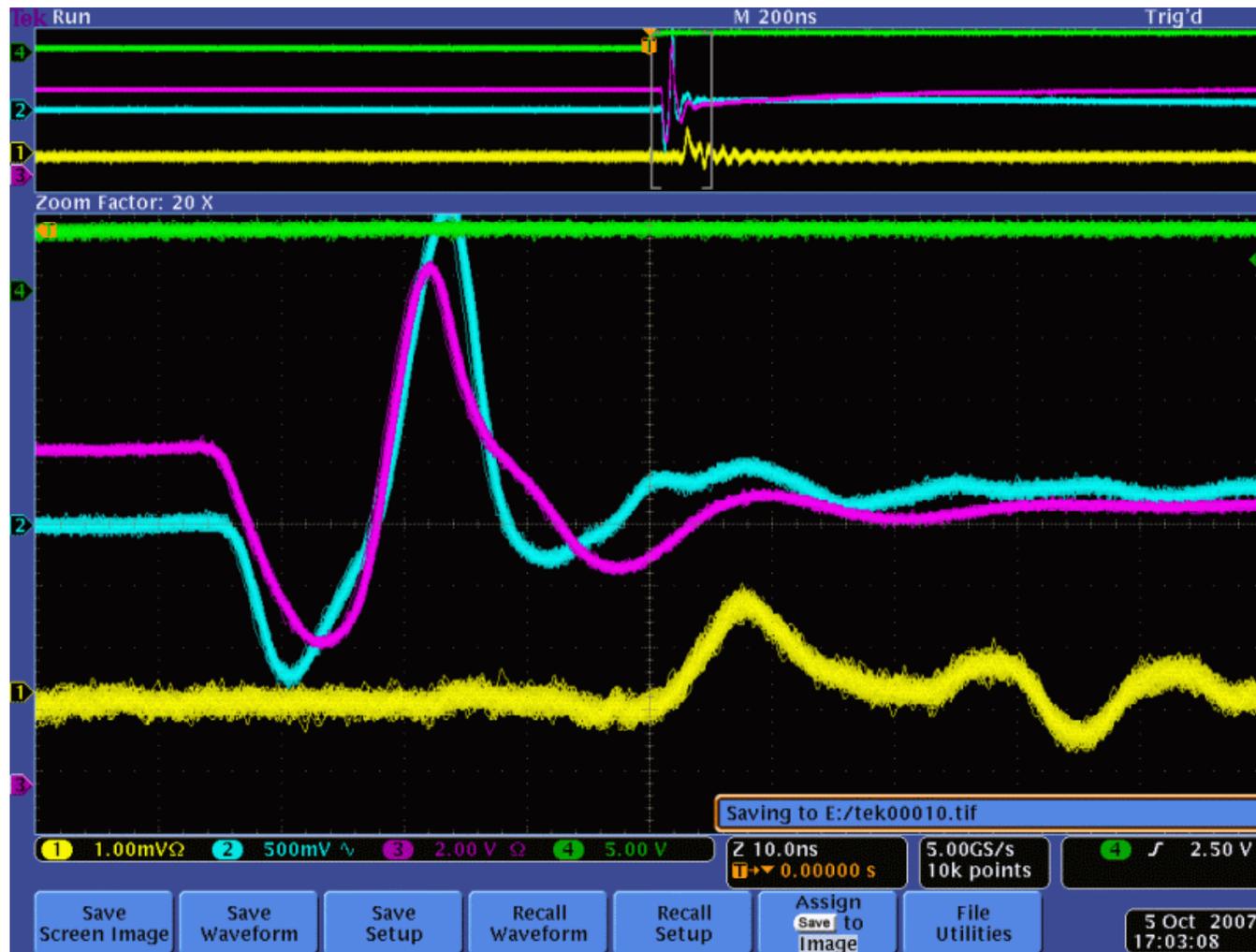

Response to high amplitude

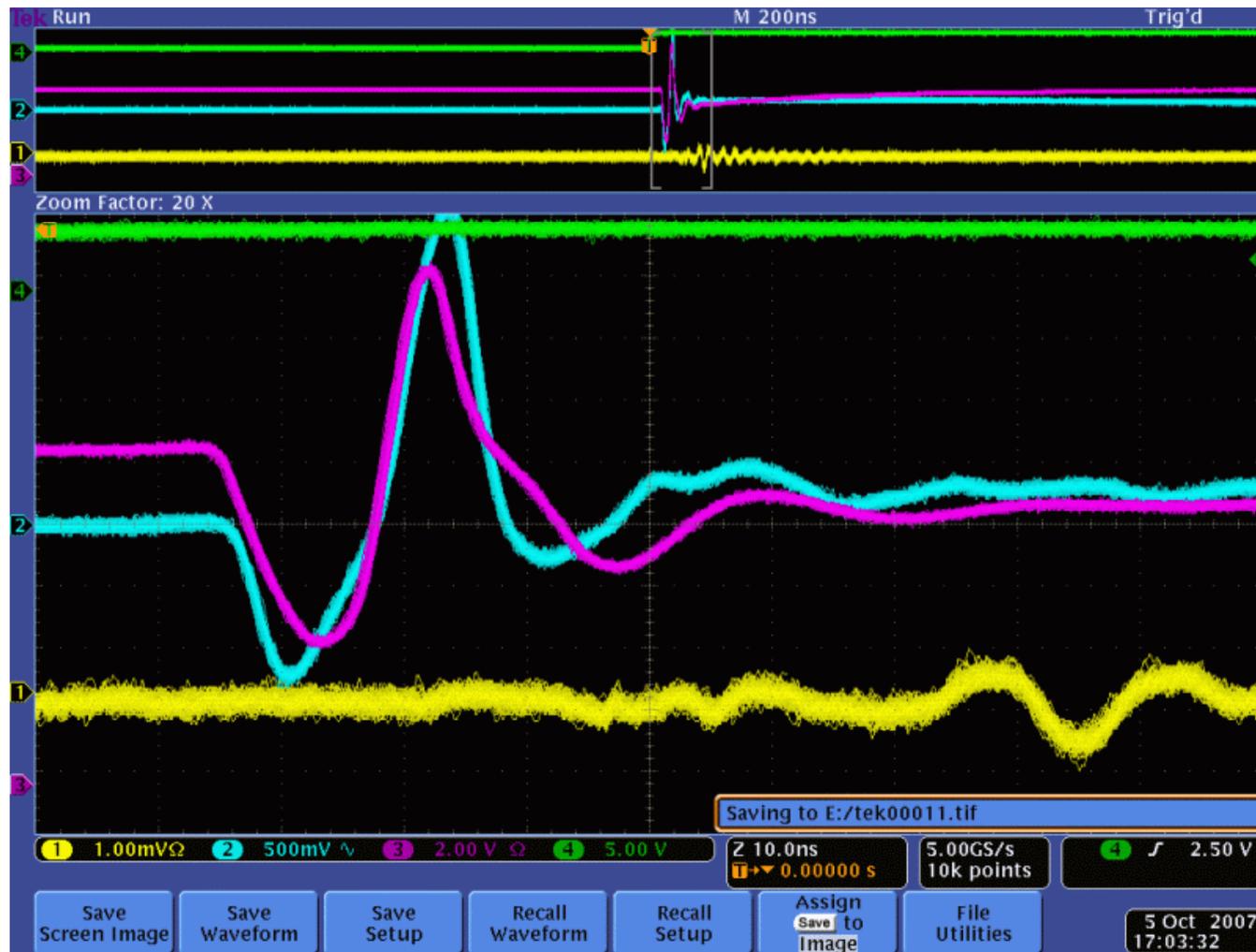- The Light from LED was optically blocked to PIN.



Conclusion

- QR LED driver is very promising technique to reduce Electro-Magnetic-Interferences
- PCB of the two-channel QR LED driver is being designed now
- End of October - PCB will be assembled – ready for tests
- November – summary report to EUDET
- November – measurements of light transfer in side-emitting fibres