

Electronics Developments for SITRA

Silicon strips readout using
Deep Sub-Micron Technologies

Jean-François Genat

on behalf of

A. Comerma-Montells³, W. Da Silva¹, J. David¹, M. Dhellot¹, D. Fougeron², D. Gascon³,
R. Hermel², J-F. Huppert¹, F. Kapusta¹, H. Lebbolo¹, T.H. Pham¹, F. Rossel¹, A. Savoy-Navarro¹,
R. Sefri¹, S. Vilalte²

¹ LPNHE Paris, ² LAPP Annecy, ³UEB Barcelona

Work in the framework of the SiLC (Silicon for the Linear Collider), R&D Collaboration
and the EUDET I3-FP6 European Project

**EUDET Annual meeting October 8-10th 2007 Ecole Polytechnique
Palaiseau, France**

Outline

- **Detector data** 2
- Technologies 5
- Front-End Electronics 7
- 4-channel 130nm chip 11
- 128-channel chip 30
- Conclusion 39

Silicon strips detector

Assume:

- A few 10^6 Silicon strips
- 10 - 60 cm long,
- Thickness 200–500 μm
- Strip pitch 50–200 μm
- Single sided, AC or DC coupled
- Strixels ?, 3D ?

Millions of channels:
Integration of k-scale channels readout chips

Silicon strips data at the ILC

- **Pulse height:** Cluster centroid to get a few μm position resolution
Detector pulse analog sampling
- **Time:** 150-300 ns for BC identification, **80ns sampling**
Shaping time of the order of the microsecond

Outline

- Detector data 2
- **Technologies** 5
- Front-End Electronics 7
- 130nm chip 11
- 128 channels chip 30
- Conclusion 39

Technologies

Silicon detector and VLSI technologies allow to improve detector and front-end electronics integration

Front-end chips:

- Thin CMOS processes 130, 90 nm available from Europractice (IMEC, Leuven)
- Chip thinning down to 50 μm

More channels on a chip, more functionalities, less power

Connectivity:

- On detector bump (stud)-bonding (flip-chip) 50-100 μm pads
- 3D interconnections even less...

**Smaller pitch detectors, better position and time resolution.
Less material**

Outline

- Detector data 2
- Technologies 5
- **Front-End Electronics 7**
- 130nm chips 11
- 128-channel chip 30
- Conclusion 39

Integrated functionalities

- Full readout chain integration in a single chip
 - Preamp-shaper
 - Trigger decision on analog sums : Sparse data scan
 - Sampling: Analog pipe-line
 - Analog event buffering: occupancy: 8-16 deep event buffer
 - On-chip digitization 10-bit ADC
 - Buffering and pre-processing:
Centroids, Least square fits, Lossless compression and error codes
 - Calibration and calibration management
 - Power switching (ILC duty cycle)
- Presently 128 channels in 130nm CMOS under design at LPNHE/LAPP/UEB having in view 512-1024 channels


Front-End Chip goals

- Integrate 512-1024 channels in 90nm CMOS:

- Amplifiers: - 30 mV/MIP over 30 MIP range
- Shapers: - Two ranges: 500ns-1 μ s, 1 μ s-3 μ s
- Sparsifier: - Threshold the sum of 3-5 adjacent channels
- Samplers: - 8 samples at 80ns sampling clock period
- Event buffer 8-16 deep
- Noise baseline:
Measured with 180nm CMOS:
375 + 10.5 e-/pF @ 3 μ s shaping, 210 μ W power
S/N = 20 @ 90cm long strips
- ADC: - 10 bits
- Buffering, digital pre-processing
- Calibration
- Power switching can save a factor up to 200

ILC timing: 1 ms: ~ 3-6000 trains @150-300ns / BC
199ms in between

Foreseen Front-end architecture

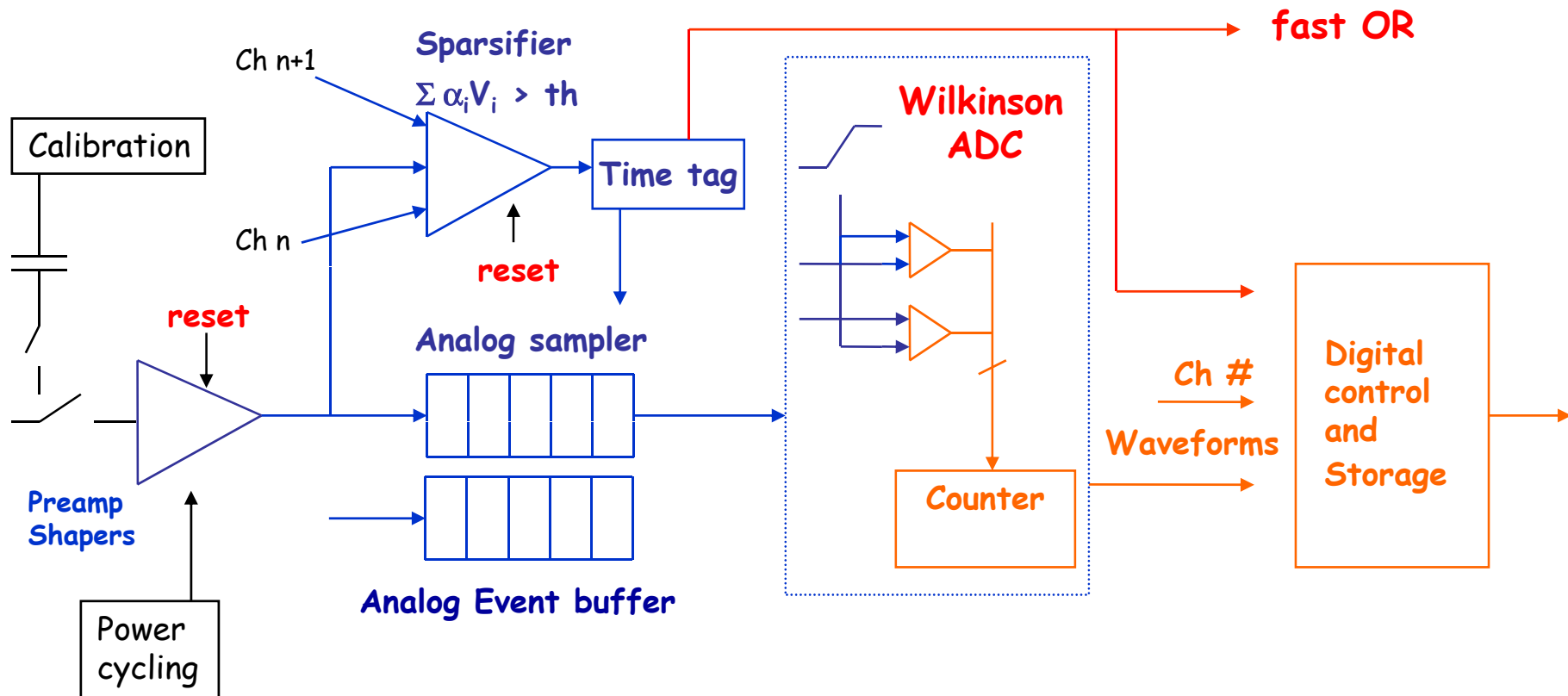

Charge 1-30 MIP, Time resolution: BC tagging 150-300ns
80ns analog pulse sampling

Technology: Deep Sub-Micron CMOS 130-90nm

Outline

- Detector data 2
- Technologies 5
- Front-End Electronics 7
- **130nm chips 11**
- 128 channels chip 30
- Conclusion 39

History

- 2004-2006 180nm chip: OK with radio-active source
- 2006-2007 130nm 4-channel: Beam tests this week at CERN
- 2007 130nm 1-channel: Improved analog pipe-line, calibration
- 2007-2008 130nm 128 channels: True mixed design
All analog blocks validated
Digital under design.
- 2009 k-channels chip

Front-end in 130nm

130nm CMOS:

- Smaller
- Faster
- Less power
- Will be (is) dominant in industry
- (More radiation tolerant)


Drawbacks:

- Reduced voltage swing (Electric field constant)
- Noise slightly increased (1/f)
- Leaks (gate/subthreshold channel)
- Design rules more constraining
- Models more complex, not always up to date

Millions of channels:
Integration of k-scale channels readout chips

UMC CMOS Technology parameters

	180 nm	130nm
• 3.3V transistors	yes	yes
• Logic supply	1.8V	1.2V
• Metals layers	6 Al	8 Cu
• MIM capacitors	1fF/mm ²	1.5 fF/mm ²
• Transistors	Three Vt options	Low leakage option

 

May be used for analog storage during ~ 1 ms

2006-7 Chips

Both under test

130nm CMOS


Chip -1 4 channels

- Preamp-shapers + Sparsifier
- Pipeline 1
- ADC
- Digital

Chip -2 One channel

- Preamp-shapers + Sparsifier
- DC servo
- Pipeline 2 (improved)
- DAC
- Test structures: MOSFETS, passive


4-channel Chip

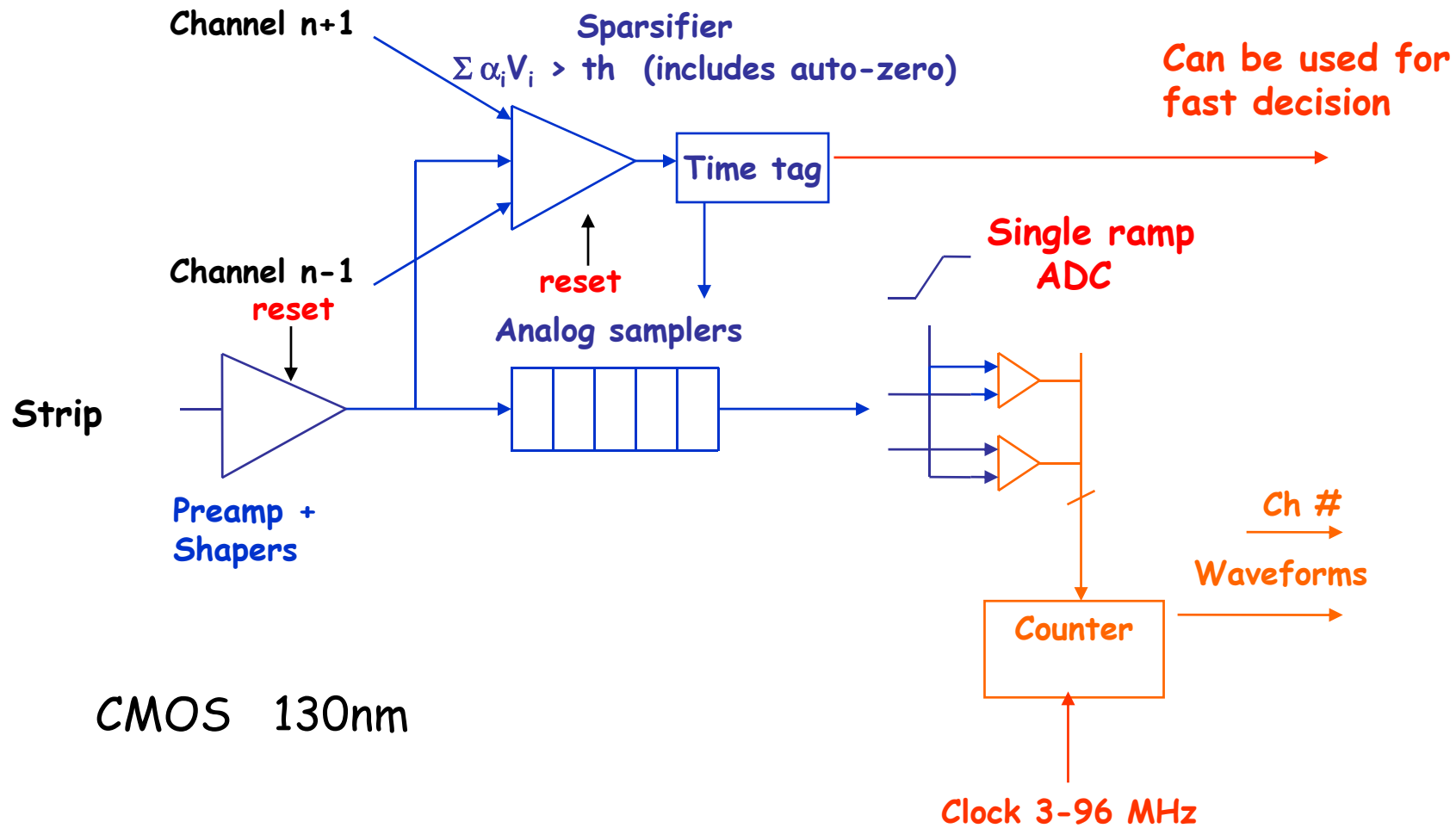


4-channel 130nm Silicon



180nm 130nm

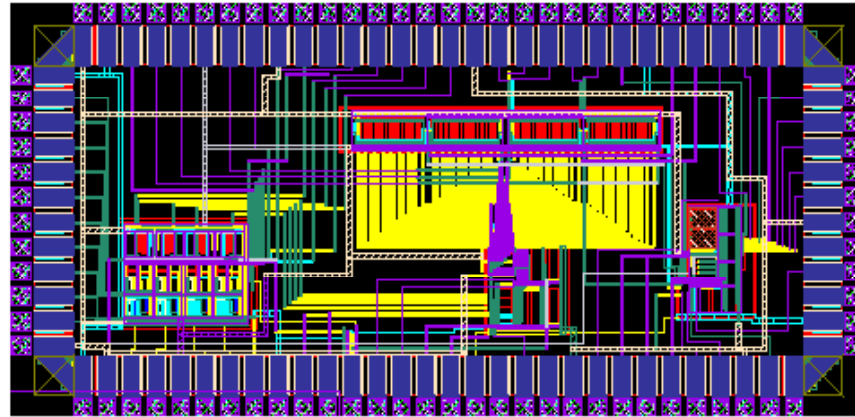

 Layout of the 130nm chip including sampling and A/D conversion




Picture

4-channel chip layout

Amplifier, Shaper, Sparsifier 90*350 μm^2

Analog sampler 250*100 μm^2

 




A/D 90*200 μm^2

Layout of the 130nm chip including sampling and A/D conversion

Results

Measured gain - linearities

Preamp output

   

Preamp and Shaper:


Shaper output

Gain = 29mV/MIP
 Dynamic range = 20MIPs 1%
 30 MIPs 5%

Peaking time = 0.8-2.5µs / 0.5-3µs expected

130nm vs 180nm chip noise results


 
Gain OK: 29 mV/MIP OK
 Dynamics: 30 MIPS @ 5%, 20 MIPS 1% OK
 Peaking time: 0.8 - 2.5 μ s (0.7 - 3 μ s targeted)



Power (Preamp+ Shaper) = 245 μ W

Noise:	130nm @ 0.8 μ s :	850 + 14	e-/pF	245 μ W	(150+95)
	130nm @ 2 μ s :	625 + 9	e-/pF		
	[180nm @ 3 μ s :	375 + 10.5	e-/pF	210 μ W	(70+140)]

Digitized analog pipeline output

  

Simulation of the analog pipeline (analog)

Measured output of the ADC (pulser)

Waveform distorted due to 1pF parasitic capacitance of the output pad connected for analog diagnostics on 2 out of four channels


Traces cut using IFB to get all shaper channels operational to ADC for beam tests

Chip 2 includes a voltage buffer between shaper and ADC


Digitized analog pipeline output

Laser response of detector + 130nm chip

Digitized shaper output

 


From pulser

 


From Laser diode + Silicon detector

ADC evaluation

 

Noise= 4 LSBs

10 bits OK

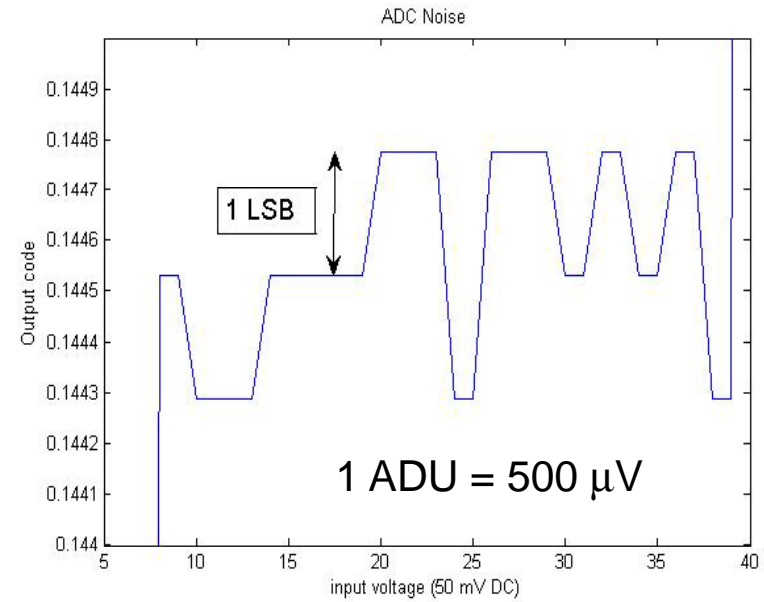

130-1 chip's tests to come

- Lab tests: Measure ADC extensively

- Linearities Integral, differential
- Noise Fixed pattern, random
- Speed Maximum clock rate
- Accuracy Effective number of bits

- Beam tests at CERN next week

130 nm-2

LAPP Annecy le Vieux R. Hermel, D. Fougeron
LPNHE Paris T-H. Pham, R. Sefri

One channel test version in 130nm including:

- Preamp + shaper
- Improved pipeline (output buffer)
- Calibration channel (calibration caps)
- Calibration DAC

Presently under test at LAPP Annecy:

If OK, all analog blocks will be validated for a multi-channel version in 130nm aiming to read a full detector in 2008

130-2 tests under work (LAPP Annecy)

Measure improved pipeline extensively

Denis Fougeron's (LAPP Annecy) design

- Linearities
Integral, differential
- Noise
Pedestal fixed pattern, random noise
Maximum clock rate
- Droop
Hold data for 1 ms at the ILC
- ADC Driving

Some issues with 130nm design

- Noise likely modeled pessimistic, but measured quite acceptable
90nm could be less noisy (Manghisoni, Perugia 2006)
- Lower power supplies voltages reducing dynamic range
- Design rules more constraining
- Some (via densities) not available under Cadence
Calibre (Mentor) required.
- Low Vt transistors leaky (Low leakage option available at regular Vt)



Manageable, UMC design kits user friendly,
Europractice very helpful.

130-90nm noise evaluation (STM process)



Noise and inversion region

Manghisoni et al FE2006 Perugia

  

- At low drain current both devices work in the weak inversion region → channel thermal noise is roughly the same for both devices
- At high drain current, a significant difference in the channel thermal noise can be detected ← device from the 90 nm technology works closer to weak inversion region
- Better 1/f noise performance provided by the STM 90 nm technology

Outline

- Detector data 2
- Technologies 5
- Front-End Electronics 7
- 130nm chips 11
- 128-channel chip 29
- Conclusion 38

128-channel chip

Goal: Equip a full detector

- Experience from lab test bench + laser/source and 2007 beam-tests
- Full 128-channels with :
 - Preamp-shapers
 - Sparsifier
 - Pipeline (8-sampling + 8-deep event buffer)
 - 12bits ADC
 - Digital
 - Calibration
 - Power cycling

128-channel chip

Improvements wrt chip 130-1:

- Increase order of the shaper to 3 should reduce noise by 20-30% at a moderate increase in DC power.
- Pipeline (8-sampling + 8-deep event buffer) includes a buffer to drive the ADC.
- Full digital control
- Full calibration and channel disable
- Power cycling

128-channel chip

Paris, September 27-28th 2007 A. Comerma (Barcelone), Thanh Hung Pham, JFG
 Tentative specs for a Silicon strips 128-channel readout chip

I/O

Preamp

128	Inputs				128
128	Outputs				
1	Bias_preamp	Control DAC	6 bits		
1	V_ref	“	“		1
1	Bias_buf “	“	“		1

Shaper

	Inputs				
128	Outputs				
1	Bias_shaper	“	“		1
2	V_pole, v_zero	“	“		1


Sparsifier

3 x 128	Inputs				
128	Outputs				
1	Auto-zero control				
1	Bias_sum_1	“	“		1
1	Bias_sum_2	“	“		1
1	Bias_comp	“	“		1
1	Threshold	“	“		1
128	Outputs				

4 more pages...

Chip splits in 14 functional blocks

128-channel chip

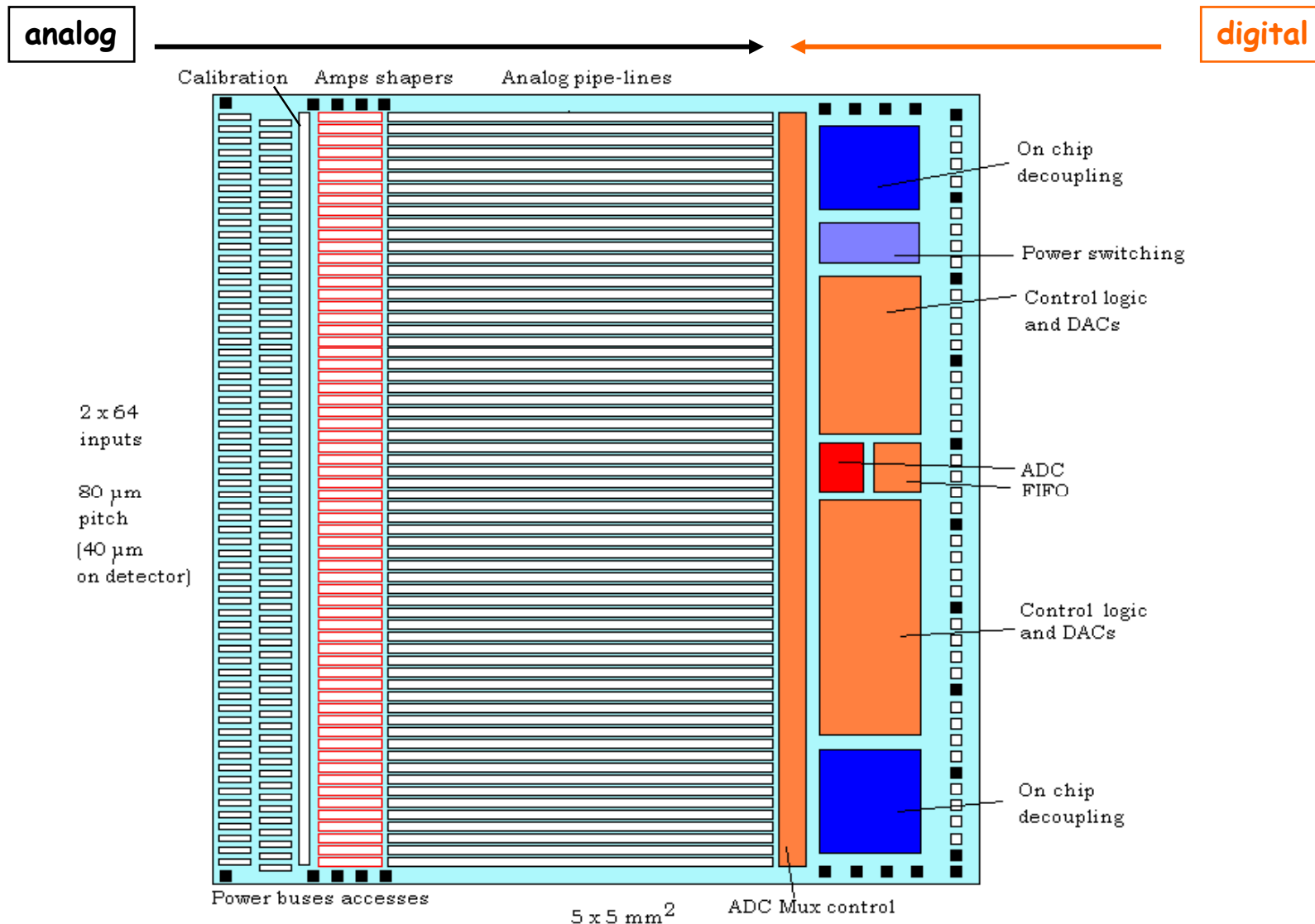

Tentative floor-planning

128 channel chip
 UMC CMOS 130nm Mixed-mode process

Connexion to detector and external

Layout allows :

- Wire-bonding
- Stud-bonding
- Bump-bonding
- Even 3D interconnect...


Planned Digital Front-End

- Chip control
- Buffer memory
- Processing for
 - Calibrations
 - Amplitude and time least squares estimation, centroids
 - Raw data lossless compression
- Tools
 - Cadence DSM Place and Route tool
 - Digital libraries in 130nm CMOS available
 - Synthesis from VHDL/Verilog
 - SRAM
 - Some IPs: PLLs

Need for a mixed-mode simulator

Power cycling

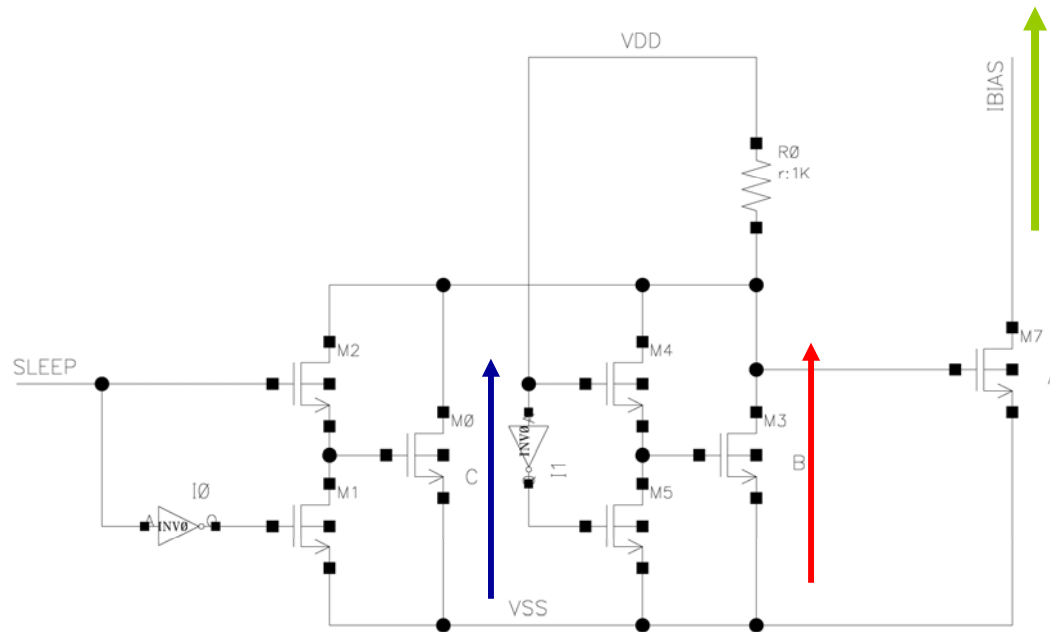Switch the current sources between zero and a small fraction (10^{-2} to 10^{-3}) of their nominal values



This option switches the current source feeding both the preamplifier & shaper between 2 values:


Zero or a *small fraction* (0.1% - 1%) of biasing current is held during « power off ».

Zero-power option tested on 180nm chip (slow, but works)

Schedule

- Nov '07 - Complete 130-1 and -2 chips tests
- December '07 - Complete analog and digital blocks
- January '07 - Merge
- February '08 - Submission, test bench development
- Card development for TPC+Silicon tests
- May '08 - Tests: lab
- July '08 - Connexion to HPK detectors
- Tests with HPK detectors: laser, source
- Beam tests.
- September '08 - OK

Shaper output noise

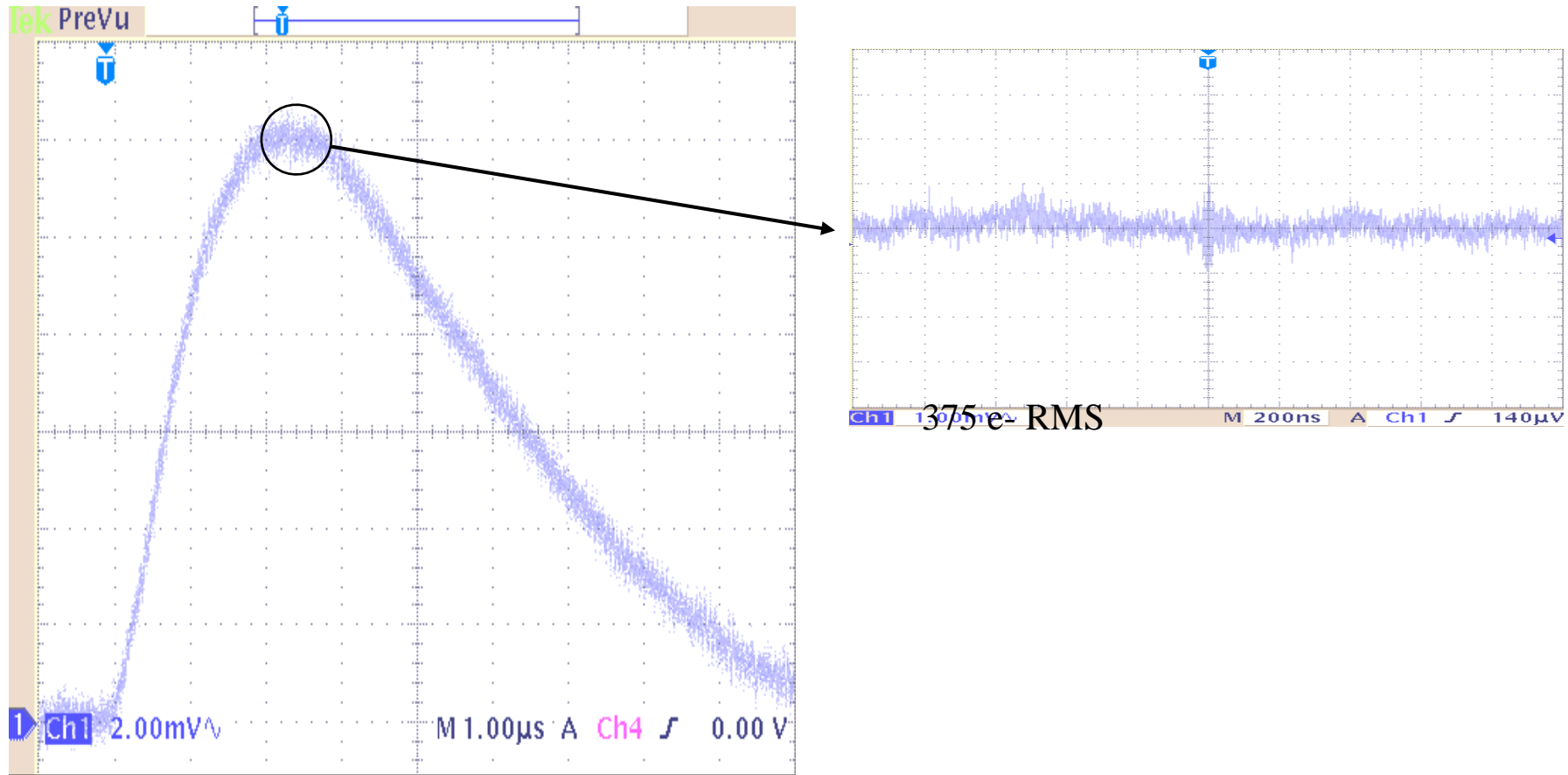

375 e- +10.4 e-/pF input noise with chip-on-board wiring
275 + 8.9/pF simulated

Tests Conclusions

12 chips tested ('05)

The UMC CMOS 180nm process is mature and reliable:

- Models mainly OK
- Only one transistor failure over 12 chips
- Process spreads of a few %

Beam tests in October '06 at DESY

Encouraging results regarding CMOS DSM

—————→ go to 130nm

Conclusion


These CMOS 130 designs and first test results demonstrate the feasibility of a highly integrated front-end for Silicon strips (or large pixels) with

- DC power under $500\mu\text{W}/\text{ch}$
- Silicon area under $50 \times 1000 \mu^2/\text{ch}$

The End ..41

Backup

Process spreads

 


Preamp gains statistics

Process spreads within a wafer: 3.3 %

43

Shaper output noise

 

375 e- +10.4 e-/pF input noise with chip-on-board wiring
275 + 8.9/pF simulated

Tests Conclusions

12 chips tested ('05)

The UMC CMOS 180nm process is mature and reliable:

- Models mainly OK
- Only one transistor failure over 12 chips
- Process spreads of a few %


Beam tests in October '06 at DESY

Encouraging results regarding CMOS DSM

—————→ go to 130nm

Possible issues: noise: 130nm vs 180nm (simulation)

PMOS

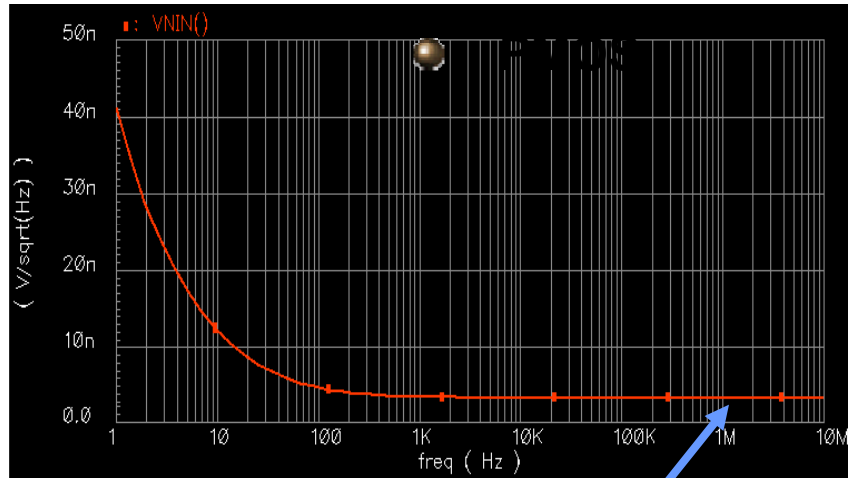


180nm

$g_m = 944.4 \mu S$

$1 \text{ MHz} \rightarrow 3.508 \text{ nV}/\sqrt{\text{Hz}}$

 Thermal noise hand calculation = $3.42 \text{ nV}/\sqrt{\text{Hz}}$



130nm

$g_m = 815.245 \mu S$

$1 \text{ MHz} \rightarrow 7.16 \text{ nV}/\sqrt{\text{Hz}}$

Thermal noise hand calculation = $3.68 \text{ nV}/\sqrt{\text{Hz}}$

Thermal noise measured by Wladimir Gromov (NIKHEF) with IBM130nm OK

46

Transistors leaks

- Gate-channel due to tunnel effect
- Through channel when transistor switched-off


 


Figure 1.2 I_{gate} and subthreshold leakage versus technology.

Wiring Detector to FE Chips

~~Wire bonding~~


Flip Chip Technology

 

Courtesy: Marty Breidenbach (Cal SiD)

OR (later)

Noise summary (180nm)

 

3D Wiring

Process flow for 3D Chip

- 3 tier chip (tier 1 may be CMOS)
 - 0.18 um (all layers)
 - SOI simplifies via formation
- Single vendor processing

1) Fabricate individual tiers



May 2006

FEE 2006


2) Invert, align, and bond wafer 2 to wafer 1



3) Remove handle silicon from wafer 2, etch 3D Vias, deposit and CMP tungsten



 4) Invert, align and bond wafer 3 to wafer 2/1 assembly, remove wafer 3 handle wafer, form 3D vias from tier 2 to tier 3





36

Courtesy: Ray Yarema, FEE 2006, Perugia

Chip connection

- Wire bonding
 - Only periphery of chip available for IO connections
 - Mechanical bonding of one pin at a time (sequential)
 - Cooling from back of chip
 - High inductance ($\sim 1\text{nH}$)
 - Mechanical breakage risk (i.e. CMS, CDF)
- Flip-chip
 - Whole chip area available for IO connections
 - Automatic alignment
 - One step process (parallel)
 - Cooling via balls (front) and back if required
 - Thermal matching between chip and substrate required
 - Low inductance ($\sim 0.1\text{nH}$)

  

Manuel Lozano (CNM Barcelona)



Bump bonding flip chip technology

- Electrical connection of chip to substrate or chip to chip face to face

flip chip

- Use of small metal bumps

bump bonding

  

- Process steps:
 - Pad metal conditioning:
Under Bump Metallisation (UBM)
 - Bump growing in one or two of the elements
 - Flip chip and alignment
 - Reflow
 - Optionally underfilling

52


Manuel Lozano (CNM Barcelona)

Bump bonding flip chip technology


- Expensive technology
 - Especially for small quantities (as in HEP)
 - Big overhead of NRE costs
- Minimal pitch reported: 18 μm but ...
- Few commercial companies for fine pitch applications ($< 75 \mu\text{m}$)
- Bumping technologies
 - Evaporation through metallic mask
 - Evaporation with thick photoresist
 - Screen printing
 - Stud bumping (SBB)
 - Electroplating
 - Electroless plating
 - Conductive Polymer Bumps
 - Indium evaporation

Noise: 130nm vs 180nm (simulation)

NMOS :

 

 130nm
W/L = 50u/0.5u
Ids=48.0505u, Vgs=260mV, Vds=1.2V
gm=772.031uS, gms=245.341uS, gds=6.3575uS
1MHz --> 24.65nV/sqrt(Hz)
100MHz --> 5nV/sqrt(Hz)
Thermal noise hand calculation = 3.78nV/sqrt(Hz)



180nm
W/L=50u/0.5u
Ids=47uA, Vgs=300mV, Vds=1.2V
gm=842.8uS, gms=141.2uS, gds=16.05uS
1MHz --> 4nV/sqrt(Hz)
10MHz --> 3.49nV/sqrt(Hz)
Thermal noise hand calculation = 3.62nV/sqrt(Hz)