



Status Report on ADC developments @ LPC

ILC Group

IN2P3

INSTITUT NATIONAL DE PHYSIQUE NUCLÉAIRE
ET DE PHYSIQUE DES PARTICULES



13/09/2007

Manen @ Calice meeting Prague 2007

1



Ecal VFE ADC : requirements

- **Requirements for ADC**

- Precision 10 – 12 bits
- Ultra low power, 25 μ W per channel
- Compactness, electronics embedded in detector




*Ultra-low
POWER
is the
KEY issue
(C. de la Taille)*

- **Three main developments @ LPC**

- Wilkinson ADC 12 bits easy to implement in SKIROC but too slow for ILC
- Pipeline ADC 10 bits tested and measured
- New design : cyclic and pipelined ADC 12 bits
 - **Building blocks for 3V power supply**




12 bits Wilkinson 3.5V ADC in SKIROC

 

Designed by Gérard Bohner

- **Characteristics:**
 - Techno: **BiCMOS SiGe 0.35 μ m**
 - Power supply: **3.5V**
 - Conversion time : **80 μ s @50MHz**
 - Differential architecture
 - Open loop ramp generator
 - Gray counter
 - Die area: **0.12 mm²**

Wilkinson ADC architecture

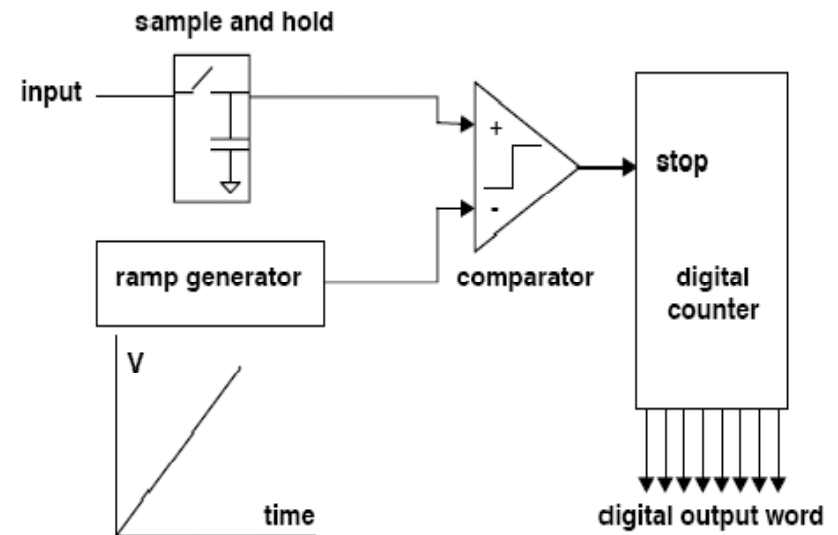



Consumption for 12 bits Wilkinson ADC



- **Dynamic consumption : 3 mW**
- **Conversion time: 80 us @ 50MHz**
- **Assuming:**
 - 128 channels per VFE chip
 - 1 ADC per channel so 128 ADC per chip
 - 5 events max per channel (memory depth)
- With **power cycling**, the **integrated consumption** per channel of the A/D conversion can be estimated by:

$$\frac{P_w \times T_{conv} \times Mem.}{Time_cycle} = \frac{3mW \times 80\mu s \times 5}{200ms} = 6.2 \mu W/ch$$

with P_w : power cons. of one channel
 T_{conv} : time for one conversion
 Mem : memory depth of one channel
 $Time_cycle$: time between two trains

The ON-setting time effects can be neglected.




Performance from simulation of 12 bits Wilkinson ADC

- **Resolution:** 12 bits
- **Consumption:** 3 mW
- **Conversion time:** 80 μ s (@ 50MHz)
- Current source (ramp generator):
 - **Input dynamic signal:** 1V Common Mode
 - **2V differential ramp generator**
 - **T° sensitivity :** 40 ppm/°C max (20 to 50°C)
 - **Power supply sensitivity:** 5 ppm/V (\pm 50 mV)

NonLinearity from simulation:

 - $< \pm 500 \mu$ V up to 125mV
- $< 0.1\%$ from 125mV to 1V




Test in progress thank to the testbench designed by LAL



Pipeline ADC architecture

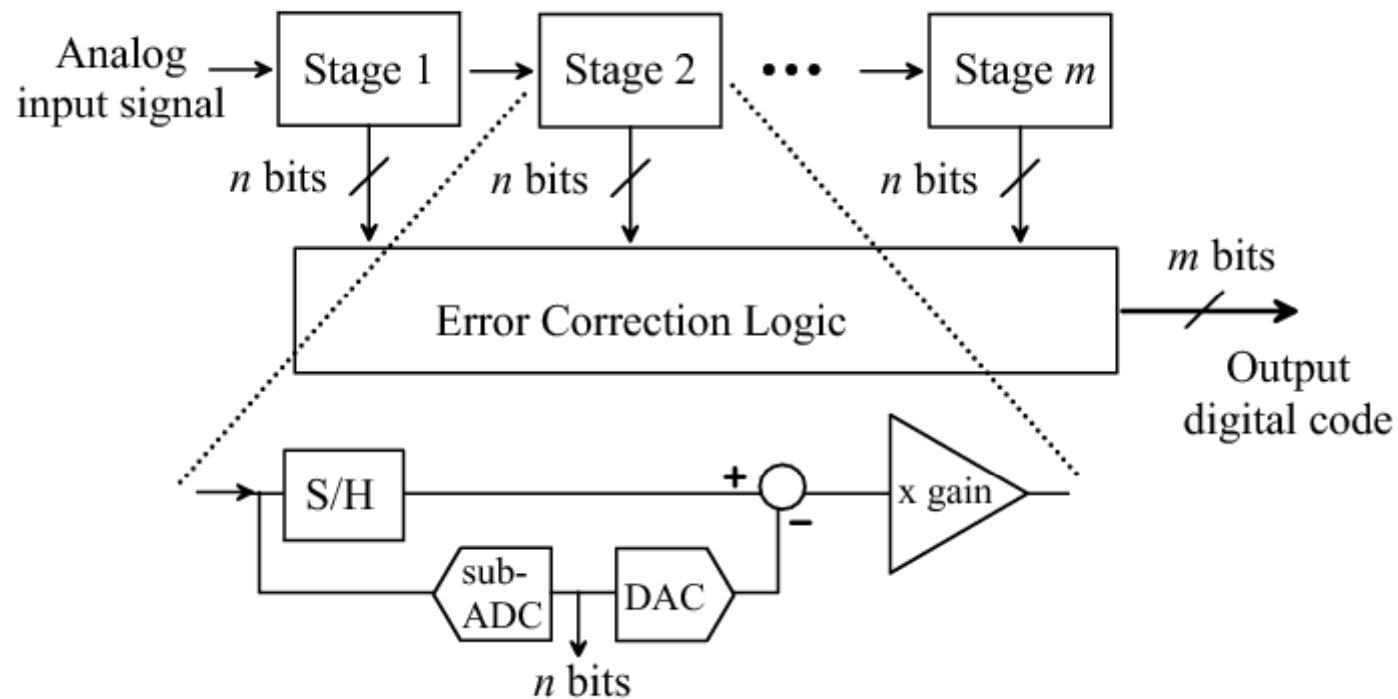- Linearity mainly affected by the precision of the amplifier gain
- 1.5 bit per stage architecture
- Comparator offset tolerated $\pm 250\text{mV}$ for 2V range







10-bits Pipeline 5V ADC

■ Characteristics:

  - Technology: Austriamicrosystems CMOS 0.35 μm
- Power supply: 5V (digital: 2.5V)
- Clock (sampling) frequency: 4 MHz (MS/s)
- 10 bits \rightarrow 10 stages
- 1.5bit/stage and differential architecture
- Die area: 1.2 mm²





Consumption for 10 bits pipeline ADC



- **Dynamic consumption : 35 mW**
- **Conversion time: 250ns @ 4MHz**
- **Assuming:**
 - 128 channels per VFE chip
 - 1 ADC per chip
 - 5 events max per channel (memory depth)
- With **power cycling**, the **integrated consumption** per channel of the A/D conversion can be estimated by:

$$\frac{P_w \times T_{conv} \times Mem.}{Time_cycle} = \frac{35mW \times 250ns \times 5}{200ms} = 0.22 \mu W/ch$$

with P_w : power cons. of one channel
 T_{conv} : time for one conversion
 $Mem.$: memory depth of one channel
 $Time_cycle$: time between two trains

The ON-setting time and pipeline latency effects can be neglected.



Measurement setup for ADC


Test Bench:

Designed by Roméo Bonnefoy

- Generic board for ADC tests
- Analogue signal generator: DAC 16 bits (DAC8830)
- PC/LabView Slow Control through USB interface
- Data processing with Scilab package

Chip under test

USB link

 

Static measurements :

- Input ADC signal: ramp from 0 to 2V
- 2048 steps -- 50 measurements / step





Performance measured for Pipeline ADC



Performance measured:


- Resolution: 10 bits
- Consumption: 35 mW
- Conversion time: 0.25 μ s (@ 4MHz)

NonLinearity (measured):

 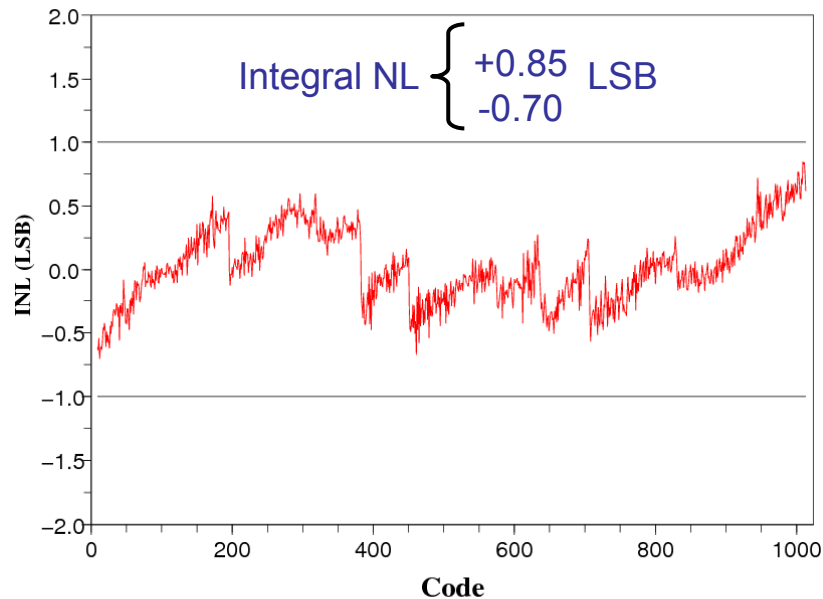




Noise performance for Pipeline ADC

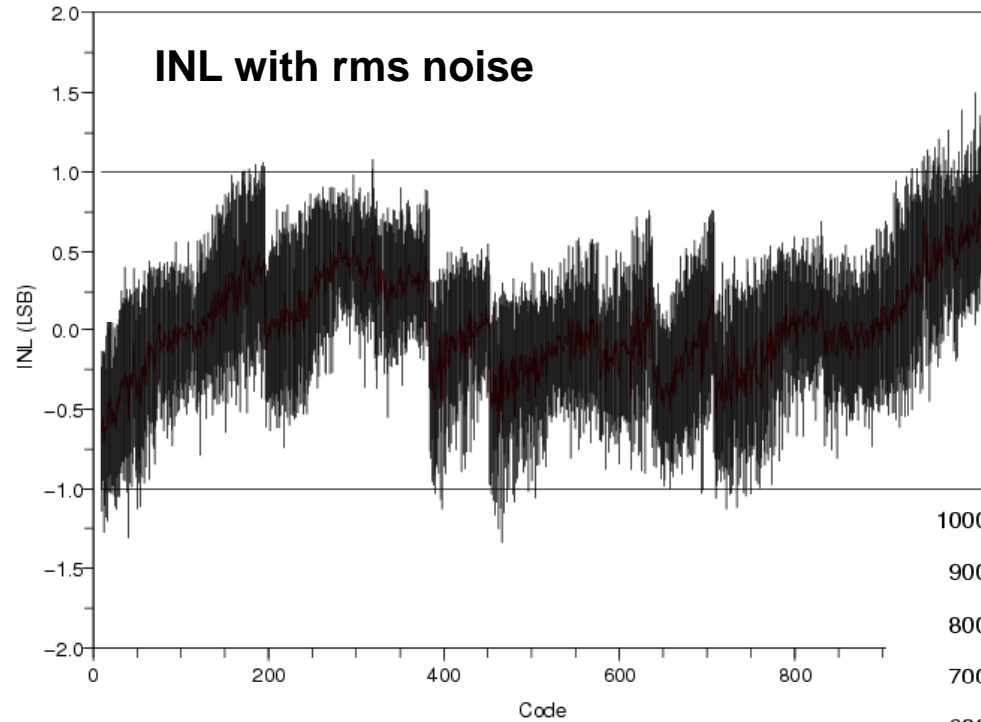

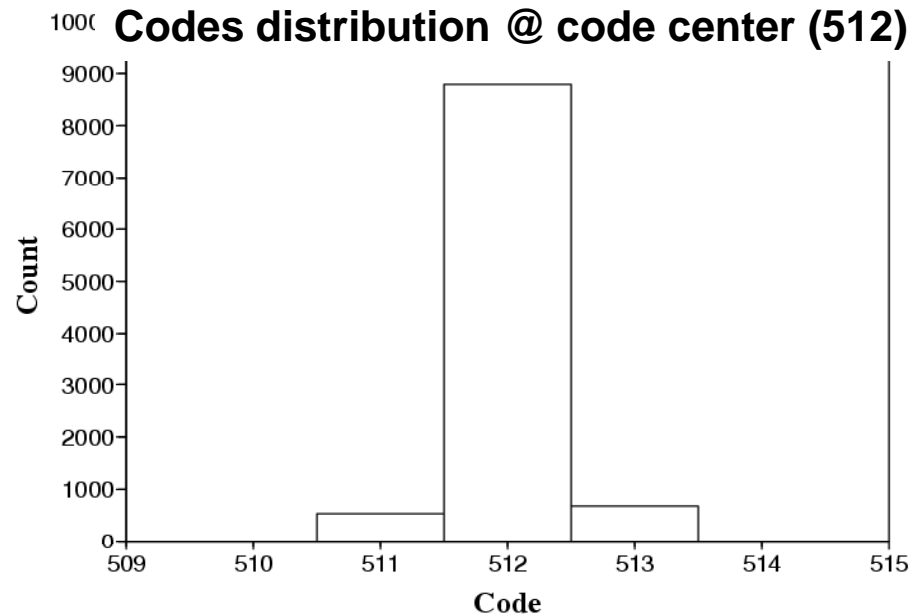Measured noise
(including the setup noise):
 $\sigma < 0.5$ LSB





12 bits – 3V buildings blocks developments

- **Objectives :**

- Design a 12 bits pipeline or cyclic ADC
- Gain 2 accuracy multiply by 4
 - 10 bits ADC accuracy is 1/1000
 - 12 bits ADC accuracy is 1/4000

- **Two chips designed to characterize two main elements**

- Comparator
- Gain 2 amplifier




Comparator test results for 12 bits ADC

• **Characteristics:**


- Technology: CMOS 0.35 μ m
- Power supply: 3V
- Clock frequency: 10 MHz
- Differential architecture
- Consumption 68uA
- 7 chips tested

Average Sensitivity: 1.6 mV
Average Offset : 4.2 mV
Fullfit 12 bits precision requirements

 SENSITIVITY VARIATION FOR 10 MHZ FREQUENCY COMPARATOR



 
OFFSET VARIATION FOR 10 MHZ FREQUENCY COMPARATOR





Gain 2 amplifier for 12 bits ADC

 - **Characteristics:**
 - Technology: CMOS 0.35 μ m AMS
 - Power supply: 3V
 - Differential architecture
 - Die area 11mm²
 - 84 pins



- **Calice_07_07 in July 2007**
 - 3V Gain 2 amplifiers with different layout structures capable to reach 12 bits
 - One ADC stage 12 bits 3V
 - Integrated shaper with analog memory



Summary

- **12 bits Wilkinson ADC**
 - Under test
 - Compactness, 128 wilkinson ADC per chip, die area of $(128 \times 0.12) \text{mm}^2$ for 128 ch.
 - Consumption, $6.2 \mu\text{W}/\text{ch}$, $\approx 30\%$ total power of one channel

- **10 bits pipeline ADC**
 - Precision, INL: $-0.70/+0.85$ LSB , DNL: $-0.46/+0.56$ LSB, Noise: <0.5 LSB
 - Compactness, one pipeline ADC per chip, die area of 1.2mm^2 for 128 ch.
 - Consumption, $0.22 \mu\text{W}/\text{ch}$, $\approx 1\%$ total power of one channel

- **Under study (the best candidate): 12 bits cyclic ADC**
 - Compactness, one ADC per chip around 0.2mm^2 for 128ch
 - Consumption, $0.22 \mu\text{W}/\text{ch}$, $\approx 1\%$ total power of one channel
 - Possibility to have 1 ADC per channel