A fast LED driver prototype for HCAL calibration

CALICE meeting Prague

CALICE, SEP13, 2007

1

Proposal for calibration system

- New LED driver with reduced crosstalk
- A tunable calibration light in the range 0 to 100MIP
- Simplification of the optical system: one LED -> one side emitting fibre, one row of scintillator tiles
- PIN photo diode, do we need them?

LED driver strategy for SiPM calibration

- At AHCAL prototype (uses SiPM), we used CMB, calibration system with UV-LED 400nm driven by very fast rectangular pulses (1ns rise/fall time).
- Steep Rectangular waveform satisfied the needs to vary pulse-width, BUT creates a lots of harmonics and then it converts to electromagnetic crosstalk!
- We have found fixed pulse-width to about 6ns, we can go to use narrow band ->smooth waveform ≈ less RF interference = Quasi Resonant LED driver (single pulse)


Quasi-Resonant LED driver LC circuit, heavily dumped

Simulation

- ~ 5ns puls width (slightly depends on the amplitude)
- 33nH PCB inductance, no ferromagnetic core

- Prototyping
- Used my lovely single side copper foil PCB
- We needs more work to components optimisation


QR LED driver Simulation

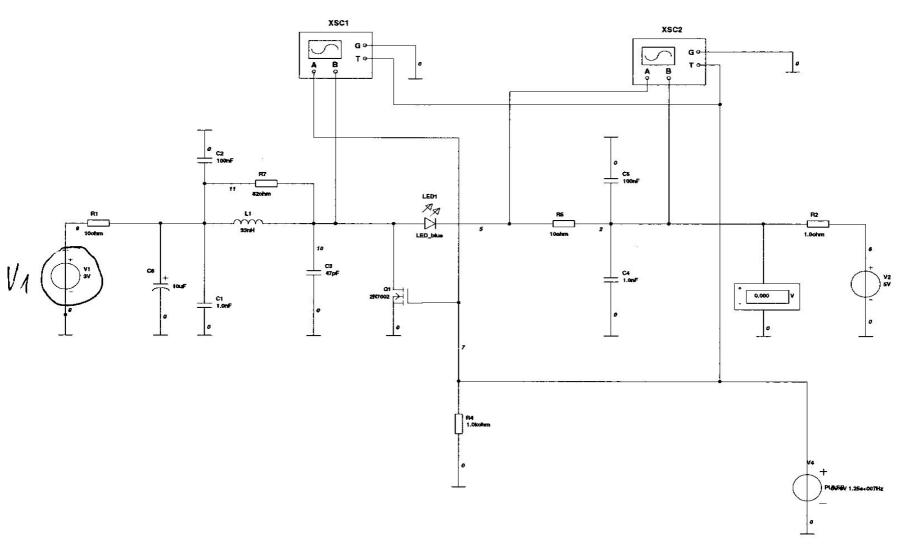

Simulation at 1.5V amplitude

- XSC1:
- Upper trace sync pulse
- Lower trace voltage at LED hot end


• XSC2: Lower trace LED current

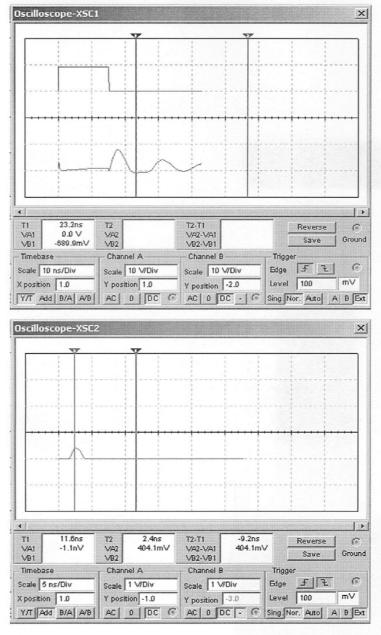

 $V_{I} = 1, JV$

Simulation at 3V

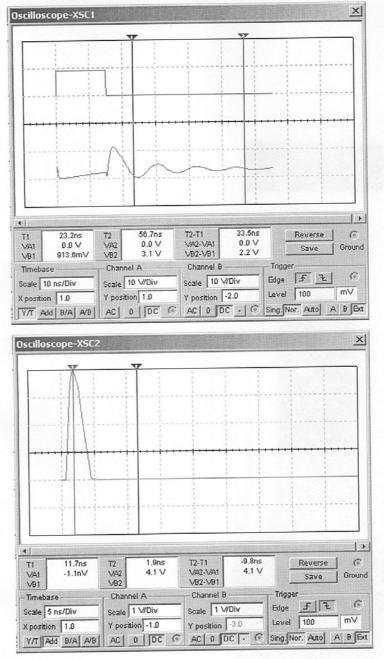- XSC1:
- Upper trace sync pulse
- Lower trace voltage at LED hot end




 $V_1 = 3V$

• XSC2: Lower trace LED current


Ivo Polak, IoP Prague

Prototype of QR LED driver

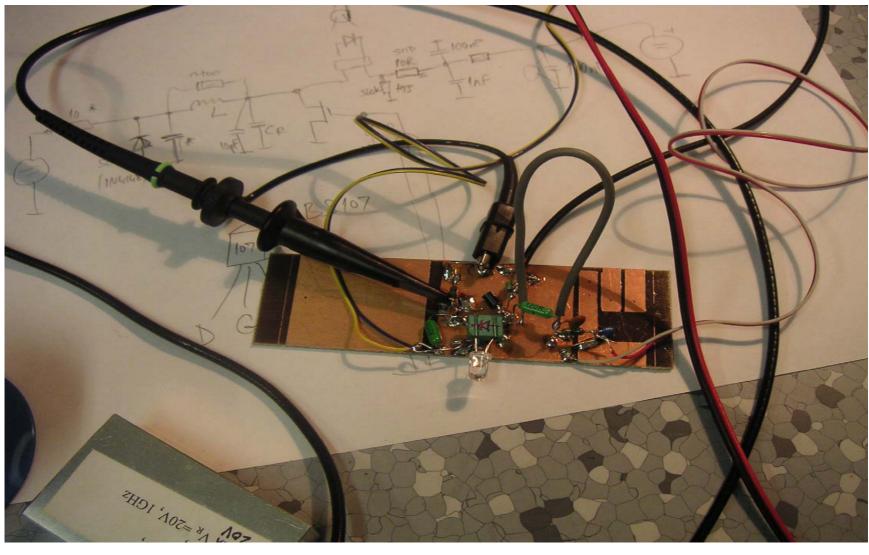


CALICE, SEP13, 2007

LED current waveform (GRN) a=3

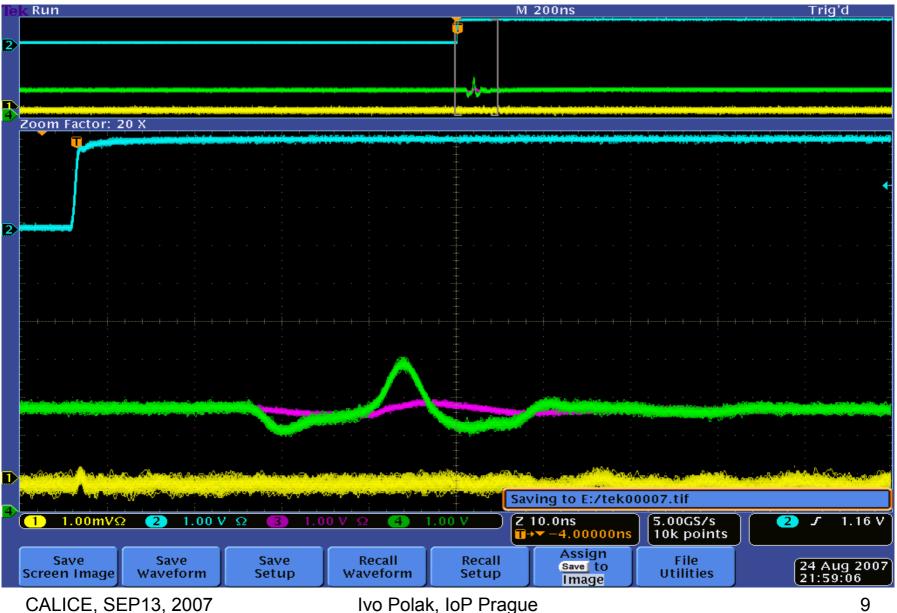

LED current waveform (GRN) a=2

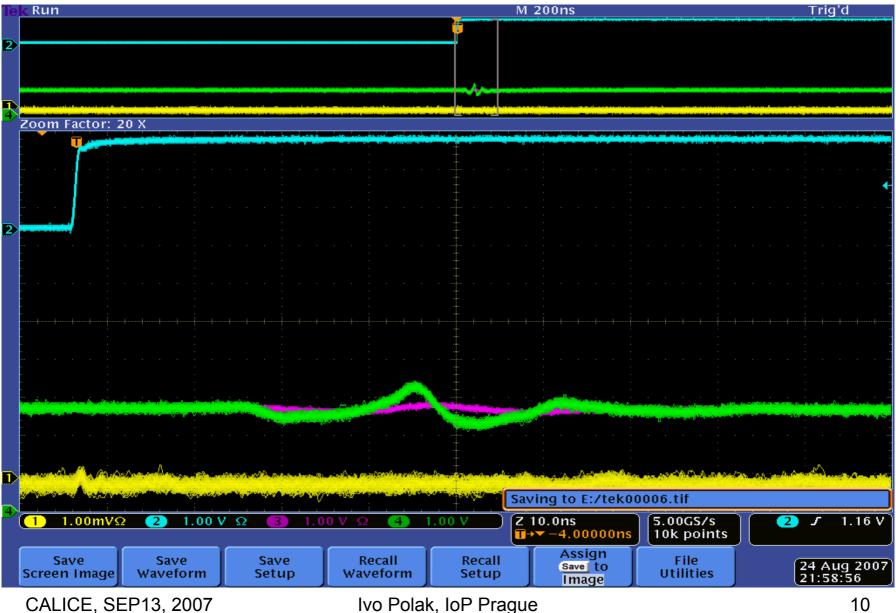

LED current waveform (GRN) a=1

Te	e <mark>k</mark> Run					M 200ns	Trig'd	
2								
	Zoom Factor: 20 X	ور المراجع						
	· · · · · · · · · · ·							· · · · · · ·
								•
								· · · · ·
2								
	· · · · · · · · ·							
	• • •							· . · .
								· · · · · · · · · · ·
		1	AN ACT A STATE OF A ST	L. C. R. Sandard M. S. S. S.		hand a second second state		
	······································				· · ·			· · · · · · · · · · · · · · · · · · ·
							And Man	
D		Martin Barrison State		desille antitals on molarity	a Alterization and a second applying	antivititiona Ito Davit Artik védal	A STORE WARMAN A MONTH A STORE AND	allen helde in det helde en helde bester
		e for the second of	Barren a Annalisa kart	AN AN ANA		Saving to E:/tek	00005.tif	
4	(1) 1.00mVΩ (2) 1.00 V Ω (3) 1.00 V Ω (4) 1.00				1.00 V 💦	Z 10.0ns	2 <i>J</i> 1.16 V	
					□ →▼ -4.00000ns		10k points	
		Save	Save	Recall	Recall	Assign Save to	File	24 Aug 2007
	Screen Image Wa	aveform	Setup	Waveform	Setup	Image	Utilities	24 Aug 2007 21:58:44
	CALICE, SEP1	3, 2007	Ivo Polak, IoP Prague					11

Conclusion

- QR LED driver is very promising technique to reduce Electro-Magnetic-Interferences
- During September we plan to have a single channel protoboard for lab tests with PIN-photodiodes
- In October two-channel QR LED driver on PCB ready to measure light transfer in side-emitting fibres