




The problem of power distribution (PPD) for tracking detectors. A SLHC R&D snap shot

Marc Weber (RAL)

ILC and LHC/Super-LHC trackers share two major challenges
(albeit at different scale):


How to limit

 Power consumption and **detector mass ?**



Power distribution, the topic of this talk relates to both of these

Challenges for SLHC trackers

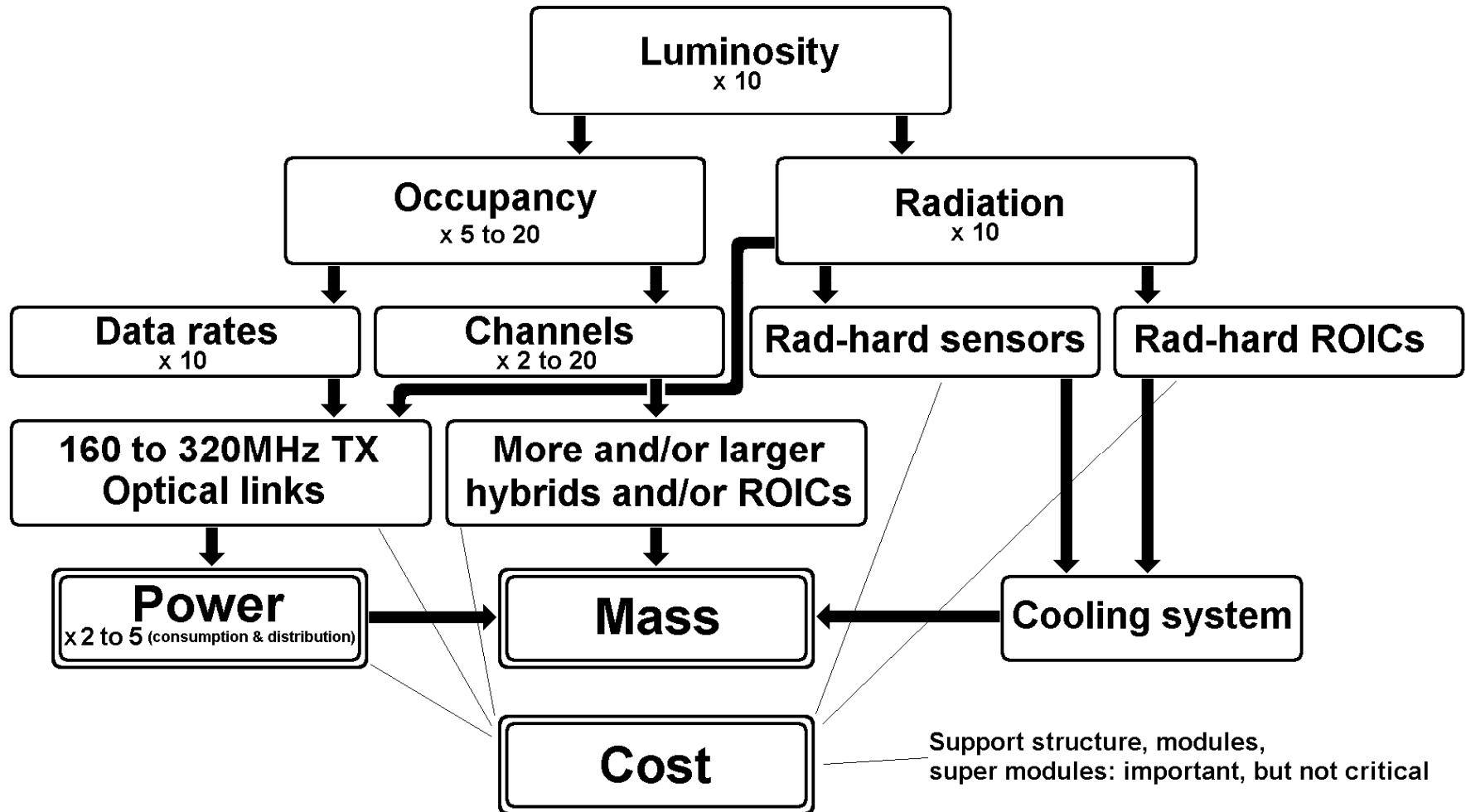

Powering at LHC proved tough and led to an undesired performance penalty, in particular for forward tracking

	ATLAS pixels	CMS pixels	ATLAS strips	CMS strips
Number of modules	1744	1440	4088	15148
Total number of channels	80 M	66 M	6.2 M	10 M
Total rack power incl. optical links and cable losses	30 kW	7 kW	45 kW	67 kW
ROIC name and technology	FE-I3 0.25 μm CMOS	PSI46 0.25 μm CMOS	ABCD 0.8 μm bi-CMOS	APV25 0.25 μm CMOS
ROIC analog (digital) voltage	1.6 V (2.0 V)	1.5 V (2.5 V)	3.5 V (4 V)	1.25/2.5 V (2.5 V)
ROIC power consumption/channel	84 μW	40 μW	3.6 mW	2.9 mW
Total ROIC current	3.8 kA	1.5 kA	6 kA	15 kA
Cable length (one way)/resistance (round trip)	~110 m	~50 m	~110 m/4.5 Ω	34-62 m
Power efficiency	~20%	~42%	~50%	52%
Power distribution schemes	IP ⁴	PP ⁵	IP	PP
Local regulators (near/on-detector)	Yes	Yes	No	Yes

Power distribution at LHC

Depending on experiment (ATLAS and CMS) and detector type (pixels or strips):

- 6 – 80M channels
- 4 – 15K detector modules
- 7-70 kW of rack power for readout electronics (*due to radiation*)
- 50 m to 110 m long power cables (one way) (*due to detector size/energy*)
- 20-50% power efficiency

Constraints: limited space to feed through cables; requirement of minimum mass; need to minimize thermal losses in cables; packaging constraints on detector

SLHC trackers will have 5 to 10 times more channels than LHC ⇔

Power distribution concept must change radically

Why independent powering fails at SLHC ?

Current per electronic channel \sim constant, but many more channels

1. Don't get 5 or 10 times more cables in
2. Power efficiency is too low (50% ATLAS SCT \Leftrightarrow \sim 15% SLHC)
3. Cable material budget: 0.2% of R.L. per layer (barrel normal incidence) \Leftrightarrow 1% or 2% SLHC
4. Packaging constraints

Each reason by itself is probably sufficient for a No-No



Why powering R&D ?



Front
view on
ATLAS
tracker
barrel

**Cannot afford cable pollution anymore and don't need to.
New systems will be much better**

(cable number, material performance; packaging; power efficiency)

How we will fix the cable pollution?


Minimize module power consumption in the first place.

Minimize the current through cables. There are only two ways:


- a) recycling current (Serial Powering) or*
- b) “high-voltage” power lines plus DC-DC conversion*

Both require local “power supplies” (regulators or converters) on the detector module ⇔ PS design challenge + system challenge


How we will fix the cable pollution?

 


Serial powering

 

DC-DC buck converter

 


DC-DC charge pump

 

Piezoelectric transformer

Serial powering

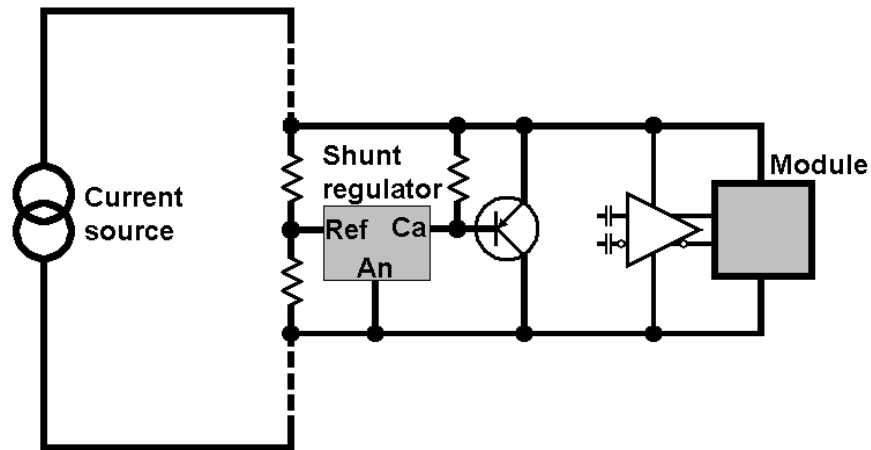

Send constant current from module to module; local shunt regulators to define module voltage.

Different modules sit at different potential \Leftrightarrow need AC-coupling of signals (was a bit of a nuisance but not an issue)

Unorthodox, “crazy”, but elegant. Also used for LHC magnets...

New approaches offer remarkable benefits: reduction of cable volume by factor 10-20; increase of power efficiency by factor 2-5...

A few comments

Serial powering is an old idea. First implemented for ATLAS pixels by Bonn University. Picked up ~2 years ago by RAL for strips

Initially we were mostly worried about noise/electrical performance of these multi-module systems (apart from failure and loss of many modules)


Wrongly! *SP systems tend to be quiet:*

- a) local regulator on module helps*
- b) Current in the chain is constant \Leftrightarrow no IR drops*



Serial powering circuitry evolution



SSPPCB - 2006/7 -
38 mm x 9 mm

 


SPPCB - 2006 -
111 mm x 83 mm




SPPCB - 2006 -
150mm x 150mm

  


Tests with ATLAS SCT modules or hybrids

 


SCT module test set-up

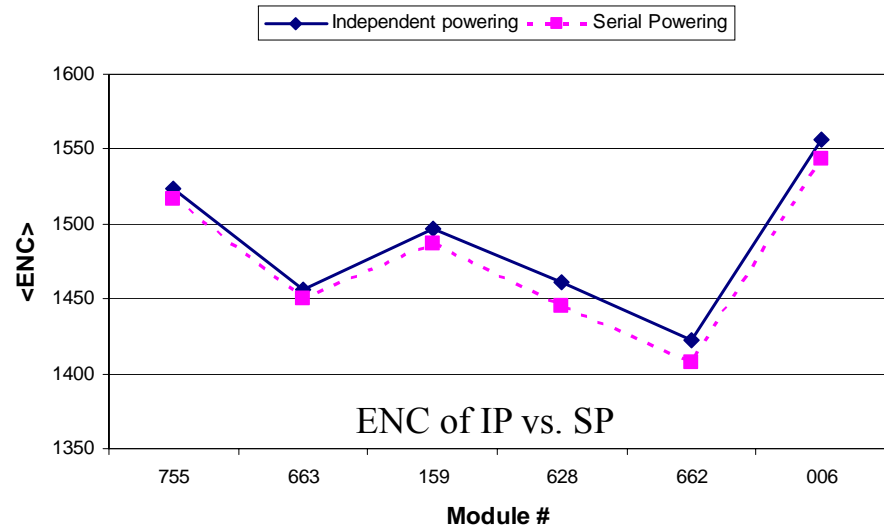

Noise vs injected noise frequency

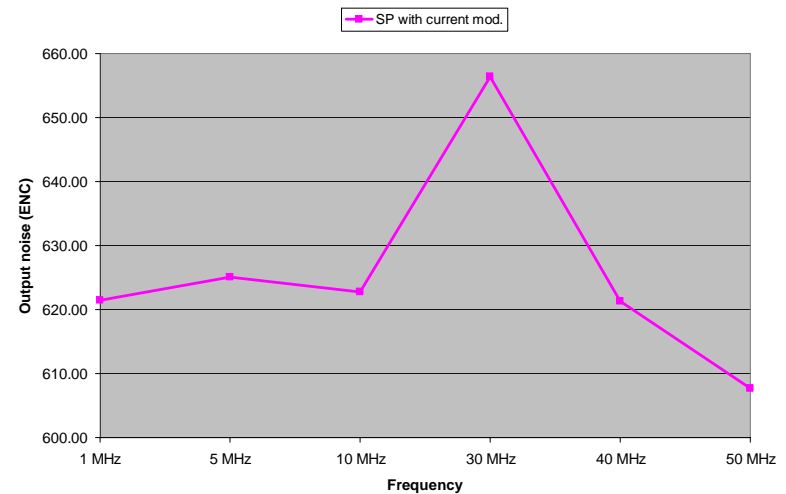


ENC with current modulation of 20 mA

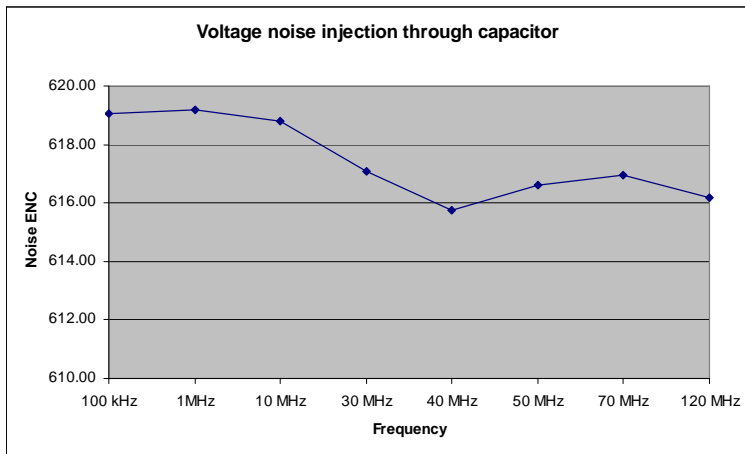


ENC with injection of external voltage pulse into power line (1V pp through 15 pF)

Many results, noise looking good. So far only commercial electronics


Objects we built and tested so far

 

ATLAS SCT module tests

 

 Six ABCD hybrid with SP for 30 module stage



6-module serial powering stage

Next step are design of custom electronics

Main difficulties: high current requirement and limited HEP IC design experience in this area.


Benefits: much reduced output impedance; much reduced real-estate; radiation-hardness

	Required range	Desirable range
Output voltage	1.2 V – 1.8 V	1.2 – 2.8 V
Output current	> 2 A	> 4 A
Dynamic output impedance	10 Ω at < 10 MHz	0.1 Ω at < 100 kHz 0.5 Ω at < 10 MHz
Magnetic field operation	> 4 T	> 4 T
Radiation-tolerance	10 ¹⁵ n/cm ² 100 MRad	10 ¹⁶ n/cm ² 500 MRad
Size		100-250 mm ²
Inefficiency	<20%	~5%
Minimum EMI	EMI susceptibility is detector specific. Limits for radiative EMI (e.g. from inductor coils) are not yet understood. For conducted EMI, 40 dB μ A of common-mode should not be exceeded in the frequency range of 100 kHz to 30 MHz.	
High reliability	System dependent. Targeted module power failure rate: < 1% per module over 5 years of operation	

Table 2: Specification for SLHC power regulators, converters or transformers. See the text for explanations.


Serial Powering Schemes - Motivation

1) External shunt regulator + transistor

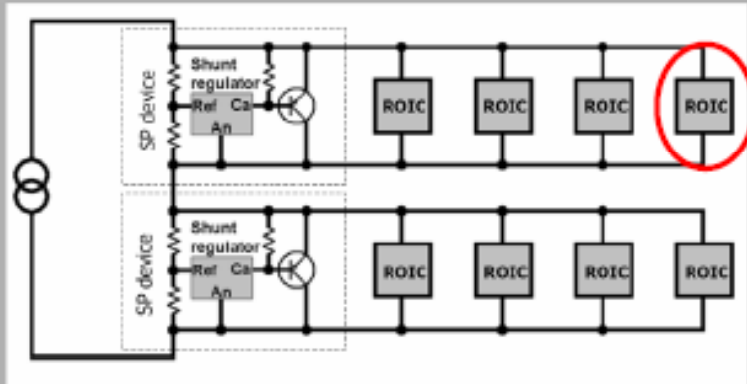


Good approach, but implies a **high current shunt**
 -> limited experience in HEP-IC community
 SP device enables to operate non SP-ROIC in SP mode

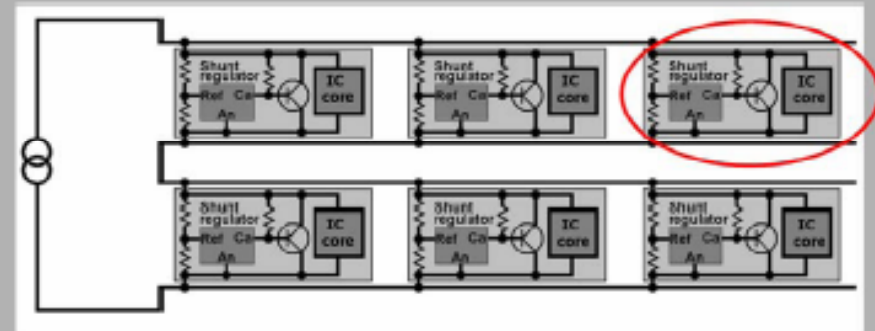2) Internal shunt regulator + transistor in each ROIC



Disadvantage: many power supplies in parallel
Matching issue can cause hot spots and potentially kill chips

 3) External SR + parallel shunt transistor in ROIC



- choice of architecture **not obvious**, detailed studies anticipated by RAL/LBNL (M.Weber, C.Haber)
- **SPI chip should cover scheme (1) and (3)**
- scheme (2) can be realized by any ROIC standalone

feedback however **more challenging** and depends on implementation

Interlude: SPi chip

General purpose SP interface

Overall layout and design: Marcel Trimpl, FNAL
LVDS part and stand-alone SR: Mitch Newcomer
and Nandor Dressnandt, Penn

Specification and KE: Giulio Villani, RAL

Main blocks and features:

Shunt regulator(s) and shunt transistors;


LVDS buffers; over current protection;

Shunt current sensing ADC;


TSMC 0.25 μ m CMOS with rad-hard layout;

Max. shunt current: 1 A design, “expected” 2.5 A;

Size: $\sim 14 \text{ mm}^2$; bumping

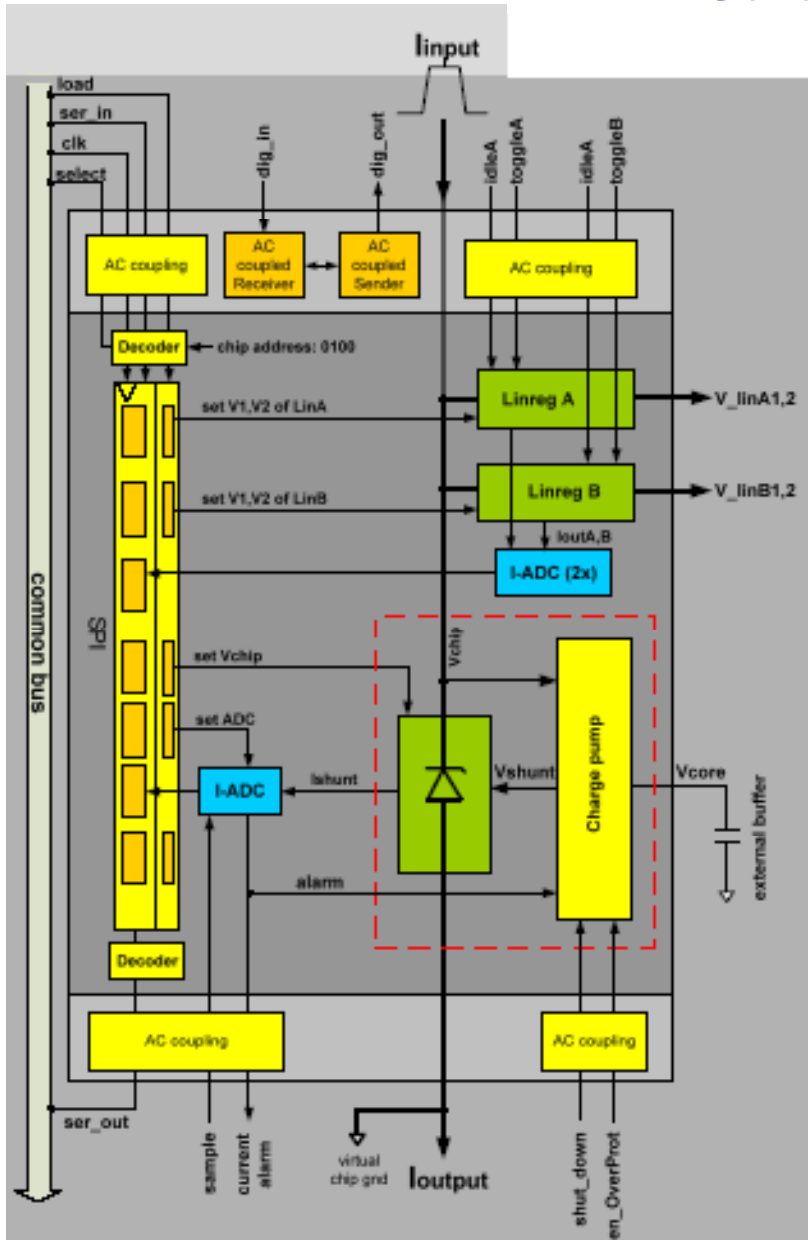

Principle of OverPower Protection

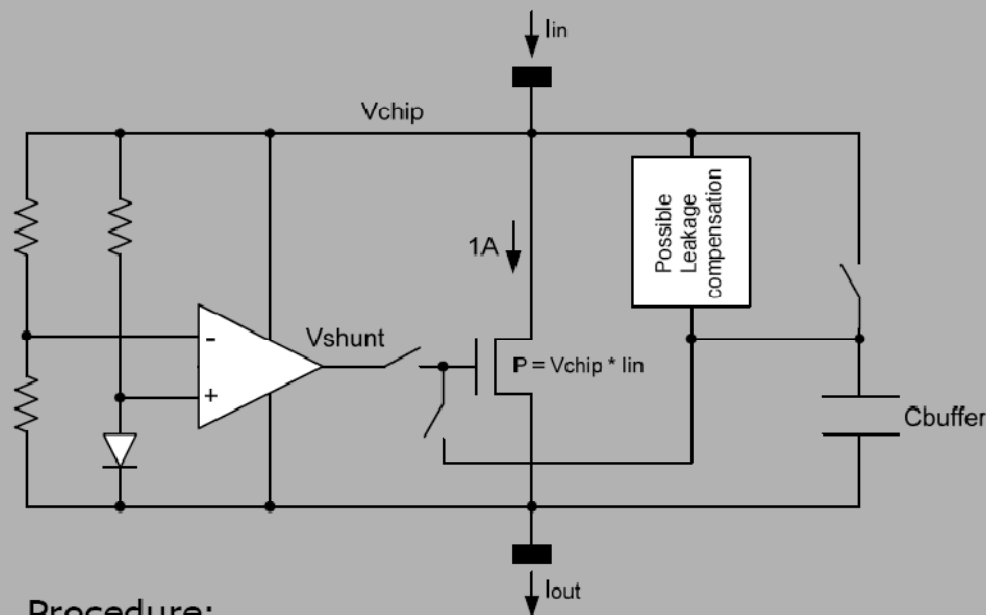

Procedure:

1. ADC reports **current alarm** or power down command
2. Amplifier decoupled, V_{shunt} connected to V_{buffer} (2.5V)
 - > forces shunt-mos in lin.region & **reduces V_{chip}** ($R_{on} * I$)
 - > whole chip collapses, only shunt maintains operatio
3. let's see how far (long) we can go using a simple buffer cap
 - very attractive for **pulsed powered schemes**
 - for permanent power down basically leakage effects need to be compensated (short ramp up to recharge)

1. OverPower is **NOT** OverCurrent
-> current should stay the same
in SP scheme!

2. Power reduction by
collapsing the chip voltage


3. Goal: reduce V_{chip} to minimum
e.g. 50mV and 4A -> **$P \sim 200mW$**
- in the order of nominal operation
- comparable to ROIC on module

-> no hot spot!

Sounds crazy, but serial powering is already!

SP architecture choices

 b) Shunt regulator + transistor in each ROIC



Integrated (custom) SR and transistor designed by Bonn worked well for pixels.

Many power supplies in parallel; Addresses high-current limitation and provides protection. Difficulty is matching and switch-on behaviour of shunt transistors.

Must avoid hot spots that kill one shunt transistor after the other.

Specific implementation in ATLAS ABC-Next

Prototype chip for Si strip readout in Upgrade Inner Tracker

Binary readout

Front-end optimised for short strips

Positive or negative input charge


Readout clock up to 160 Mbits/sec

250 nm CMOS (IBM) technology

2.5 V digital power supply (100 mA)


2.2 V analogue power supply (30 mA)

Compatible with serial powering scheme

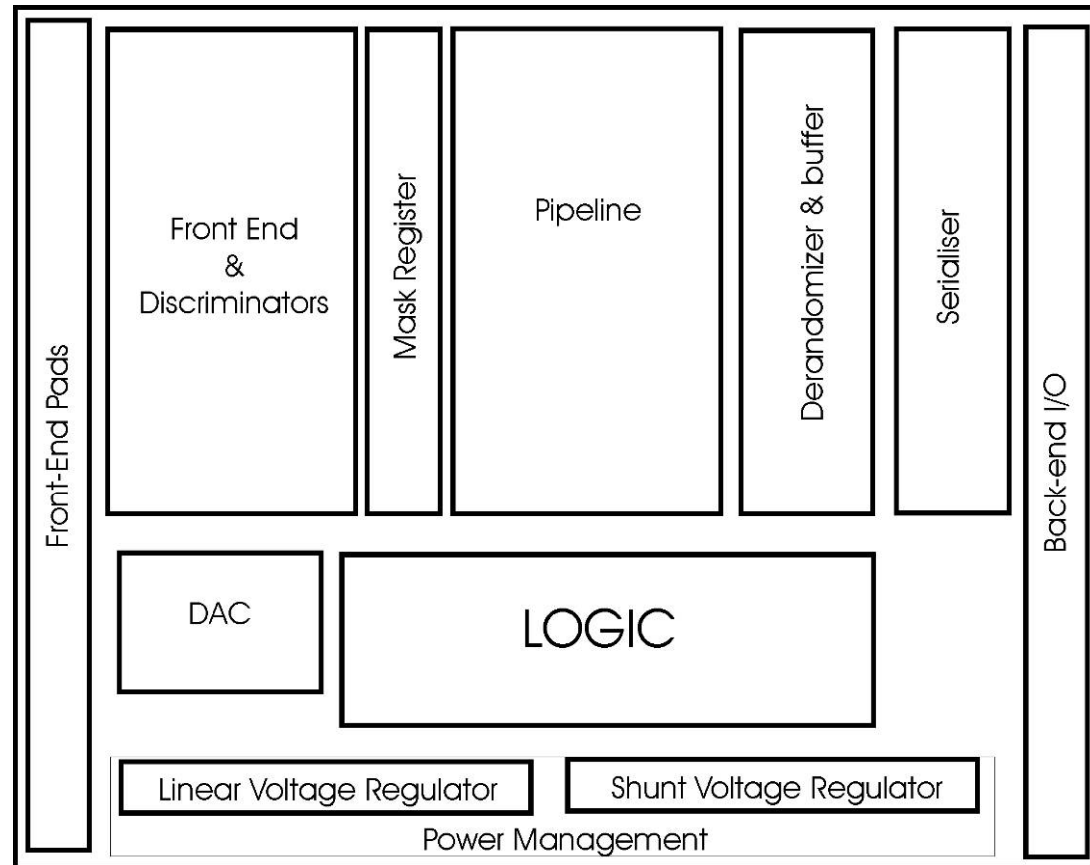

Full shunt regulator on chip - design concept

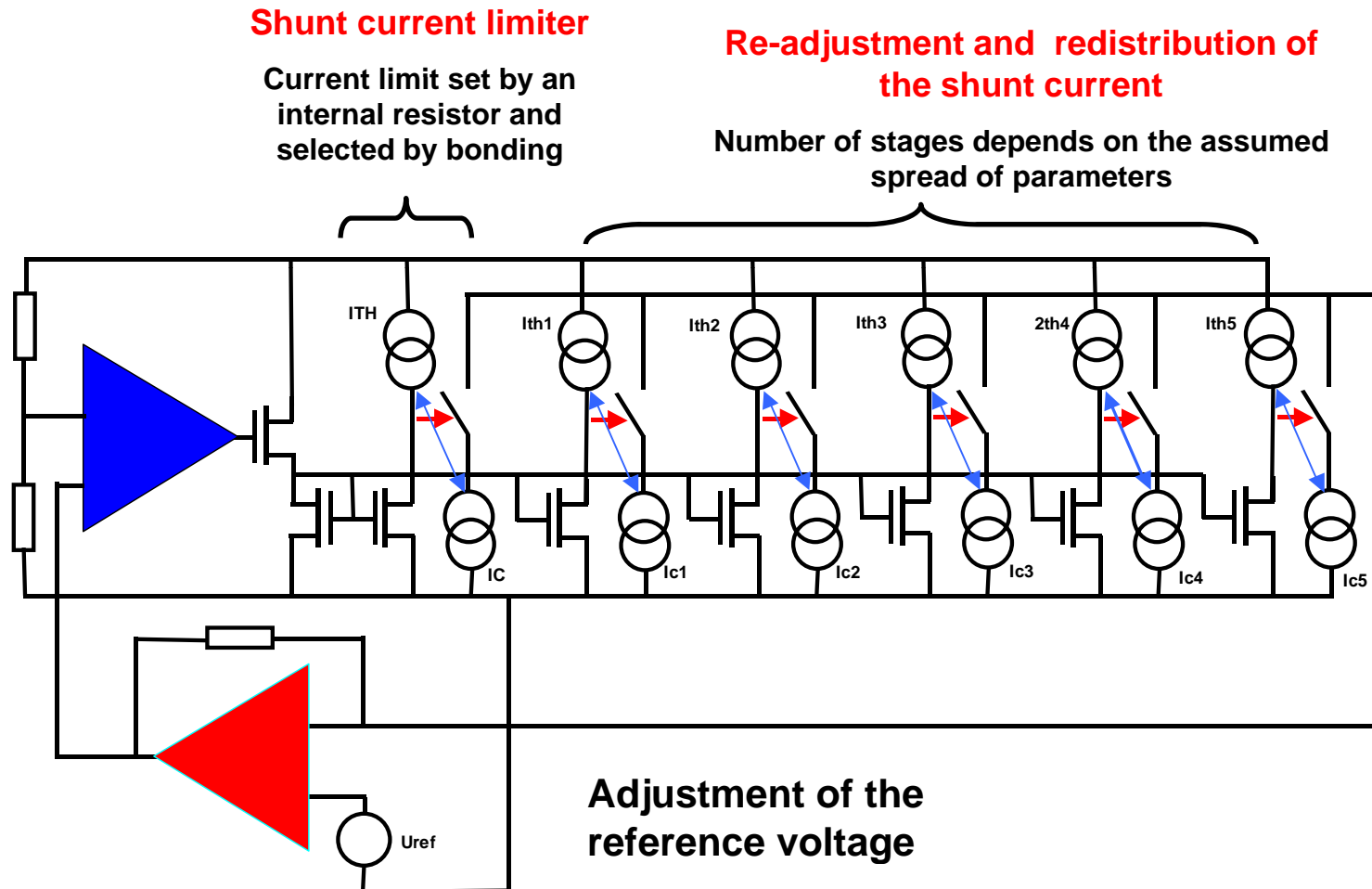Need democratic distribution of shunt current, not winner takes it all.



20

Conclusions

Solving PPD for SLHC trackers is crucial, extremely challenging and urgent.

It is unusual to gain such significant factors in a technology as mature as silicon detectors.


Power distribution R&D is a new and exciting field. International collaboration is growing. <http://indico.cern.ch/conferenceDisplay.py?confId=31377>

I expect significant spin-offs outside of PP, e.g. space and synchrotron detectors. Benefits not limited to tracking.


Appendix



 Expected performance benefit of custom SP circuitry



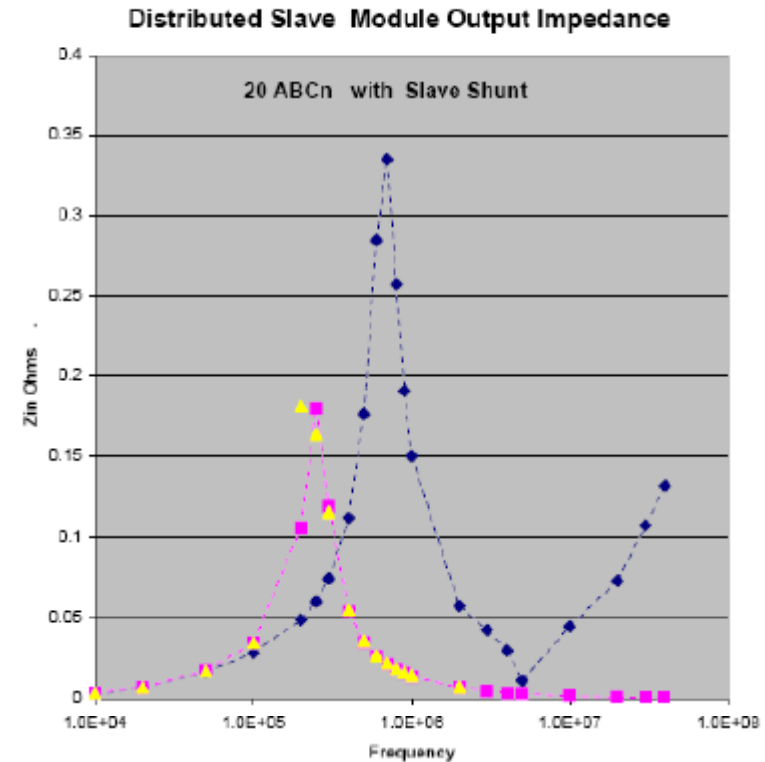Measurement (RAL): Prototype with commercial components



Simulation (Mitch Newcomer): External Shunt Regulator and Integrated Shunt Transistors

Dynamic impedance: reduced by one or two orders of magnitude!

Power efficiency for SP at LHC and SLHC


Illustration of various cases:

SCT \Leftrightarrow 4V, 1.5 A, $R=4.5\ \Omega$ \Leftrightarrow $x=1.14$; IP

SLHC \Leftrightarrow 2.5V, 2.4 A, $R=4.5\ \Omega$ \Leftrightarrow $x=4.3$; SP (only cable losses)

SLHC \Leftrightarrow 1.5V, 4 A, $R=4.5\ \Omega$ \Leftrightarrow $x=12$; SP (only cable losses)

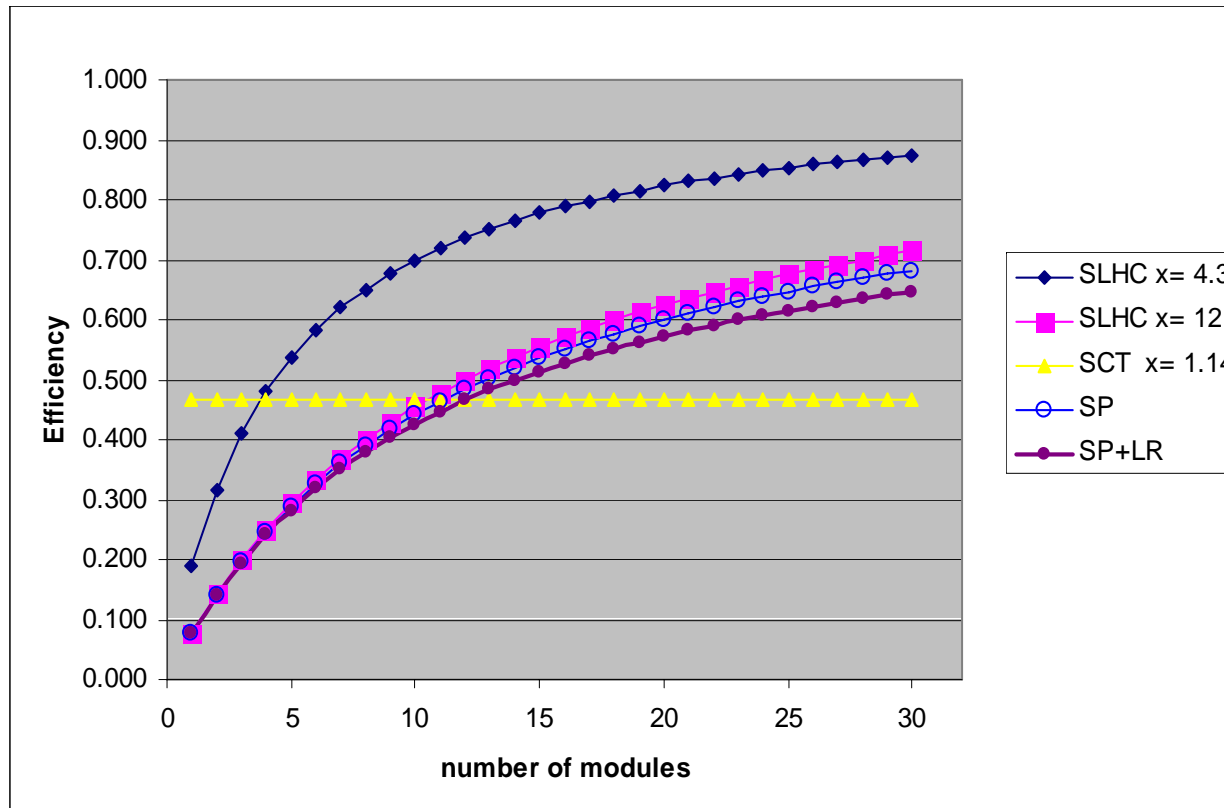same but including SR power and LR power (extrapolated from ATLAS SCT measurements)



Keep hybrid current low!

SR inefficiency ~7% for 10% digital current variation

LR for analog has similar losses


SR inefficiency is reduced for 0.13 μm CMOS

Let's work out a powering example

here $V_{\text{ROIC}} = 2.5 \text{ V}$; $I_{\text{H}} = 2.4 \text{ A}$; 20 hybrids; DC-DC gain = 20

SP: $n=20$; $I_{\text{H}} = I_{\text{PS}} = 2.4 \text{ A}$; $V_{\text{PS}} = nV_{\text{ROIC}} = 50 \text{ V}$

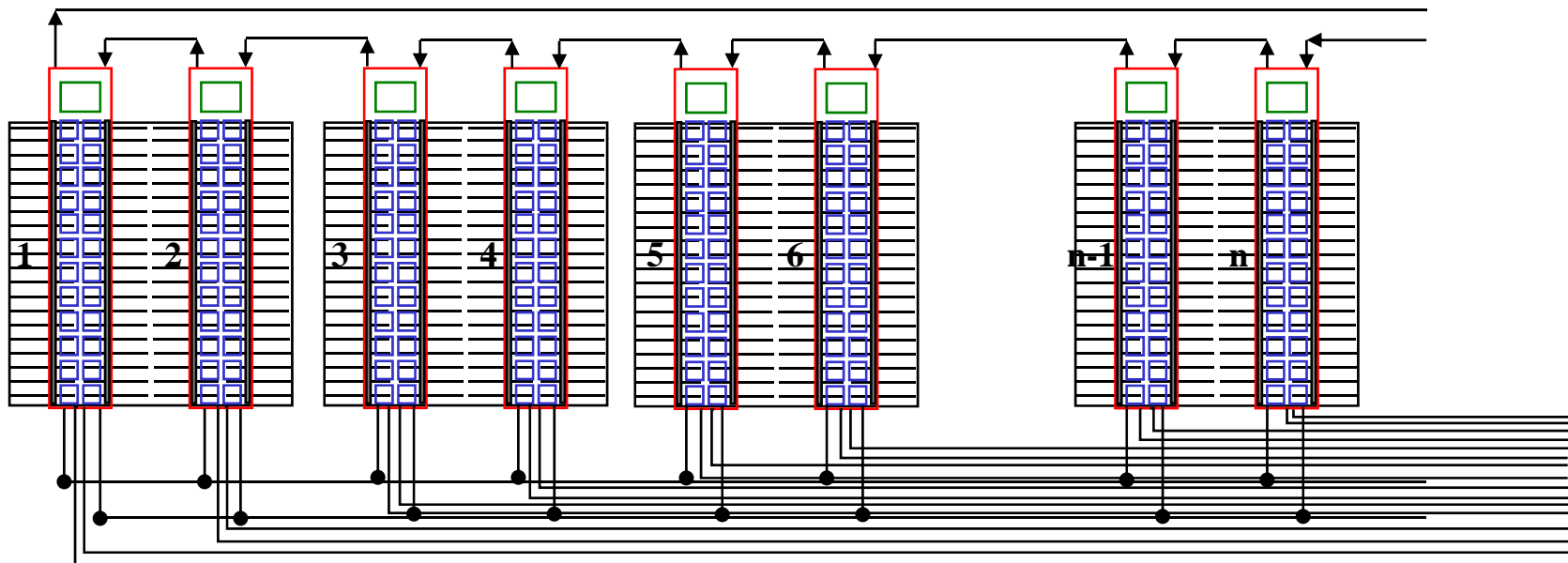Features: saves factor ~ 8 in power cables/length over ATLAS SCT



DC-DC PP: $n=20$; $g = 20$; $I_{\text{PS}} = n/g I_{\text{H}} = 2.4 \text{ A}$; $V_{\text{PS}} = gV_{\text{ROIC}} = 50 \text{ V}$

Features: saves factor ~ 8 in power cables as SP, watch IR drops $\Leftrightarrow R_{\text{cable}} \sim 0.1\text{-}1 \Omega$

DC-DC IP: $n=1$; $g = 20$; $I_{\text{PS}} = I_{\text{H}}/g = 0.12 \text{ A}$; $V_{\text{PS}} = gV_{\text{ROIC}} = 50 \text{ V}$

Features: 2x more cables than SCT \Leftrightarrow problematic for strips

Features of IP and alternative schemes

	IP	SP	DC-DC	Comment
Power efficiency	10-20%	60-80%	60-80%	Varies with I, n (SP); gain (DC-DC)
Local regulator inefficiency	0%	~10%	<20%	This is without linear regulator for analog
number of power cables	4 per hybrid	Reduction by factor 2n	Reduction by factor 2n	n = number of hybrids
Voltage control over ind. hybrids	Yes On/Off; fine-adjustment	Stand-by mode: 2.5V/1.5V -> 0.7 V; Limited fine-adjustment	Yes On/Off; limited fine-adjustment	New schemes have regulators; no fine adjustment needed
Hybrid current info	Yes	Yes (sensing current through power device)	Yes	Some power penalty for DC-DC
Hybrid voltage info	Yes (need sense wires)	Yes	Yes	Not strictly needed, since regulators
Floating hybrid power supplies	Yes	No, voltage chain	No	
Protection features	Separate set of cables for each hybrid	Local over-current protection; redundant regulators	Don't know yet	Protect against open (SP) and short (DC-DC)

Let's preserve the good features of IP ⇔ **have voltage control, current monitoring, and protection features**

Overview of activities in a nut shell

DC-DC buck converters and charge-pumps

On-(read-out) chip and dedicated stand-alone converters

Serial powering regulators implemented in

(read-out) chip and dedicated stand-alone generic chip

Studies so far were largely limited to bulky commercial devices

Program requires development of these devices for one:

-good electrical performance

-radiation hardness

-low mass/ small size

-high reliability

-high current capability

-magnetic field tolerance

-low EMI

Development of these devices also requires their validation with detector modules or chains of detector modules