 


Steering and Readout Chips for DEPFET Sensor Matrices



Schaltungstechnik
und Simulation

Prof. Peter Fischer,
Dr. Ivan Peric,
Christian Kreidl

christian.kreidl@ziti.uni-heidelberg.de


ILC Vertex Workshop

21.-24.04.2008

Villa Vigoni, Como, Italy

- Switcher3 Steering Chip
 - Requirement + Features
 - Block Diagrams
 - Test Results
- DCD2 Readout Chip
 - Requirement + Features
 - Block Diagrams
 - Test Results
- short: Bump Bonding Status
 - Bumping
 - Dummy-Chips
 - Flipping

Switcher3 DEPFET Steering Chip

 


23.04.2008

Steering and Readout Chips
for DEPFET Sensor Matrices

Chair of Circuit Design
University of Heidelberg
Germany


Switcher3 Requirements

 - steering chip for gate- and clear-signals
- high voltage **9V signals**
- **radiation hard** design
 - high voltage technology not suitable because of thick gate oxides
- 20pF matrix capacitance
- **fast** signal edges: <10ns risetime for 20pF load
- 128 channels
- not trivial **switching sequences**
- **bump** pitch of 180 μm , allows pixel sizes down to 24 μm
- \leq 50MHz row rate




Switcher3 features

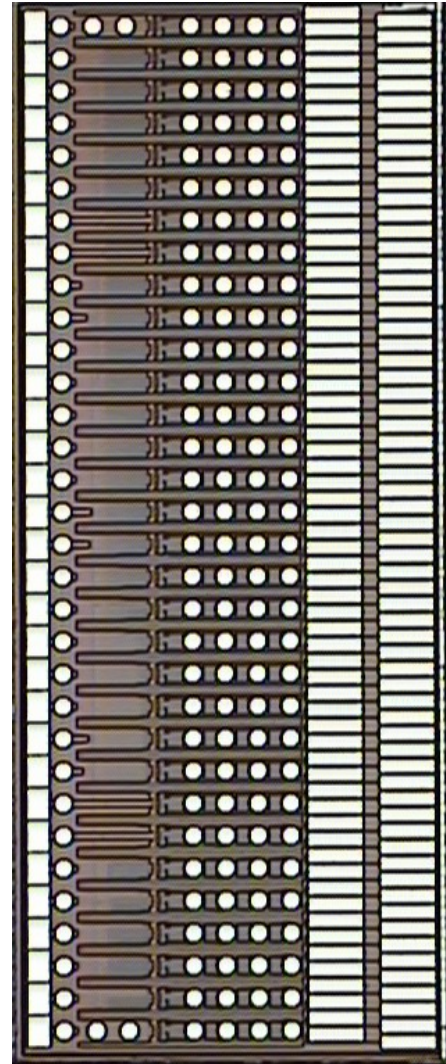- 9V switching using three **stacked** 3.3V transistors
 - needs twin-well technology (AMS h35b4)
 - capacitive coupling of digital and analog blocks
- **radiation hard** design, no HV-transistors
- 128 channels
 - **bump bonding**, wire bonding for compatibility
- sequencer
 - allows **non trivial switching sequences**
 - 4 commands, 64 lines program code length




Block Diagram

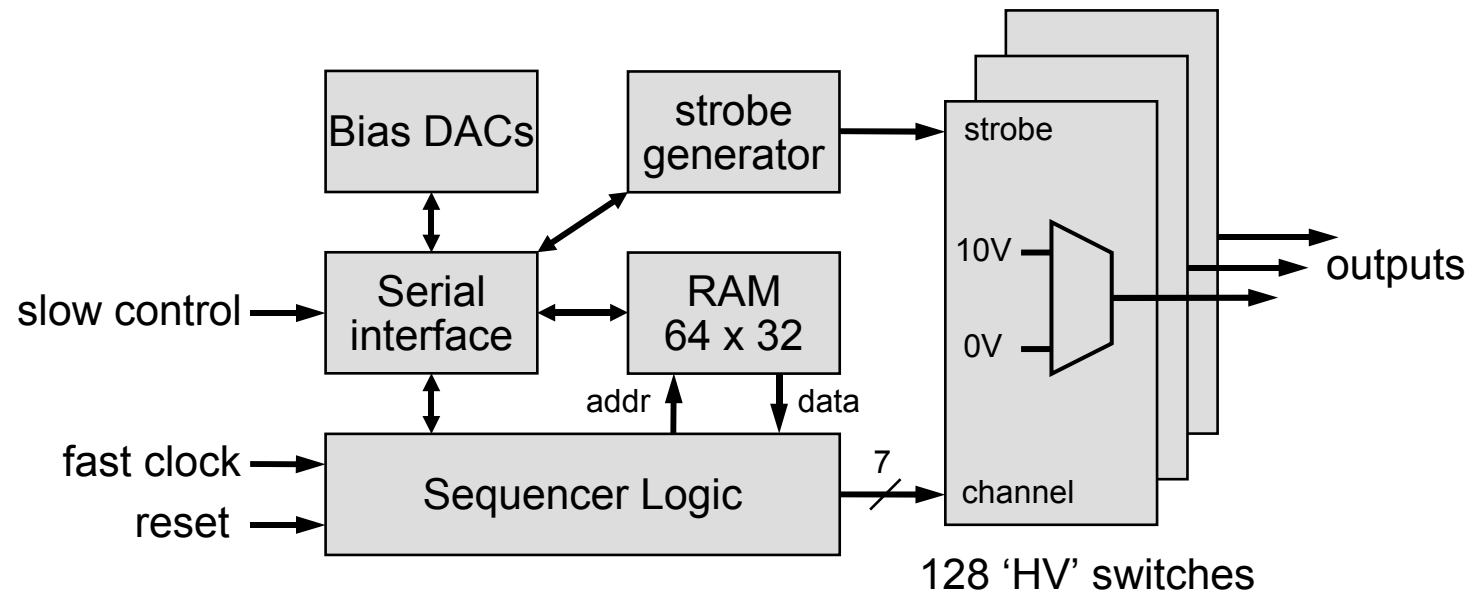


Stacked Transistors

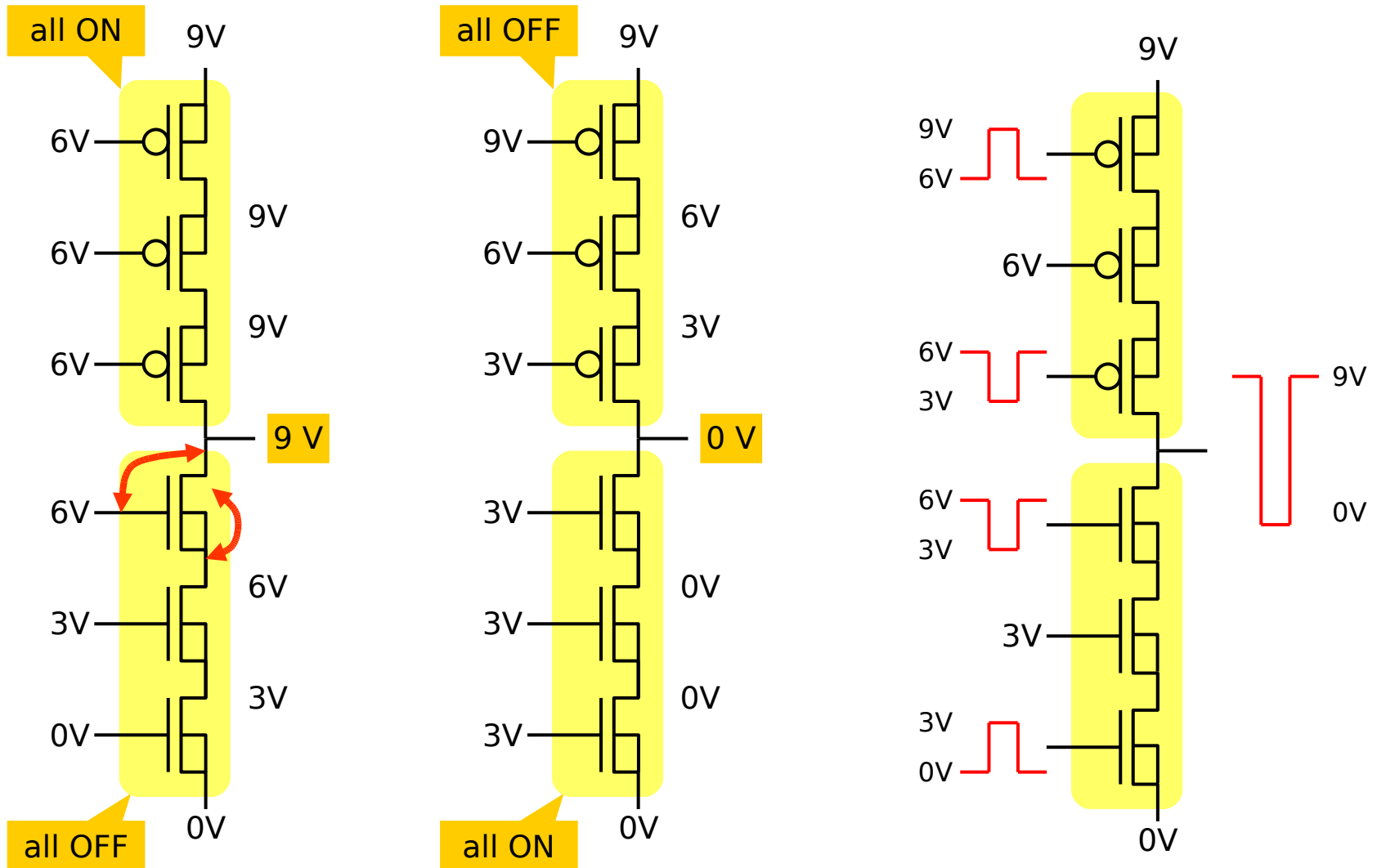- Use 3 **stacked transistors**. Assume 3V per stage: $V_{DD} = 3 \times 3V = 9V$





Cap Coupling

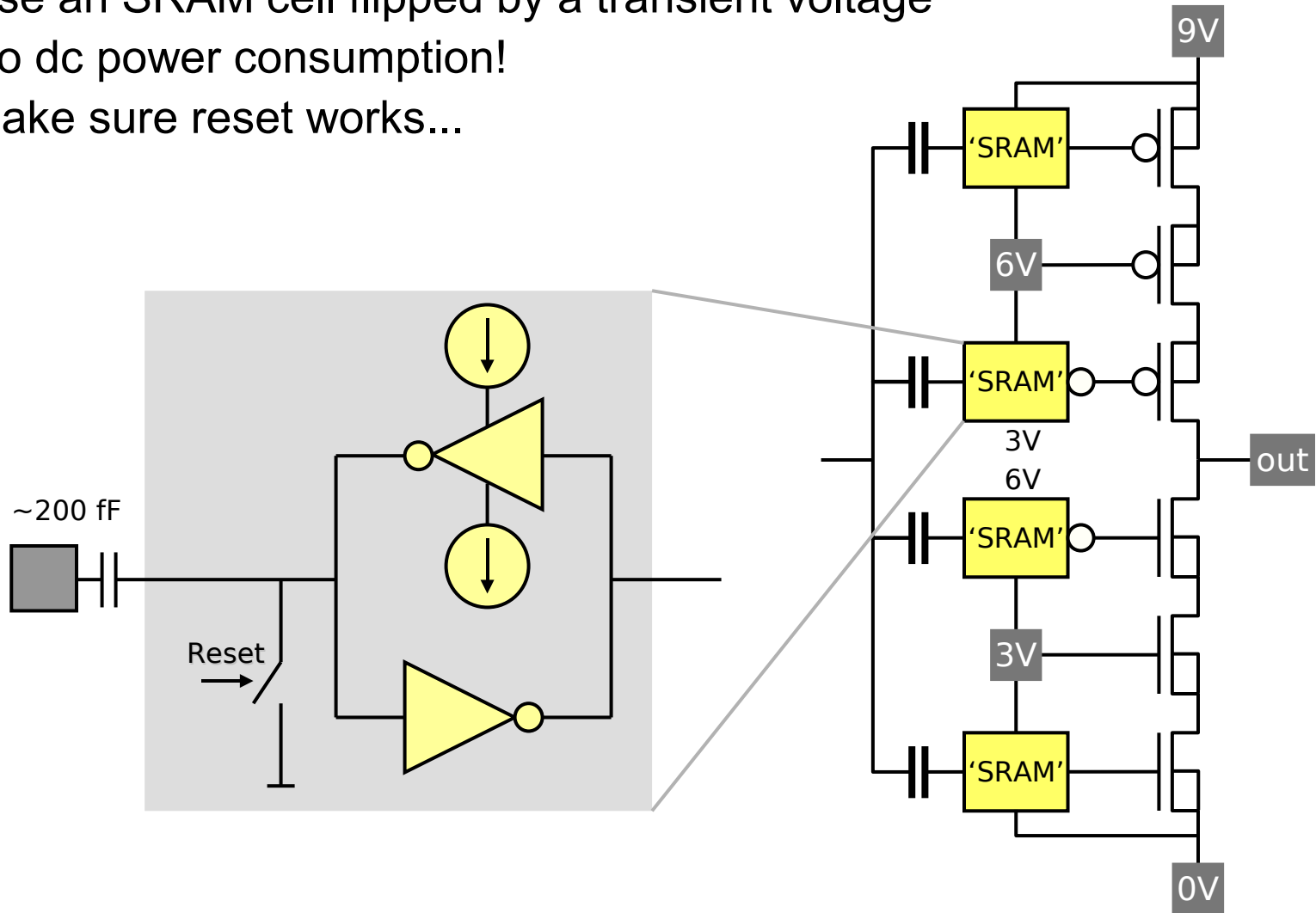- Use an SRAM cell flipped by a transient voltage
- No dc power consumption!
- make sure reset works...



Sequencer

 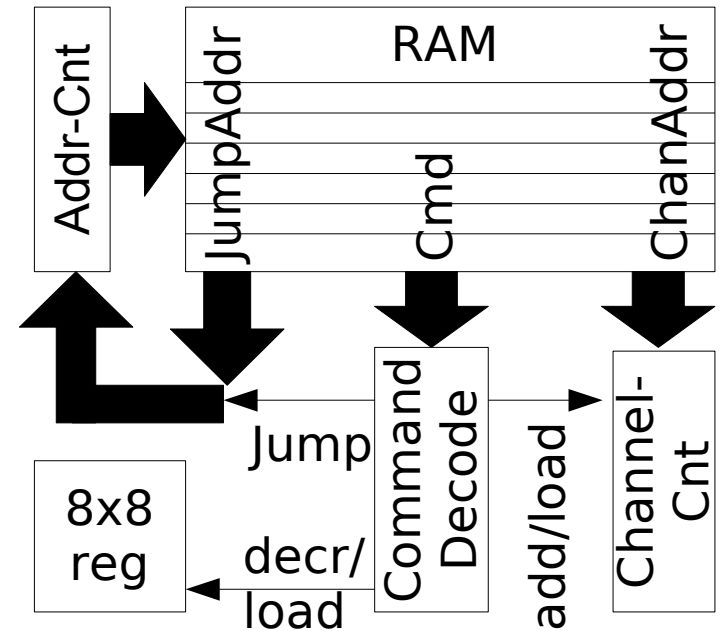
- May need nonlinear scans
 - scan high occupancy more often
- Simple but flexible
 - jumping, looping,
 - absolute/relative channel addressing
- 64 words program length



Sequencer - Commands

- 64 RAM lines, i.e. command lines
- 4 commands
 - JUMP: jump <addr> <chanCMD> <chanNr>
 - LOAD: load <reg> <value> <chanCMD> <chanNr>
 - BNZDEC: bnzdec <reg> <jumpaddr> <chanCMD> <chanNr>
 - JMP_COND: jmp_cond <addr> <chanCMD> <chanNr>
- chanCMD
 - switches channel on or off
 - channel addressing can be absolute or indirect
 - on / off: add chanNr to channel counter, negative values allowed
 - onabs / offabs: chanNr is absolute
- 8 registers for looping using BNZDEC command
 - 8bit wide
 - coding done via complicated LFSR


Analog Test - Falling Edge vs. C_{load}

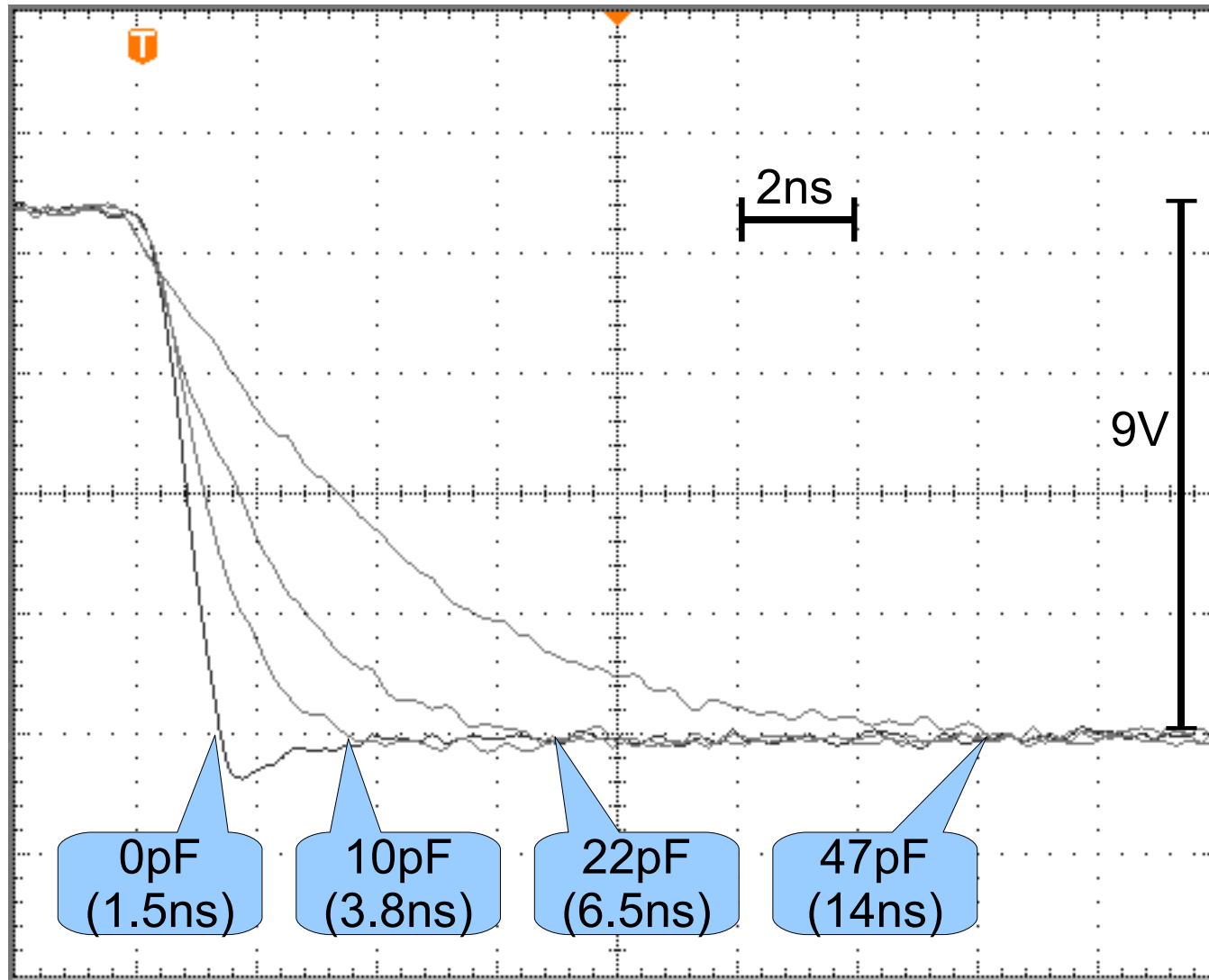

Sequencer - Maximum Speed with C_{load}


150MHz
22pF

0:	jump	1	onabs	29
1:	jump	2	onabs	33
2:	jump	3	offabs	33
3:	jump	4	onabs	29
4:	jump	5	onabs	29
5:	jump	6	onabs	33
6:	jump	0	offabs	33

 

- Summary
 - all parts of chip are working
 - 150MHz max speed
 - 25mA on 9V supply for 22pF load @100MHz
 - 30mA on VDD @100MHz (0.4mW/output)
 - 8ns settling time from 0V to 9V on rising edge @22pF
 - 6.5ns settling time from 9V to 0V on falling edge @22pF
 - long term stress test passed
- Next Steps
 - irradiation (test structures were unaffected by ~1 Mrad)
 - operation with DEPFET matrices

 Drain Current Digitizer - DCD2 DEPFET readout chip



23.04.2008


Steering and Readout Chips
for DEPFET Sensor Matrices

Chair of Circuit Design
University of Heidelberg
Germany

14


DCD Requirements

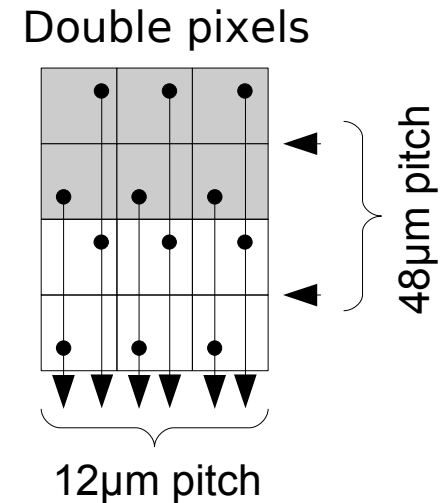- Matrix organized as double pixels ($24\mu\text{m} \times 24\mu\text{m}$)
 - $48\mu\text{m}$ Switcher steering pitch
 - **$12\mu\text{m}$** DCD readout pitch
- $I_{\text{ped}} \sim 30\mu\text{A}$
- $I_{\text{sig}} \sim 6\mu\text{A}$
- Large detector capacity $\sim 40\text{pF}$
 - 2000 pixels + 5cm bus
- Speed goal: 25MHz row rate, 12.5MHz double row rate




DCD features


- UMC 0.18 μ m 1.8V technology
- regulated cascode
- offset subtraction
- two 8bit algorithmic ADC per channel
 - 6.25MHz each, 12.5MHz sampling rate
 - small layout: 110 μ m x 50 μ m
 - low power: 2mW/channel
 - 144 ADCs on final chip, high speed output @600MHz LVDS
- consequent current mode signal processing
- no zero suppression
 - occupancy in ILC so high, that benefit of 0-supp too small
- Bump bonding with pixel logic & ADC placed around pad
- Radiation Hard Design
- NMOS in triple well, guard ring around analog part

 


Block Diagramm

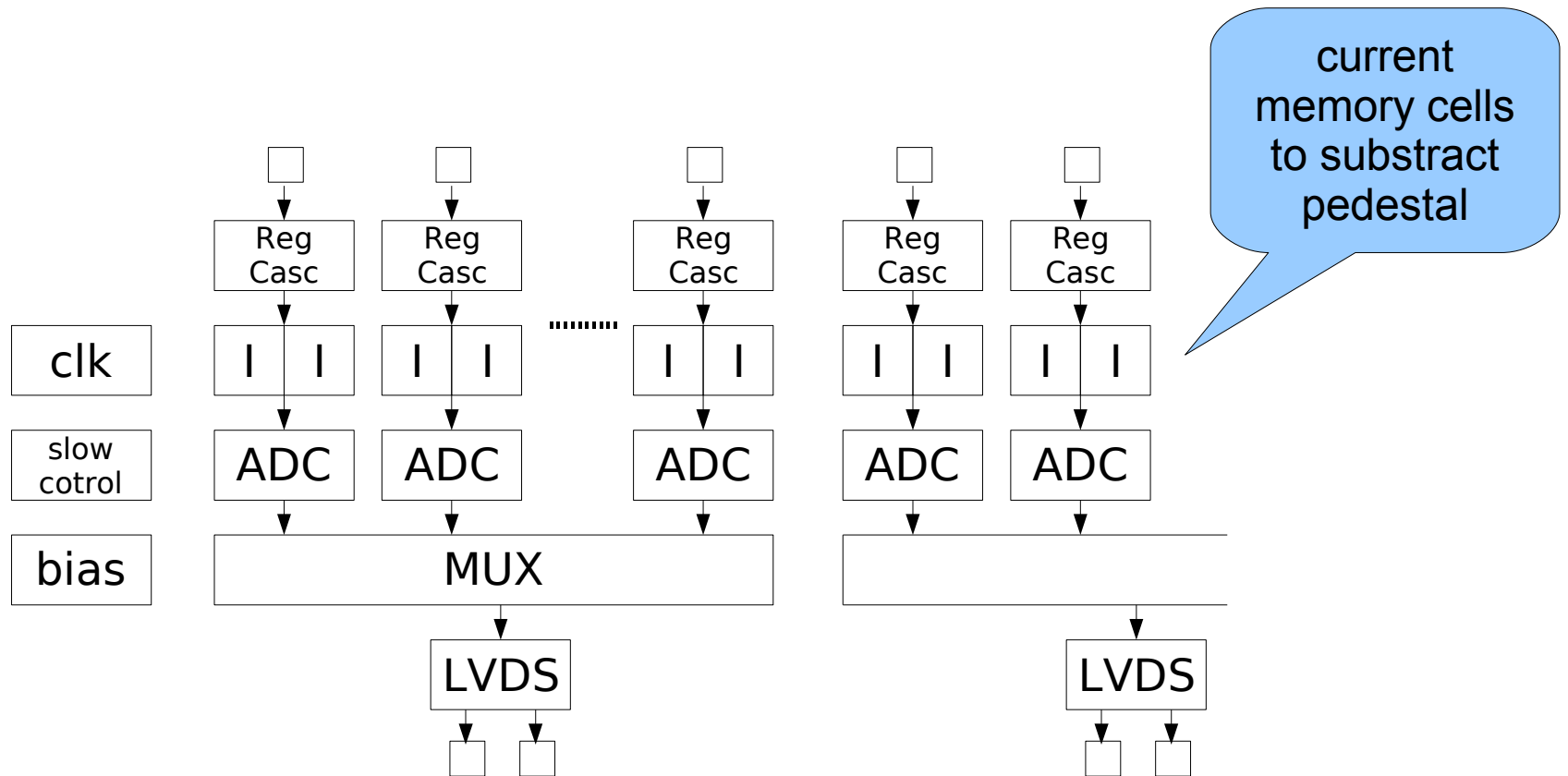


ADC - working principle

 

 
- algorithmic ADC
- insensitive to reference shifts by using 1.5bit



Channel Layout

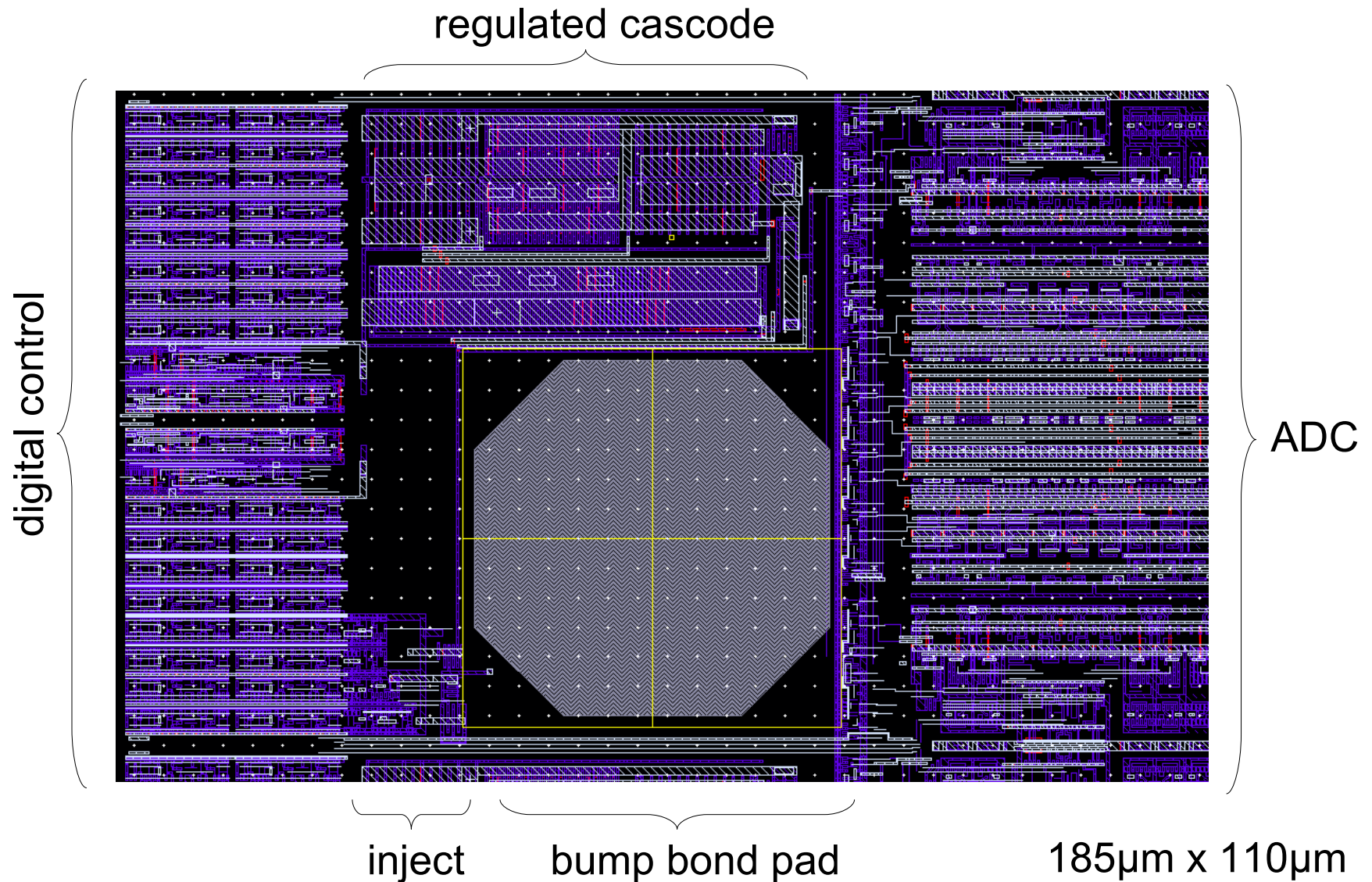

Chip Layout

 

DACs



inputs with ADCs

LVDS outputs

- Designed:
 - Cascode: 1.24mW
 - Curr. Mem. Cells: 0.19mW
 - ADC: 1.97mW
 - LVDS: 0.9mW

 - Total: 4.3mW per channel
- Measured with present settings:
 - Total: 3.54mW per channel



Regulated Cascode

 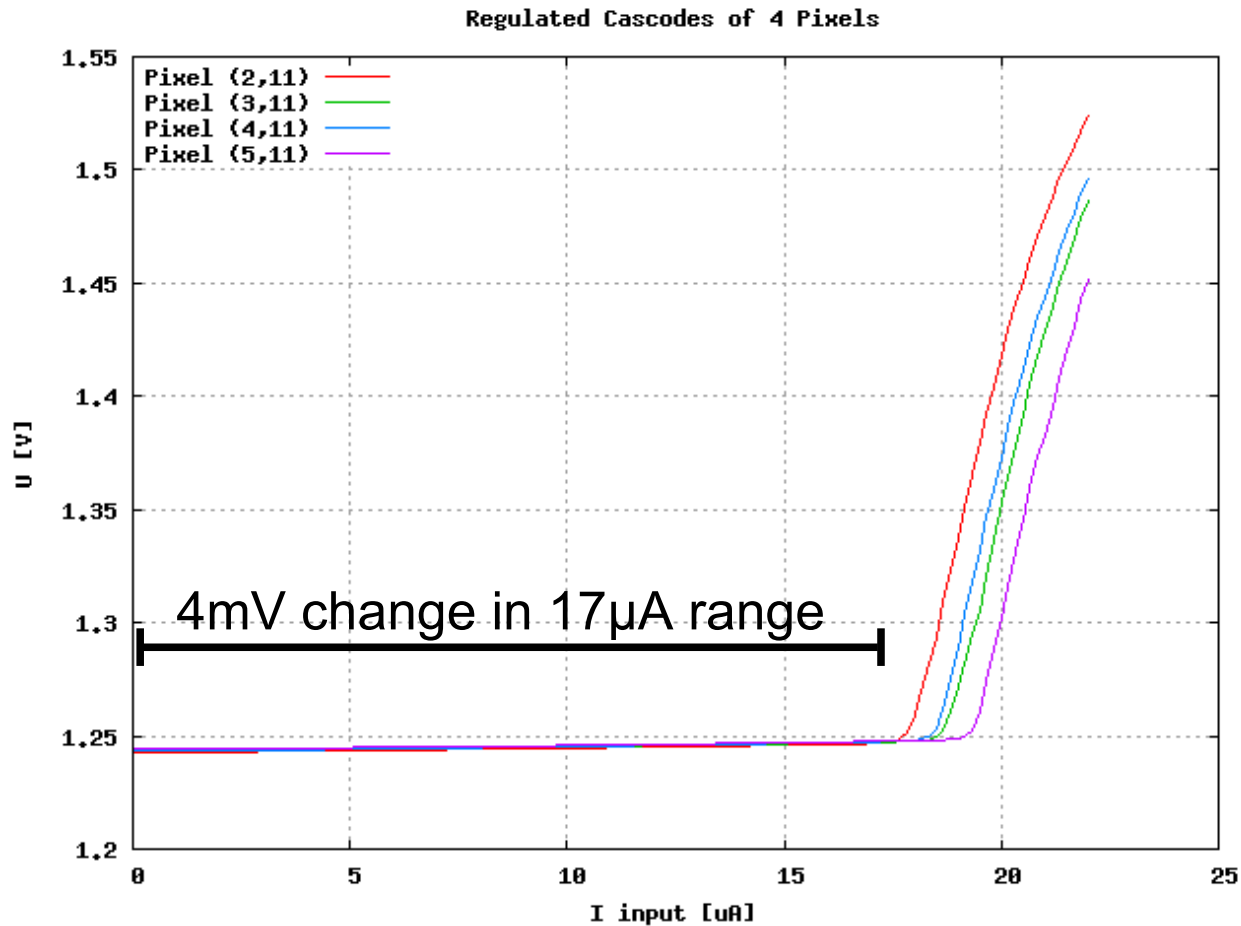

- can regulate for currents up to 17µA
- only 4mV voltage changes



Current Memory Cells

Current Memory Cells of 4 Pixels

  



current memory cell for offset subtraction can store in range $-9\mu\text{A}..9\mu\text{A}$

ADC

 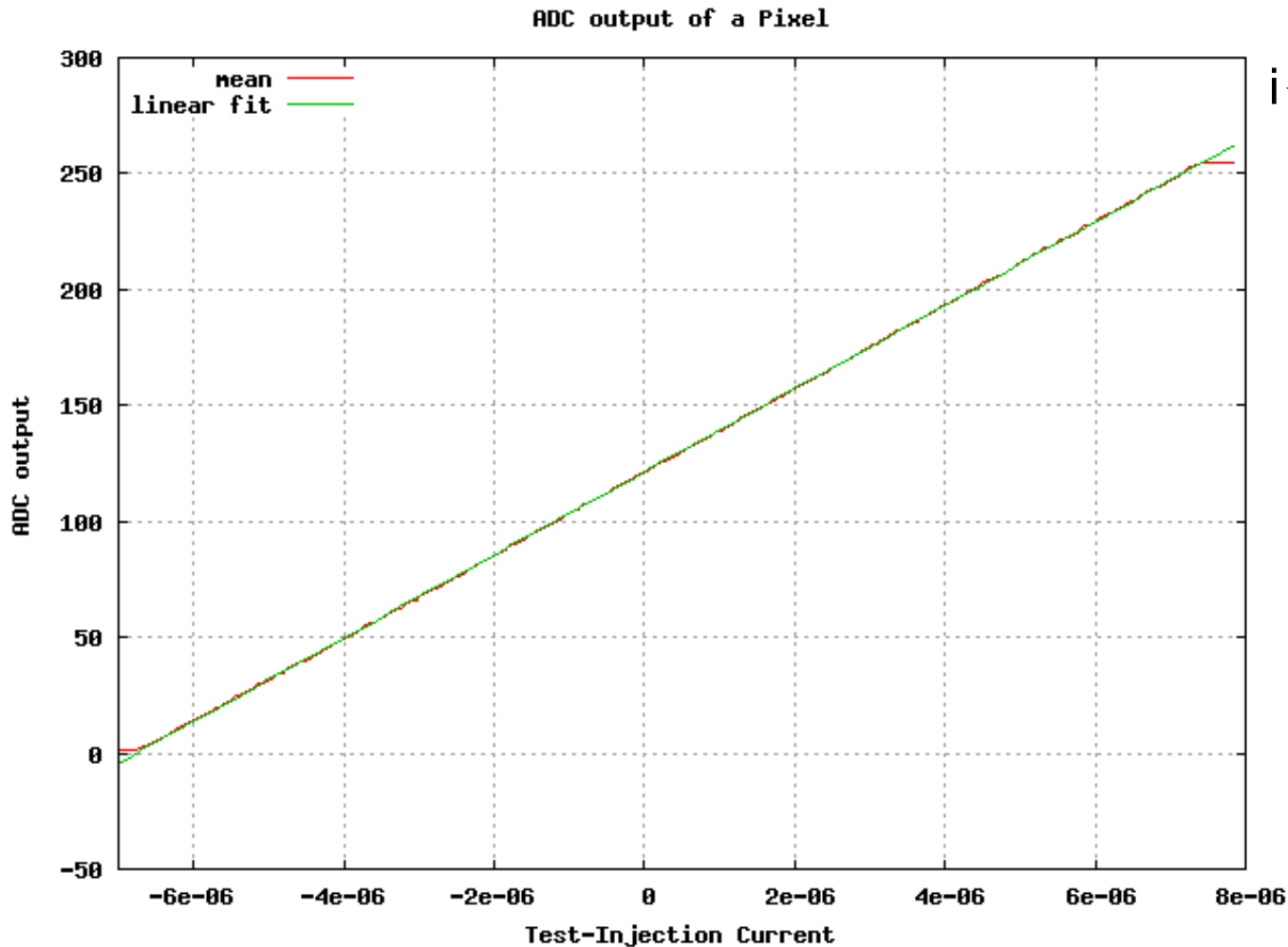

full 8bit ADC range, good linearity of ADC


Pedestal Subtraction

 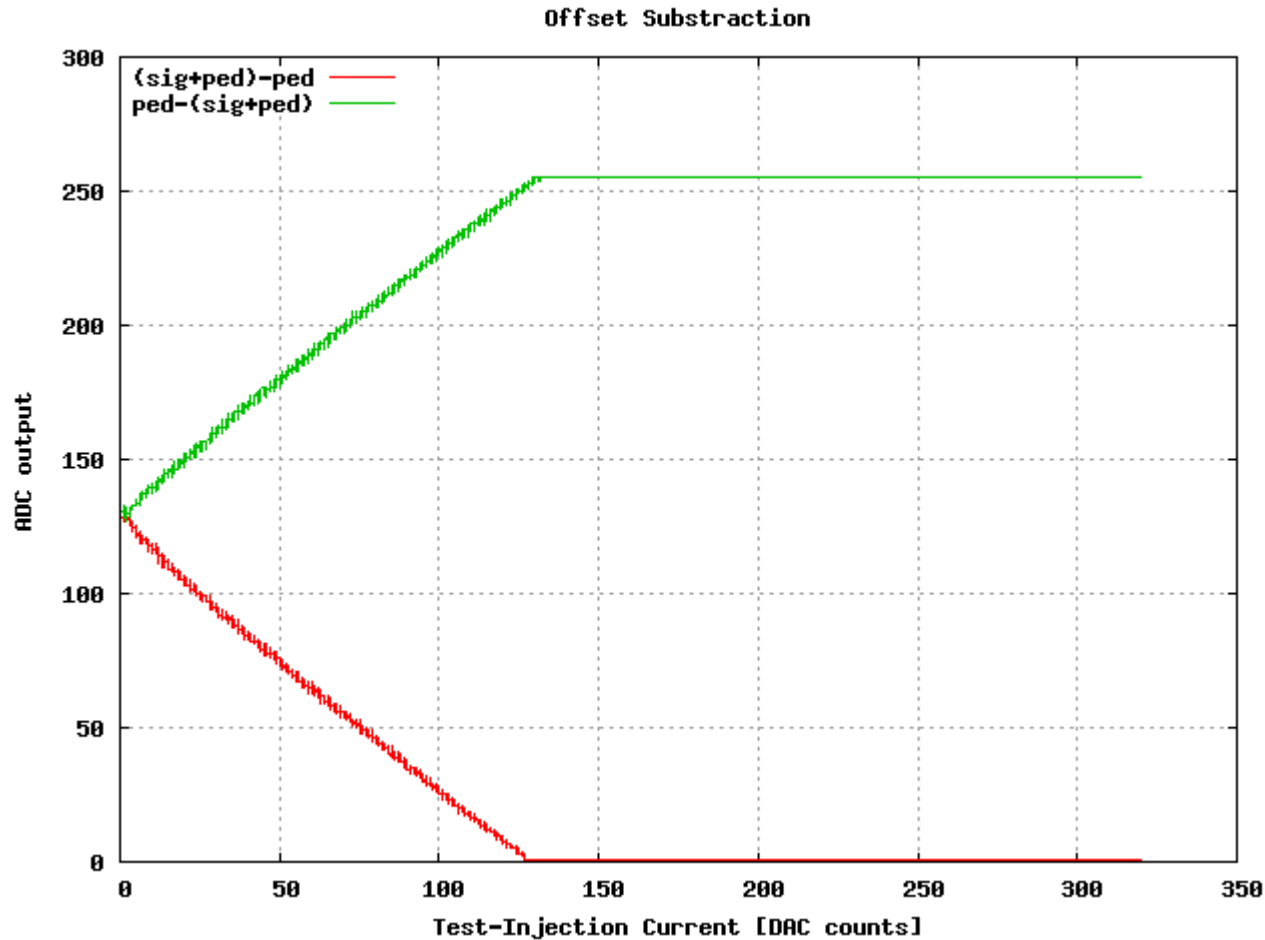

- subtraction working
- design flaw: shifting current subtracted as pedestal
 - only half ADC range available

Current Sampling Speed: First Look

- 44pF: ~ 60ns

 

sampling

sig+ped ●

ped ●


inject

sig+ped ●

ped ●

sig+ped ●


ped ●

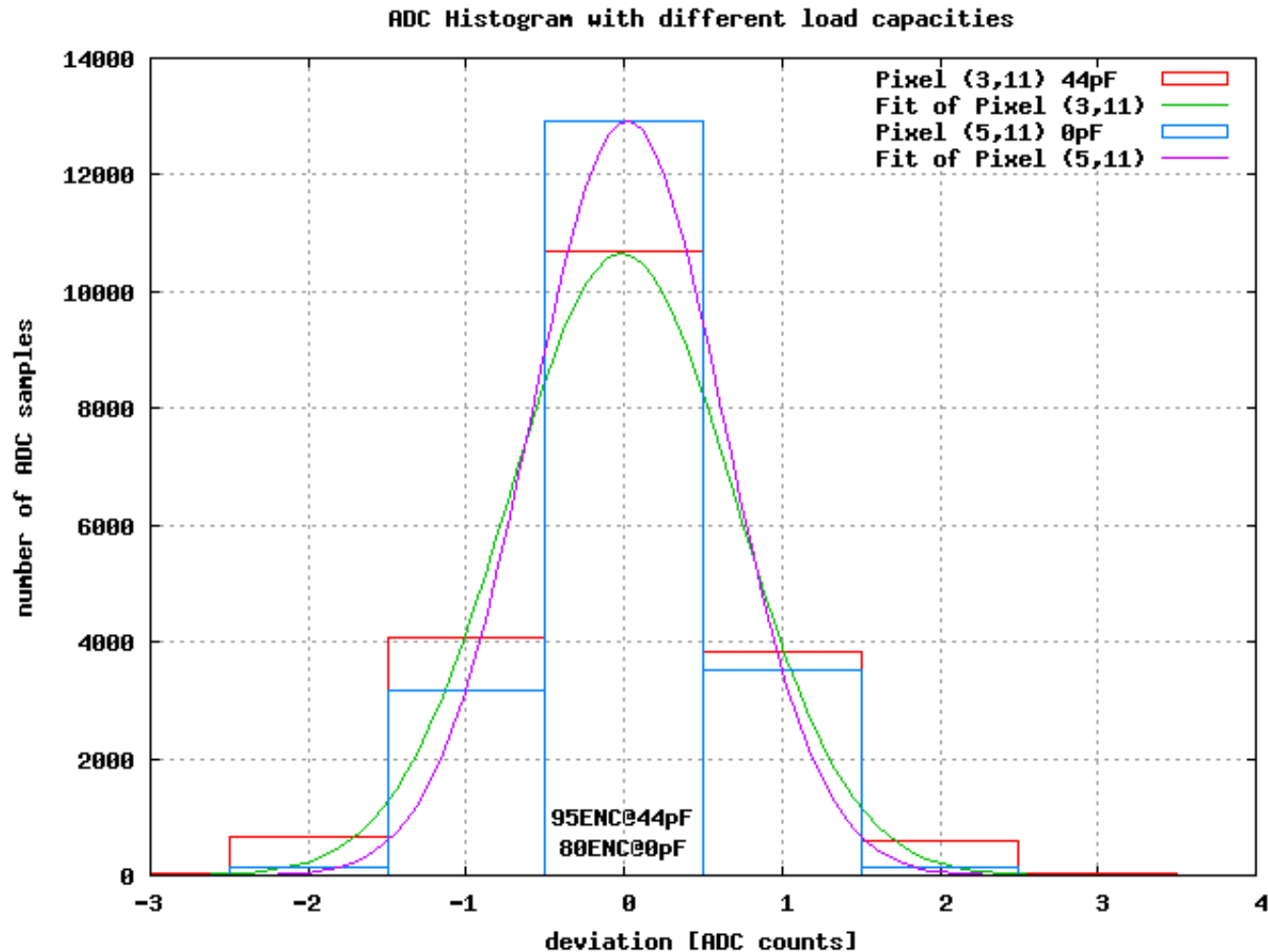

- ENC=95e⁻ (47nA) for 44pF capacitor


High Speed

 - DCD 600MHz clock input divided by 6 for ADC control -> 100MHz
- PCB not designed for high speed -> 48MHz max
- DCD debug mode: clock ADC control externally
 - ADC control runs currently at 48MHz
- High Speed Board is available at Uni-Bonn to run DCD with >600MHz
 - tests start soon




Summary + Next Steps

- Summary
 - Chip working at half of the desired speed right now
 - all digital parts working
 - Regulated Cascode for up to $17\mu\text{A}$ with only 4mV
 - Current memory cells can store in range $-9\mu\text{A}..9\mu\text{A}$
 - ADC
 - full range ok
 - runs currently with half of possible speed
- Next Steps
 - Run DCD2 at 600MHz
 - Run DCD2 with DEPFET-Matrix and Switcher3
 - fix current shifting to digitize full range when in double sampling mode
 - submit full size chip
 - irradiation

 

Bump Bonding Status

 

Schaltungstechnik
und Simulation

Christian Kreidl

christian.kreidl@ziti.uni-heidelberg.de



ILC Vertex Workshop

21.-24.04.2008

Villa Vigoni, Como, Italy

Interconnect Technology

 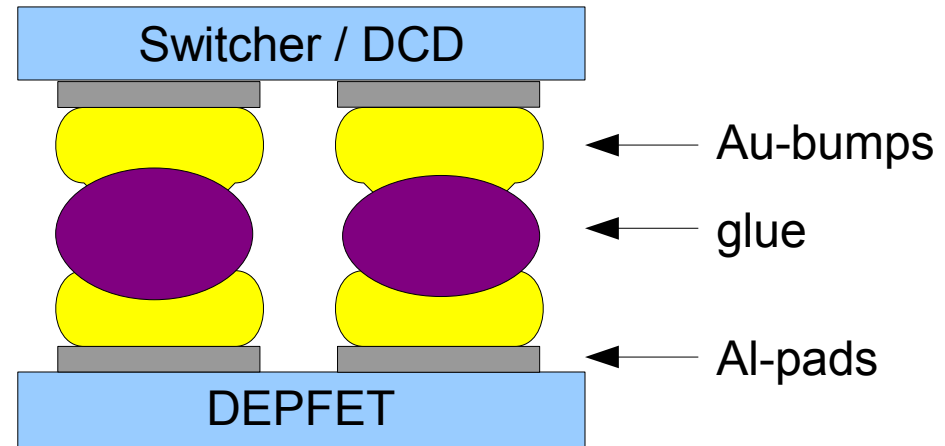- 60 μm bump-pad diameter
- 100 μm pad pitch
- added material:
4,5 μm equivalent Si thickness
across active area




smashed ball, 48 μm free-air-ball, 17,5 μm wire


65 μm smashed
25 μm wire

New Bonder

 - half-automatic machine
 - manual placing and aligning of chip (3min)
 - automatic bondprocess (9min/160bumps)
- full size Switcher3 and DCD2 chips:
 - single die mounting on bonder works
 - programmed bumping works
- wire is sheared off




1 bump

 

2 stacked bumps




bumped chip

 


SuS@Uni-Heidelberg

DCD dummy chip with 224 bumps

 


Dummy Chips

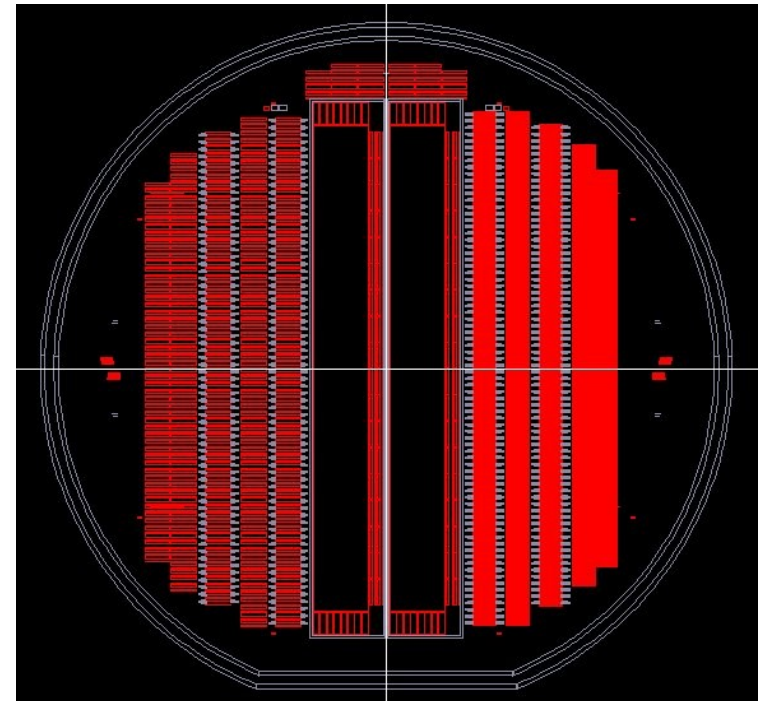- several wafers with dummy chips available
- manufactured in HLL, Munich (DEPFET process)
- snake structures for interconnect testing
- 130 full size Switcher3 chip-substrate pairs
- 150 full size DCD pairs
- 2 full size ILC dummy modules
- silicon chips with Al pads
- one metal layer




Switcher3 dummy

 

SuS@Uni-Heidelberg

Switcher3 dummy chip and substrate
164 pads

DCD dummy

 

SuS@Uni-Heidelberg

DCD dummy chip and substrate
224 pads


ILC Dummy

- full size ILC module (mechanical demonstrator)
- 16 DCD
- 36 Switcher3
- 9488 bump-bonds
- 11,9cmx1,6cm



Dummy Chip Flipping


 
- flipped Switcher3 and DCD dummies
- all bumps connected
- no shorts
- R of traces $>$ R of bump bonds



flipped Switcher3 dummy


Triple Dummies

  - to learn how to flip low chip-pitch
- chips broke due to non-flat bond head
- but flipping pitch is possible



Next steps

 - flip some more chips
- flip on tripple substrate
- create ILC module with Switchers and DCDs



Thank you for
your attention!

