



SKIROC ADC measurements and cyclic ADC development @ LPC Clermont-Ferrand

Laurent ROYER, Samuel MANEN

IN2P3

INSTITUT NATIONAL DE PHYSIQUE NUCLÉAIRE
ET DE PHYSIQUE DES PARTICULES




Royer @ Calice/Eudet electronic meeting Orsay June 2008




Reminder: one channel of SKIROC

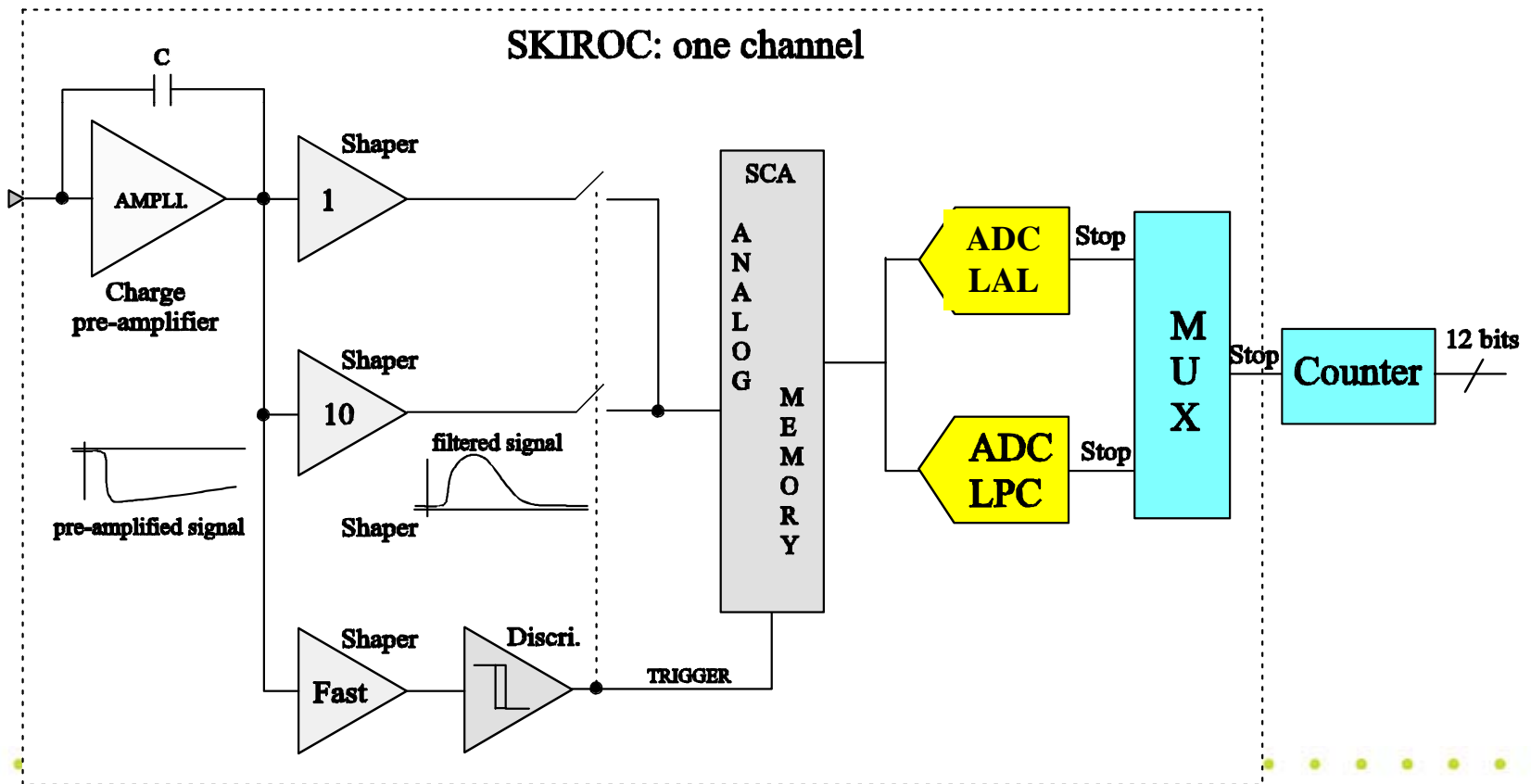- Two ramp ADC: one from LAL, one from LPC
- Resolution of 12 bits, $80\mu\text{s}@50\text{MHz}$
- Mux. to select data output with slow control
- Power pulsing implemented on ADC





Setup of test bench @ LPC

 

Main difference with LAL setup: external reference ADC to acquire the analog probe signal



Setup of test bench @ LPC

- Use of an external ADC to acquire the input of Skiroc ADC through the analog probe


- Automatic test with a single PC to control via 3 USB ports:

- SKIROC
- the pulse generator
- The reference ADC

With a linear probe buffer & ADC AD7684

Function transfer of ADC under test:
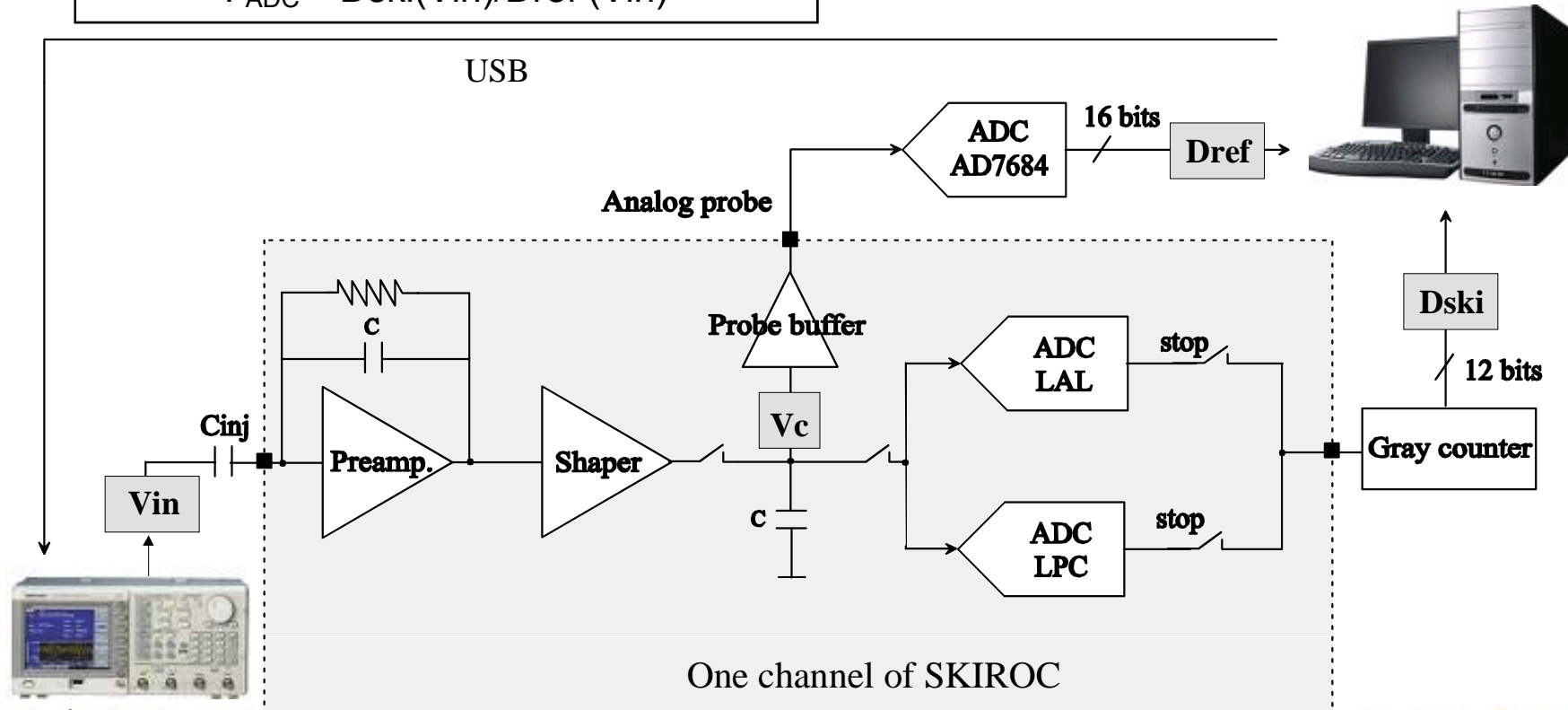
$$F_{ADC} = D_{ski}(V_{in})/D_{ref}(V_{in})$$




Pulse generator



Simulated linearity of the probe buffer



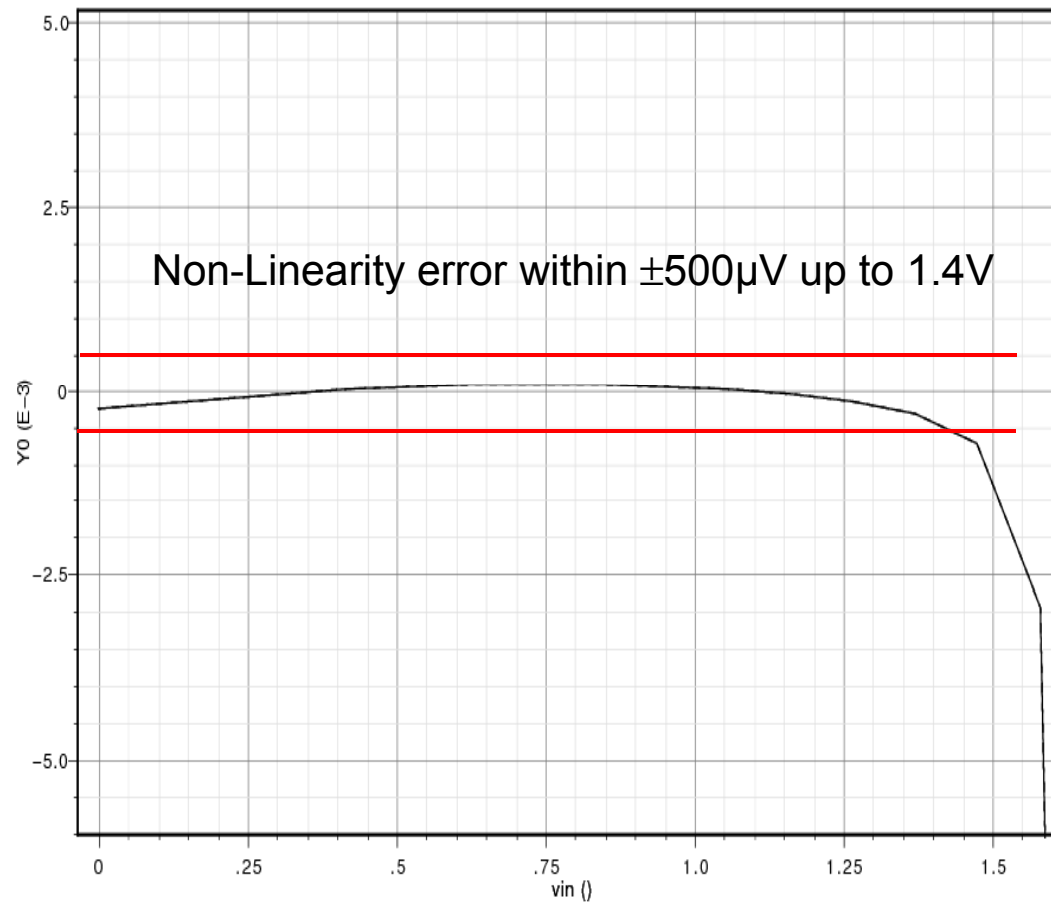
In simulation, no significant non-linearity introduced by the probe buffer





Pedestal measurements

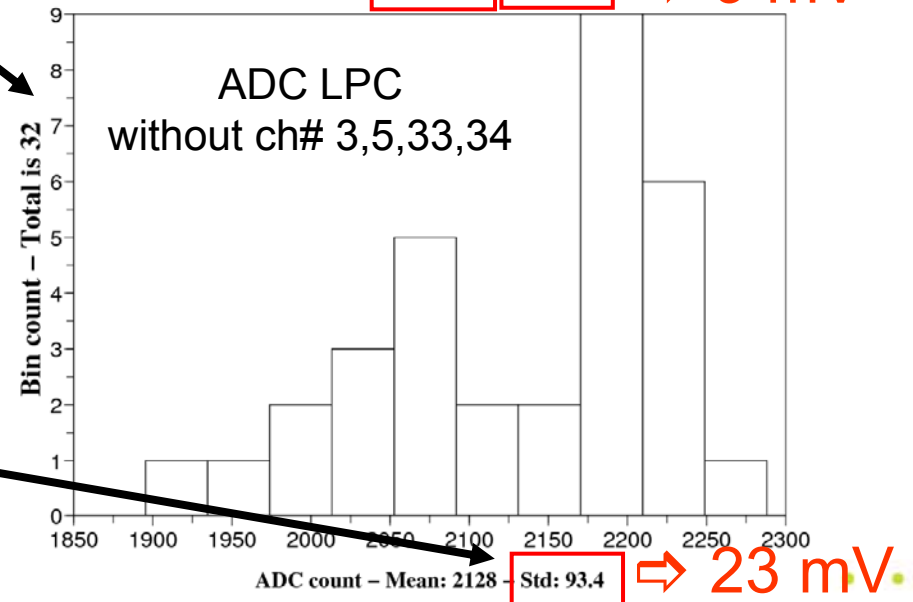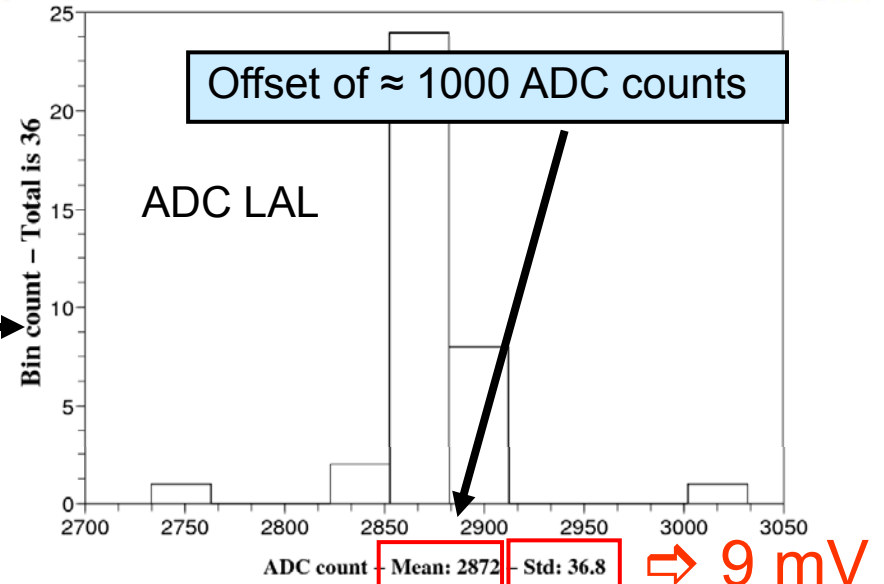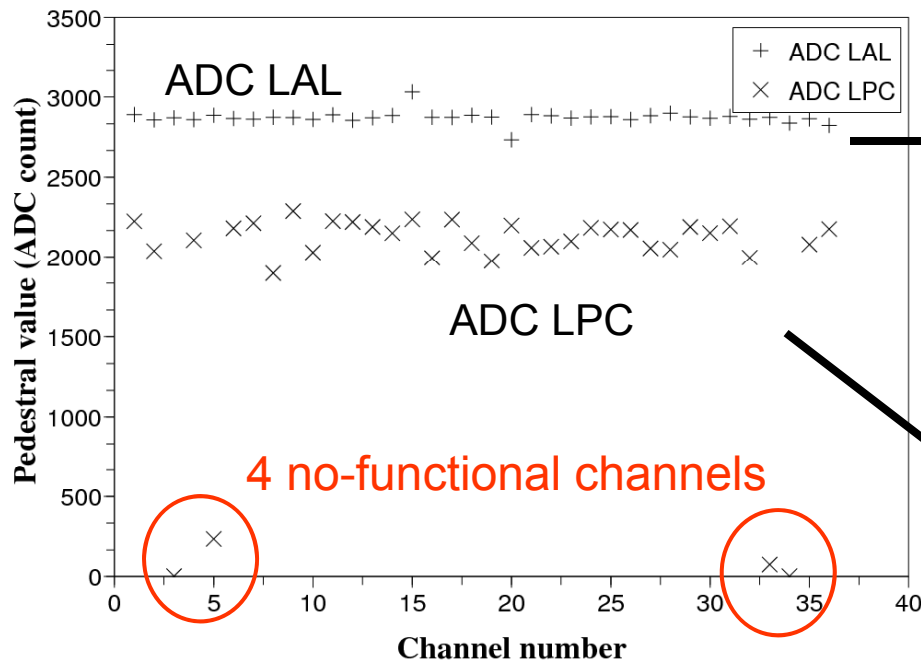Measurements @ $\frac{1}{2}$ full dynamic range
(≈ 2000 ADC counts)







- Pedestal dispersion mainly due to comparator offsets
- Latest version comparator designed @ LPC has offset dispersion lower than 5mV (standard deviation)



Noise measurements



No input signal

0.7V input pulse voltage

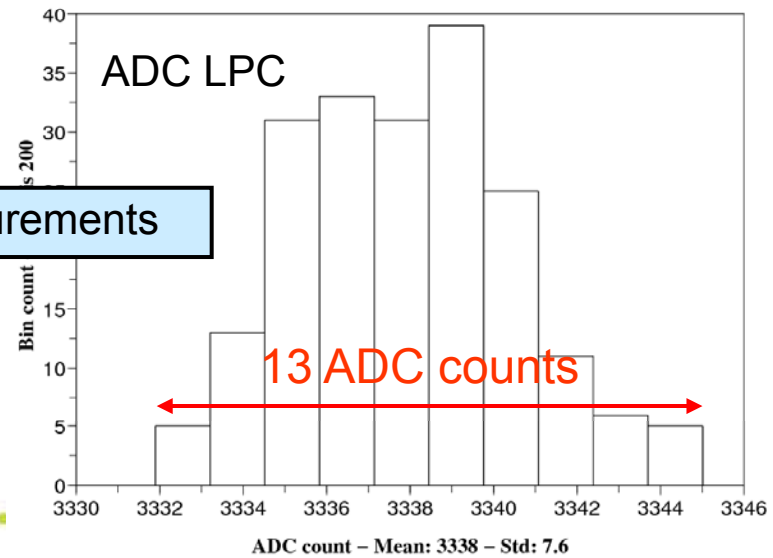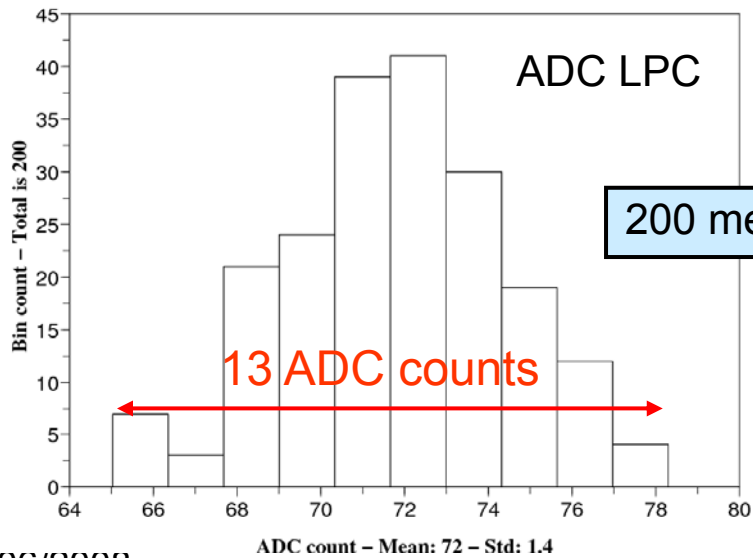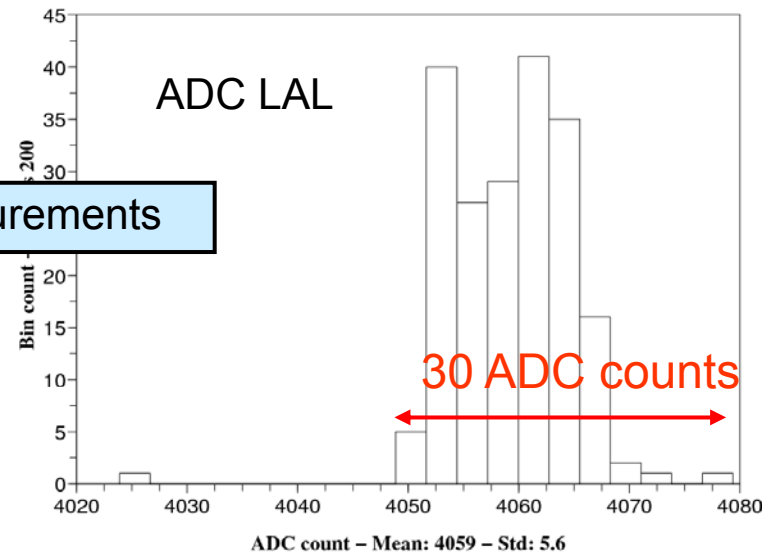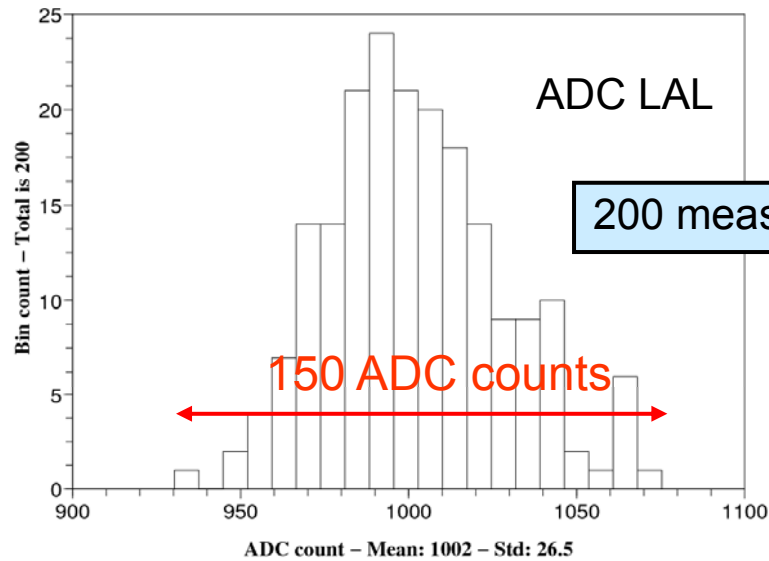




Linearity measurements

 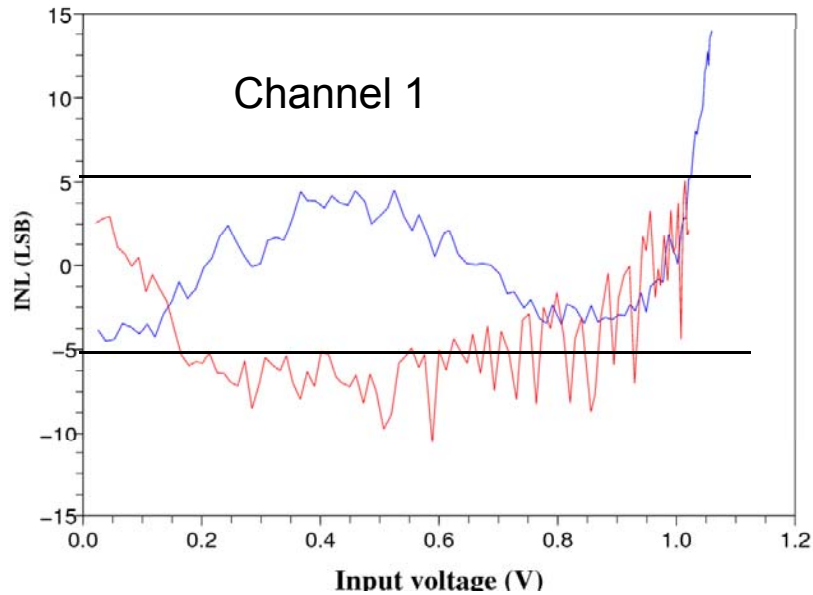

Red: ADC LAL
Blue: ADC LPC


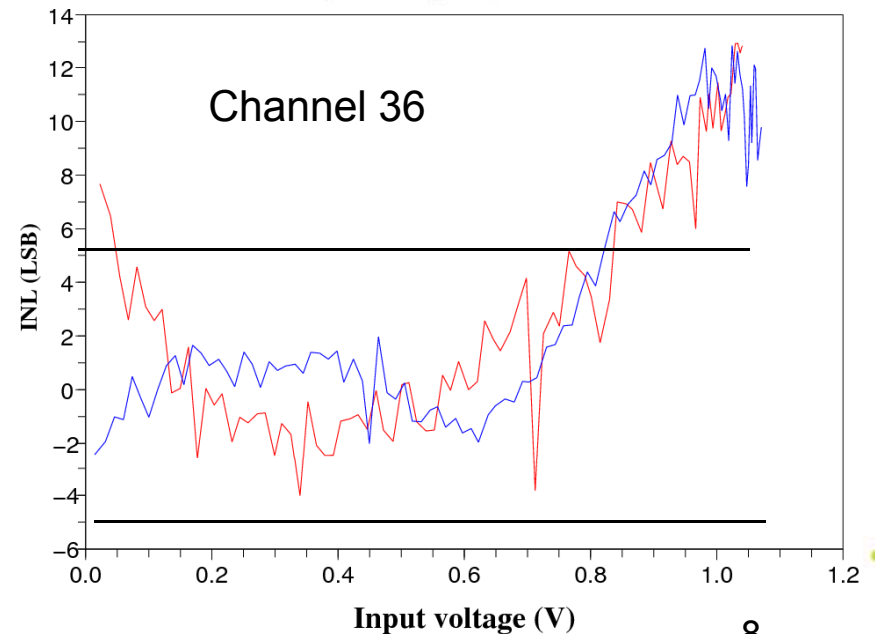
- 200 steps from 0 to 1.1V, mean value of 10 meas./step
- Non-Linearity within ± 5 LSB up to ≈ 0.8 V
- Nearly similar curves for the 2 ADCs
 - Linearity performance limited by the setup of the test ??





A 12-bit cyclic ADC (1)

- A 12-bit cyclic ADC sent to fabrication the 21th of March
- Delivery expected this week
- ADC designed with the validated building blocks (Amplifier & Comparator) of our 10-bit pipeline ADC (published in IEEE NS in June 08)
- Advantages of the cyclic architecture:
 - Small area: $(700 \times 250) \mu\text{m}^2$
 - One ADC/channel for the final 64ch. chip
 - Intrinsic serial output data
 - Good tradeoff between speed, resolution & consumption

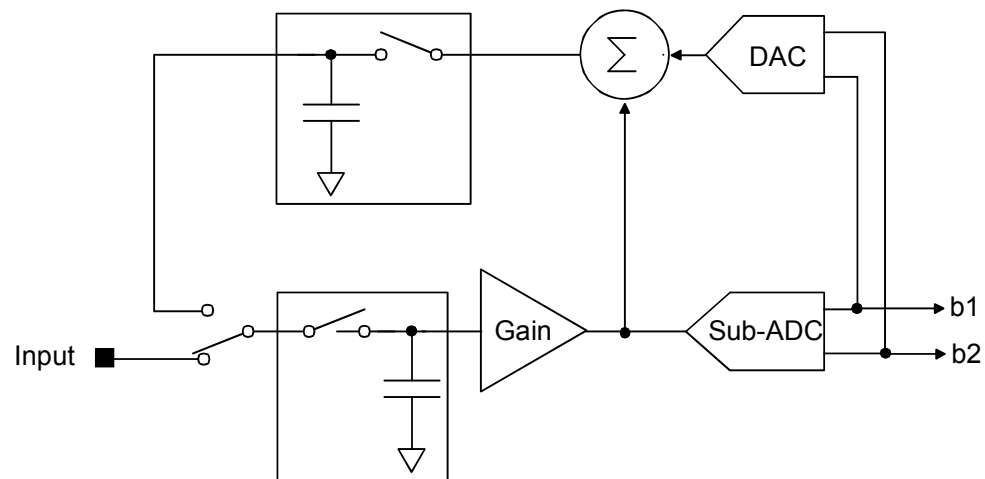 



Conclusion

SKIROC measurements:

- Test bench in Clermont is now operational (thanks to Mowafak, Francois, Julien @ LAL)
- Preliminary results @ LPC show:
 - Lower pedestal dispersion for ADC LAL but offset
 - LAL ADC noisier than LPC one
 - Similar linearity for both ADC with resolution limited to ≈ 9 bits
- Discussion with LAL required :
 - To compare LAL/LPC results
 - To understand results (pedestal offset, noise vs amplitude, non-linearity...)
 - To program complementary meas.
 - Power pulsing
 - Improved linearity meas.
 - ...

Cyclic ADC:

- Our best candidate for the final 64-channels VFE chip
- Performance of the 1st prototype evaluated in June/July





SPARE

02/06/2008



Linearity measurements

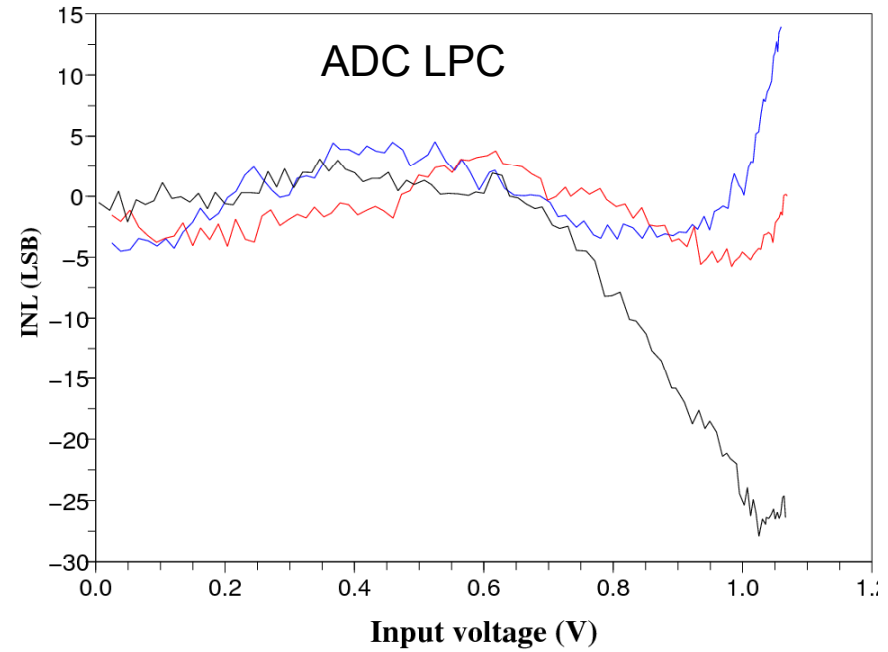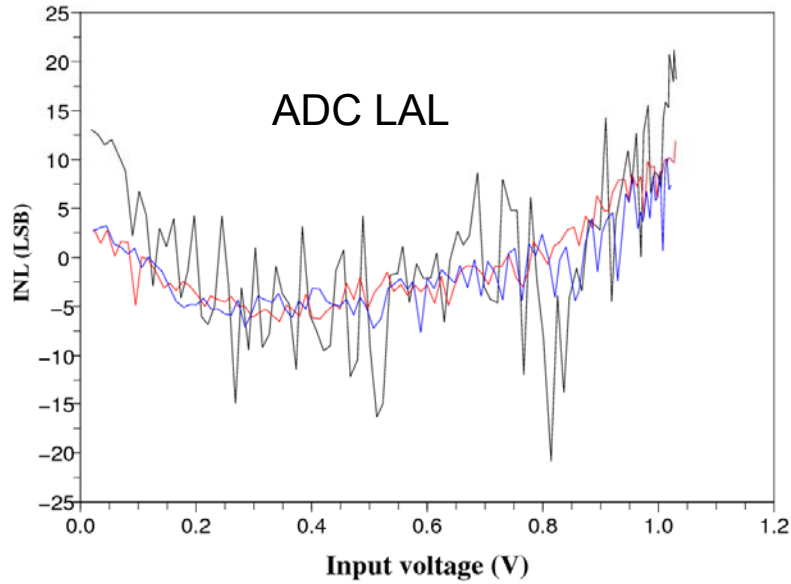



Reminder: one channel of SKIROC

