



# A 12-bit cyclic ADC dedicated to the VFE electronics of Si-W Ecal

Laurent ROYER, Samuel MANEN  
LPC Clermont-Ferrand


**IN2P3**

INSTITUT NATIONAL DE PHYSIQUE NUCLÉAIRE  
ET DE PHYSIQUE DES PARTICULES






# VFE electronics of Si-W Ecal

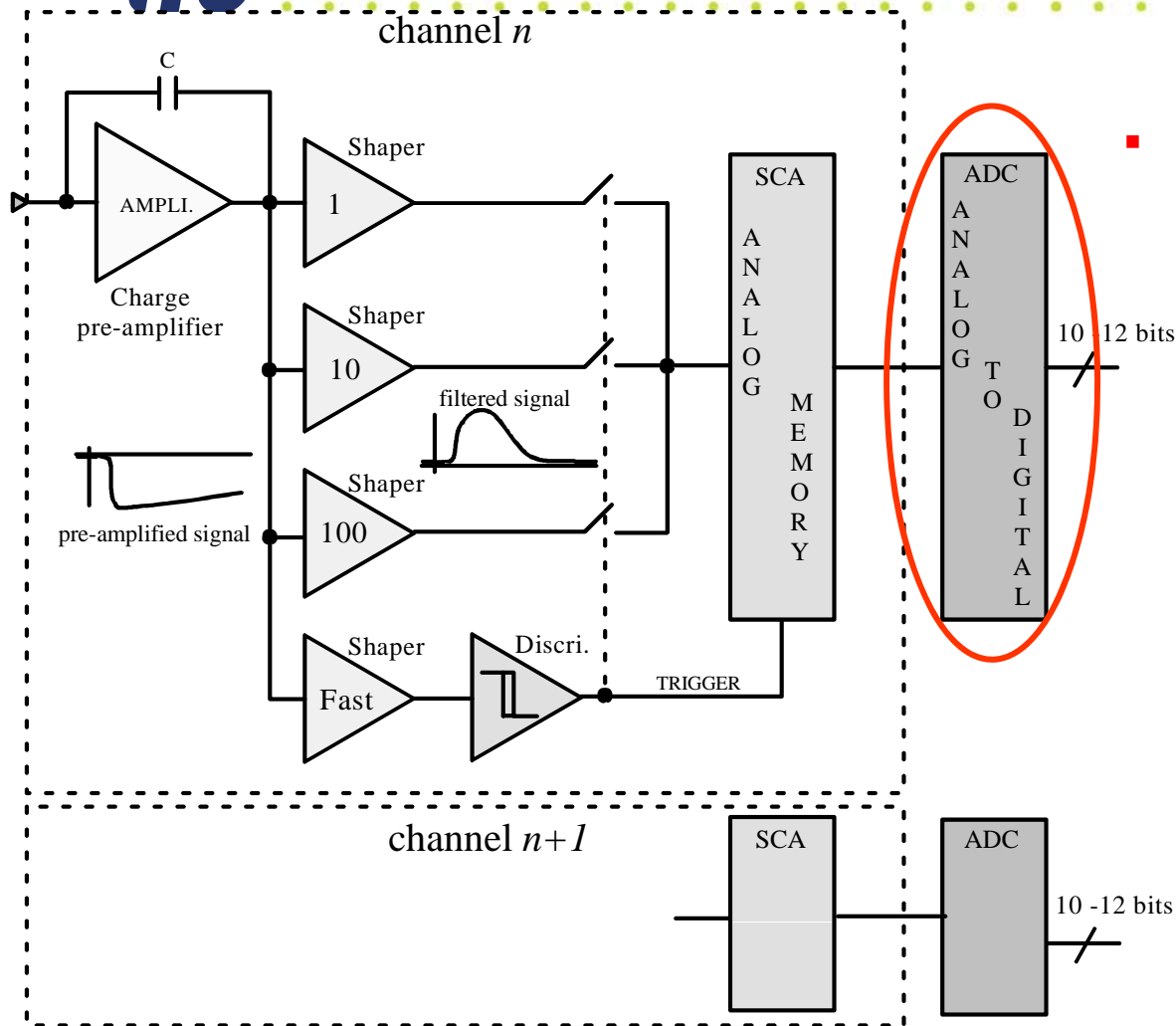

 
## ▪ Main requirements for the ADC:

- Ultra low power:
  - **2.5 $\mu$ W/ch** (10% of the VFE power budget)
  - **Power pulsing needed**
- Resolution:
  - **10 bits if 3-gain shaping**
  - **12 bits if 2-gain shaping**
- Time of conversion: time budget of 500  $\mu$ s to convert all data of all triggered channels
- Die area:
  - **as small as possible...**
  - (0.225 mm<sup>2</sup> per each channel of Skiroc without ADC)**





# Proposal: one ADC per channel

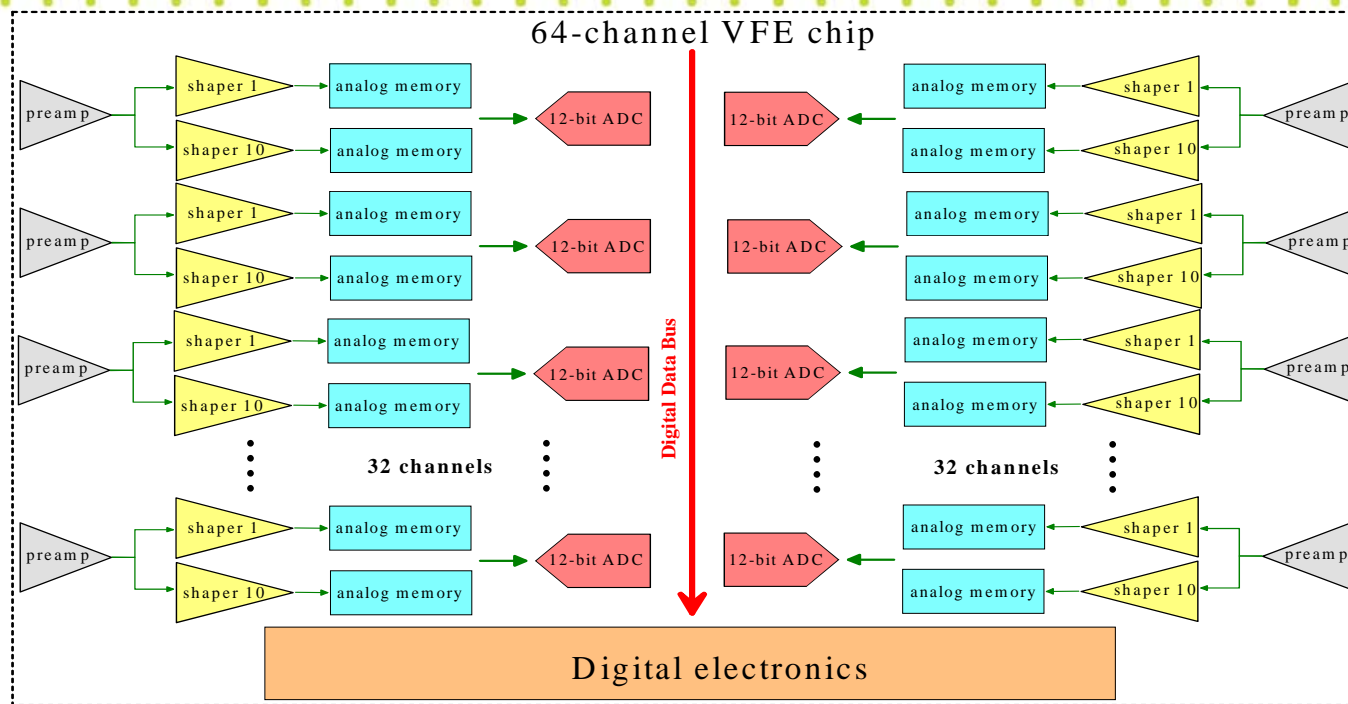


## With one-ADC-per-channel architecture:

- ☺ Short analog sensitive wires from memory to ADC
- ☺ A digital Data Bus far from sensitive analog signals } ⇒ Integrity of analog signals saved
- ☺ Only ADCs of triggered channels powered ON ⇒ Power saved
- ☺ Conversions of channels done in parallel ⇒ No "fast" ADC required
- ☹ Pedestal dispersion of ADC "added" to the dispersion of the analog part .... but calibrated




# Two candidates for the architecture of the ADC

**Pipeline ADC**

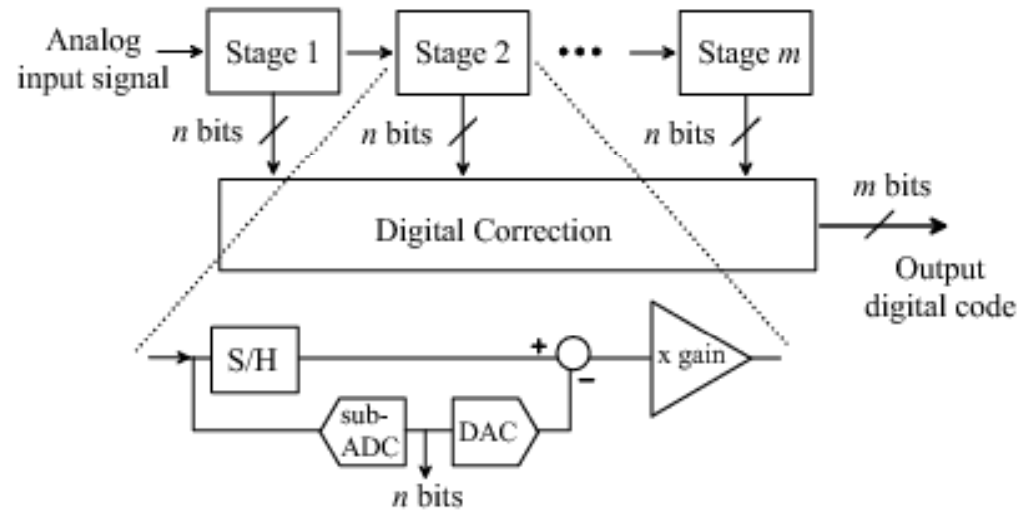

**Cyclic ADC**

 



# Pipeline and Cyclic performance

	Cyclic	Pipeline
Resolution	12 bits	12 bits
Time for one conversion	12 clock periods	1 clock period <sup>(1)</sup>
Power consumption (norm.)	1	12 down to $\approx 6$ <sup>(2)</sup>
Integrated power cons. (time * power cons.)	12	12 down to $\approx 6$ <sup>(2)</sup>
Area	1	12 down to $\approx 10$ <sup>(3)</sup>

<sup>1</sup> after a latency of 12 clocks period for the first conversion

<sup>2</sup> if a power optimization on each stage is implemented


<sup>3</sup> if a capacitor size optimization per each stage is implemented


 
# A 12-bit cyclic ADC (1)

The 12-bit cyclic ADC prototype designed @ LPC Clermont:

- Sent to fabrication in March 08, 10 chips delivered with delay in July
- Technology: 0.35  $\mu\text{m}$  CMOS Austriamicrosystems
- ADC designed with the validated building blocks (Amplifier & Comparator) of our 10-bit pipeline ADC (published in IEEE NS in June 08) but optimized for the 12-bit precision requirement
  - enhanced building blocks tested with a dedicated chip (July 07)
- 1.5 bit architecture (2 bits per cycle)
  - relaxed constraints on offsets of comparators
- External bits processing (deserializer & 1.5bit algorithm)
- Power pulsing system implemented



Layout of the chip





# A 12-bit cyclic ADC (2)

- Performance of the cyclic ADC:
  - Improved architecture: calculation of two bits during one clock period
  - Time of conversion: 7 $\mu$ s w/ 1MHz clock freq.
  - 1 ampli. + 2\*2 comp. + 2 capacitors arrays
  - Consumption: 4 mW/3.5V
  - Integrated cons. with power pulsing:
    - ✓ 0.7  $\mu$ W with analog memory depth of 5 events
    - ✓ 2.2  $\mu$ W with analog memory depth of 16 events
  - Area: 0.175 mm<sup>2</sup>



	Optimized Cyclic	Pipeline
Resolution	12 bits	12 bits
Time for one conversion	<del>12</del> 7 clock periods	1 clock period <sup>(1)</sup>
Power consumption	<del>4</del> $\approx$ 1.1	12 down to $\approx$ 6 <sup>(2)</sup>
Integrated power	<del>12</del> $\approx$ 7.7	12 down to $\approx$ 6 <sup>(2)</sup>
Area	<del>1</del> $\approx$ 1.5	12 down to $\approx$ 10 <sup>(3)</sup>

2 conversion phases with a single ampli.

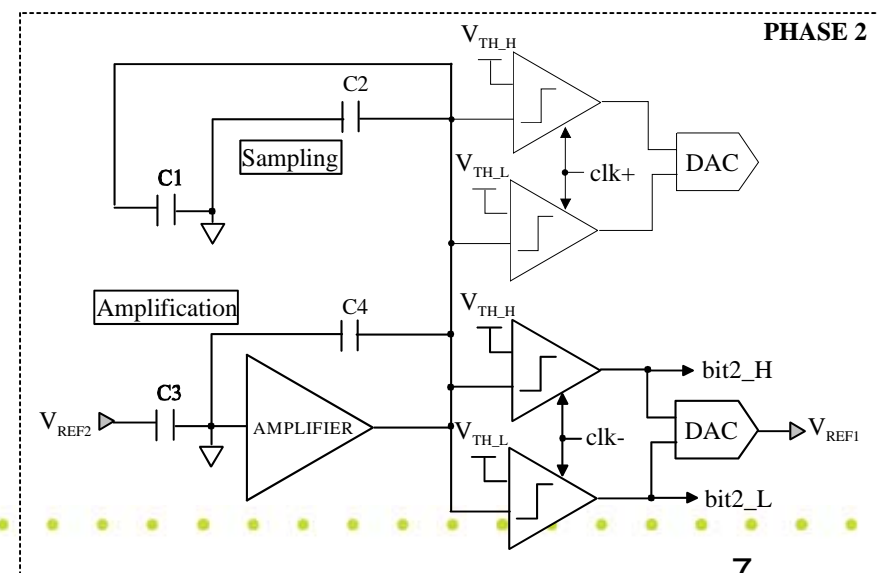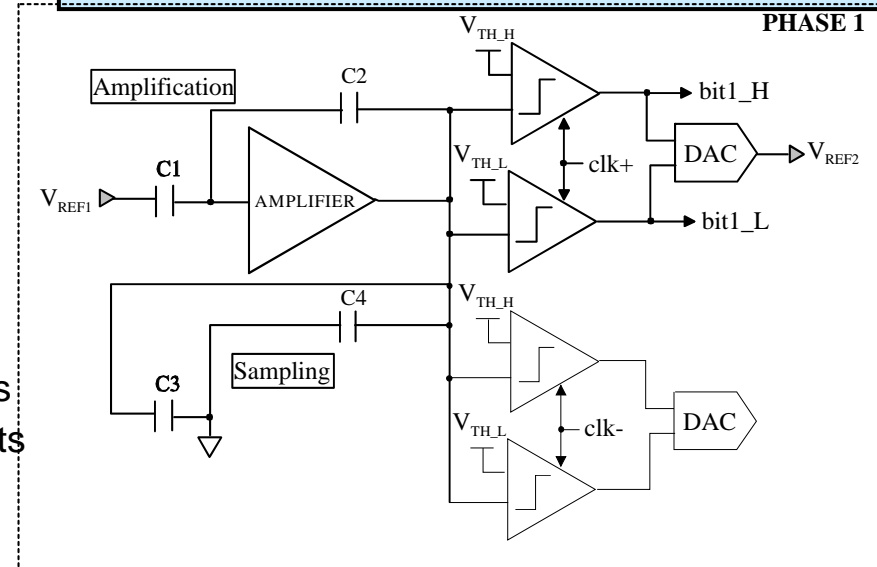




# Very First results of measurement

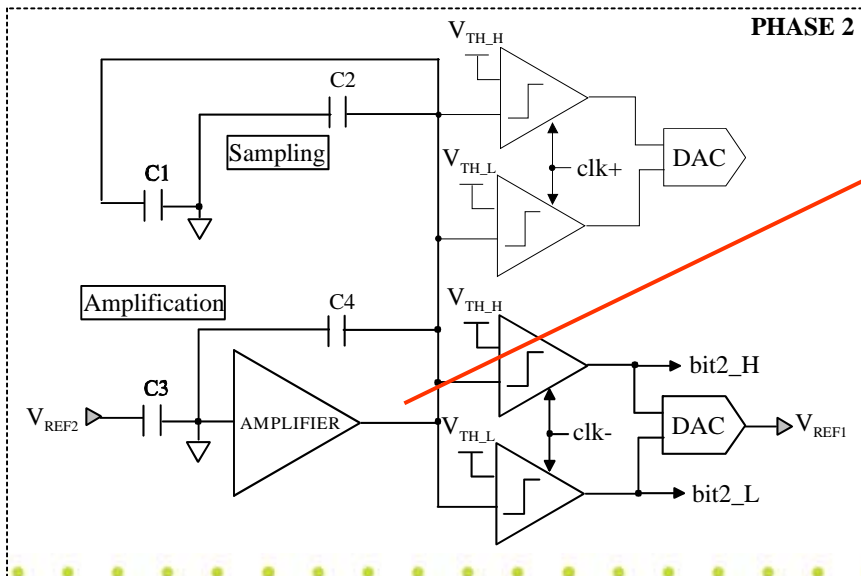 



Oscillogram of the chip under test

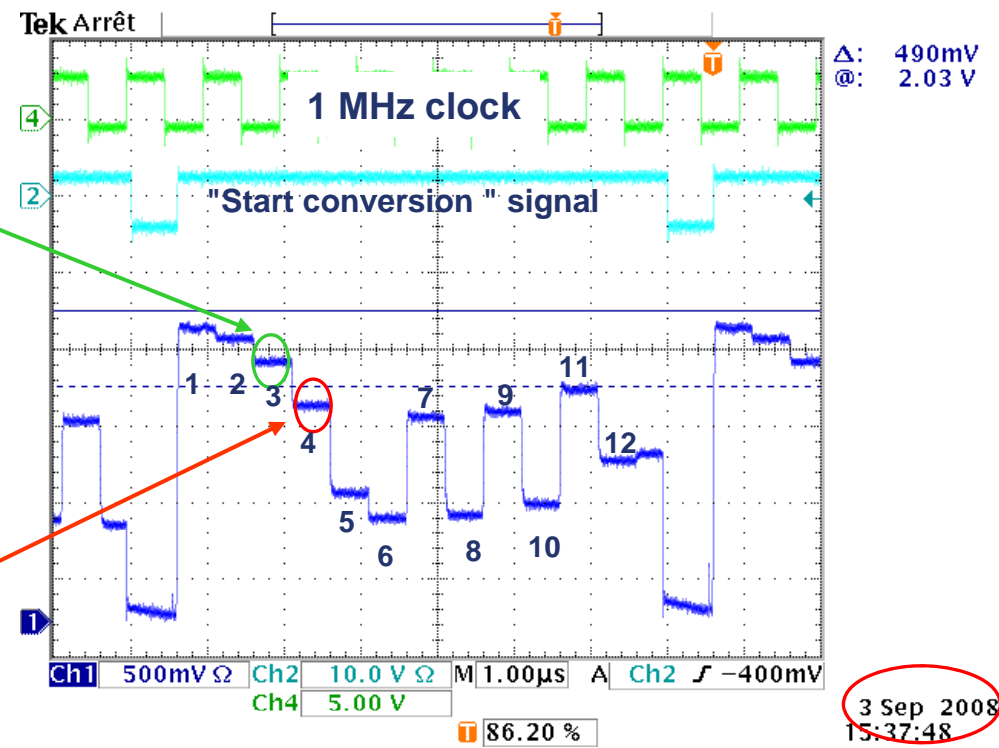






# Very First results of measurement

 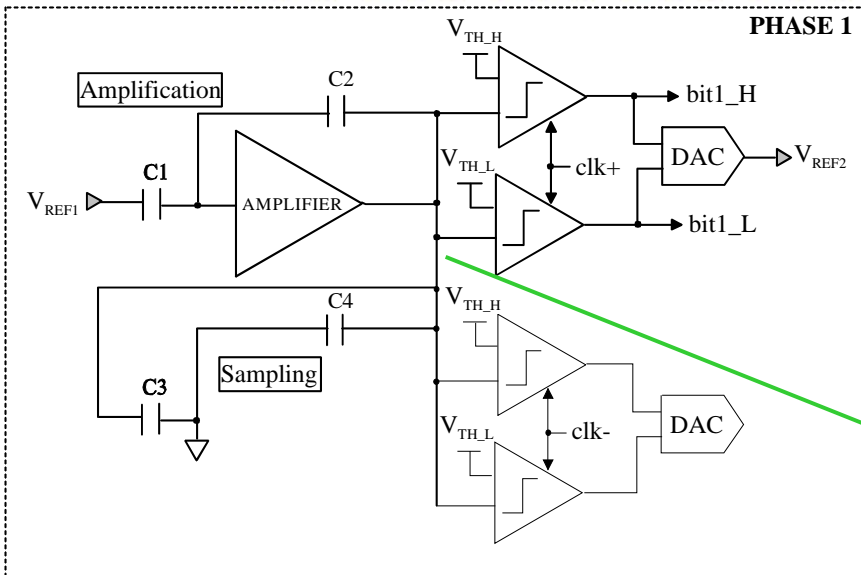


Oscillogram of the chip under test

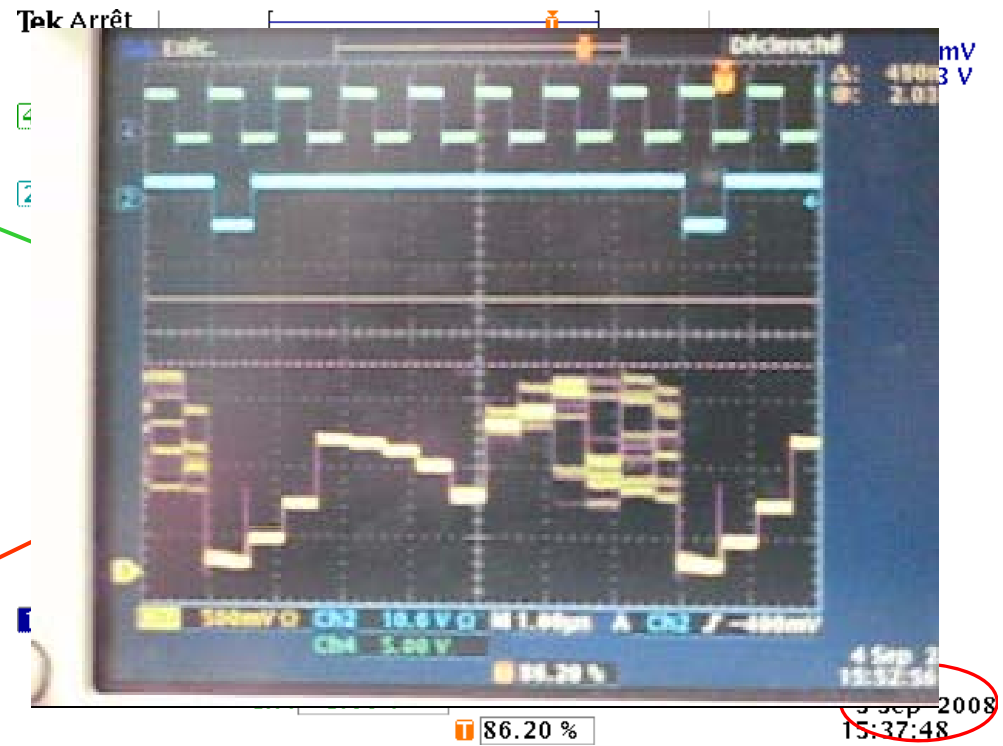




# Measured Integral Non-Linearity (INL)

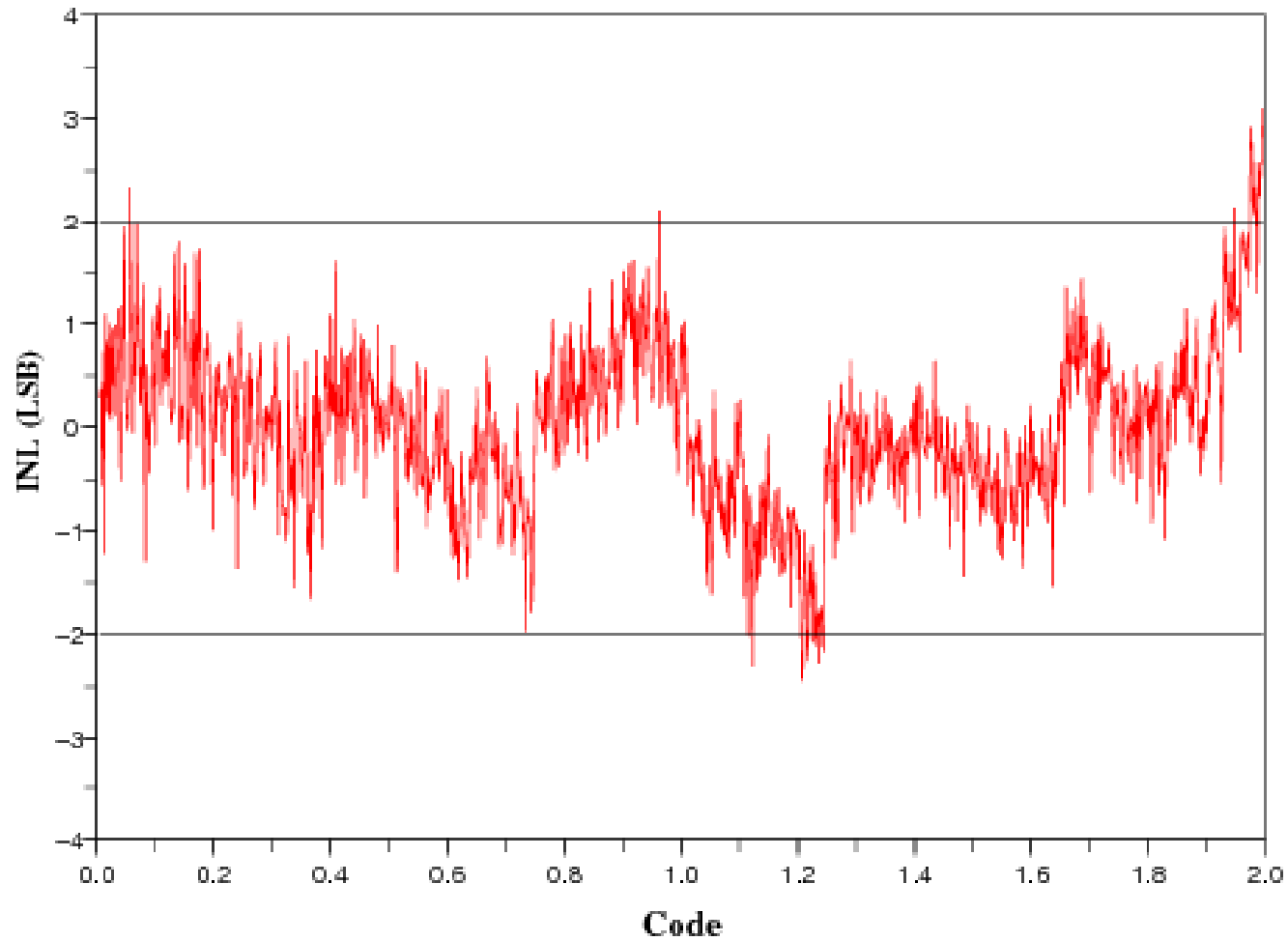




## Both simulated and measured INL

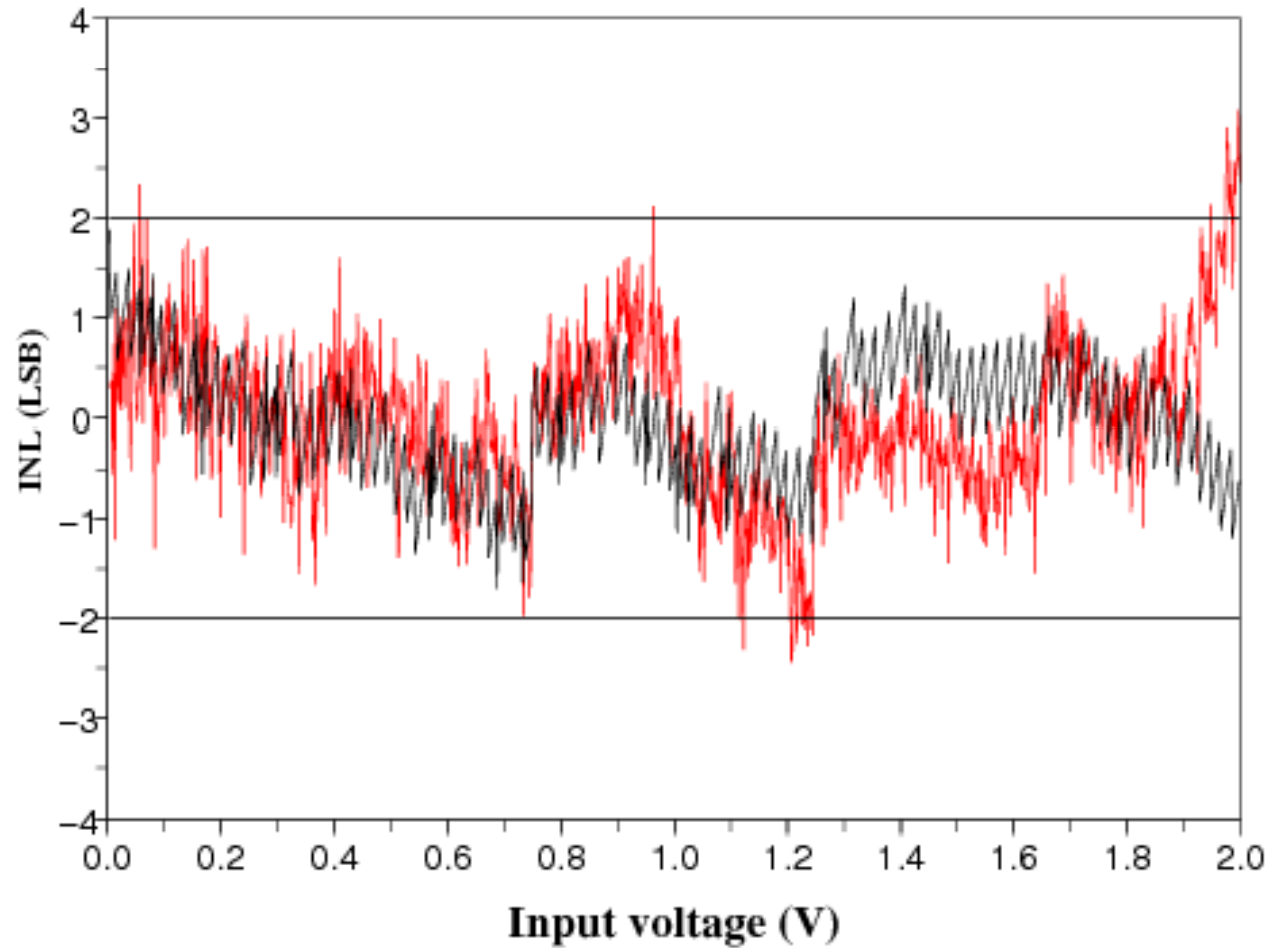



 
# Measured Differential Non-Linearity (DNL)





# Noise measurement

## Code fluctuation @ 1V

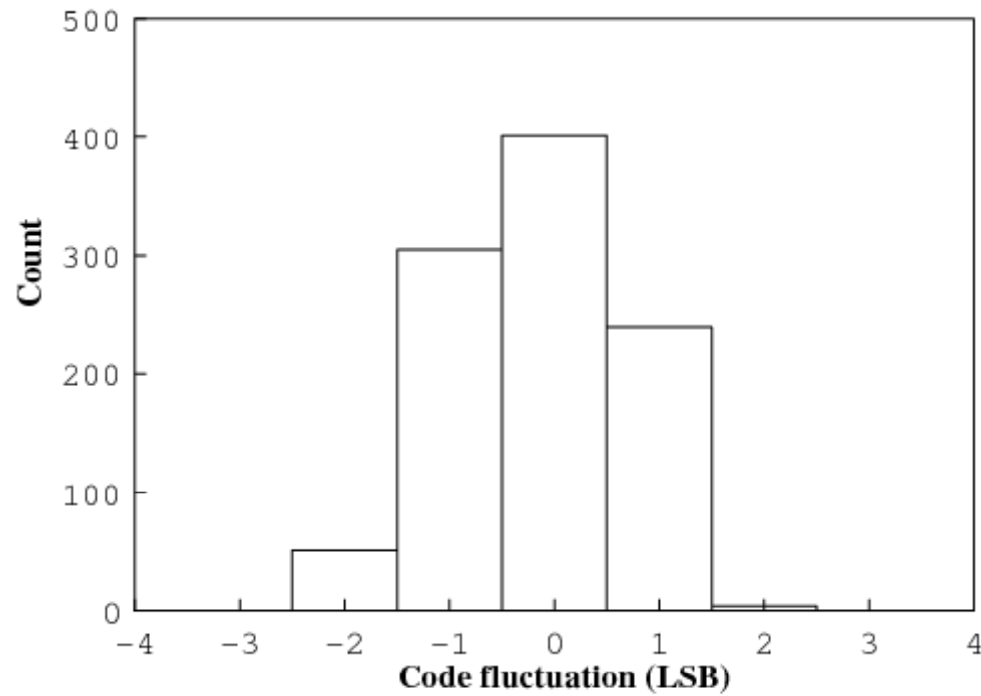

**Standard deviation = 0.84 LSB (420 $\mu$ V)**



# Conclusion

- ❑ A 12-bit cyclic ADC prototype, dedicated to Calice, is fabricated and under test
- ❑ First measured performance is in accordance with simulations (speed, resolution, power cons., noise)
- ❑ Next measurements have to evaluate:
  - Dispersion of the performance on the 10 chips produced
  - Dependence of performance with clock frequency
  - Performance of the Power pulsing (recovery time of the biasing)

Results will be presented during the next IEEE meeting in Dresden



# One ADC per $n$ channel

