

A 130nm CMOS Digitizer Chip for Silicon Strips readout at the ILC



Thanh Hung Pham

on behalf of

W. Da Silva¹, J. David¹, M. Dhellot¹, D. Fougeron², R. Hermel², J-F. Huppert¹, **J-F. Genat¹**
F. Kapusta¹, H. Lebbolo¹, F. Rossel¹, **A. Savoy-Navarro¹**, **R. Sefri¹**, S. Vilalte², A. Charpy¹, C. Ciobanu¹, A. Comerma³, D. Gascon³,
A.D Barrientos³

¹LPNHE Paris, ²LAPP Annecy, ³University of Barcelona

Work in the framework of the SiLC (Silicon for the Linear Collider), R&D Collaboration
and the EUDET I3-FP6 European Project

Outline

- *Silicon strips readout*
- *Front-End Electronics*
- *The 4-channel evaluation chip in 130nm CMOS*
- *The 88 channel chip*
- *Conclusion*

Silicon strips detectors at the ILC

Envelope around the central tracking device

Assume:

- A few 10^6 Silicon strips
- 10 - 30 cm long,
- Thickness 200–300 μm
- Strip pitch 50 μm
- AC coupled (DC coupled if necessary)

→ Millions of channels
Integration of k-scale channels readout chip

Silicon strips data

- **Pulse height:** Cluster centroid to get a few μm position resolution

→ *Detector pulse analog sampling*

- **Time:** 150-300 ns for BC identification

→ *Shaping time of the order of the microsecond
depending upon strip length (capacitance)*

→ **80ns analog pulse sampling and on-chip digitization**

Outline

- *Silicon strips readout*
- *Front-End Electronics*
- *The 4-channel evaluation chip in 130nm CMOS*
- *The 88 channel chip*
- *Conclusion*

Functionalities to be integrated

- Full readout chain integration in a single chip
 - Preamp-shaper
 - Sparsification
 - Sampling
 - Analog event buffering:
 - On-chip digitization
 - Buffering and pre-processing:
Centroids, least square fits, lossless compression and error codes
 - Calibration and calibration management
 - Power switching (ILC duty cycle)
- Trigger decision on analog sums
8-deep sampling analog pipe-line
Occupancy: 8-16 deep event buffer
10-bit ADC


Front-End chip numbers

Goal: Integrate 512-1024 channels in 90nm CMOS:

- **Amplifiers:** - 30 mV/MIP over 30 MIP range
- **Shapers:** - ranges: 500ns-3 μ s
- **Sparsifier:** - Threshold the sum of 3-5 adjacent channels
- **Samplers:** - 8 samples at 80-640ns variable sampling clock period
 - Event buffer 8-16 deep
- **Noise baseline:**
Measured with 180nm CMOS:
375 + 10.5 e-/pF @ 3 μ s shaping, 210 μ W power
S/N ~ 20
- **ADC:** - 10 bits
- **Buffering, digital pre-processing**
- **Calibration**
- **Power switching can save a factor up to 200**

ILC timing: 1 ms: ~ 3000 trains @ 360ns / BC 199ms in between

Front-end architecture

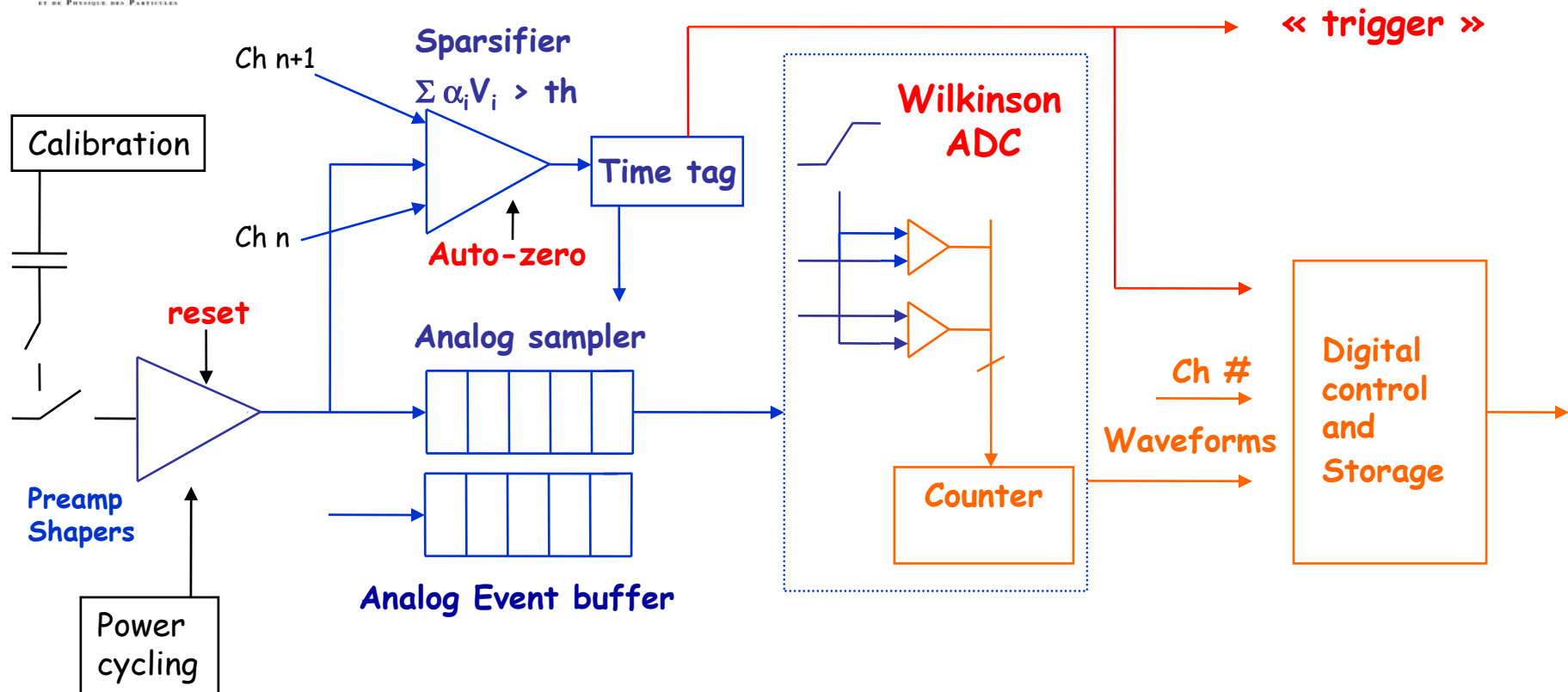

Charge 1-30 MIP, Time resolution: BC tagging 150-300ns
80ns analog pulse sampling

Technology: Deep Sub-Micron CMOS 130-90nm

Outline

- *Silicon strips readout*
- *Front-End Electronics*
- *The 4-channel evaluation chip in 130nm CMOS*
- *The 88 channel chip*
- *Conclusion*

Front-end in 130nm

Motivation for 130nm CMOS:

- Smaller
- Faster
- Less power
- Will be (is) dominant in industry
- (More radiation tolerant)

Drawbacks:

- Reduced voltage swing (Electric field constant)
- Noise slightly increased ($1/f$)
- Leaks (gate/subthreshold channel)
- Design rules more constraining
- Models more complex, not always up to date

UMC CMOS Technology parameters


180 nm

130nm

• 3.3V transistors	yes	yes
• Logic supply	1.8V	1.2V
• Metals layers	6 Al	8 Cu
• MIM capacitors	1fF/μm ²	1.5 fF/μm ²
• Transistors	Three Vt options	Low leakage option


Help from IMEC Europractice (Leuven, Belgium): Paul Malisse, Erwin Deumens

4-channel Chip

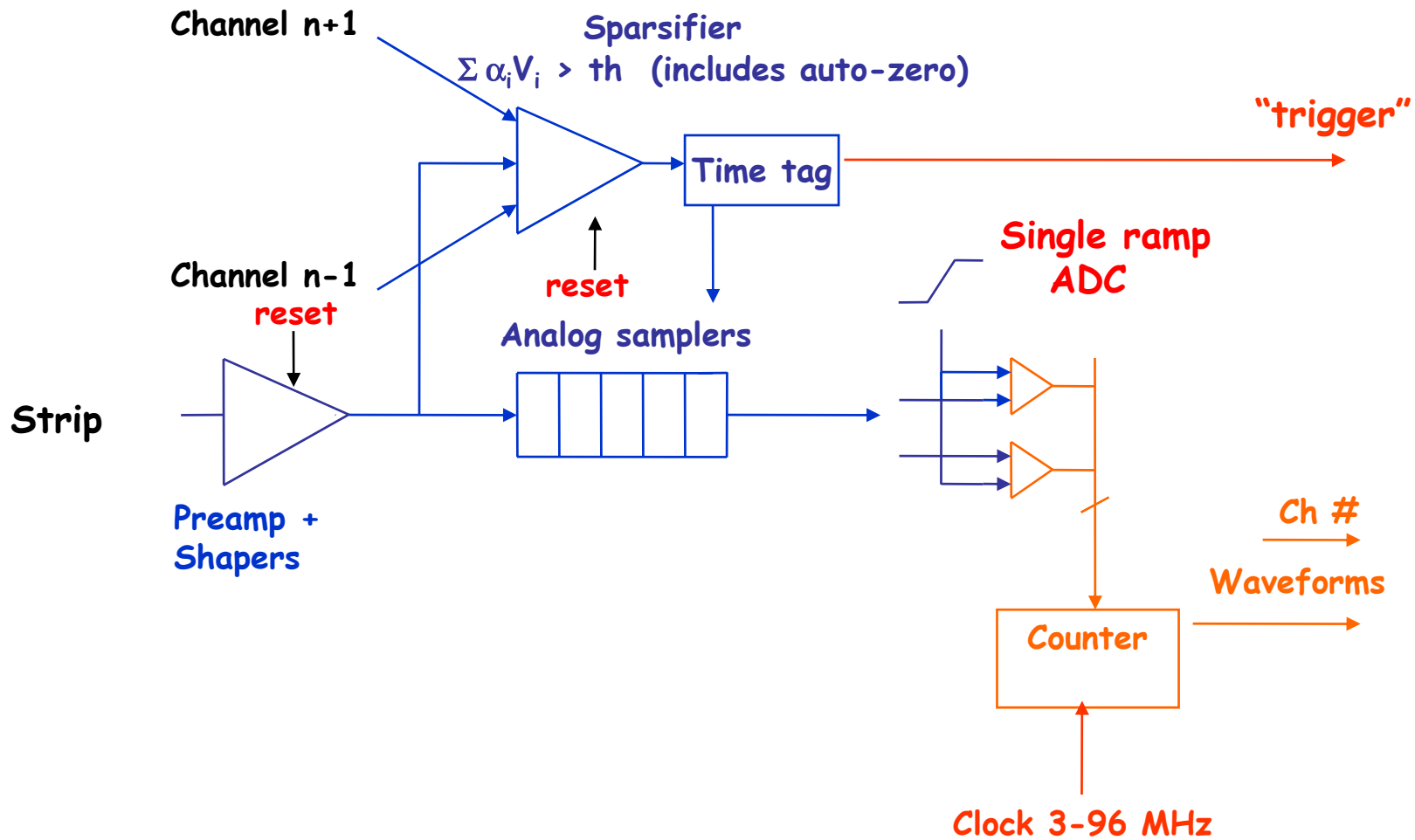

4-channel chip layout

 Amplifier, Shaper, Sparsifier $90 \times 350 \mu\text{m}^2$ Analog sampler $250 \times 100 \mu\text{m}^2$




A/D $90 \times 200 \mu\text{m}^2$



180nm 130nm

Layout of the 130nm chip including sampling and A/D conversion


Photo

 



Preamp-shaper results

Measured gain - linearities

Preamp output

 

Shaper output

  


Preamp and Shaper:

Gain = 29mV/MIP
 Dynamic range = 20MIPs 1%
 30 MIPs 5%

Peaking time = 0.8-2.5µs / 0.5-3µs expected

Noise results

 



Power (Preamp+ Shaper) = 245 μ W

Noise:	130nm @ 0.8 μs :	850 + 14	e⁻/pF	245 μW	(150+95)
	130nm @ 2 μs :	625 + 9	e⁻/pF		
	180nm @ 3 μs :	375 + 10.5	e⁻/pF	210 μW	(70+140)

Digitized analog pipeline output

Laser response of detector + 130nm chip

Digitized shaper output

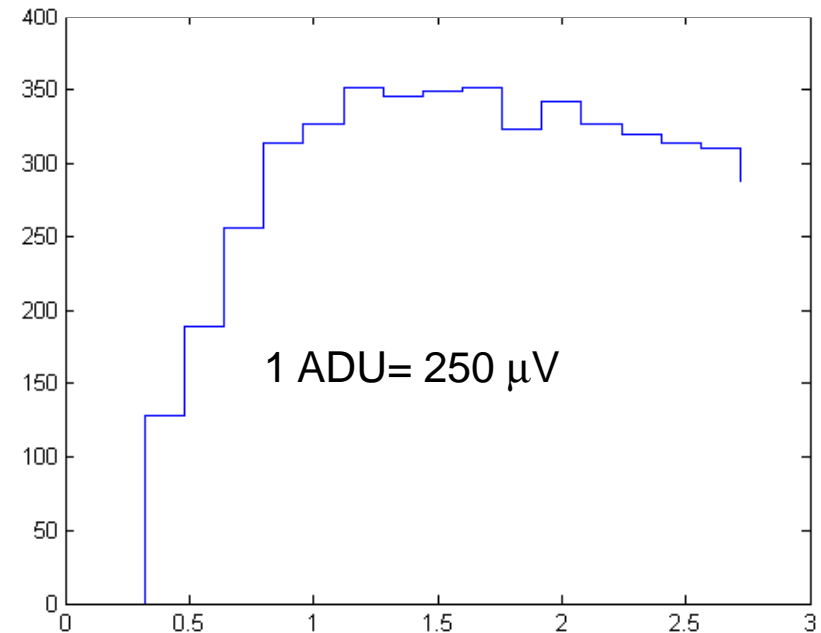 


Sampling rate = 12 MHz
Readout rate = 10 KHz

From calibration pulser as input

From Laser diode + Silicon detector

ADC TEST

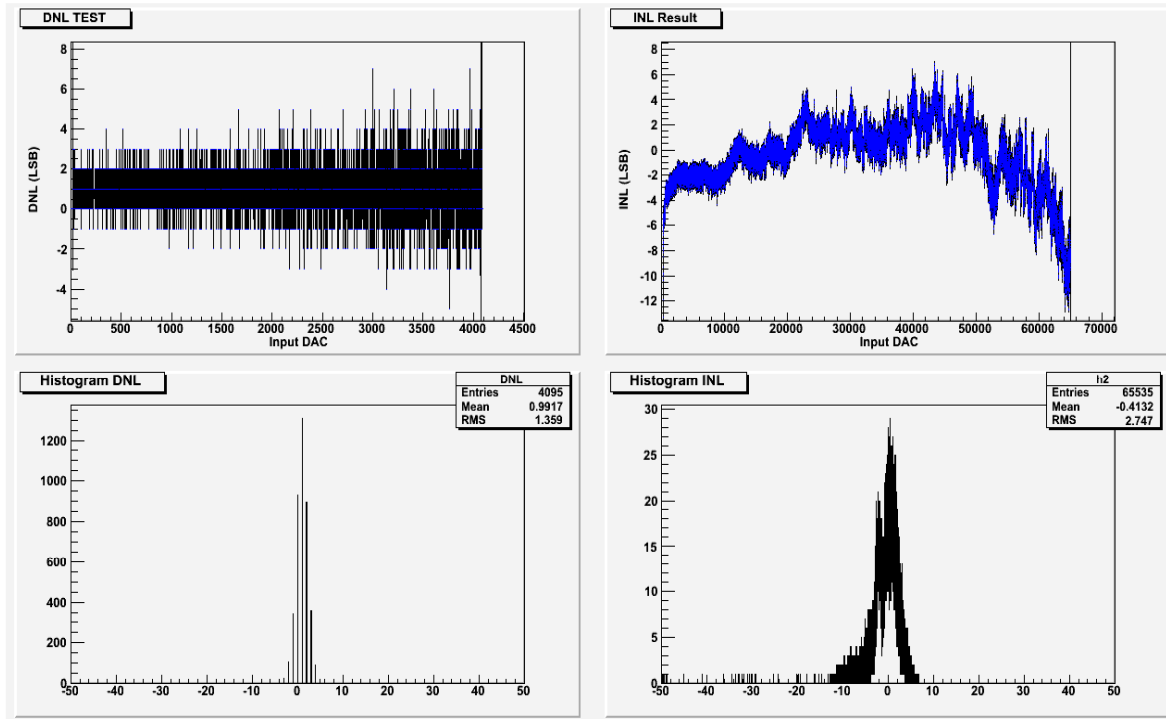

DAC Input :

Dynamic : 0 – 1V

Offset : ~1V

ADC Output :

From 50 bin to 3780 bin:

+INLmax = 7 LSB


+INLrms = 2.74 LSB

+DNLmax = 7 LSB

+DNLrms = 1.36 LSB


→ ~ 9b effective in the worst case

CERN Beam tests results

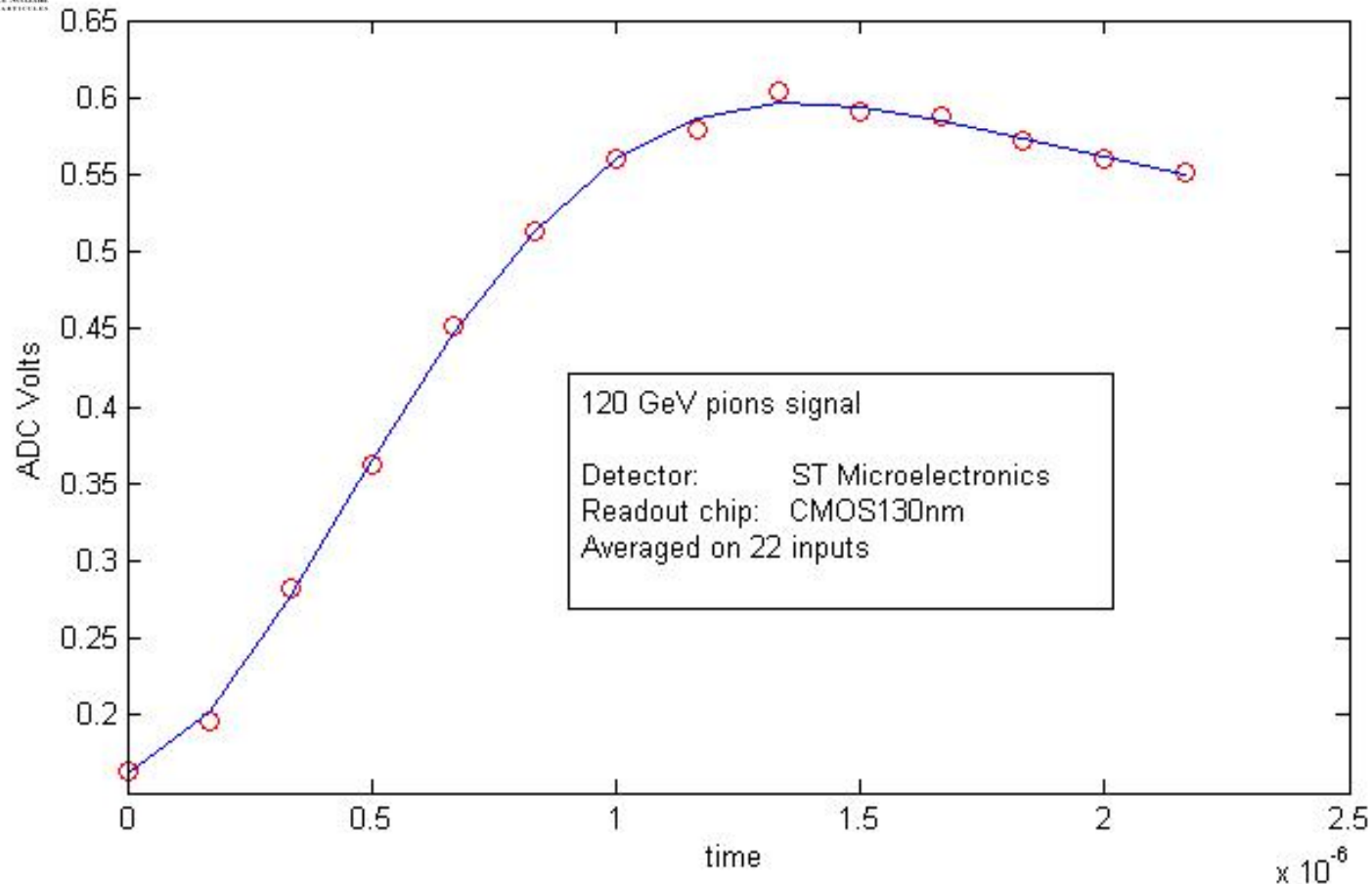


- Averaged response of 120 GeV pions through 500 μm thick Silicon detector
- Pedestal subtracted off-line, then digitized shaper waveform OK.

130nm chip test-beam response

 

Study : /data/dasilva/silc/test3/dataTest/datacern/Beam_Wilfrid/LC_3X_20_oct_02h12m00s.txt

Signal to noise ratio: Chip 1 - Strip 3

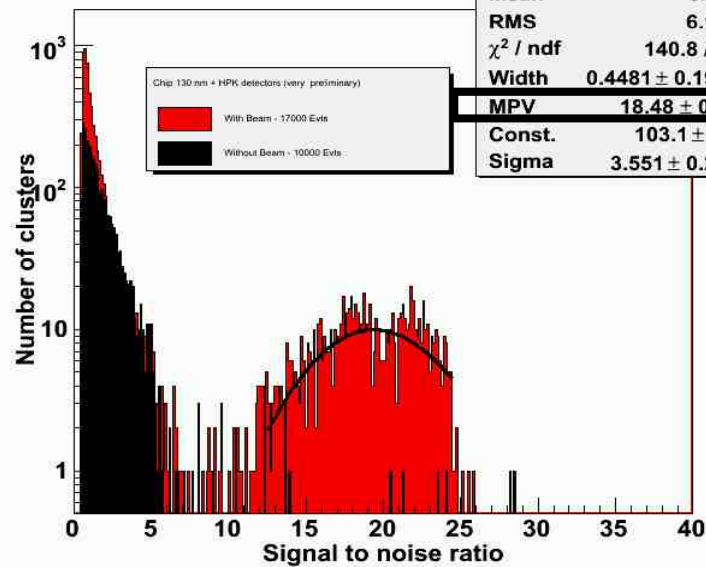


**Signal to Noise ratio
From beam-tests**




IN2P3
INSTITUT NATIONAL DE PHYSIQUE NUCLÉAIRE
ET DE PHYSIQUE DES PARTICULES

130nm Sr⁹⁰ radio active source

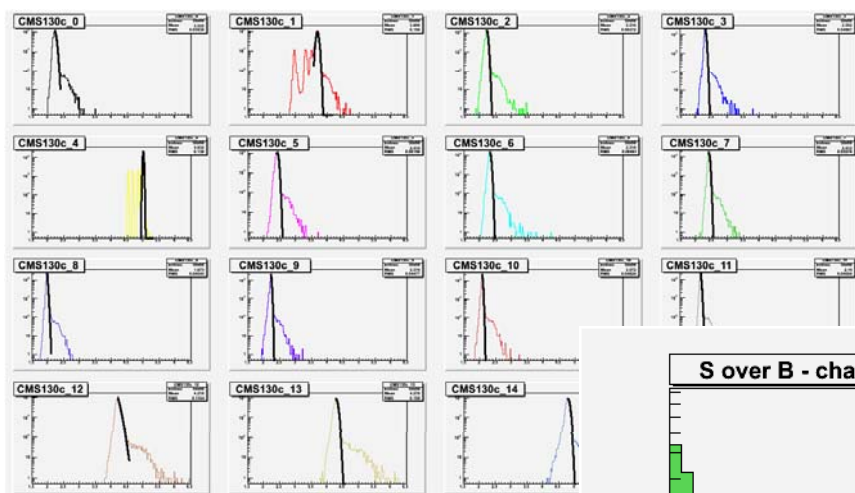

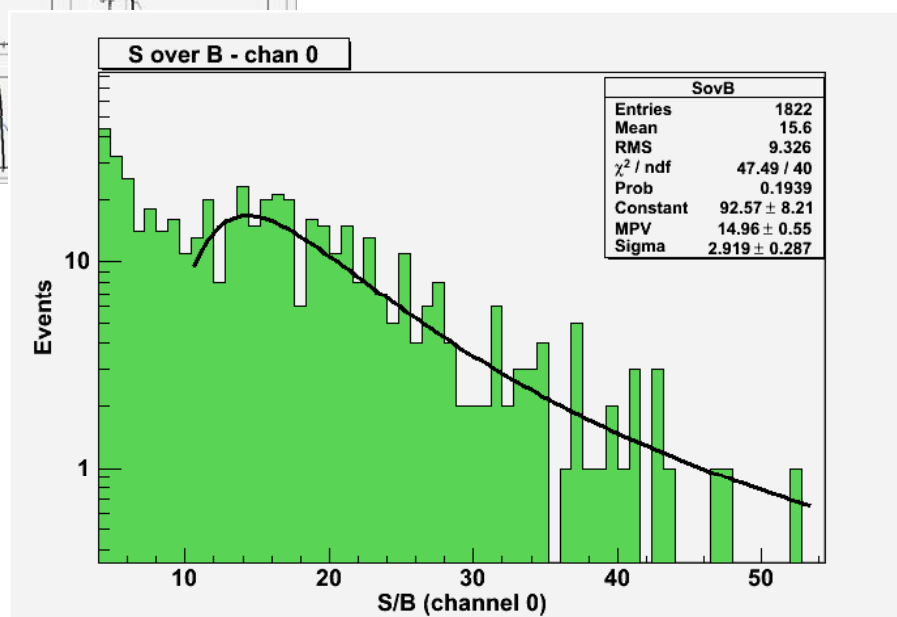
**Signal to Noise ratio
From Sr⁹⁰ radio-
active source
(HPK sensors)**



Outline

- *Silicon strips readout*
- *Front-End Electronics*
- *The 4-channel evaluation chip in 130nm CMOS*
- *The 88 channel chip*
- *Conclusion*

Block diagram

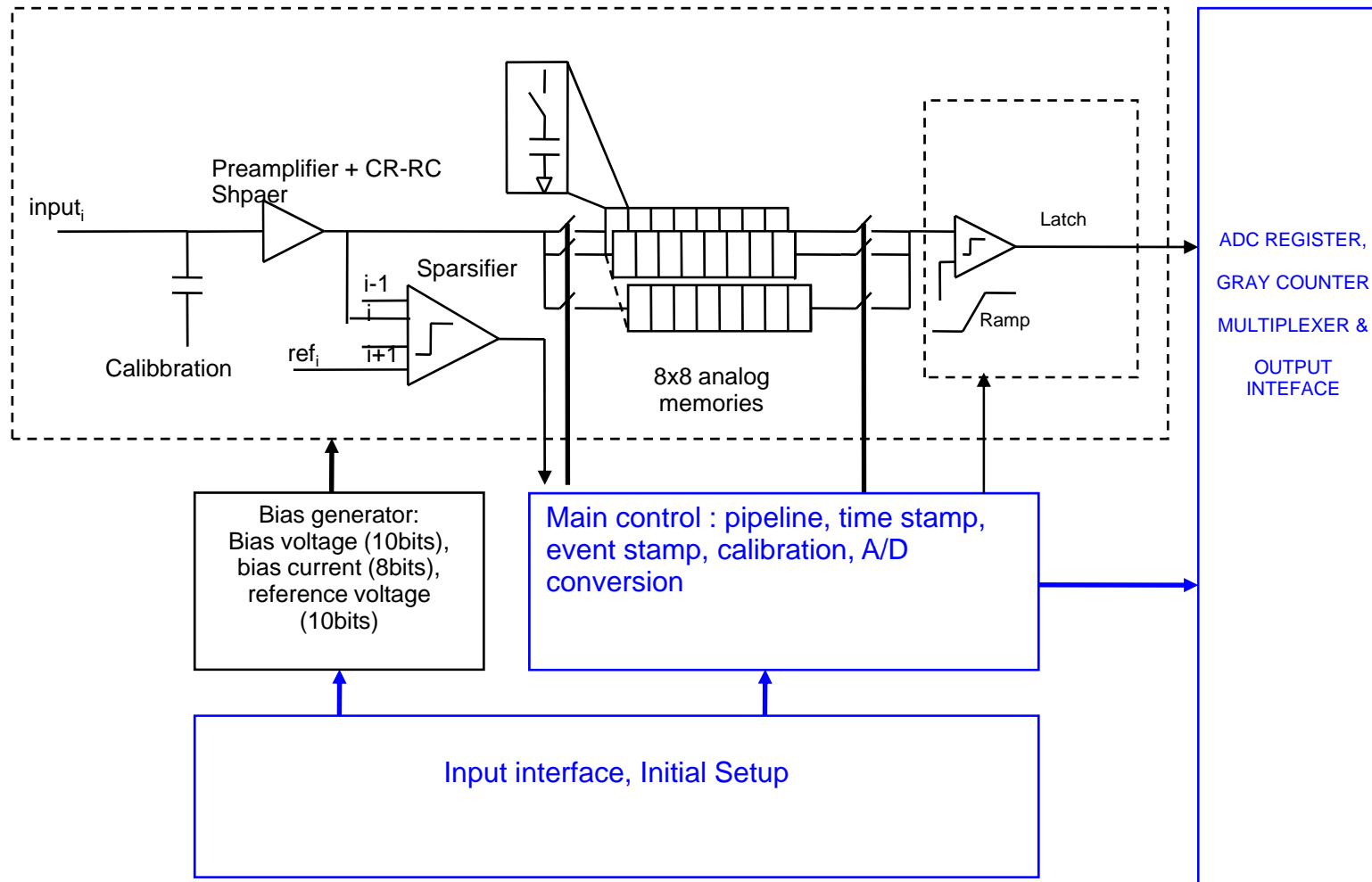

88 channels chip

Electrics:

- Consumptions : ~ 1.1mW/channel
- LVTTL digital IN/OUT

Features:

- 88 channels in 130nm CMOS
(Preamplifier, Shaper, Sparsifier, 2D 8x8 analog memories, 12 bits ADC)

- Integrated calibration
- Power switching
- Digital controls


(Bias, threshold, sampling, zero suppression data out, time/event stamp, power switching control, serial in/out interface)

Two samples :

60 naked dies

20 packaged dies

88 channels chip

 


Digital control

I/O Interface

Bias
generator

88 Analog
channels

 

Designed :

Jan/08 – Juin/08

Contribution:

Analog : LPNHE

Digital : UB


Reception:

Naked die : Sep 12th 08

Packaged die : Mid October/08
(Expected)

Layout of 88 channels
readout circuit (5mmx10mm)

88 channels chip

 

CQFP 208

- 50 analog input
including 1 test channel

-> Functional test,
productivity

88 channels chip

❖ Functional test with packaged chip

- Front-end board -> already designed (will be soon available)
- DAQ Software

“simplified” version -> charged by University of Barcelone

- > Initialization, probe digital signal
- > Confirm the functionality of the chip
- > Power test (bias voltage, current)
- > Test channel : Preamplifier, Shaper ...

“developed” version -> under development, charged by LPNHE+UB

- > ADC characterization
- > Calibration scan
- > Optimization ...

❖ Beam/radio active source test (detector + naked die)

- Front-end board -> already designed (4 naked chips/module)
- DAQ Software

Previewed extension in actual acquisition system (FPGA board + soft)
(see Alexandre’s talk)

Conclusion

The CMOS 130nm design and test results demonstrate the feasibility of a highly integrated front-end for Silicon strips (or large pixels).

The new 88 channels chip is available for the test. This chip will be able to equip the large silicon strip modules and confirm the strategy of the development

The end...

EUDET ANNUAL MEETING OCT 6th-8th 2008, NIKHEF