

Omega

ASIC Skiroc 2

Digital part

Frédéric DULUCQ


08-09/06/2009

What's new for the digital part ?

- Improved SCA management (Spiroc like)
 - SCA depth of 15: limited by memory size (5 in Skiroc1)
 - 64 channels (36 in Skiroc1)
- New SlowControl registers
- Start/EndReadOut daisy chain improved. EndRO is calibrated (2-3 clock ticks) and synchronized on falling edge
- Compatible with SPIROC1&2 acquisition management
 - Possibility to use a Notrig signal (erase current SCA depth)
- Many other improvements (some from other chips):
 - Hit channel data now stored in analog part (near SCA)
 - Glitchfree signals added
 - Default configuration
 - Internal ADC management (registers)


Slow Control (1/2): Extra FF

 - Improve shift registers daisy chain between / inside ASICs:
 - Add opposite edge FF on each SC bits



- Consequences:
 - Chip "N" sends data at falling edge and chip "N+1" captures at rising edge (time margin = half period clock)
 - Area of SC doubled (N SC bits \rightarrow 2N SC Flip Flops)
 - No change for the DIF software (N SC bits \rightarrow N clock tick to load SC)

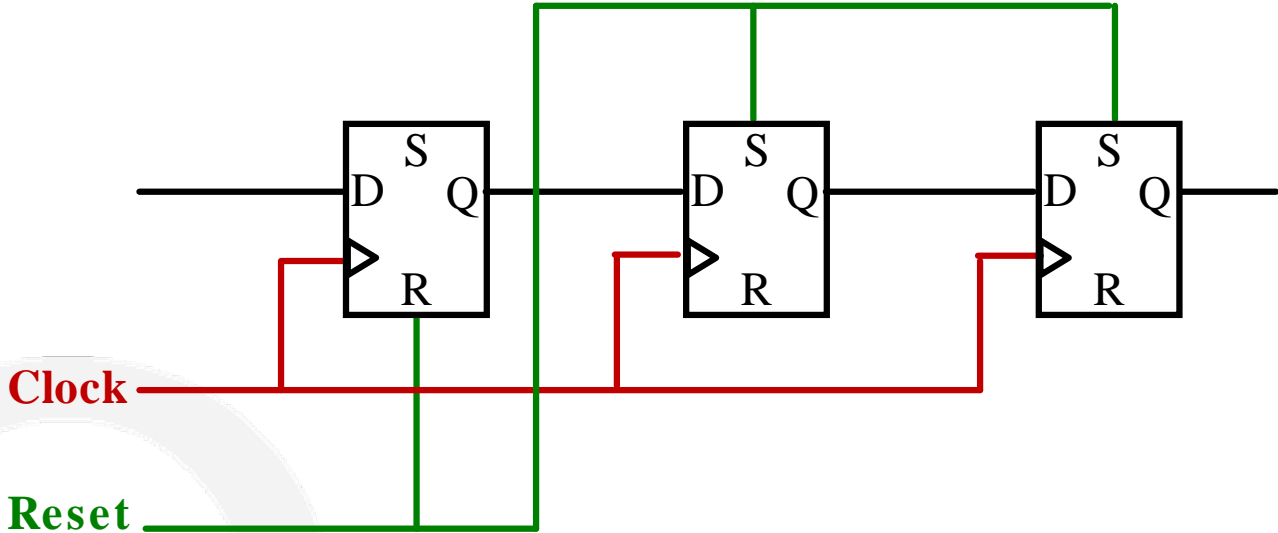- Use Set / Reset of Flip-Flops for default configuration of SC





Example default configuration : "011"

- Implemented for digital interfaces (HARDROC2) → Now Skiroc2


DIF Management like all ROC Chips



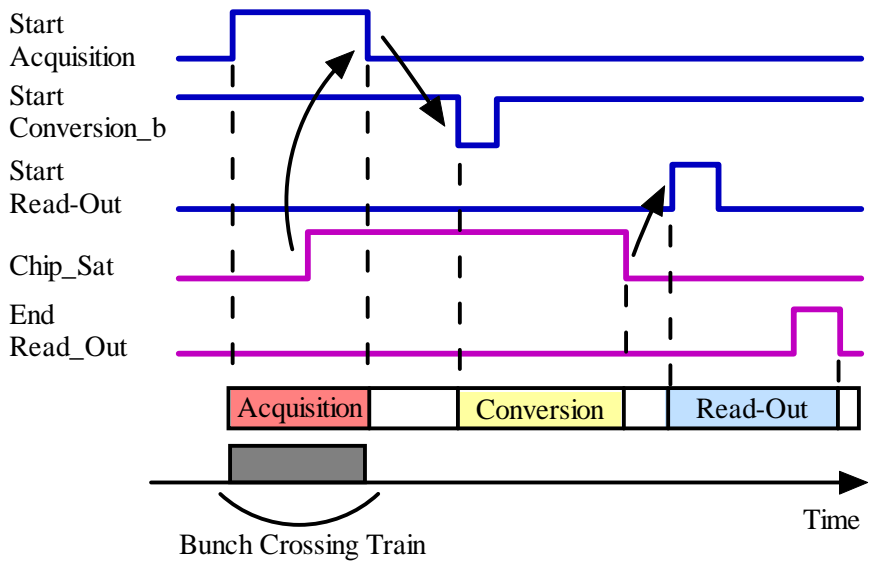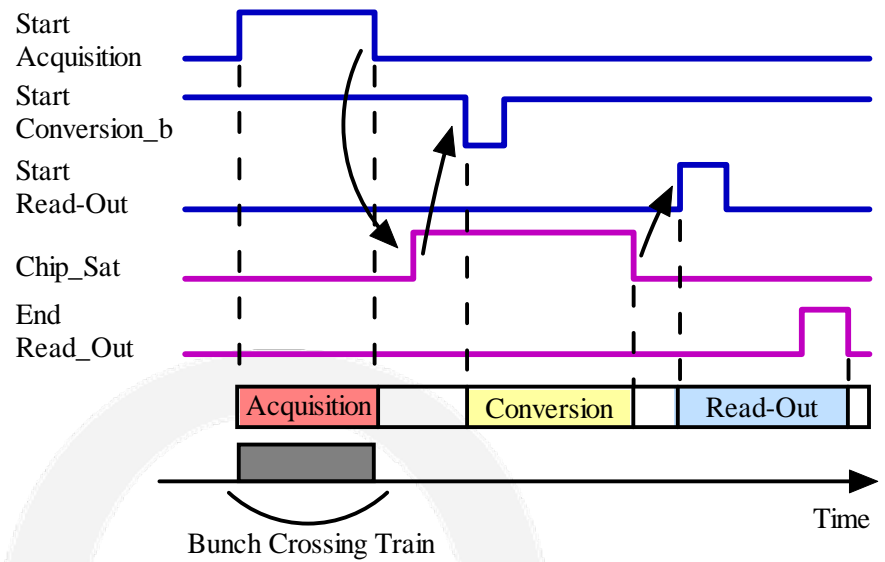- Same driving sequence for all ROC chips (Hardroc2, Spiroc and Skiroc)
➔ "StartAcquisition" active on level.



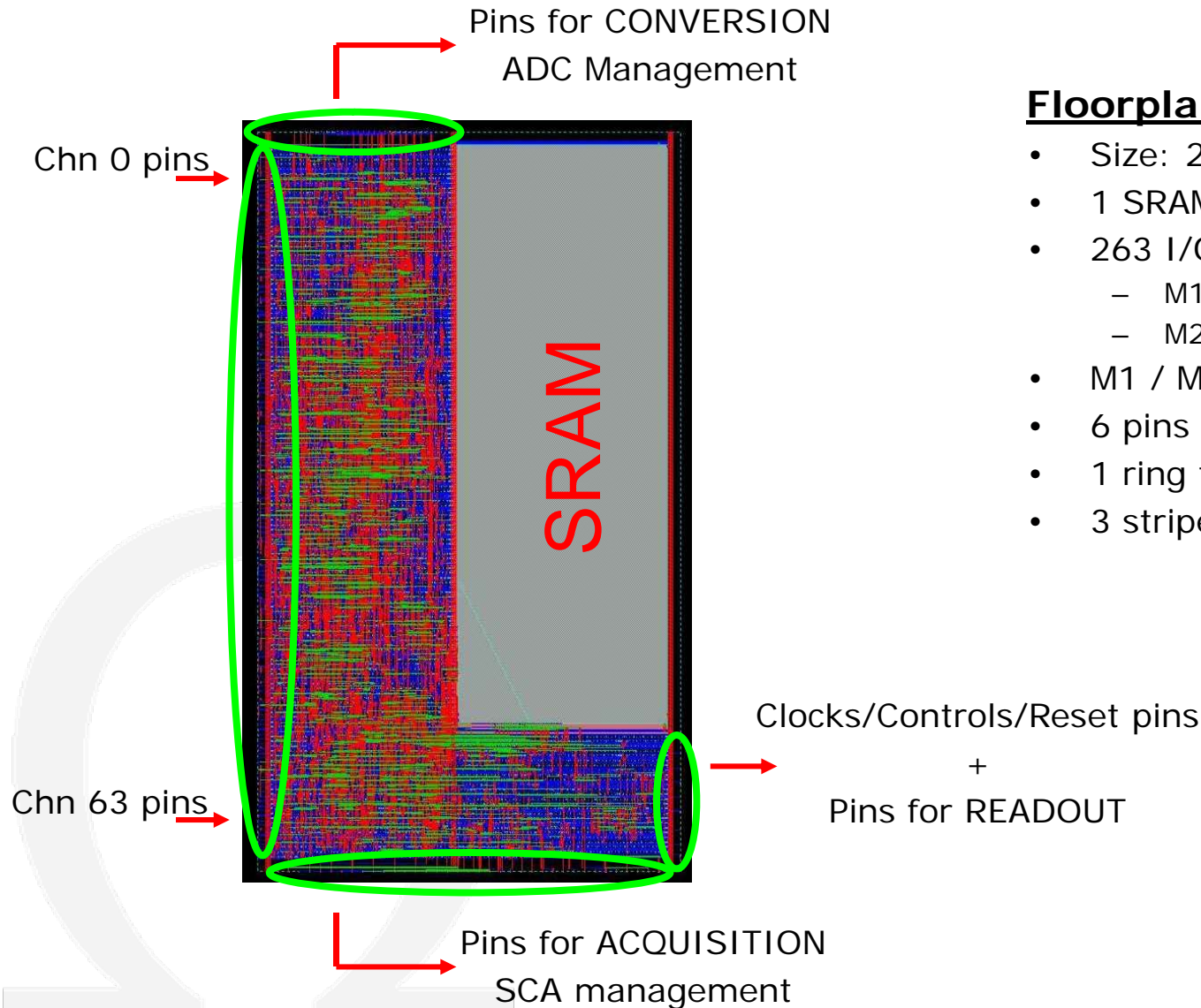
- ChipSat allows the DIF to know:
 - When to start the conversion after the falling edge of the StartAcq: ChipSat @ '1'
 - When the conversion is finished: ChipSat going from '1' to '0'
- If one chip stuck the ChipSat, DIF always has the possibility to use a timeout (should be around 4ms for Skiroc2)



Floorplan features:

- Size: 2800x1600 um
- 1 SRAM 2048x16: 2188x791 um
- 263 I/Os
 - M1 for Left / Right
 - M2 for Top / Bottom
- M1 / M2 / M3 used for layout
- 6 pins for VDD and 6 for GND
- 1 ring for SRAM
- 3 stripes of power

Memory mapping

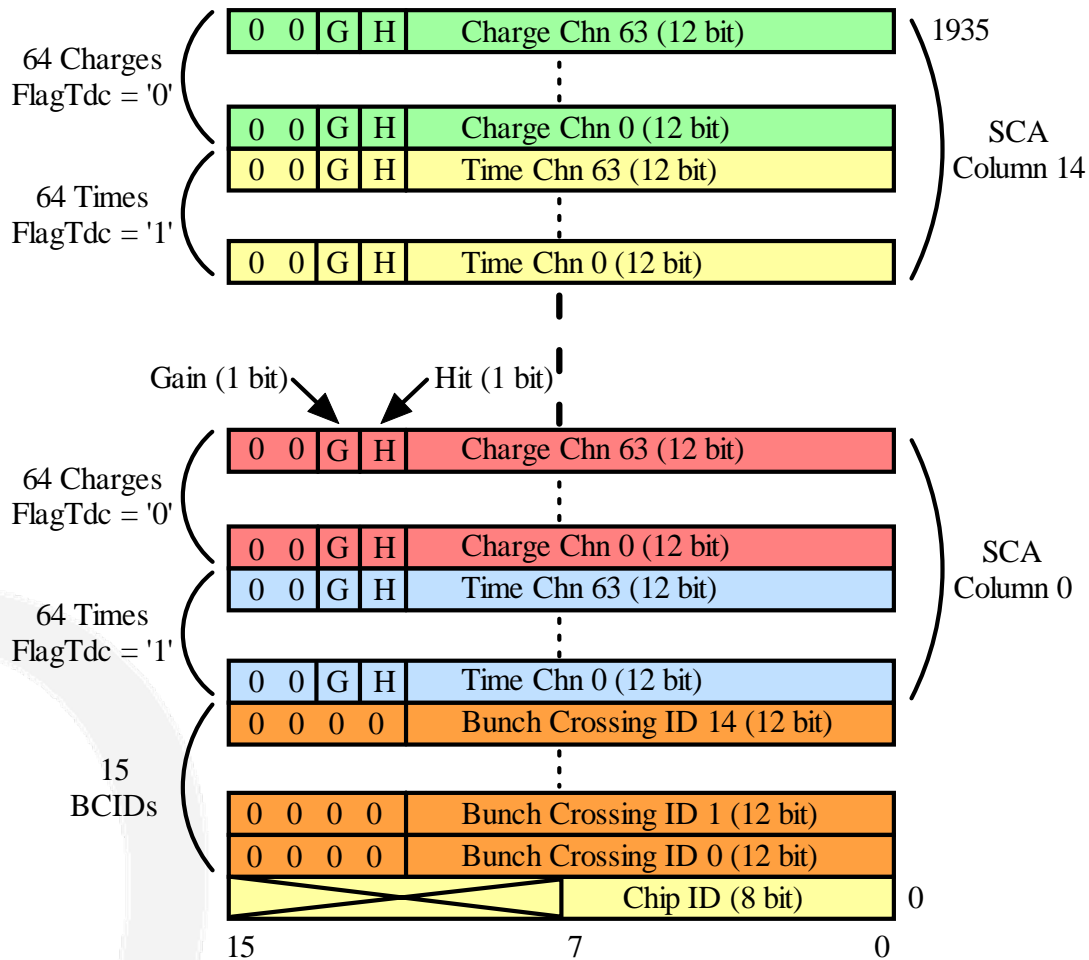

- Amount of bits in memory:
 - For 0 trigger $\Rightarrow N_{data} = 0$
 - For $0 < n < 16$ $\Rightarrow N_{data} = (1 + n + 64n + 64n) \times 16$ (ID & BCID & Charge & Time)