

PCB DEVELOPMENTS AT IPNL (PCB and ASIC)

- PCB for 1m² of RPC with HR2

*William TROMEUR, Hervé MATHEZ, Yannick ZOCCARATO
Imad LAKTINEH, Christophe COMBARET, Rodolphe DELLA-NEGRA, Didier BON
(CNRS IN2P3 IPNL)*

Collaboration with LAL

1 m² PCB MAIN SPECIFICATIONS

(sane as 1 m² with HR1)

ASU PCB Design

- 24 x 64 1 sq cm pads
- 24 Hardroc 2 Asics chained in plastic package (very thin 1.2 mm)

1 m² PCB board :

- 6 ASUs
- 144 Hardroc2 Asics


DIF boards :

- 1 DIF for 2 ASU : 3 DIFs

HR2 :

- ✓ All modifications are implemented
- ✓ SC by pass
- ✓ SC Clocking and so on

ASU PCB DESIGN

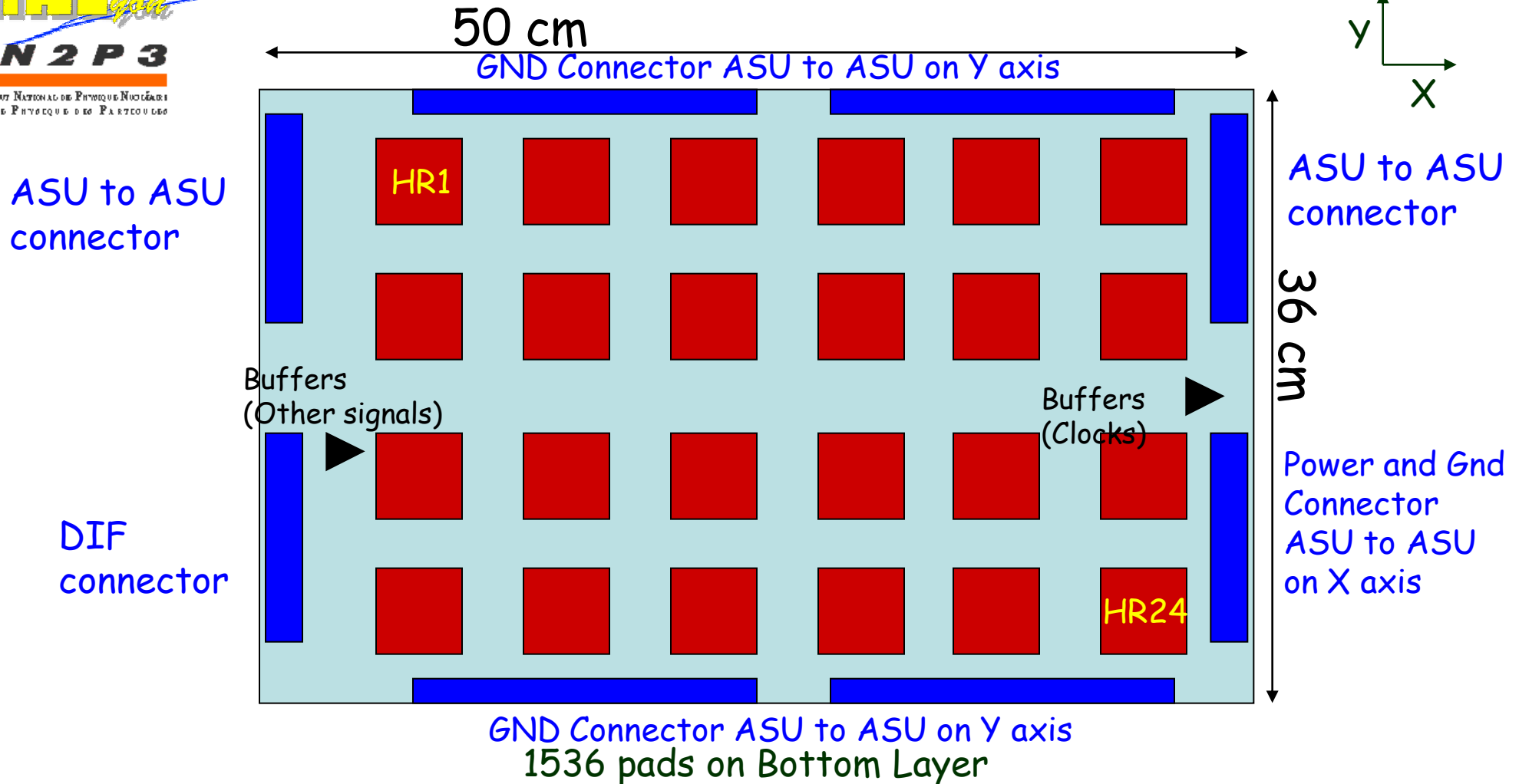


- Buried and Blind Vias (Same as the last PCB with HR1 and first PCB with 4 HR)
- *Buffer are implemented but the board must work without buffers*

1 m² PCB DESIGN interconnection


1 DIF for 2 ASUs

ASU to ASU Connection HR1

DIF Board

 

Solder or 0 ohm resistor

 


ASU 1 ASU 2

Mechanical
 Problems



 Kapton cable
 (return from manufacture
 next week)



9216 pads on Bottom Layer


1 m2 PCB DESIGN interconnection

1 DIF for 2 ASUs

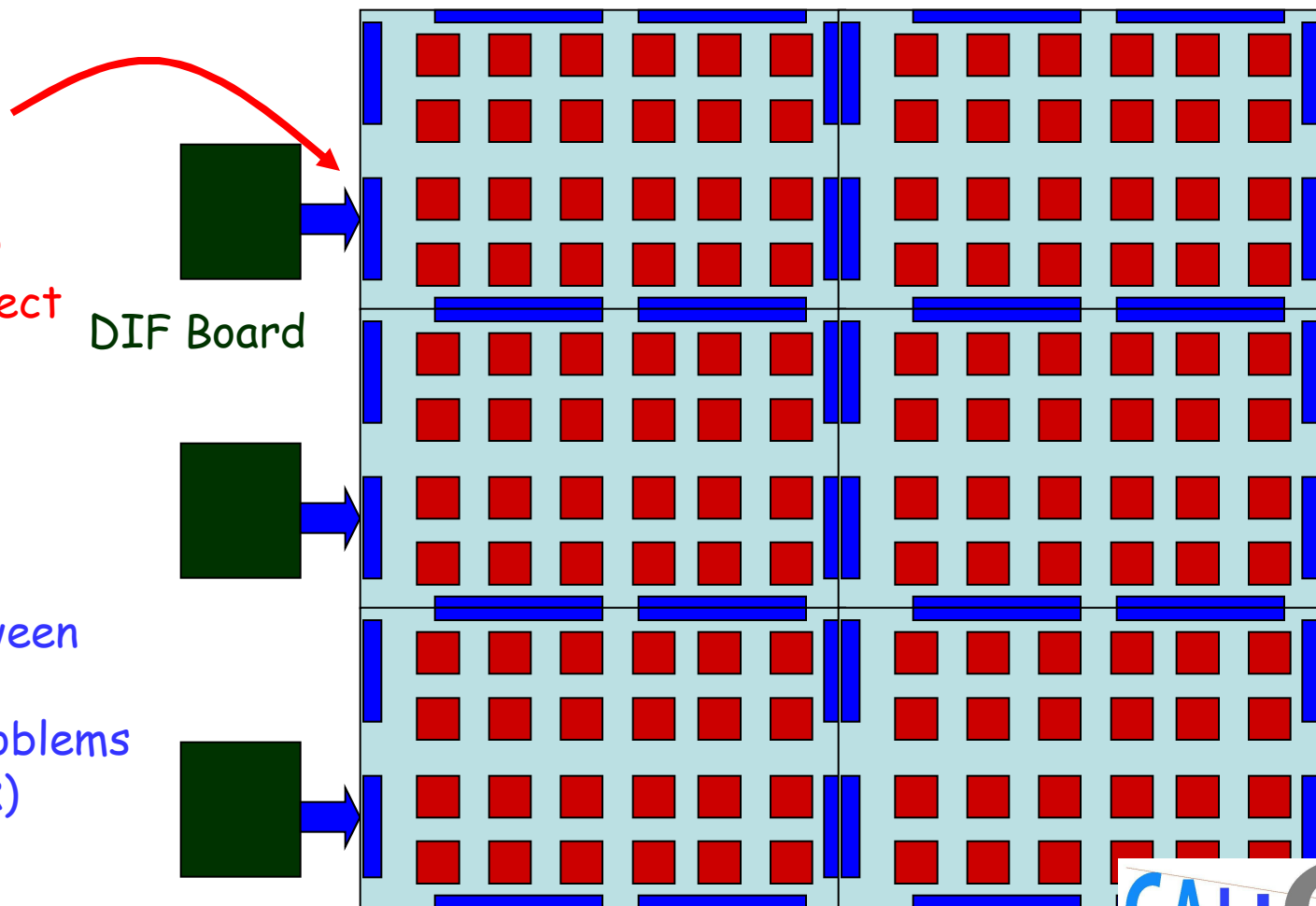Problems with 90 pins
 Samtek connector :
 Pad are teared off after
 Several connect/disconnect
 DIF board



Add a *kapton cable* between
 DIF board and ASU
 To reduce connection problems
 (will be design next week)




1 m² PCB DESIGN (Layers and next steps)

- o Layer 1 (TOP) : interconnect
- o Layer 2 : GND
- o Layer 3 : Digital signal
- o Layer 4 : Power
- o Layer 5 : GND
- o Layer 6 : PADS to Hardroc 2
- o Layer 7 : GND
- o Layer 8 (BOTTOM) : PADS

Pads to HR2 interconnects are
the same for the entire PCB
(hierarchical design)

 - *Send the first board to Fab last week for components welding*
- *The board will be fully tested at home in a few week*
- **Manufacturing the other 5 boards after test results**




ASIC DEVELOPMENT IN LYON

Hervé MATHEZ, Yannick ZOCCARATO, Renaud GAGLIONE

(CNRS IN2P3 IPNL)

Collaboration with LAL/LAPP

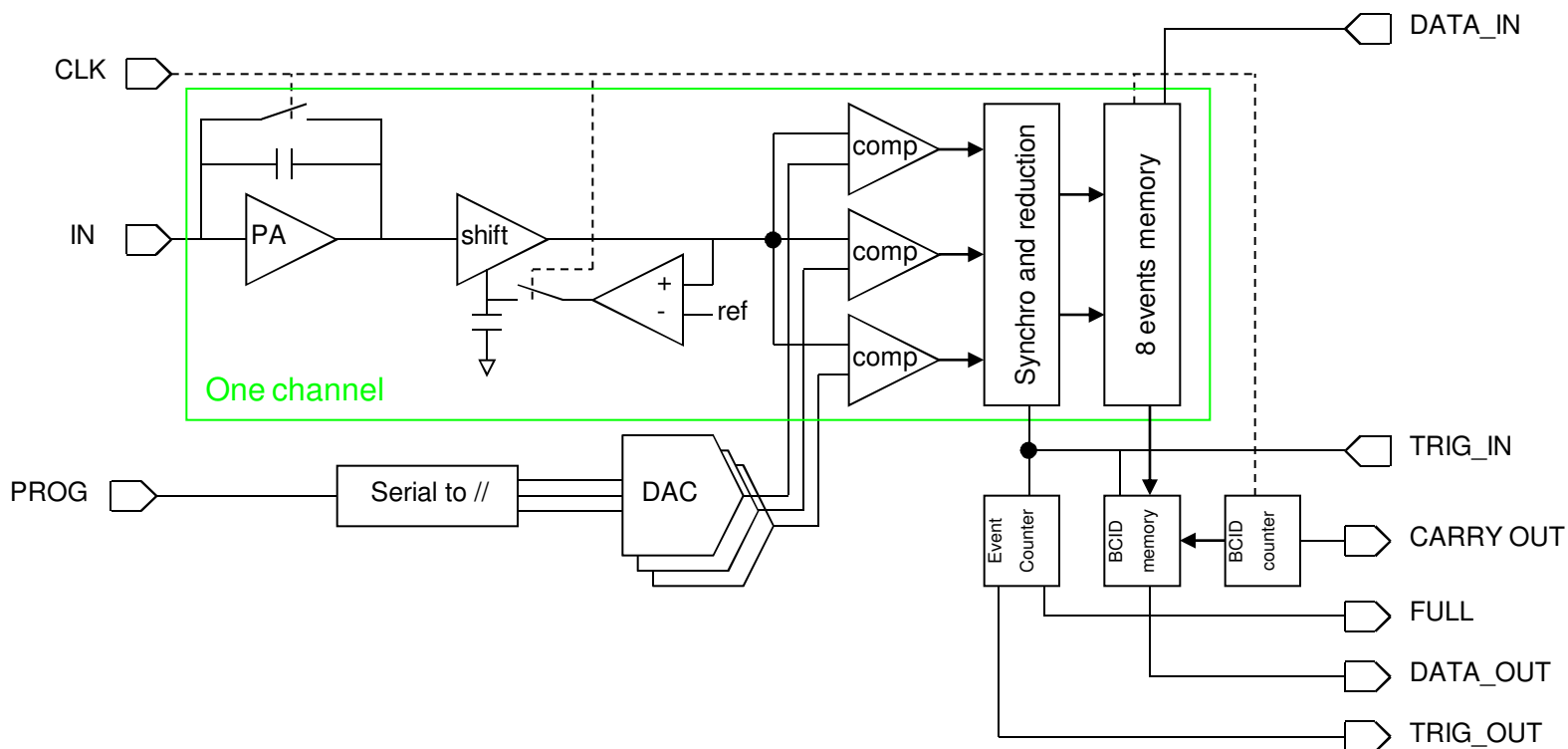
Compare input charge to 3 thresholds (set by 3 DACs) and store the 2 bits energy information



Configuration and read-out by shift register ...


DIRAC synoptic

Proposal for the next DIRAC version :

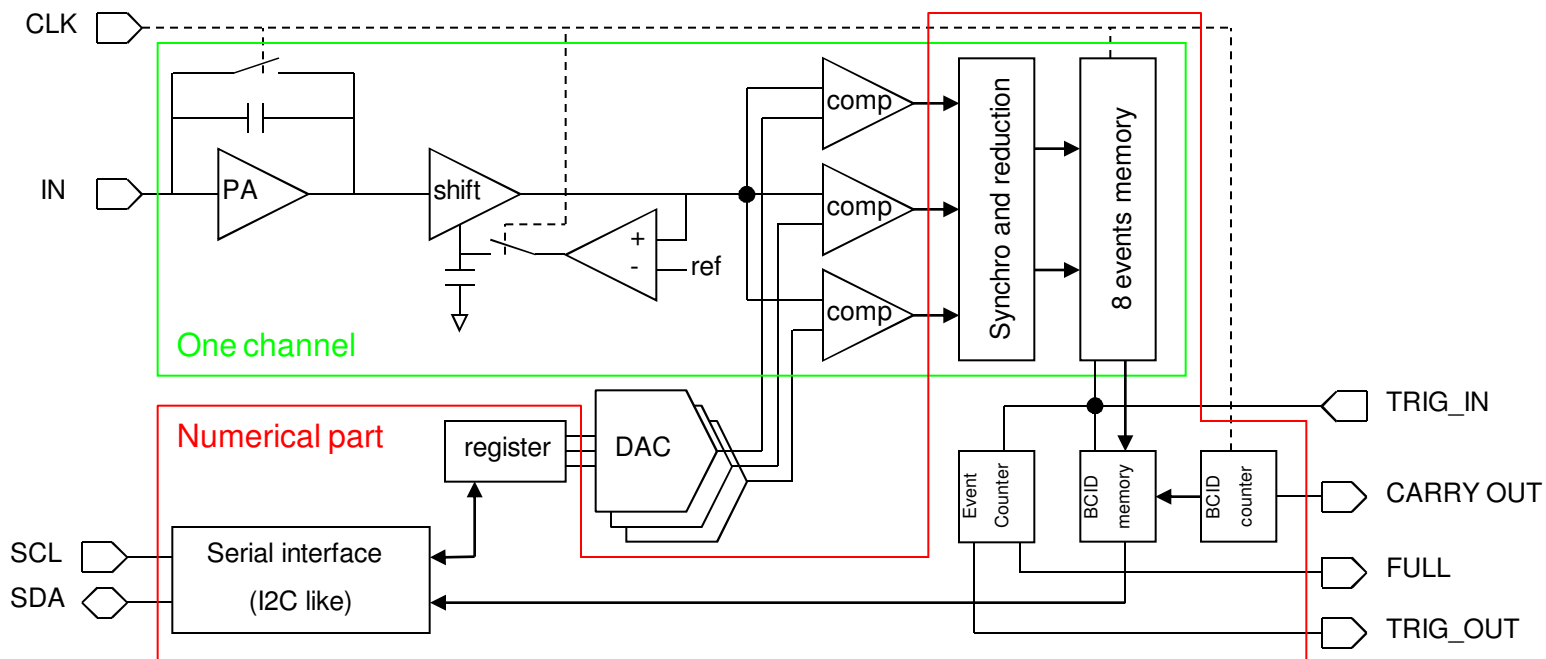


A new read out and configuration interface based on an "I2C like" link

How does the serial interface work ?

 


Each device is addressed individually by software with a unique address that can be modified by hardware pins.

 
The open drain/collector outputs provide a “wired AND” connection that allows devices to be added or removed without impact.



Write data

 

Read data

 


S = START CONDITION

P = STOP CONDITION

\bar{A} = not ACKNOWLEDGE

A = ACKNOWLEDGE

R/\bar{W} = READ / WRITE not

 

Advantages of the serial interface vs a shift register


- o Individually addressed read out and slow control.
 - o More flexible for the user
 - o easier for the pilot firmware design (DIF board)
- o The reading of sending parameters without rewriting them is possible.
- o Board routing easier (without chips chaining).
- o Less sensitive to the risk of failure propagation.

All of these advantages for a small increase of the layout surface and for a similar power consumption (still to be measured).

Layout result

"new version" with serial interface : 1.432mm²

 "old version" with shift register : 1.334mm²




- o AMS 0.35 μm in CMOS process
- o Design in VHDL.
- o Synthesis with RTL compiler.
- o Floorplanning and place and route with first Encounter (CADENCE tools).
- o Return from fab on October

- o AMS 0.35 μm in CMOS process
- o Switch integrator
- o Folded cascode with feed forward compensation technique
- o 4 gains (10pF 200fF 100fF 50fF)
 - o 100 mV/pC, 4 mV/fC, 7 mV/fC, 10 mV/fC
- o Main goal is to detect pulses as low as 2fC
- o Return from fab in October
 - o Tests will be performed with standard comparator


Simulation results

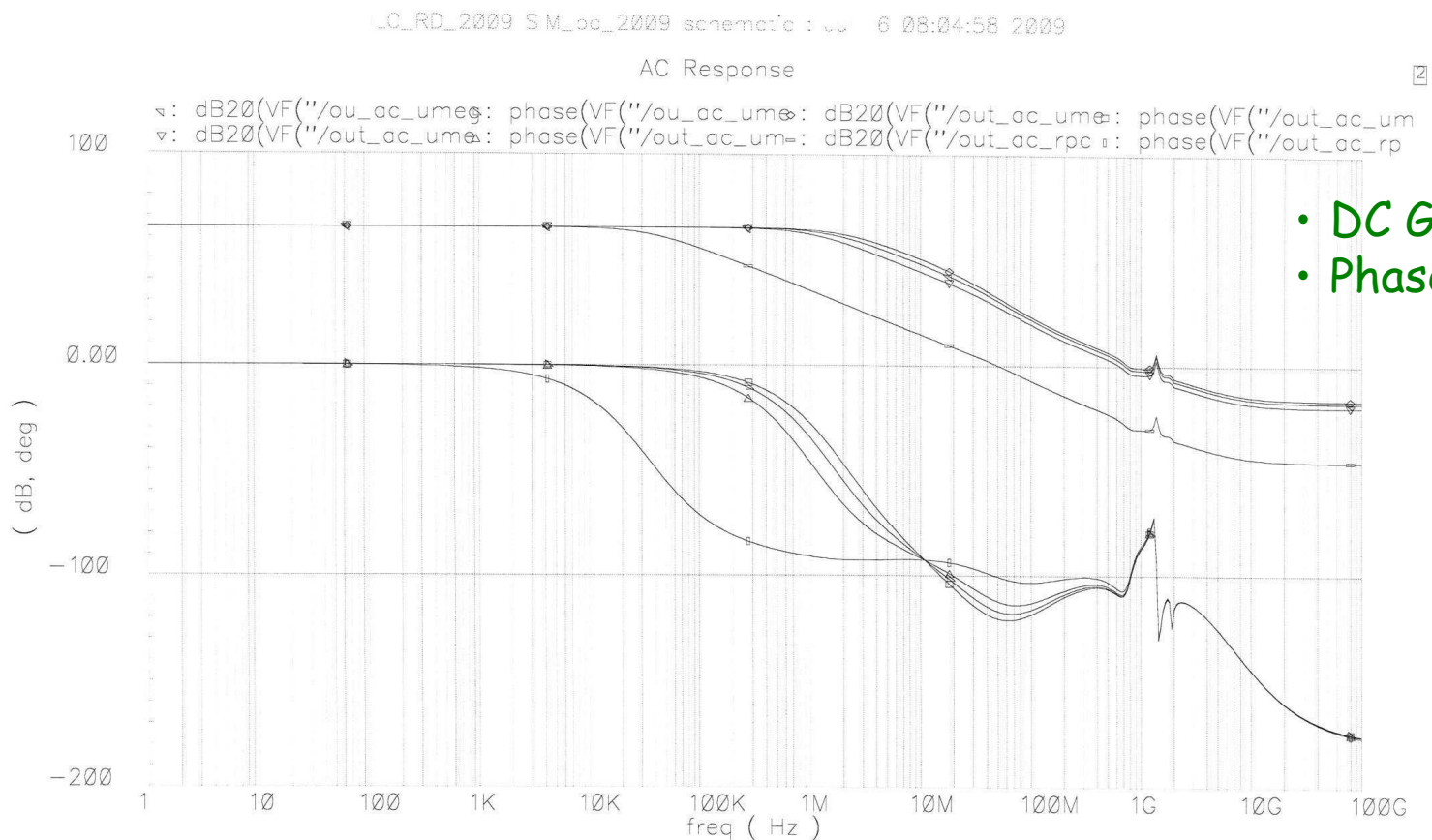AC response for the 4 integrator capacitor



- DC Gain : 70dB
- Phase margin 70 deg

Simulation results

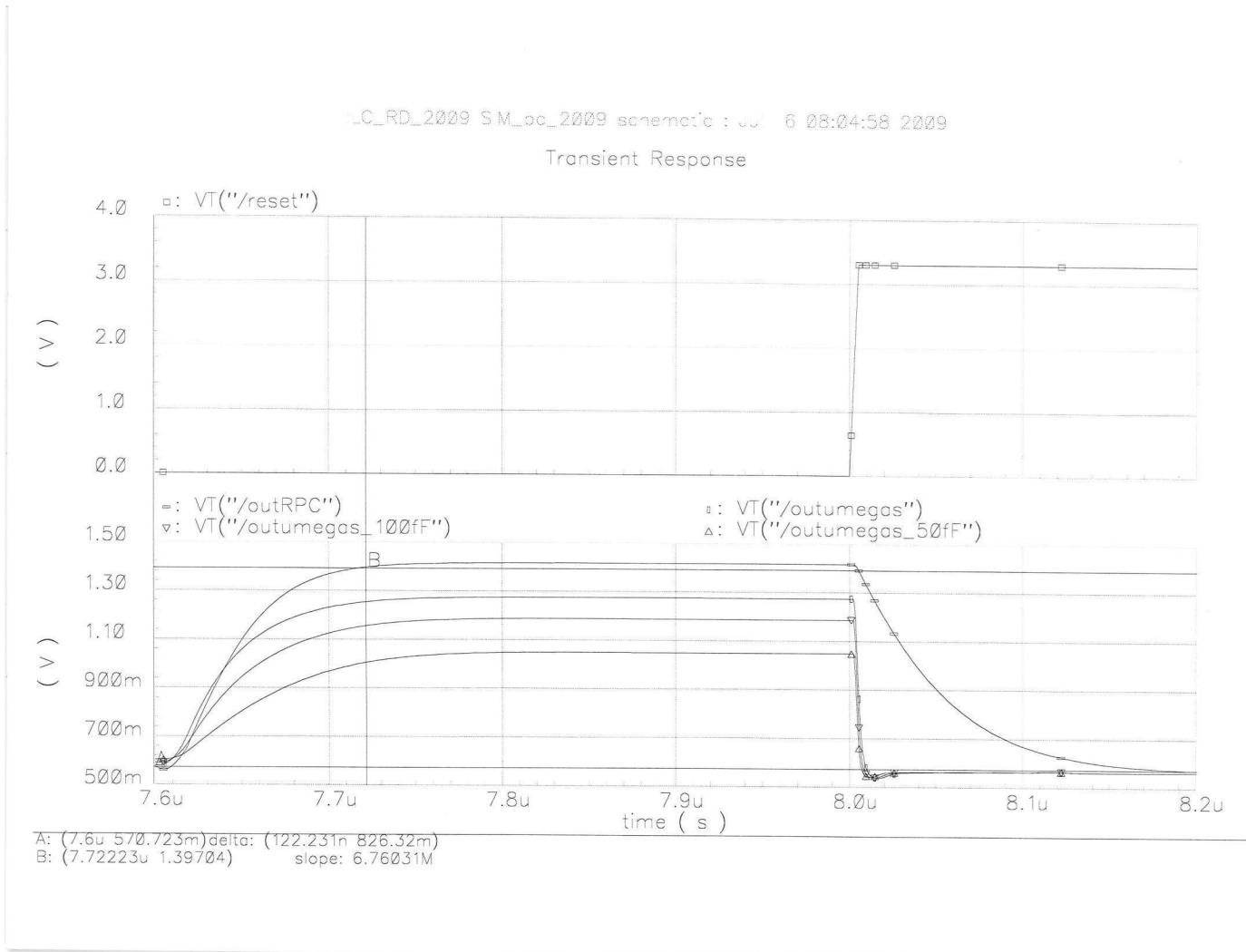


- Qin
- 8.5 pC
 - 170 fC
 - 85 fC
 - 42 fC

Simulation results

ILC_RD_2009 SIM_pa_2009_top config : Jul 9 14:26:48 2009

Transient Response

 


$Q_{in} = 170 \text{ fC}$
 $C_f = 200 \text{ fF}$

A: (4.57022u 567.814m) delta: (412.987n 12.4175m)
 B: (4.98321u 580.232m) slope: 30.0674K

Simulation results

 ILC_RD_2009 SIM_pa_2009_top config : Jul 9 14:26:48 2009



$Q_{in} = 42 \text{ fC}$
 $C_f = 50 \text{ fF}$

ASIC :

- o Return from fab : October
- o Tested before the end of this year
 - o Digital part
 - o Analog part
 - o Mixed analog and digital

- o Next step
 - o Digital part can be implemented in DIRACx/HARDROCx