

# Omega

## Status of SPIROC

Michel Bouchel, Stéphane Callier, Frédéric Daluocq, Julien Fleury, Gisele Martin-Chassard, Christophe de La Taille, Ludovic Raux



vendredi 15 janvier 2010

*Orsay MicroElectronic Group Associated*


- Plan for 2010 :
  - February 2010 dedicated production run: **2 prototypes** will be submitted:
    - A **conservative** prototype (SPIROC 2a) in which the major bugs of SPIROC 2 will be fixed
    - A **little more aggressive** prototype (SPIROC 2b) in which the major bugs of SPIROC 2 will be fixed and some light improvements will be added
  - Before the end of the year, submission of a SPIROC 3 **with more aggressive modifications and improvements**



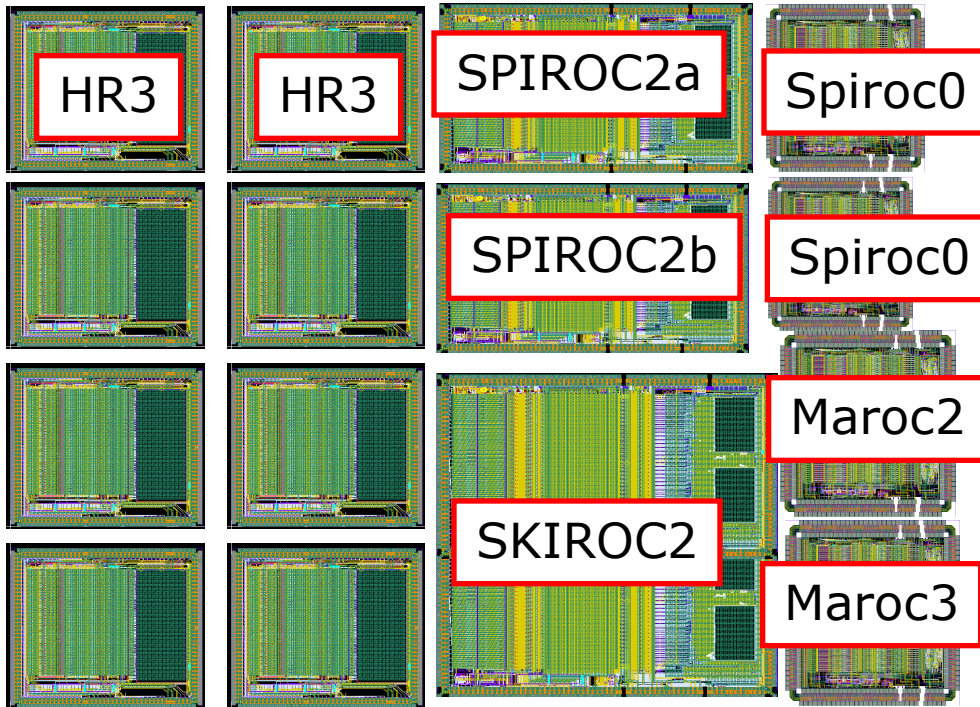
# Engineering run



- Reticle size : 18x25 mm2
  - 50-55 reticles/Wafer
  - 25 wafers needed
- Arrangement to be finalized
  - 8 Hardroc 2b => 10000 chips
  - **1 Spiroc 2a**
  - **1 Spiroc 2b**
  - 1 Skiroc 2
  - 1 Maroc 2
  - 1 Maroc 3
  - 2 Spiroc 0 (SPIROC « light » version) or 1 SPIROC 0 + 1 ParisRoc
- Will be launched as soon as measurements are complete !
  - Exp. Beg.2010




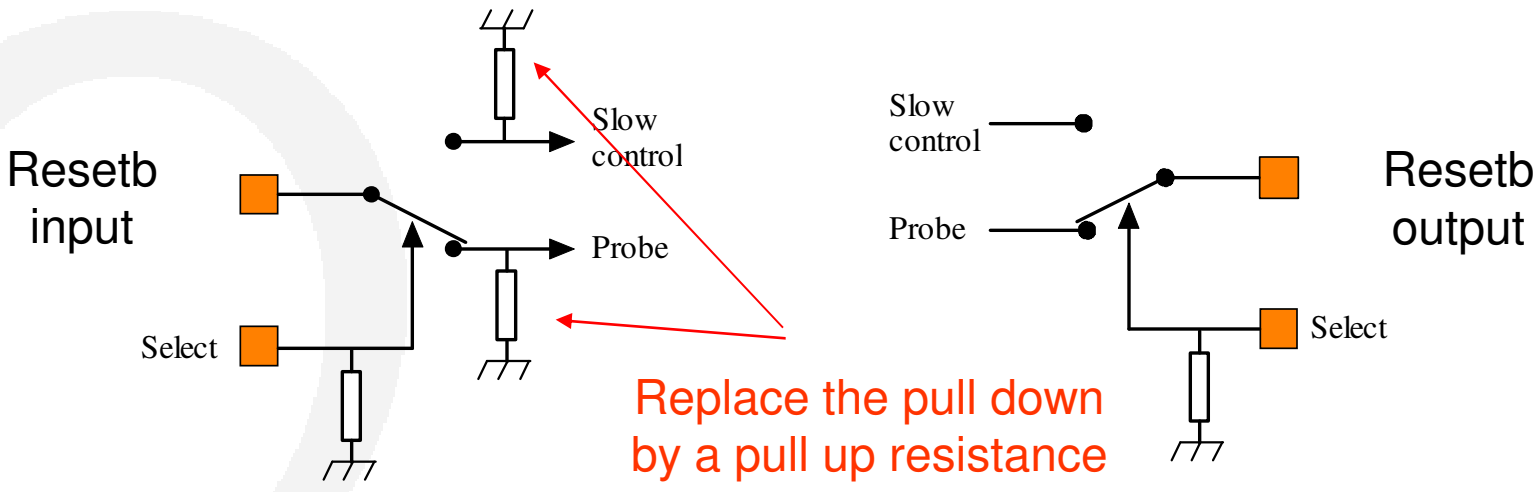
- Conservative version of SPIROC 2:
  - fix the slow control and probe bus :
    - By adding buffers in critical points as done in HARDROC2B
    - By correcting the Bug on the reset signal of the multiplexed probe and slow control register
      - » **Active low reset forced to 0 when not selected**
      - » **Intempestive reset when register is unselected**




- By putting a default Slow control set-up

• Conservative version of SPIROC 2:

 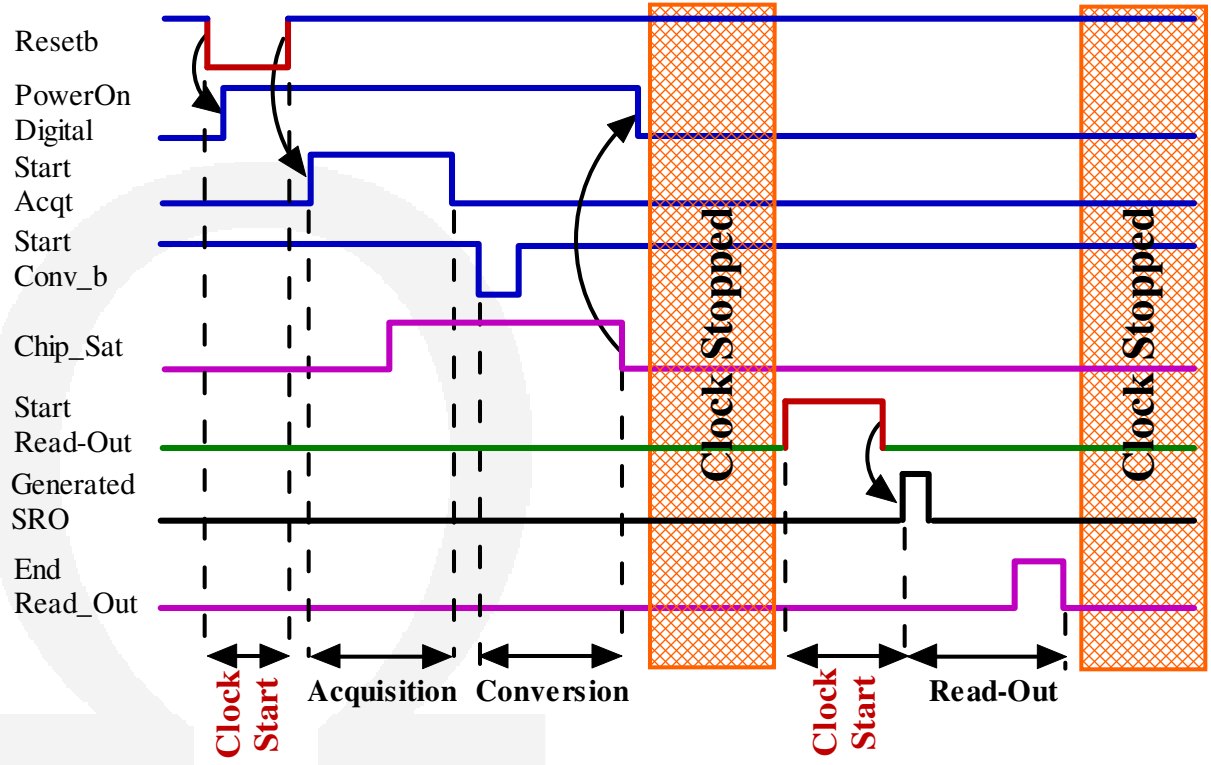- add the POD module for the 2 clock LVDS receivers to reduce idle power dissipation (already tested on Hardroc2)




 - Calibrated (LVDS start time)
- From DAQ
- From daisy chain
- From ASIC
- From POD



- Conservative version of SPIROC 2:

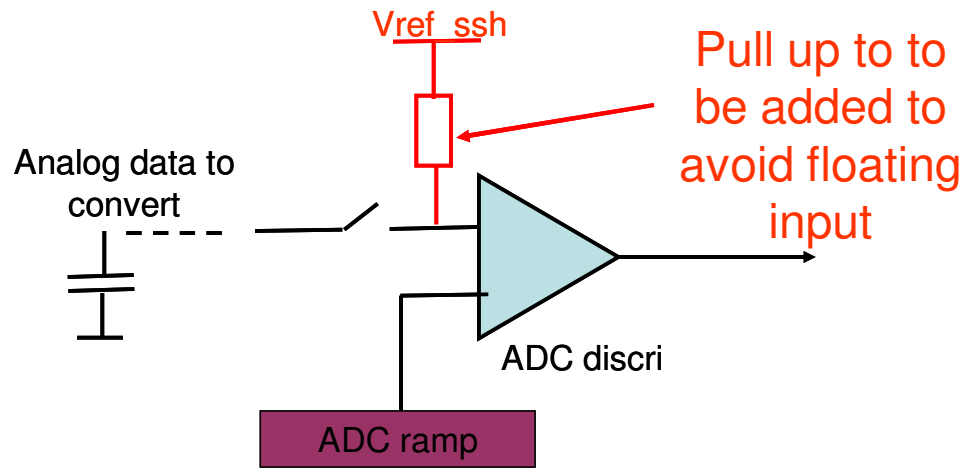- fix the first "zero-frame" by adding a pull-up to reference voltage on ADC discri input




- Put a OR36 output on a non selected
- Decrease the consumption of the low gain preamplifier





This spiroc2a prototype is ready to be submitted

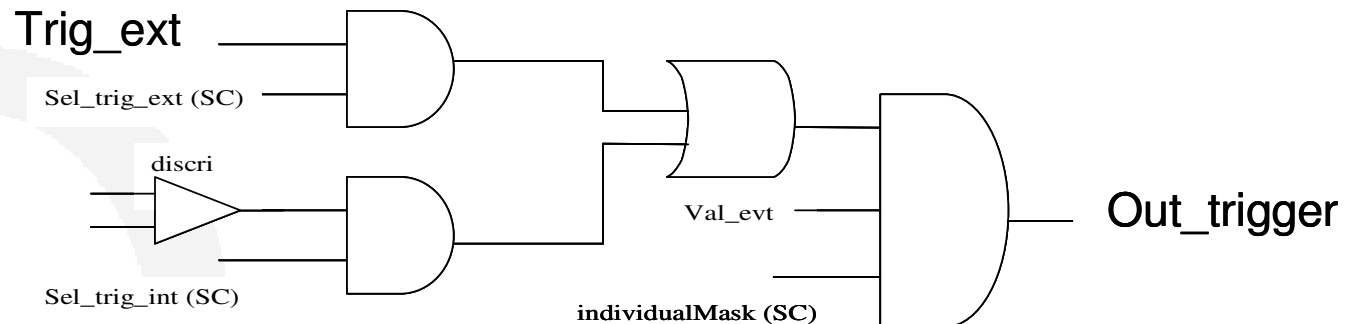- SPIROC 2a with the following improvements:
  - **New bandgap**
  - **Replace the ADC ramp by an optimized one**
  - **Replace the ADC discriminators by an improved one (PARISROC)**
  - **External trigger input (LVDS)**



- **put the improved version of 8-bit input DAC**
- **put the improved version of threshold 10-bit DAC**

# SPIROC 1&2 input DAC performances

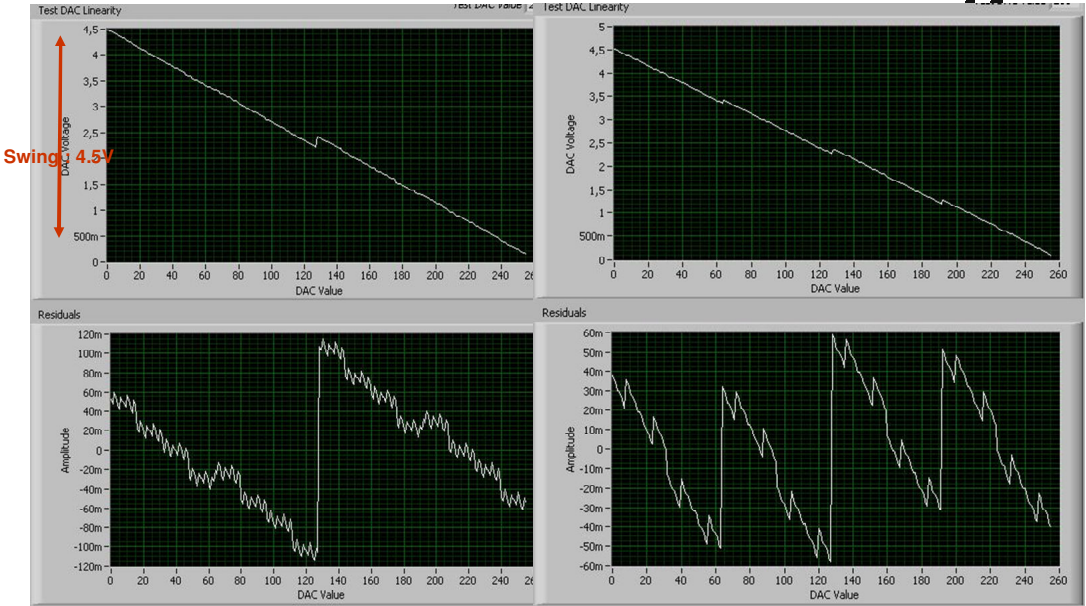 


**Linearity residuals vary from +/- 60mV  
1 to +/- 120mV (from 1.5 to 3%)**





- **Input DAC to optimize SiPM bias voltage**
- **8-bit DAC, 5V range**
- **LSB=20mV**
- **36 DAC : one per channel**
- **Ultra low power (1μW) : no power pulsing**
- **Can sink 10 μA leakage current**
- **DAC uniformity between the 36 channels : ~3%**



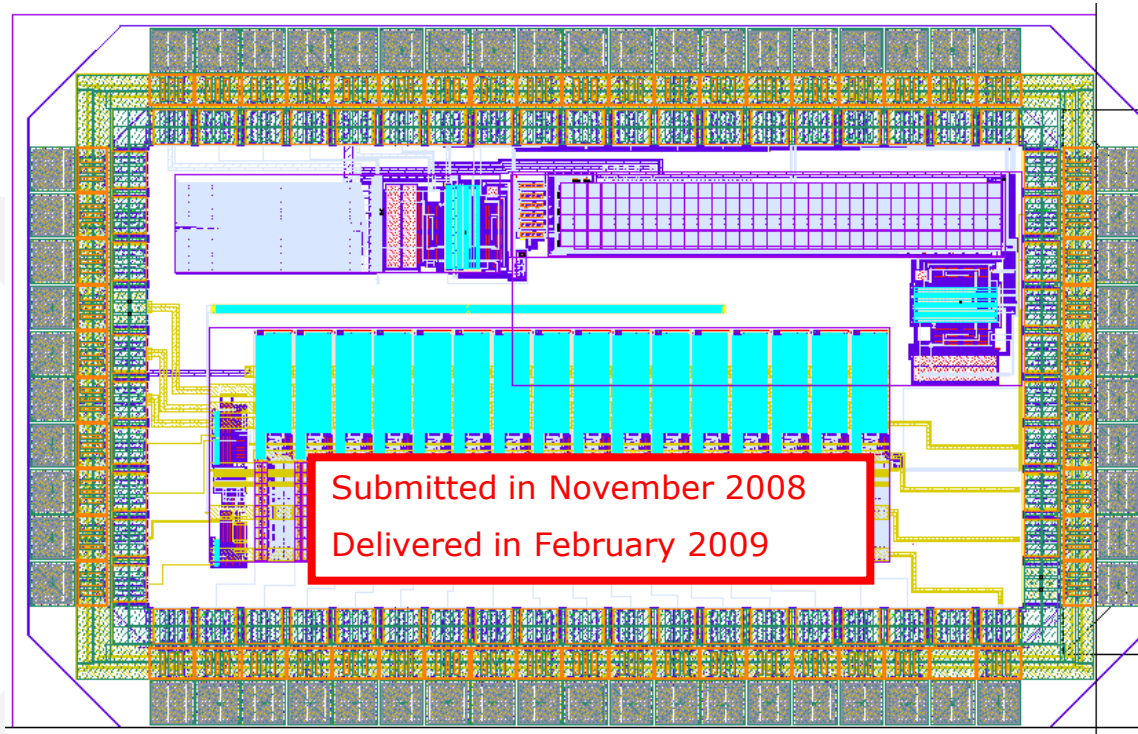- « **Building block** » funded by IN2P3 submitted november 2008
  - 2 12-bit DACs for the threshold trigger:
    - **NMOS**
    - **Bipolar**
  - 16 8-bit low power input DAC for SiPM bias
- Improved performance (linearity, uniformity channel by channel) were expected with a new layout rearrangement for a better matching


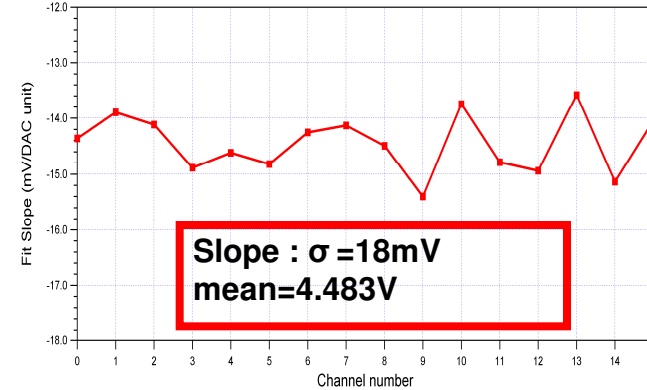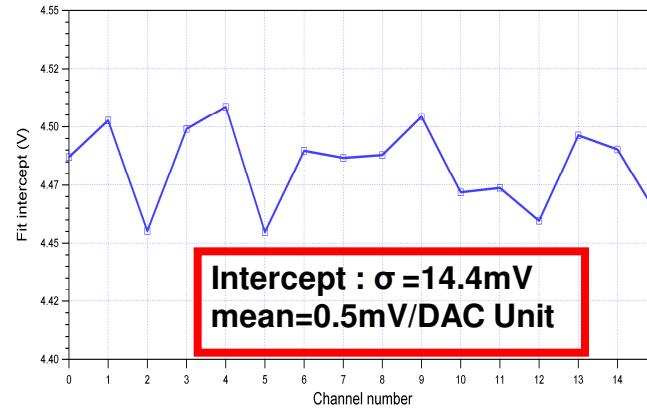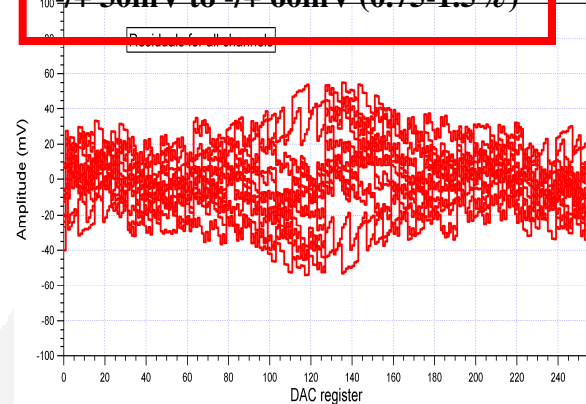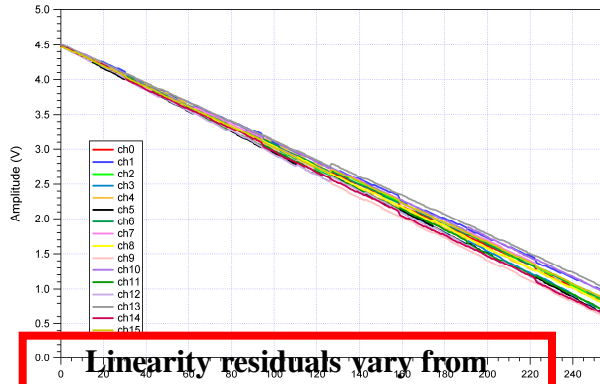
# « Building block » input DAC Performance



- Disappointing performances on the « building block » DAC only a factor 2 won
- Have to be improved by a new geometrical re-arrangement
  - New layout ready to be implemented on **SPIROC2b**

# SPIROC 3: modifications and improvements *Omega*

- SPIROC 2a + SPIROC 2b with the following improvements:
  - Preamplifier gain adjustment per channel
  - New TDC to have 100 ps accuracy (just submitted last November on PARISROC 2 Chip)
  - 8-bit input DAC : auto-regulation with respect to detector temperature
  - “Powering-up mode” of SCA columns to save power:
    - SCA columns are powered only when they are used
  - New improved and optimized digital part
  - Possibly Wei's input stage after testing
  - Possibly new I2C slow control interface

- During February : **PRODUCTION RUN**
- SPIROC 2a chip :
  - **Conservative prototype** : major bugs fixed
- SPIROC 2b chip :
  - **Conservative prototype** with « controlled » improvements submitted at the same time of the Hardroc2b production run
- SPIROC 3 chip :
  - **Agressive modifications and improvements** (before the end 2010?)









- Disappointing performances for the « building block » DAC
- Have to be improved by a new geometrical re-arrangement
  - New layout in progress...
  - DAC, auto-regulation with respect to detector temperature
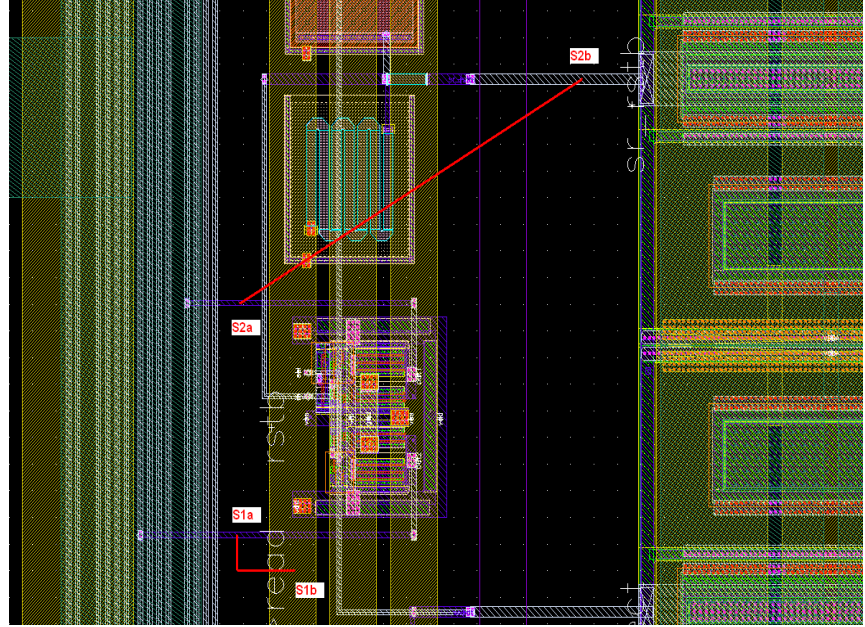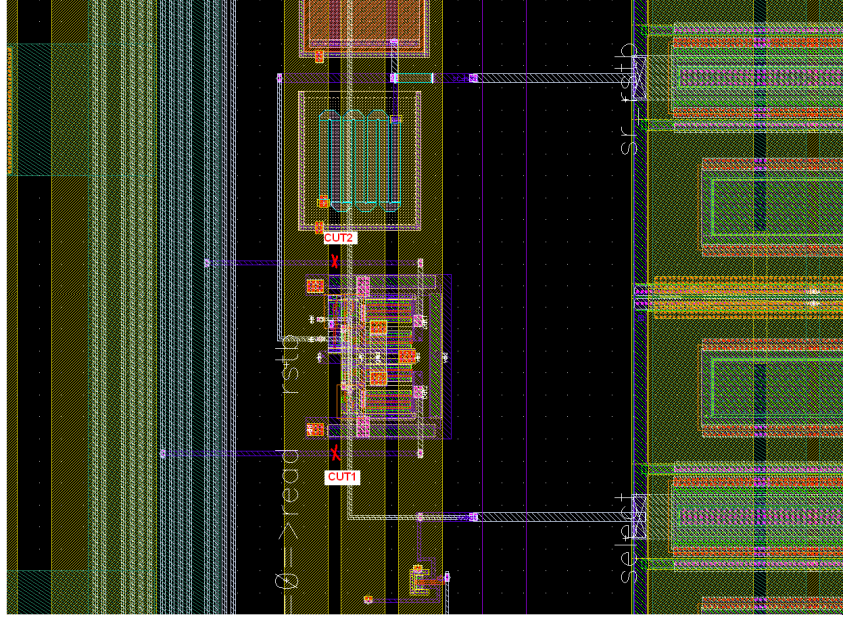  
# SPIROC 2 : slow control register





- **Bug on the reset signal of the new multiplexed probe and slow control register**
  - Active low reset forced to 0 when not selected
  - Intempestive reset when register is unselected
  - Same problem on Hardroc 2


- **Correction by SERMA Compagny : FIB ( Focused Ion Beam )**



 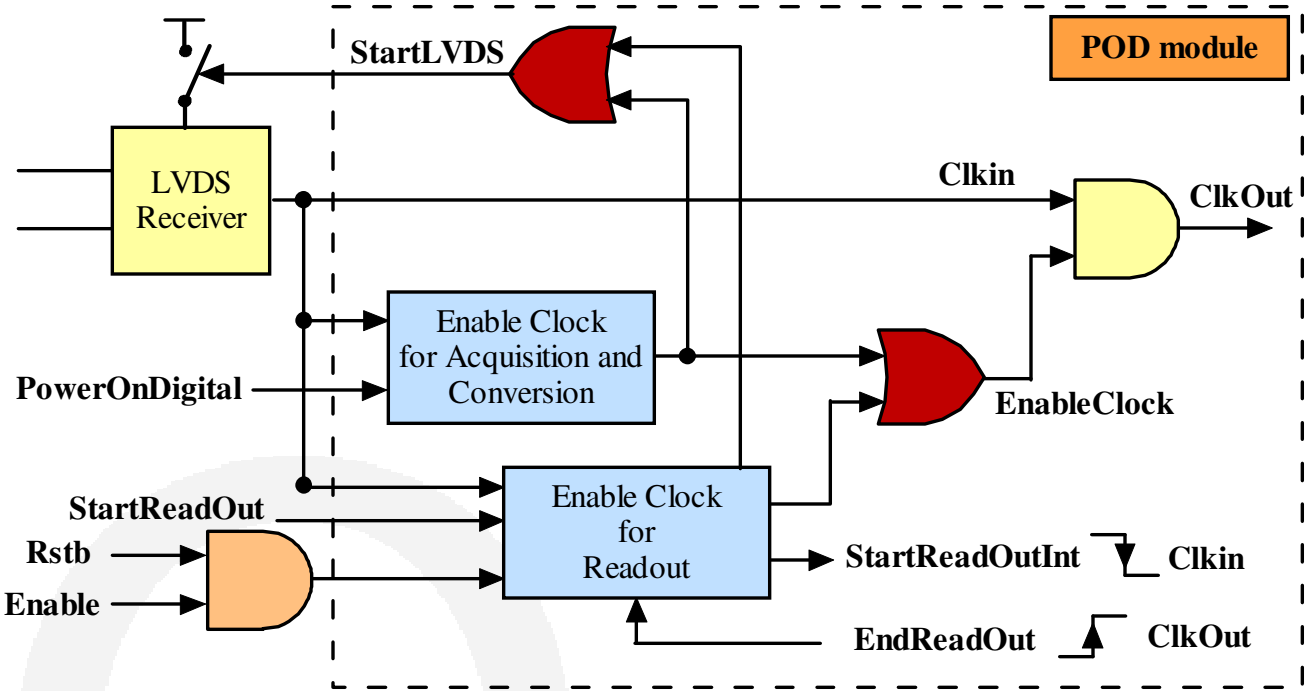
- POD module inserted for the 2 clock LVDS receivers



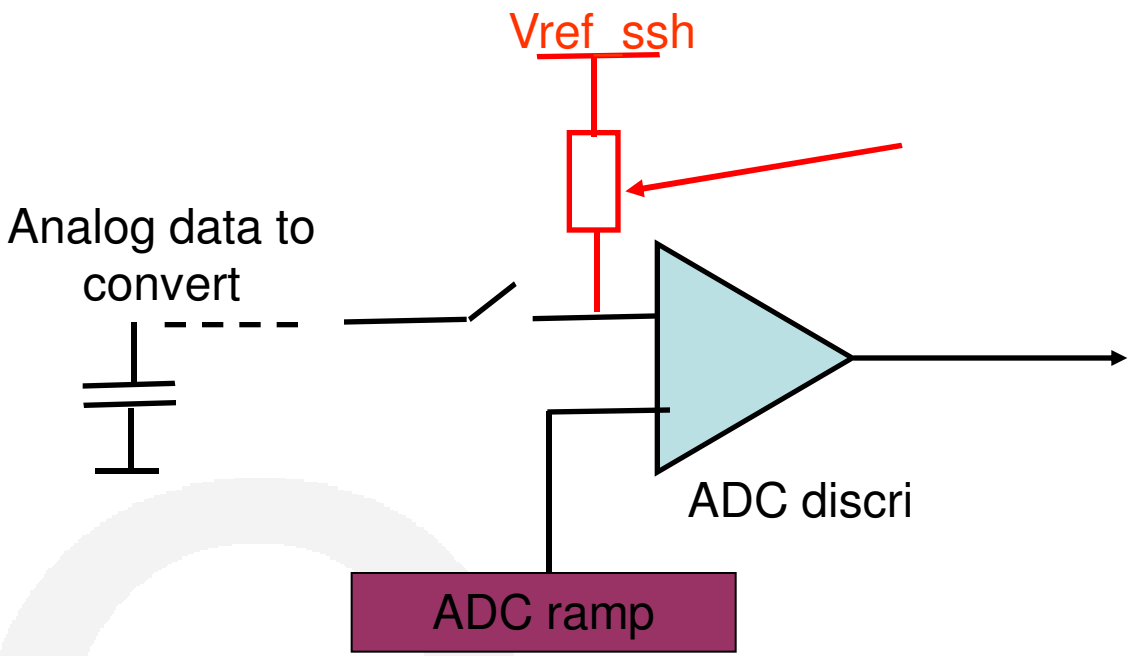- Clock is started asynchronously, enabled and stopped synchronously (at '0')
- 2 others LVDS receivers (RazChn/NoTrig and ValEvt) active during PowerOnAnalog (during bunch crossing)




 - Conservative version of SPIROC 2:
  - fix the first "zero-frame" by adding a pull-up to reference voltage on ADC discri input



This prototype is ready to be submitted


# Power On digital: sequence

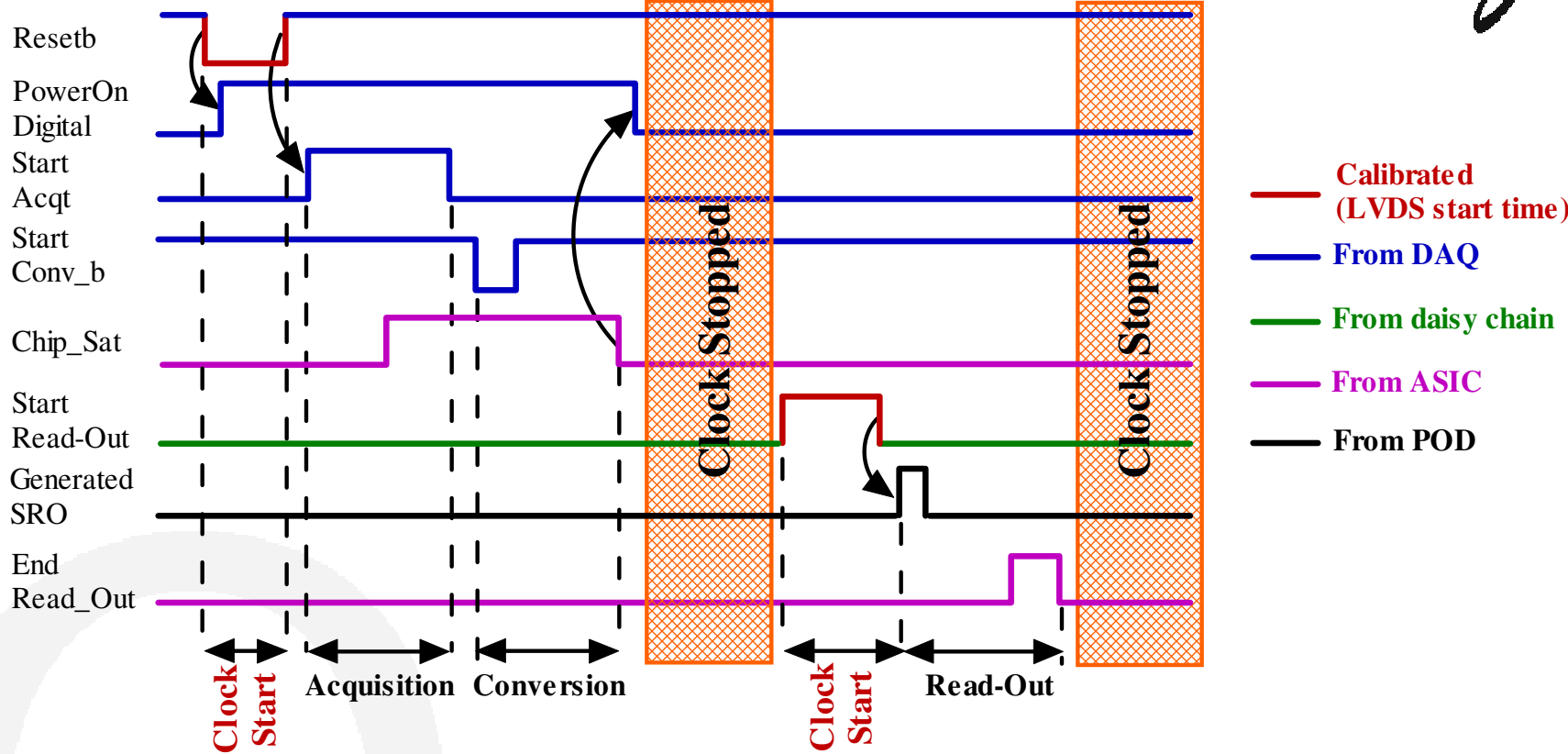


- Some security added:
  - StartReadOut managed asynchronously → low pass filter added
  - Possibility to use StartReadOut instead of the one generated by POD (like first prototype of ROC chips)
  - PowerOnDigital at '1' can force the clock



# SPIROC 1&2 input DAC performances

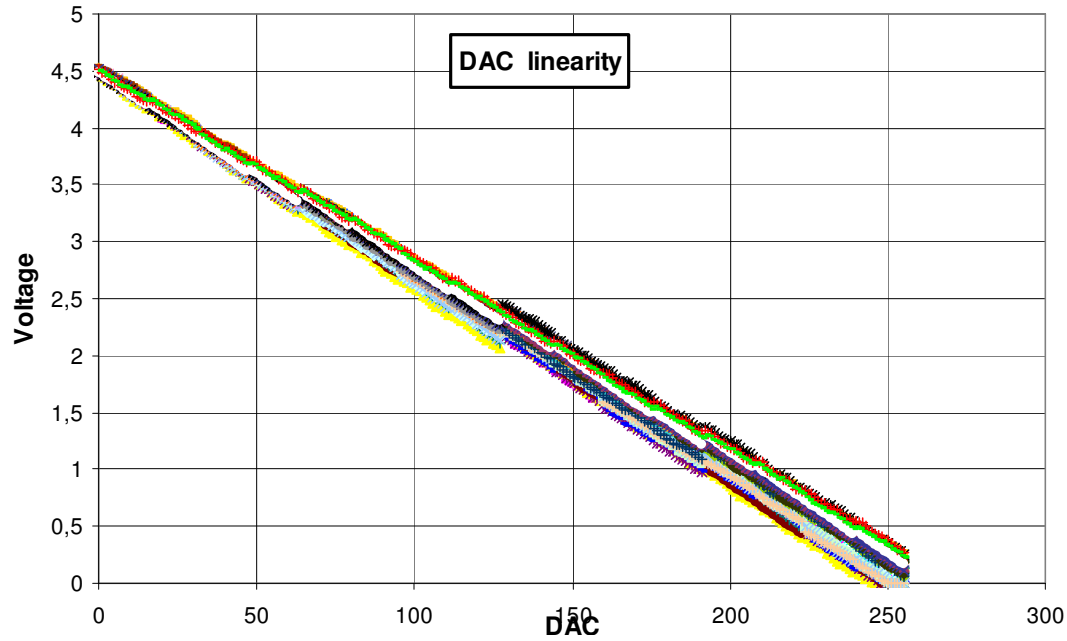


DAC slope repartition

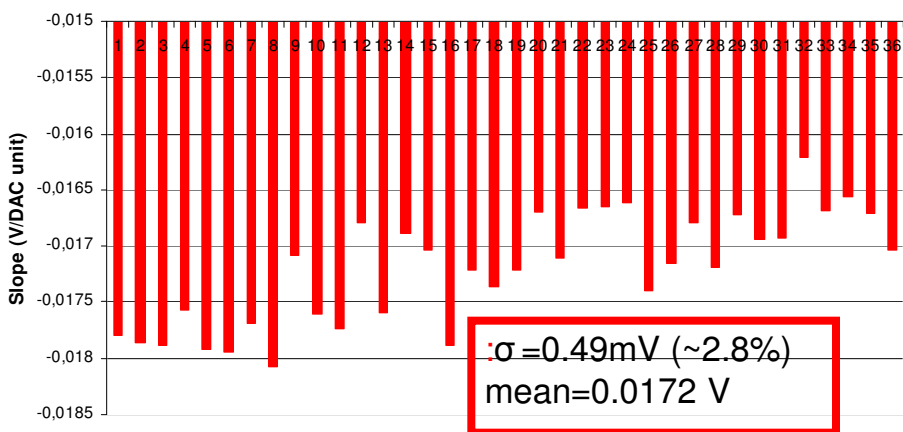

Channel

$\sigma=8\text{mV}$  ( $\sim 0.2\%$ )  
mean=4.49V



intercept repartition

 


Channel
 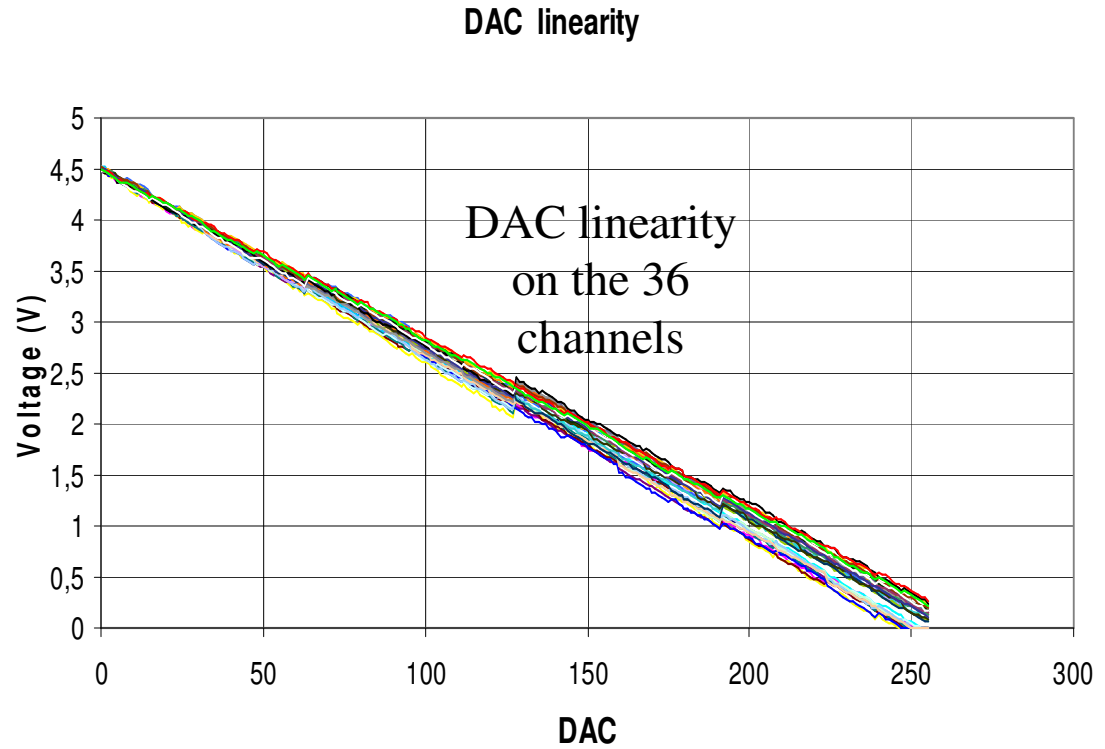
# Input DAC





- **Input DAC to optimize SiPM bias voltage**
- **8-bit DAC, 5V range**
- **LSB=20mV**
- **36 DAC : one per channel**
- **Ultra low power (1 $\mu$ W) : no power pulsing**
- **Can sink 10  $\mu$ A leakage current**
- **Linearity :  $\pm 2\%$**
- **DAC uniformity between the 36 channels :  $\sim 3\%$**



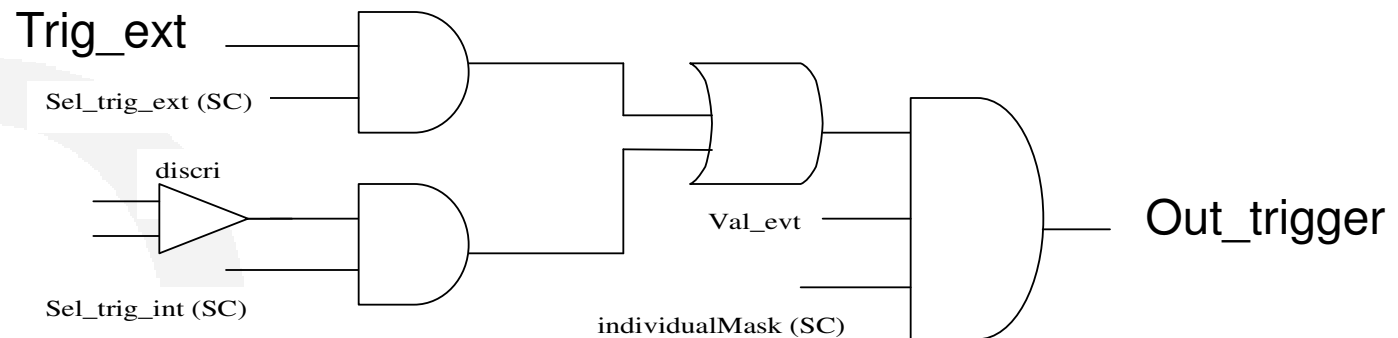

- Better performances but disappointing....
- Have to be improved by a new geometrical re-arrangement
  - New layout ready to be implemented
  - auto-regulation with respect to detector temperature

# SPIROC 1&2 input DAC performances

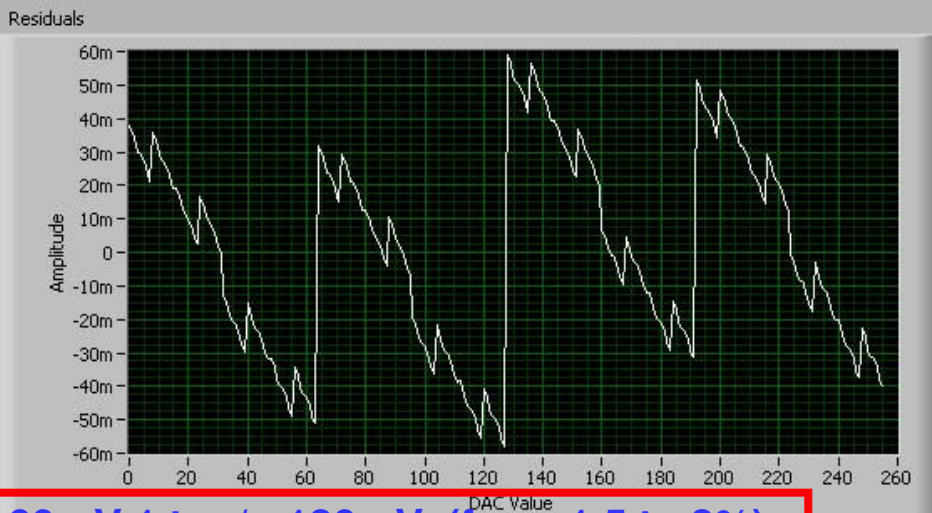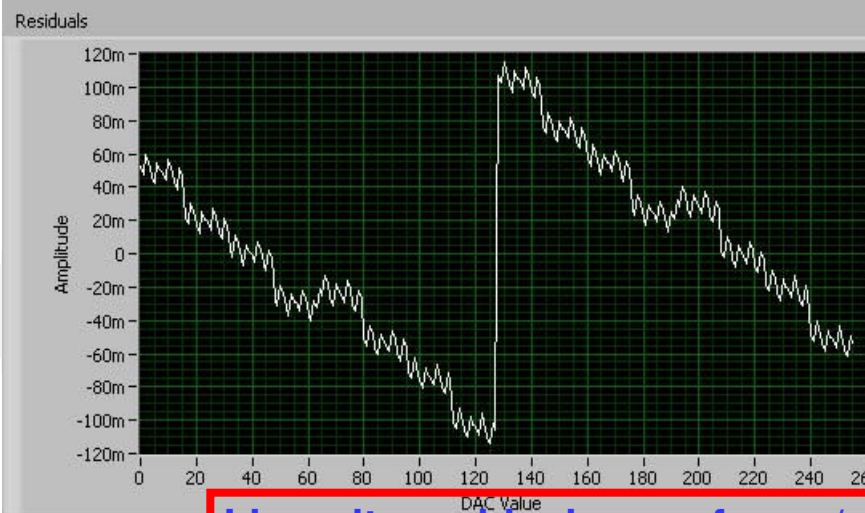  

Linearity residuals vary from  $\pm 60\text{mV}$  1 to  $\pm 120\text{mV}$  (from 1.5 to 3%)