

Progress on readout electronics for LumiCal detector

Krzysztof Swientek

Swientek@agh.edu.pl

(FCAL collaboration)


Department of Physics and Applied Computer Science
AGH University of Science and Technology

EUDET Annual Meeting, 29 – 30 September 2010, Hamburg




Outline

 - 1 Front-end electronics
- 2 ADC prototypes
- 3 Other readout issues
- 4 Summary and future plans




LumiCal readout architecture

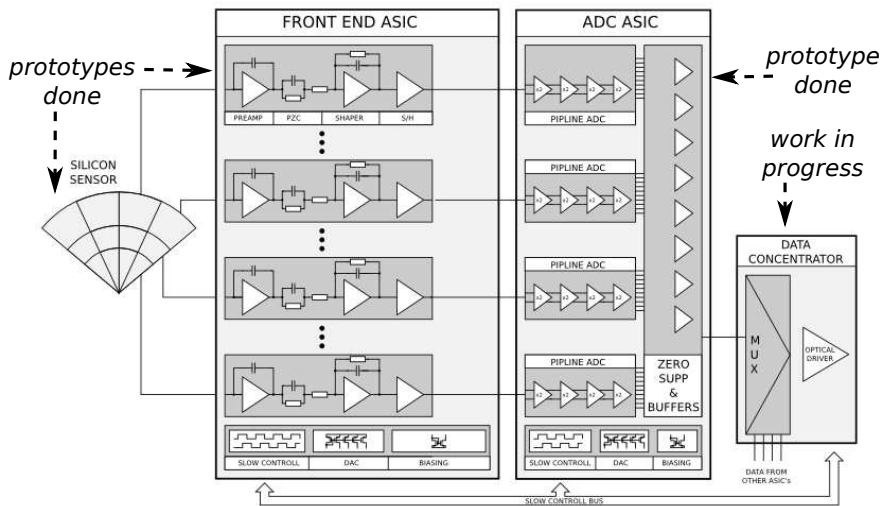


Front-end electronics I

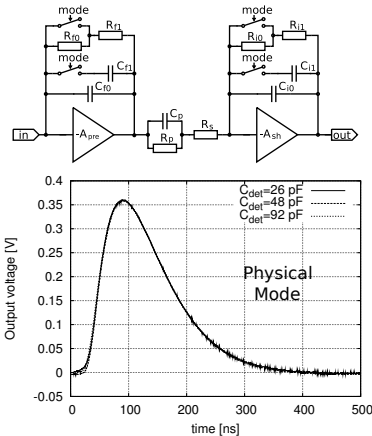- $C_{det} \approx 0 \div 100\text{pF}$
- 1st order shaper ($T_{peak} \approx 60\text{ ns}$)
- variable gain: MIP (calibration mode) and input charge up to 10 pC (physics mode)
- power: 8.9 mW/channel
- rate up to 3 MHz



Front-end electronics II


- ASIC contains 8 channels
- measured crosstalk < 1%
- prototypes fabricated and tested (tests completed)

 


AMS 0.35 μm

- 4 front-end ASICs (32 channels) were used during first test

Single channel 10-bit pipeline ADC


 


- 1st prototype: only 8 stages (fully functional)
- 2nd prototype of complete ADC (photo)
 - 9 stages + S/H
 - digital correction
 - clock and power switching
 - external reference voltages
- 2nd prototype fully functional, tests completed

 

AMS 0.35 μm

 
 
2nd ADC prototype — static and dynamic parameters



- static parameters
 - INL < 1 LSB
 - DNL < 0.5 LSB

- dynamic parameters
 - SINAD = 57.7 dB
 - ENOB = 9.3
- works well up to 25 MHz


2nd ADC prototype — power scaling

  

- power consumption scales linearly in frequency range 3 k ÷ 10 MHz
 - 0.8 mW/MHz with supply 3.0 V (plot)
 - 0.6 mW/MHz with supply 2.6 V
- useful also for CLIC

Total includes also input/output buffers


2nd ADC prototype — power switching

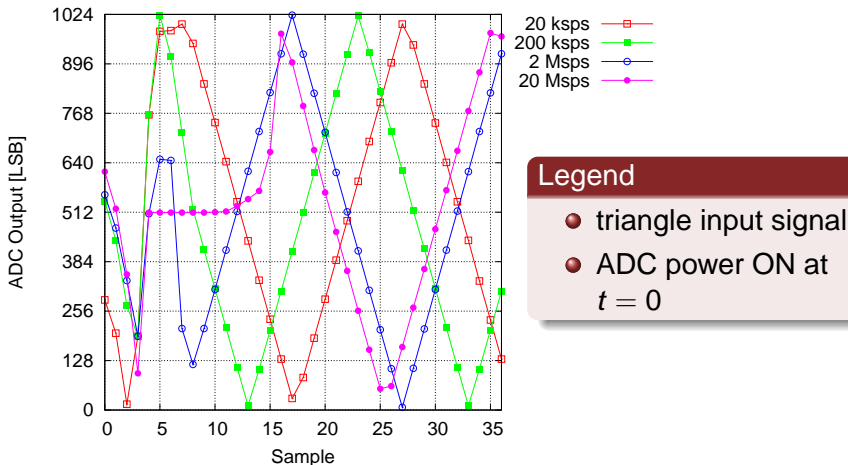

- depending on sampling frequency 8 clock cycles or 800 ns (16 clk @ 20 MHz) needed to restart correct conversion

10-bit low power high swing DAC

- 10th bit achieved by current reversing
- prototype fully functional, tests completed
- nonlinearities DNL & INL < 0.42 LSB
- ENOB = 9.8
- settling time 0.5 – 2 μm
- power consumption 0.6 mW

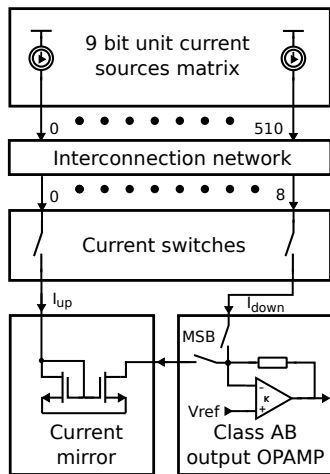


AMS 0.35 μm

Other readout peripherals

- bandgap based precise reference voltage source, prototype fully functional
- bandgap based temperature sensor, prototype fully functional
- fast LVDS driver and receiver (around 1 Gb/s), prototype fully functional
- first prototype of 1 GHz PLL based wire transceiver, prototype fully functional
- all prototypes were manufactured in AMS 0.35 technology




Multichannel ADC — layout

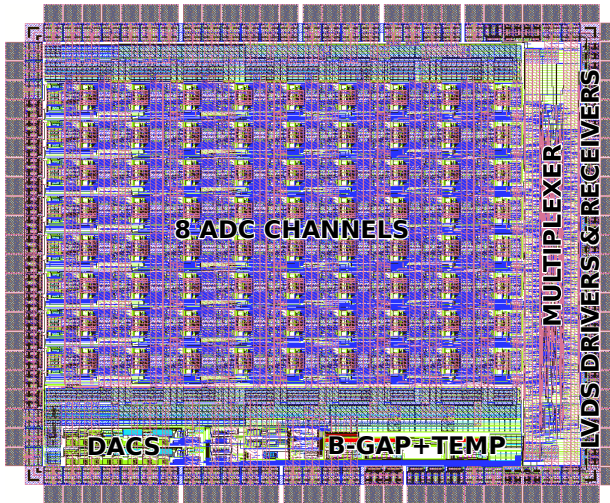


AMS 0.35 μm

Multichannel ADC — preliminary results

   - gain & offset spread < 1%
- maximum sampling frequency about 45 MHz




LumiCal data concentration

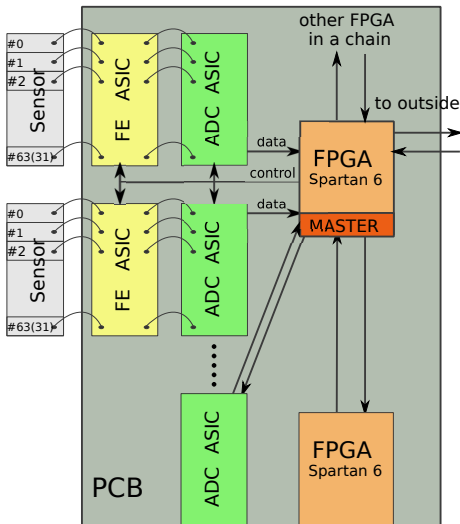


- one ADC for each FE channel
- one FPGA (or ASIC in the future) per sensor tail (256 channels — 4 or 8 ASICs)
- one master FPGA transmitting data out per detector half-layer
- master FPGA is connected to DIF — first level of standard DAQ

First tests on beam

 

 - dedicated PCB
- LumiCal sensors with fanout
- 8 front-end ASICs (64 channels)
- external ADC (multichannel ASIC ready)



EUDET milestones, deliverable and more ...

- EUDET milestones and deliverable
 - prototypes of two readout ASICs: front-end and ADC are produced, tested and ready
 - front-end functionality with fanout and sensors was confirmed during test beam
- more (in view of complete detector readout)
 - complex readout — multichannel ADC including: multiplexer, DACs, LVDS, bandgap based references and temperature sensor is in advance stage
 - works on PLL based 1 GHz wire transmitter on progress

Future plans — AIDA

- re-design of front-end ASIC according to upgraded detector specification
- design a complete multichannel readout system (already started with multichannel ADC ASIC)
- proceed with data concentration and system powering
- continue the works on fast wire transmitter (already started with first PLL prototype)
- move some readout blocks to smaller size technology (promising candidate IBM 0.13 μm , works already started)

Summary

- EUDET milestones and deliverable accomplished — prototypes of readout ASICs: front-end and ADC ready and fully working
- first test beam with sensor, fanout and front-end succeeded
- works on complete sensors readout in advanced stage (multichannel ADC, DAC, LVDS etc.)
- the goal is to have a prototype of multilayer detector at the end of AIDA