


R&D activity @ LPC Clermont-Fd dedicated to the VFE of the Si-W Ecal

Laurent ROYER, Samuel MANEN, Pascal GAY


LPC Clermont-Ferrand



 
- ✓ Sandwich structure of: thin wafers of silicon diodes & tungsten layers
 - Embedded Very Front End (VFE) electronics
 - Deeply integrated electronics
- ✓ Large dynamic range of the input signal (15 bits)
 - ✓ **0.1 MIP -> ~3 000 MIPs**
- ✓ Minimal cooling available
 - Ultra-low power : 25 μ W per VFE channel
 - ⇒ power pulsing required




 « Tracker electronics with calorimetric performance »



"Long is the road ..."

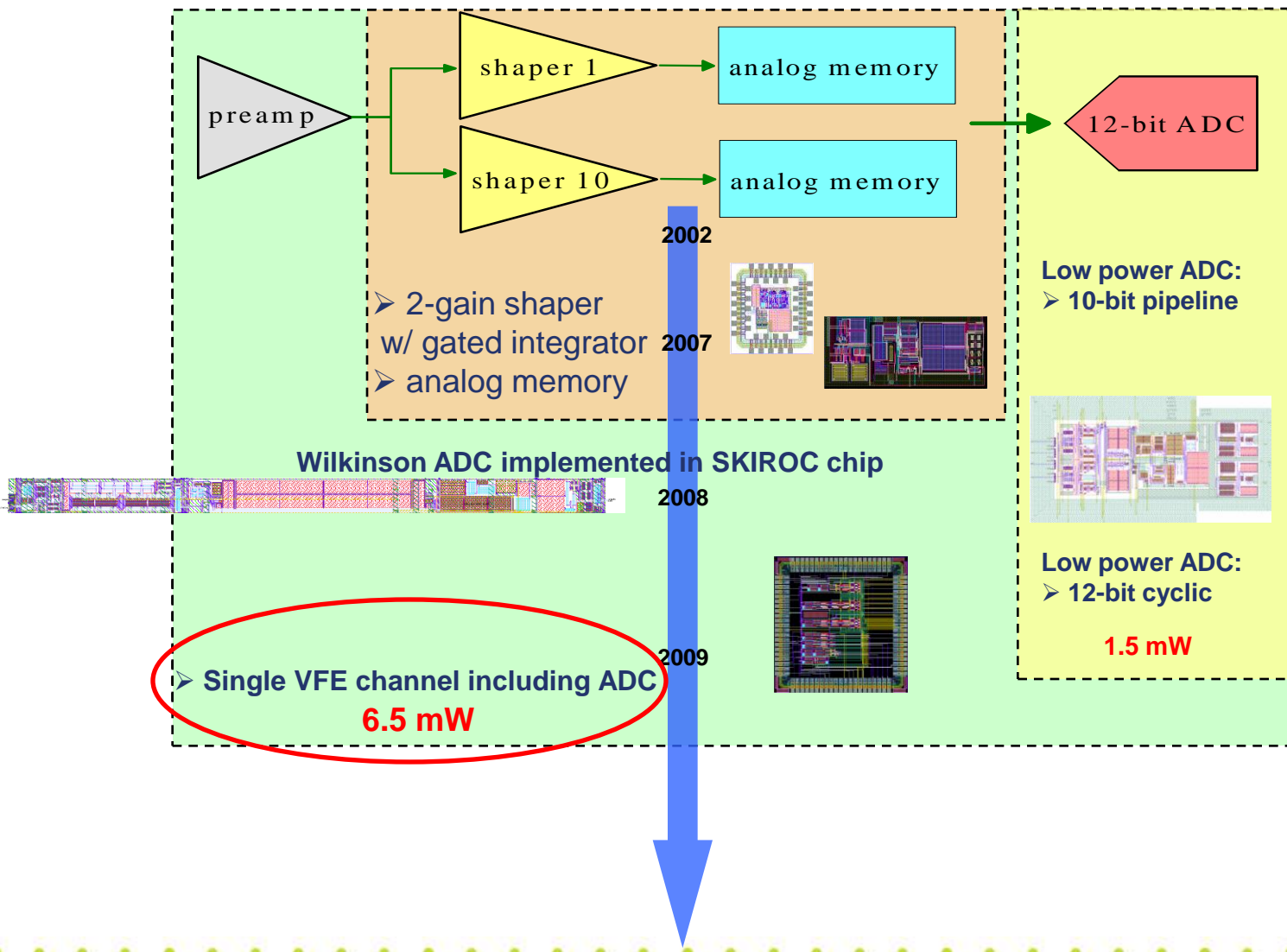

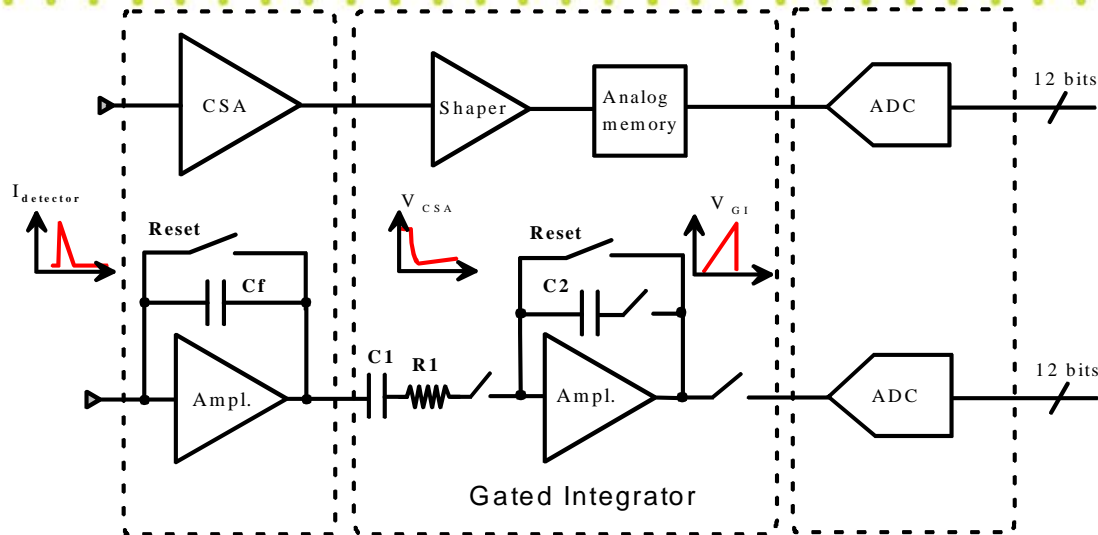

✓ Charge Preamplifier

- The amplification of the charge delivered by the detector is performed with a low-noise Charge Sensitive Amplifier (CSA)

✓ Shaper and Analog Memory

- The bandpass filter is based on a gated integrator which includes an intrinsic analog memory thanks to the integration capacitor

✓ Analog to Digital Converter

- The converter is a customized low power 12-bit cyclic ADC


✓ External digital block (in a FPGA)



- The amplifier is based on a boosted folded cascode, followed by a source follower
 - **Boosted Cascode** : High gain performance
 - **Source follower** : Low output impedance

$$V_{out} \approx -Q/C_f$$

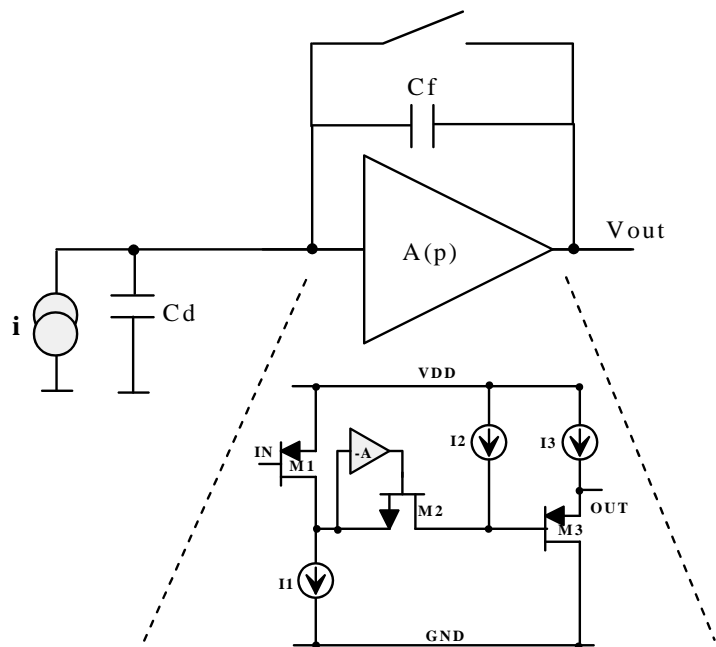Q , the charge delivered by the detector.
 C_f , the feedback capacitor.





MAIN CHARACTERISTICS OF THE CSA (SIMULATED RESULTS).

Power supply	3.3 V
Consumption	3.54 mW
$C_{Detector}$	30 pF
$C_{Feedback}$	
Transconductance	
Open Loop Gain G_{OL}	85 dB
Gain-Band Width	105 MHz
Output swing	1.0 V
ENC (with a 200 ns CCRC shaper)	0.5 fC
Dynamic range	80 dB

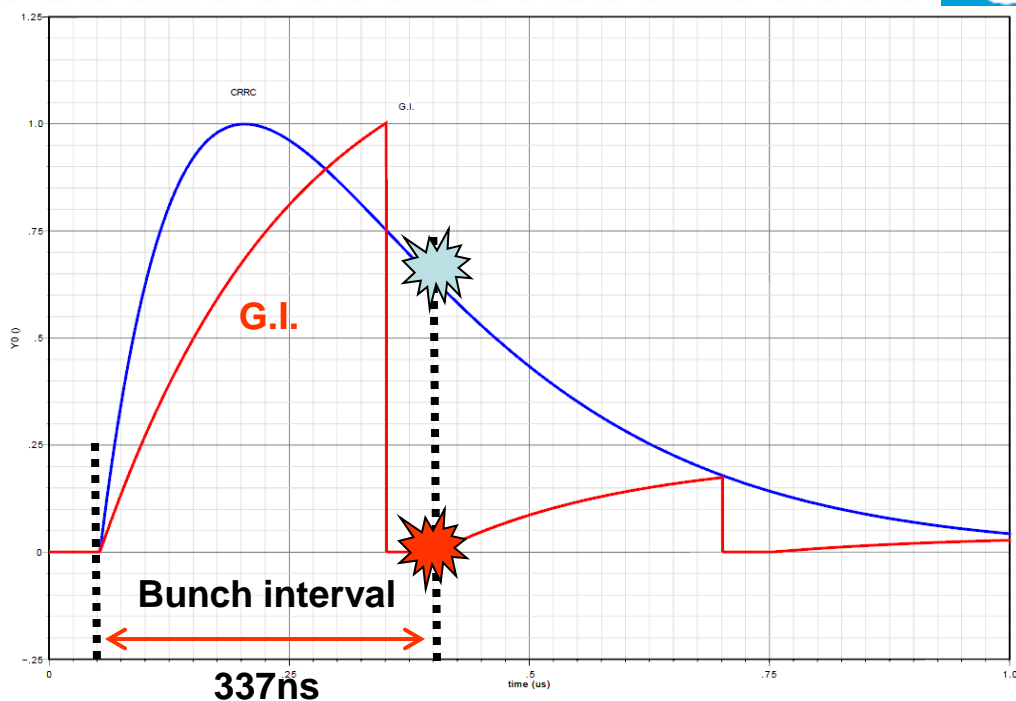
 
50% for masters of the current sources
 → can be shared by several channels







- The integration capacitor of the G.I. can be used as an analog memory cell (switch opened at the end of the integration)
 - no extra analog-memory stage required
- The fast switched reset of the capacitor of the G.I. allows a time of integration near to the bunch interval
 - no pile up
 - improved noise filtering (see next slides)

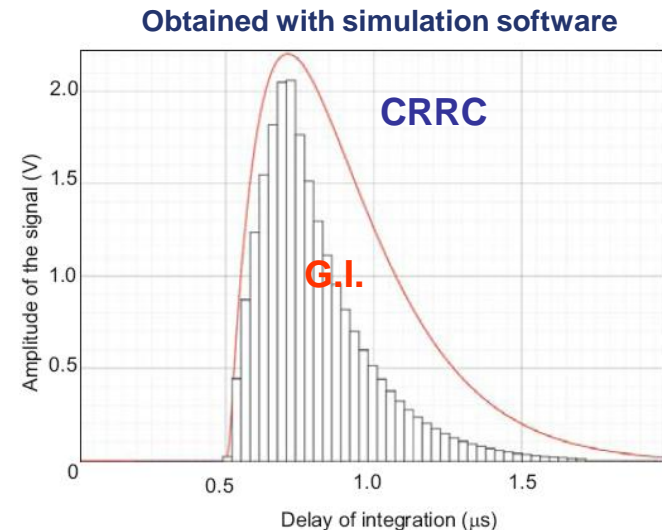 - CRRC shaper is **time invariant** filter
- Gated integrator is **time variant** filter
- **To compare performances, weighting functions $R(t)$ in time domain MUST BE USED**
- *The weighting function is the measurement of influence of a noise step generated before the measuring time on the amplitude at the measuring time*



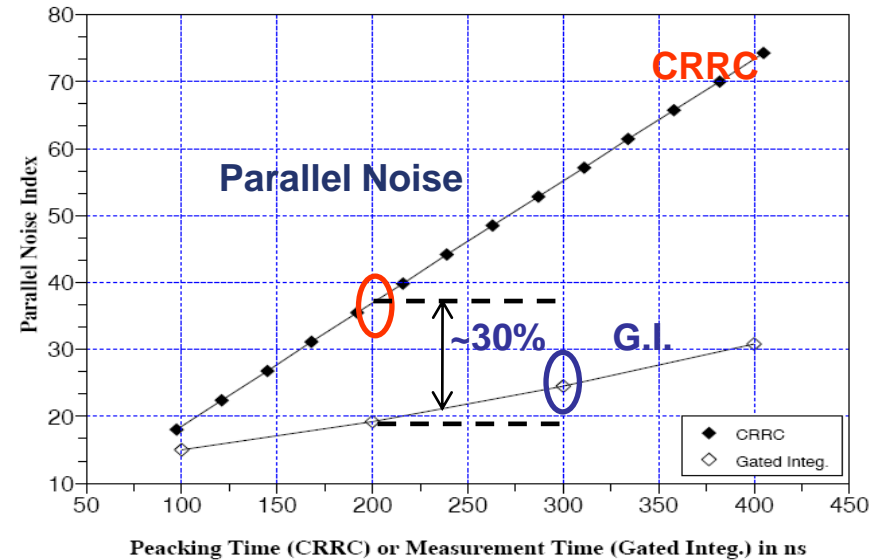 
- Noise indices have been simulated with Analog Artist (Cadence) Software for several peaking times (CRRC) and durations of integration (G.I.)




- The peaking time of the CRRC shaper is limited due to pile-up consideration
→ 200ns with a bunch crossing of 337ns (ILC).
 - For the Gated Integrator, fast reset of integration capacitor allows duration of integration near to the bunch crossing interval
→ 300ns with bunch crossing of 337ns
- both serial and parallel noise indexes can be reduced by about 30% with the G.I. filtering.



 - Variation of the noise versus the time of integration of the G.I. obtained by simulation (serial index) and by measurement
 - Dominated by serial noise.**



 

Architecture	1.5-bit/stage
Area	0.12 mm ²
Supply Voltage	3.0 V
Resolution	12 bits
Dynamique range	2.0 V differential
Time of conversion	6.8 μs
Consumption	1.5 mW
INL	3 LSB
RMS Noise	0.3 LSB



➤ The cyclic architecture is well adapted to **compact-low-power** converter.

➤ 1.5 bit per stage architecture


➤ Clock frequency: 1MHz

➤ Presented IEEE NSS 2008 Dresden

 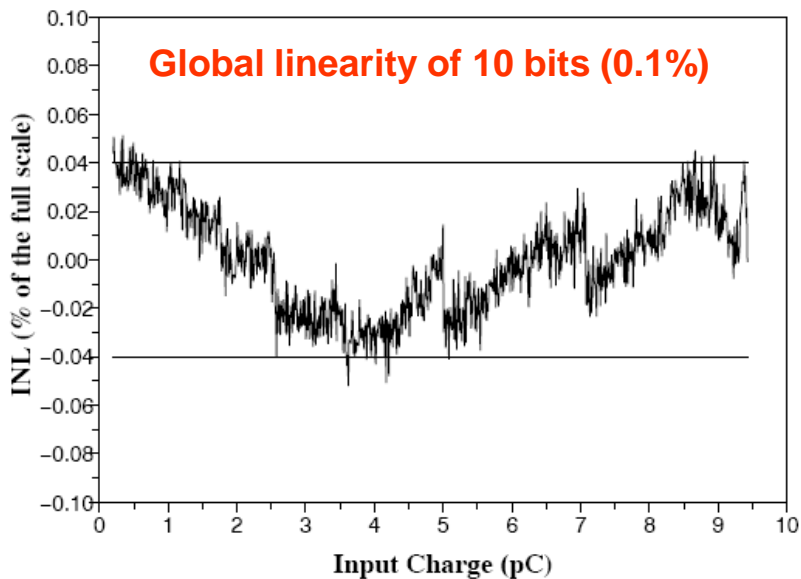
➤ “A custom 12-bit cyclic ADC for the electromagnetic calorimeter of the International Linear Collider”




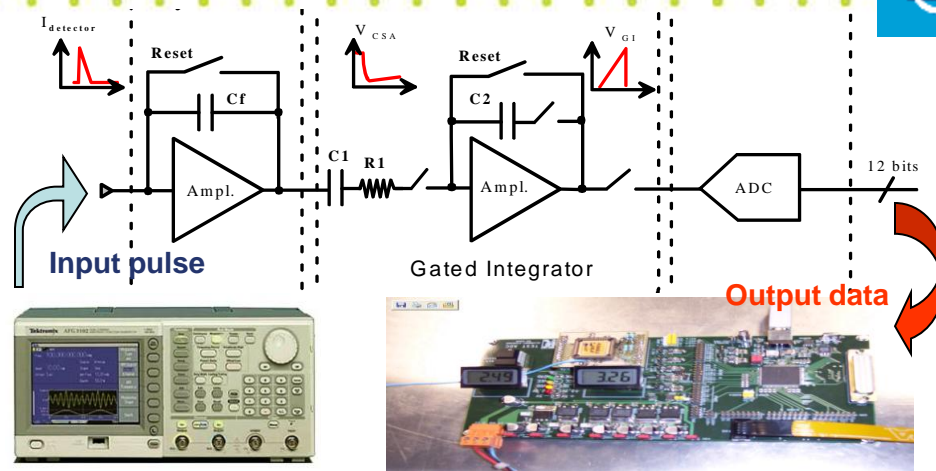
The power consumption of the channel is **6.5mW**, estimated to **25 μ W** with duty cycle of each block.



 
The standard deviation of the noise at the output of the channel is **0.76 LSB (370 μ V rms)**.
 The Equivalent Noise Charge (ENC) at the input of the channel is then lower to **2 fC**.



 
 
Dispersion of the gain of the 9 chips (in %)



 Dispersion of the offset of the 9 chips (in mV)



  - ❑ A VFE channel performing the amplification, the filtering, the memorization and the digitalization of the charge from Si detector has been designed and tested.
 - ❑ **Global Linearity better than 0.1 % (10 bits) up to 9.5 pC (2375 MIP).**
 - ❑ **ENC = 1.8 fC (0.5 MIP) with a single gain stage**
 - ❑ **Power consumption with power pulsing estimated to 25 μ W (no digital part).**






❑ Next steps

- ❑ Improvement of the dynamic range up to 15 bits
 - Reduction of the output noise of the amplifier of the Gated Integrator
 - Integration of a multi-gain system on the CSA
 - Use of a multi gain shaping
- ❑ Integration of the digital block, of the bandgap (ADC references), of the power pulsing, ...
- ❑ **Test-bench for the VFE channel**
 - ❑ realistic environment : wafer/ASU + VFE + (DIF)/DAQ
 - ❑ versatile and upgradable
 - ❑ connected to wafer test-bench already in LPC-Clfd
 - ❑ have to be discussed with LPC-Clfd management for Manpower resource
 - ❑ Synergy with the Collaboration has to be defined





spare



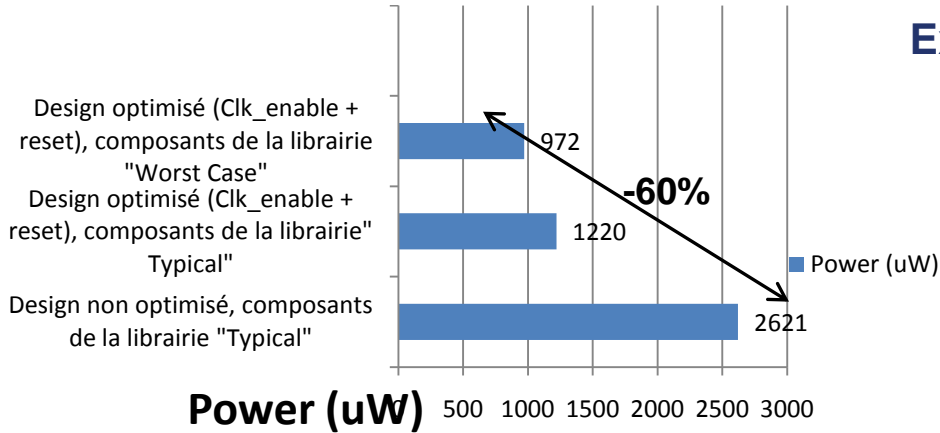

Exemple avec l'IP qui traite les Bits sortant de l'ADC (une seule conversion):
Design optimisés Vs Design simple

RTL-COMPILER (POWER, Nb PORTES)

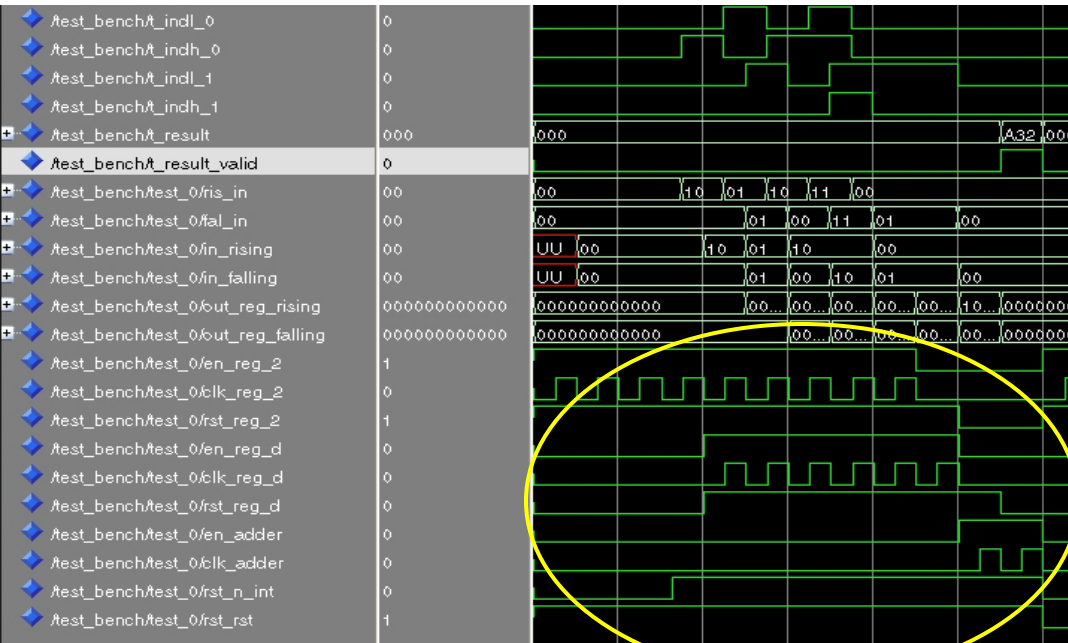 

CLOCK = 10MHz
P Worst DESIGN = 265uW
P Better DESIGN = 68 uW



Our 12-bit ADC: a VFE Building Block available for the Calice collaboration

