



UNIVERSITY OF  
LIVERPOOL





# Serial Powering for the ATLAS Inner Detector for SLHC

A. Affolder

University of Liverpool

*On behalf of the ATLAS Upgrade Community  
SP work and most of the slides “borrowed” from Bonn,  
LBL, Penn, BNL, RAL, FNAL, Krakow*

# ATLAS Phase II Tracker Upgrade

 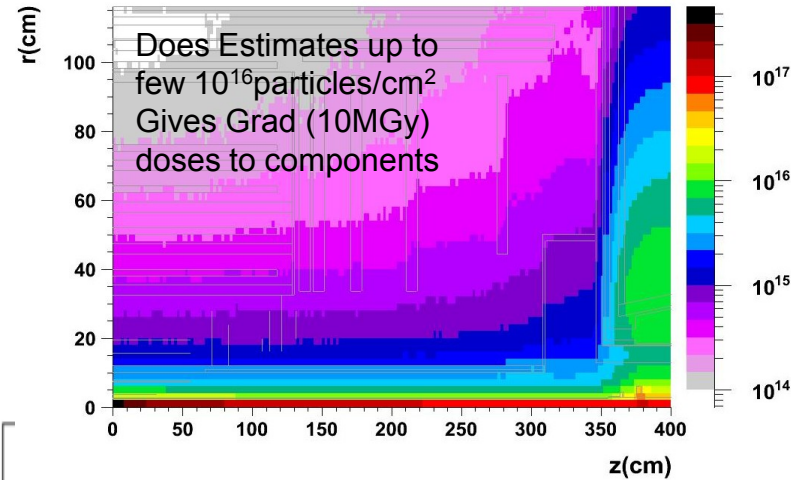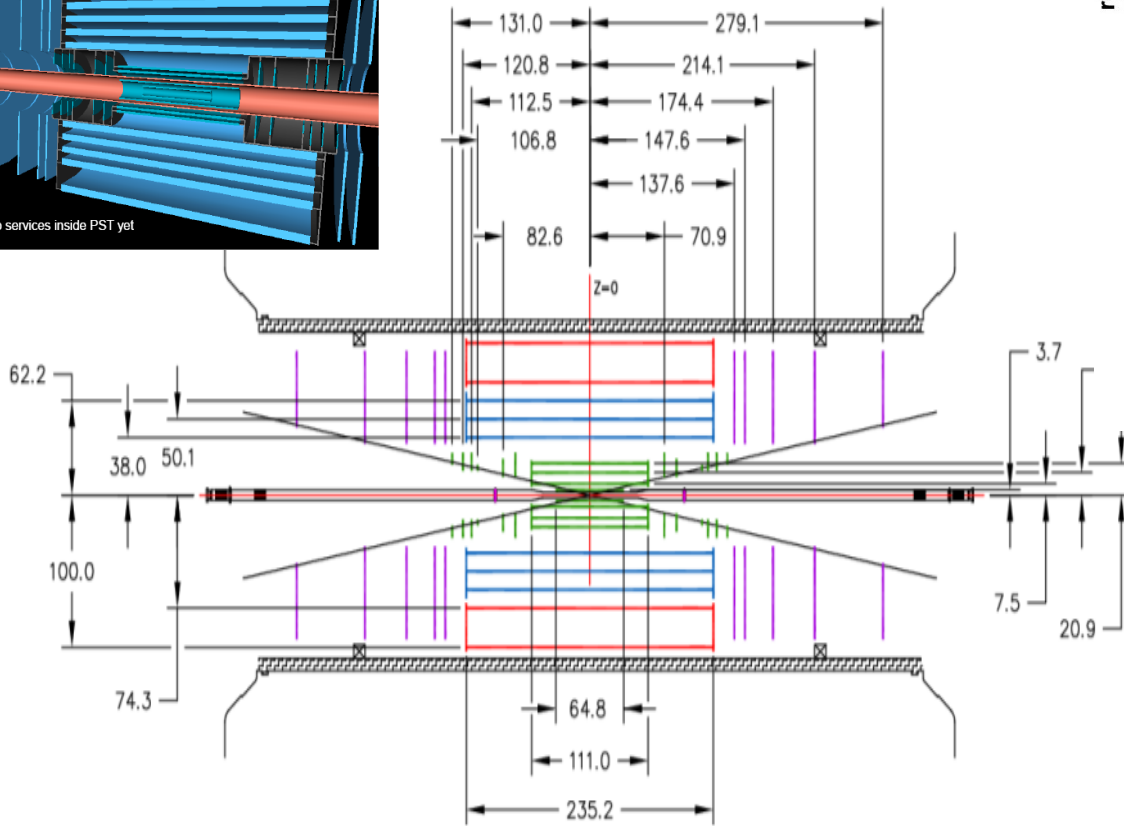 

Barrel Pixel Tracker Layers:  $r = 3.7\text{cm}, 7.5\text{cm}, 15\text{cm}, 21\text{cm}$   
 Short Strip (2.4 cm)  $\mu$ -strips (stereo layers):  $r = 38\text{cm}, 50\text{cm}, 62\text{cm}$   
 Long Strip (9.6 cm)  $\mu$ -strips (stereo layers):  $r = 74\text{cm}, 100\text{cm}$

# ATLAS pixels powering

## LHC → sLHC

FE channels: ~80M → ~455M

Total FE power: 6.7kW → 12.3kW

Total FE current: 3.8kA → 11kA


▶ @LHC: independent powering

▶ 20% efficiency

▶ Very massive

▶ LHC

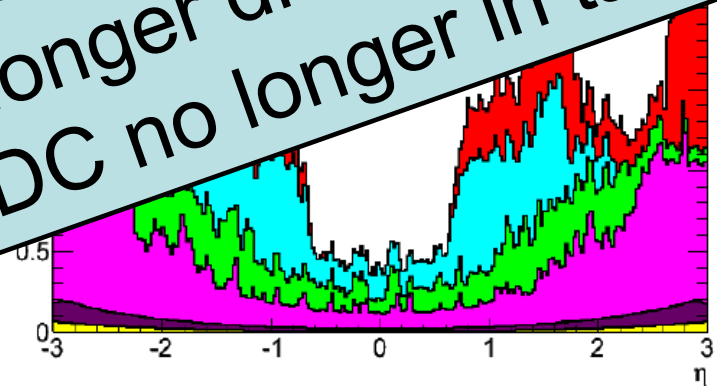Need for DC-DC or serial powering for SLHC  
silicon systems considered self-evident;  
Parallel powering no longer discussed;  
motivations for SP/DC-DC no longer in talks




ATLAS inner det. material distribution (incl. IBL)

→ Serial powering or DC-DC conversion
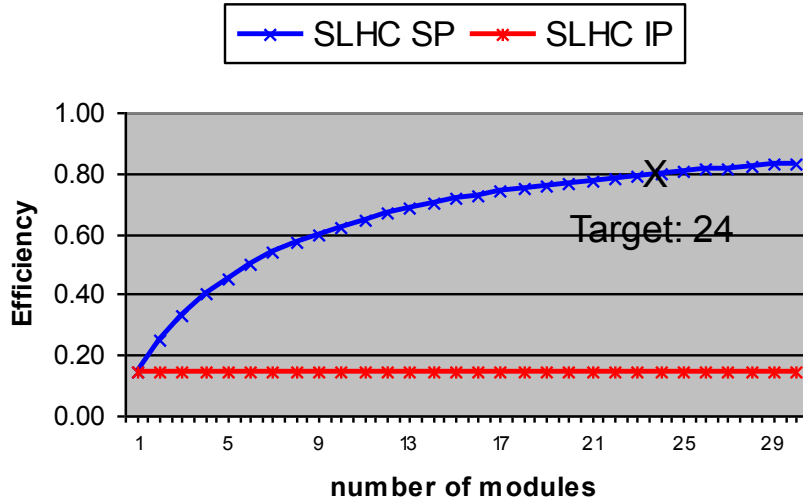
# Why Choose Serial Powering?

The power consumed by  $n$  hybrids is always  $n I V$ , but the power wasted in cabling depends upon the powering scheme!

for  $x = 6$  ( $2.5A * 3.5 \Omega / 1.5 V$ )



**10 modules in series increases efficiency by factor  $\approx 4$**

Consider  $n$  hybrids with:  
 hybrid current  $I$   
 hybrid voltage  $V$   
 off-detector cable resistance  $R$   
 DC-DC gain  $g$   
 and define  $x = IR/V$


	$I_{sm}$	$V_{drop}$	$V_{sm}$	$P_{cab}$	Efficiency: $P_{sm}/P_{total}$
<b>IP</b>	$nI$	$IR$	$V$	$nI^2R$	$1/[1 + x]$
<b>PP</b>	$nI$	$nIR$	$V$	$n^2 I^2R$	$1/[1 + nx]$
<b>SP</b>	$I$	$IR$	$nV$	$I^2R$	$1/[1 + x/n]$
<b>DC-DC</b>	$nI$ $g$	$nIR$ $g$	$gV$	$n^2 I^2R$ $g^2$	$1$ $[1 + xn/g^2]$

**=> Low  $V$  bad, large  $R$  and  $I$  are bad**

Values of these inputs are very system dependent. To get best results, they have to be considered at the design stages of ASICs, services, supports,....
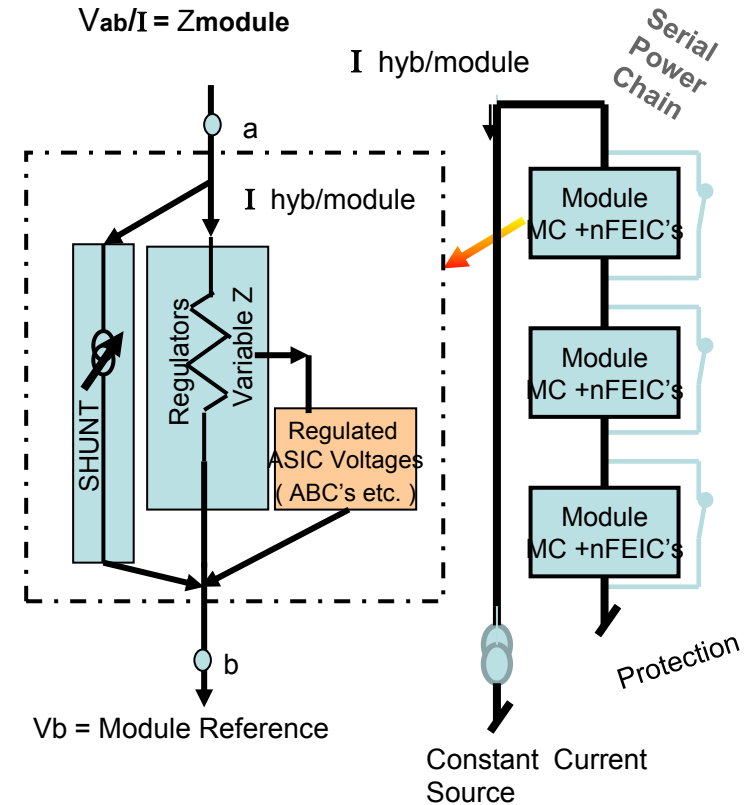
# Serial Powering Concept

- Serial Power - One cable powers 'n' modules each with an equal current.
  - Benefits:
    - Low input current
    - Higher power efficiency (70-85% for systems)
    - Low material budget (extra ~0.03% radiation length for strips, excluding bus tape traces)
    - Simple, needs minimal external components
    - Highly flexible to changes to current/voltage after design
  - Requirements:
    - Constant current source
    - More complicated ground referencing
    - AC coupled Data & Control
    - Over-voltage and Open Protection
    - Module/Chip Bypass (Slow and automated)




A good references for both Serial Power and for DCDC  
The ATLAS – CMS Power Working Group Meetings

2011-<https://indico.cern.ch/conferenceDisplay.py?confId=127662>


2010-<http://indico.cern.ch/conferenceDisplay.py?confId=85278>

# Two Shunt Layouts

 

Distributed shunt w/degraded IV characteristics


- Shunts in each FE ASICs
  - “Equivalent circuit” is a Zener diode
  - Resistor degrades IV characteristic to solve shunt turn-on mismatch issues
  - 1 regulator circuit per hybrid
  - 1 protection circuit per hybrid
  - Two voltages required generated by 1 or 2 LDOs on ASIC after shunt
- Already used in pixel FEI3 demonstrator and strip ABCn 250 nm prototype chip
- One of the possibilities for strip upgrade

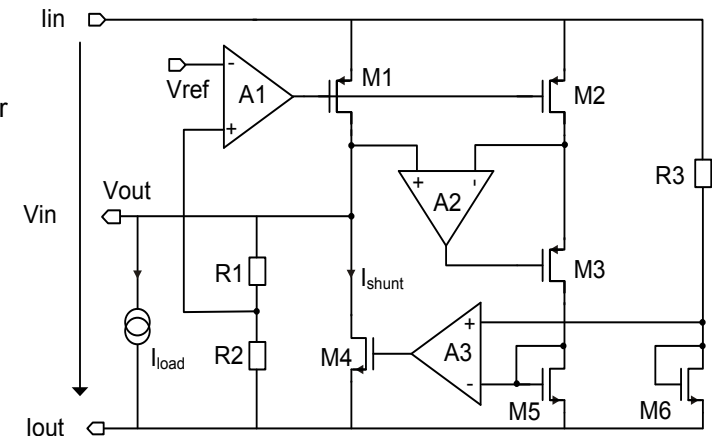


Distributed shunt/LDO

- Combined shunt/LDO pairs in parallel for each FE ASICs
  - “Equivalent circuit” is a resistor
  - Resolves shunt turn-on mismatch issues
  - Two voltages required generated by 2 Shunt-LDOs in parallel in each ASIC
    - Tunable voltage on both outputs
  - 1 protection circuit per hybrid
- Verified in 130 nm MPW submission and included and under test 130 nm FEI4 prototype pixel ASIC
- One of the possibilities for IBL and phase II pixels

# Chip Summary

 

Currently  
In Layout

 


	ABCN (250 nm)	ABCN (130 nm)	FEI4 (130 nm)
Number Channel Per Chip	128	256	26880
Number of Chips per Hybrid	20	10	4
Number of Hybrids per Chain	8-24	24-30	10-12
Digital, Analogue Voltages	2.5 V, 2.2 V	0.9 V, 1.2 V	1.2 V, 1.5 V
Digital, Analogue Currents	92 mA, 90 mA	60 mA, 102 mA	150 mA, 360 mA
Current in Chain	5 A (3.6 A)	2.2 A	2.4 A

Strip studies shown use ABCN (250  $\mu\text{m}$ )

Pixel studies shown use FEI4 (130  $\mu\text{m}$ )



# SP Strip Stave Architecture

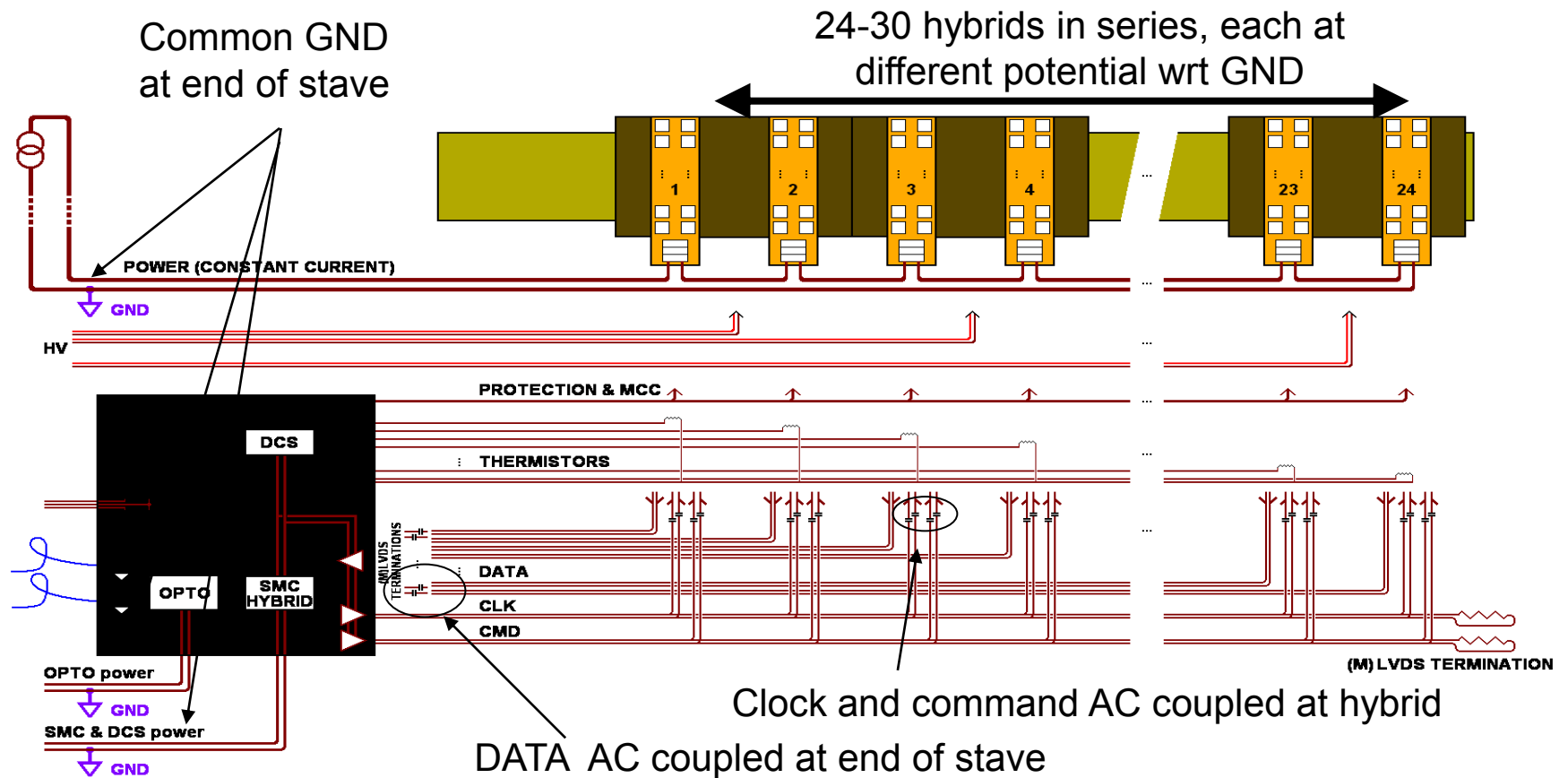


- **Hybrid with Distributed Shunt**

- Use one external shunt regulator and external SP protection
- Use each ABCN's integrated shunt transistor(s)
  - Two (redundant) shunt transistors, 140mA each


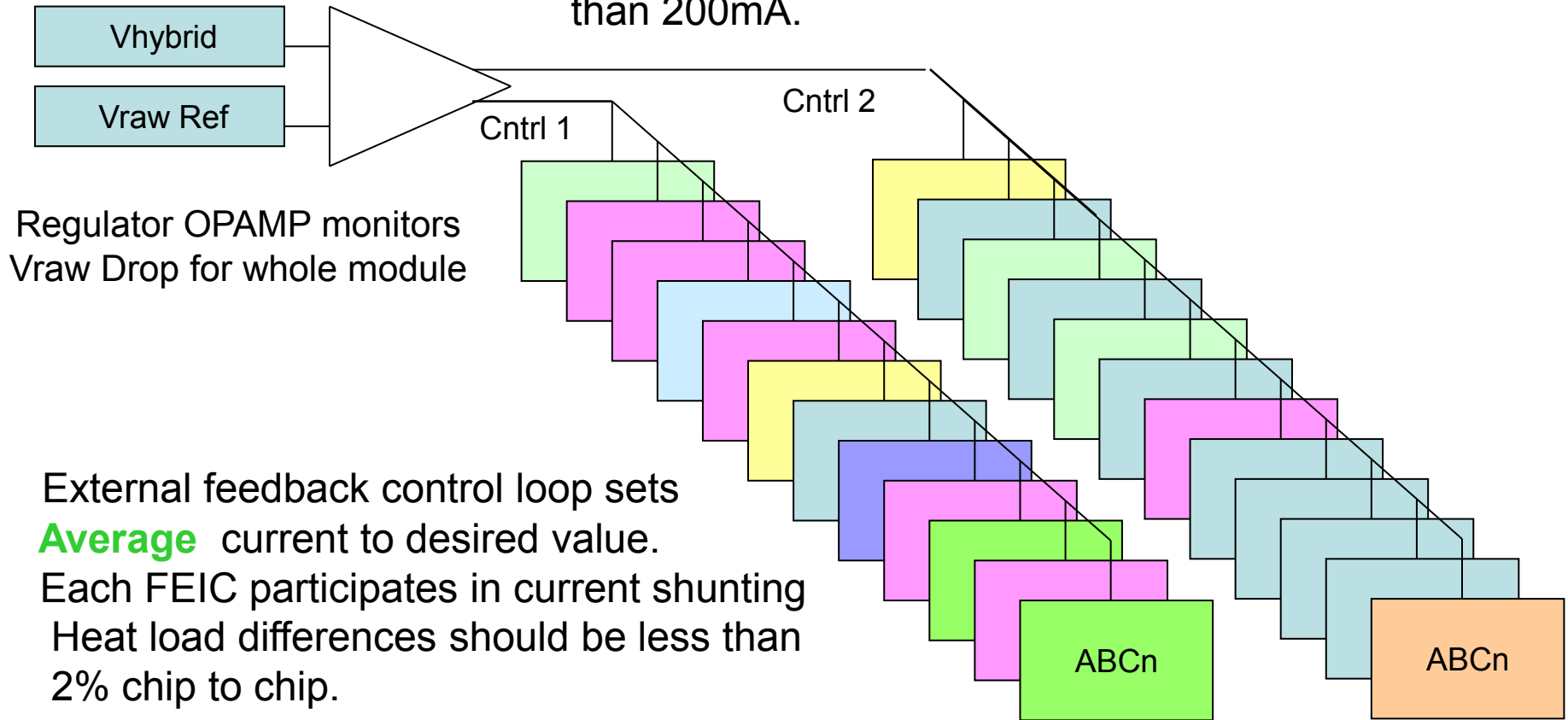
# Serial Power Control Circuit

Power current path **distributed** among ABCn chips. No interruption.  
**Highly redundant.** No chip shunts more than 200mA.





Regulator OPAMP monitors Vraw Drop for whole module

External feedback control loop sets **Average** current to desired value.  
Each FEIC participates in current shunting  
Heat load differences should be less than 2% chip to chip.
  
# Strip Electrical Test Vectors

- Frame with plug-ins for early testing of:
  - Serial Power Control
  - Serial Power Protection (discrete or custom ASIC)
  - DC-DC convertors
  - Multi-drop AC-coupled LVDS clock/control
  - Shielding/Grounding



- 4 module devices for tests of:
  - System powering effects
    - DC-DC or Serial Power
  - Shielding/Grounding
  - Noise from AC-coupled MLVDS
  - DAQ development

- Simplified full length devices for specialized tests



- Multi-drop AC coupled LVDS
- Serial power protection



# Stave Hybrids

Hybrids are designed for two powering schemes:

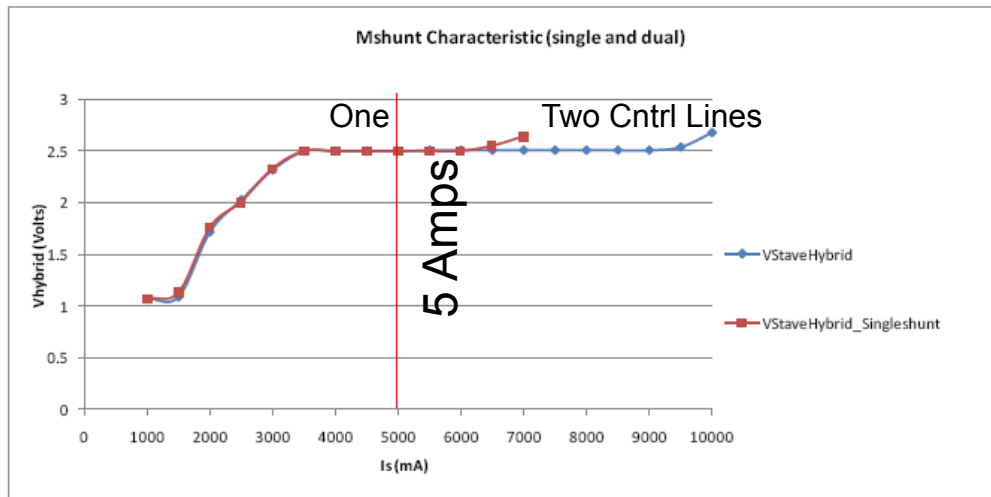 1. Parallel power, which could be provided by DCDC converters
2. Shunt regulation, using the distributed shunt regulators integrated within the ABCN-25s
  - Required for serial powering – Mshunt is the default scheme



Mshunt characteristic for single and dual shunts enabled per ABCN-25 on a 20 ASIC hybrid (expect max. Hybrid shunted current to be  $\leq 5A$ )


Single Shunt transistor enabled per ABCN-25 (20 x shunt transistors)

Shunt regulates  $V_{\text{hybrid}}$  to 2.5V at  $I_s > 3.5A$  and diverges at  $I_s < 6.5A$  (cf  $I_{\text{hybrid}} + I_{\text{smax}} (3.6 + (20 \times 0.14))) = 6.4A$ )

Dual Shunt transistors enabled per ABCN-25 (40 x shunt transistors)





Shunt regulates  $V_{\text{hybrid}}$  to 2.5V at  $I_s > 3.5A$  and diverges at  $I < 9.5A$  (cf  $I_{\text{hybrid}} + I_{\text{smax}} (3.6 + (40 \times 0.14))) = 9.2A$ )

# Stave Module Noise

 

- 2.5V per hybrid, ~5V total across the module (using constant current source)
- One hybrid is DC referenced to sensor, the other AC
- Use BCC ASICs for digital communication (AC-coupled LVDS), powered from hybrid

    **Serially powered module performs same as with parallel powering!!!**



	Parallel Power	Serial Power
Hybrid 62	590e/596e	590e/599e
Hybrid 61	585e/591e	588e/599e




# Stavelets

power and power control

Serial Power Protection PCBs

EOS Card

 


data and hybrid communication

BCC PCBs

Bus Cable

- Shortened Stave, built as electrical test-bed
  - Shielding, grounding, power, multi-drop LVDS
- First Stavelet serial powered with on-hybrid control
  - Power Protection Board (PPB) allows each SP hybrid to be bypassed under DCS control
  - Other powering options to be tested later
- Using Basic Control Chip (BCC)
  - Generates 80MHz data clock from 40MHz BC clock
  - 160Mbit/s multiplexed data per hybrid
- Readout using HSIO board from SLAC

 


HSIO + interface



# Serially Power Stavelet Noise Performance

- Used on-hybrid shunt control circuit
- Stavelet noise approaching single module tests
  - Roughly  $\sim 20 e^-$  higher
- Plan to extend tests to other SP plug-in controllers (ASICs) as they become available
- Still more work to go to get ultimate noise performance, but already acceptable for needed signal-to-noise

Noise for 16 columns of chip on stavelet

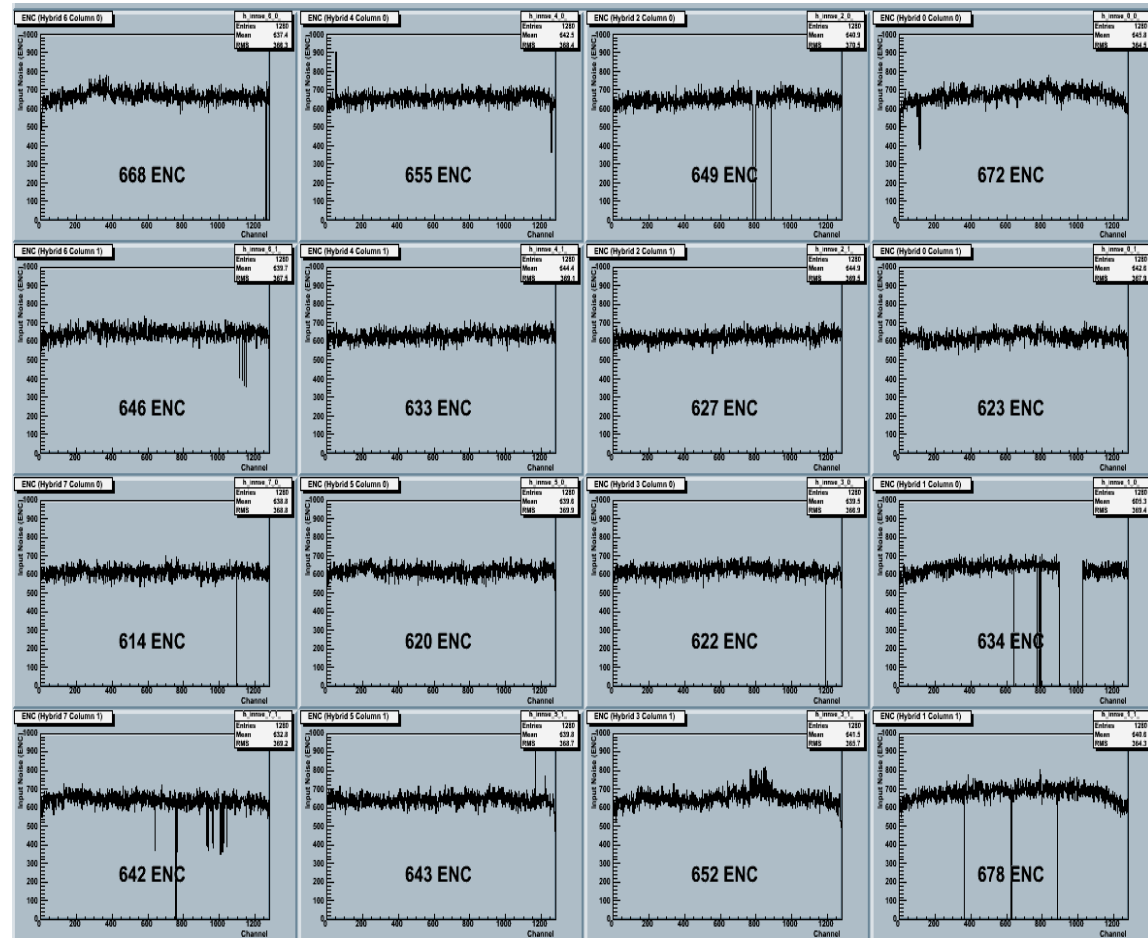


# Custom Constant Current Source

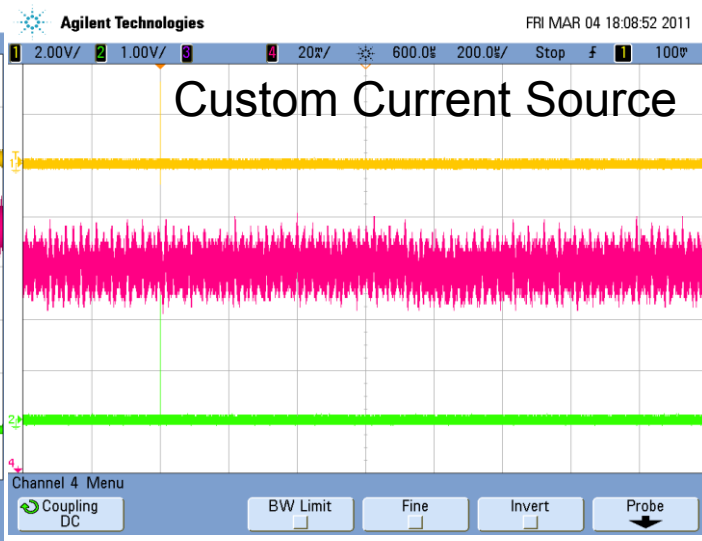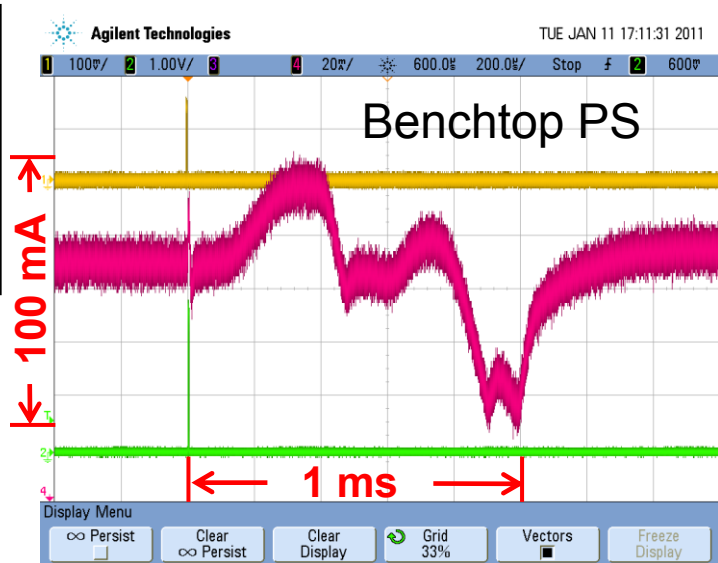

Current source is “stiffer” to ABCN25 current bump after trigger

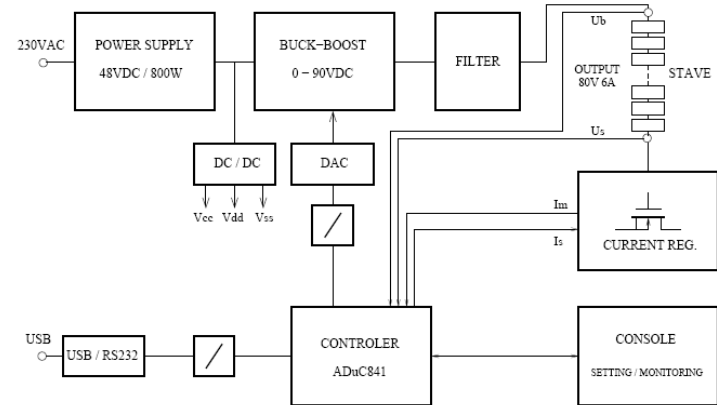- Programmable current source has been prototyped
- Designed for full-length stave, output up to 80V at 6A
- Includes isolated USB interface and overvoltage protection/interlock





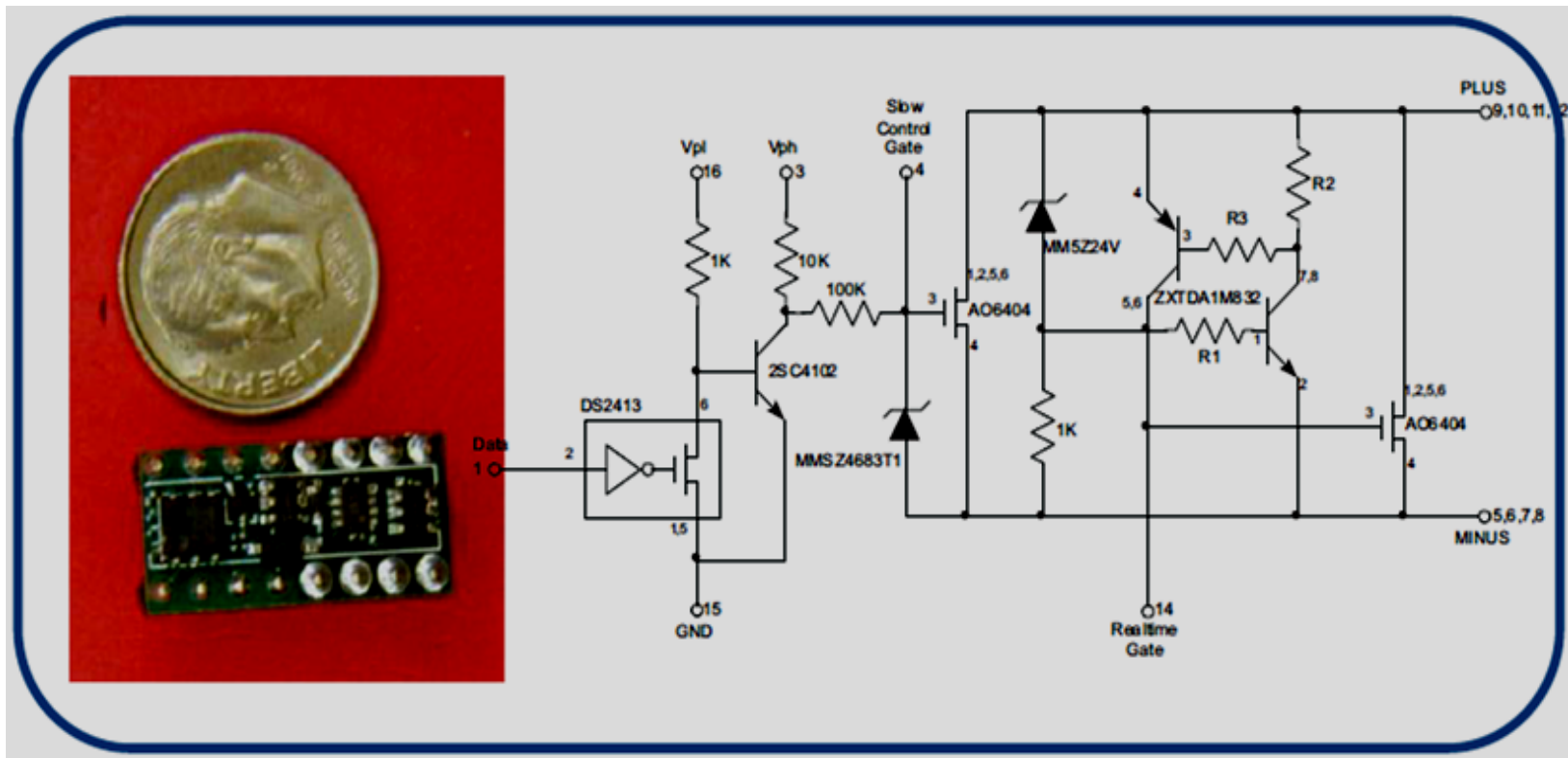
# Serial Power Protection



For first test, serial power protection circuit made with discrete components

- One wire Addressable by Hybrid Serial Power Control
- Installed on each of the 8 Stavelet Hybrids.
- An SCR function allows autonomous shut down on Over Voltage Sense




# Serial Power Protection Studies

SP System Test Board

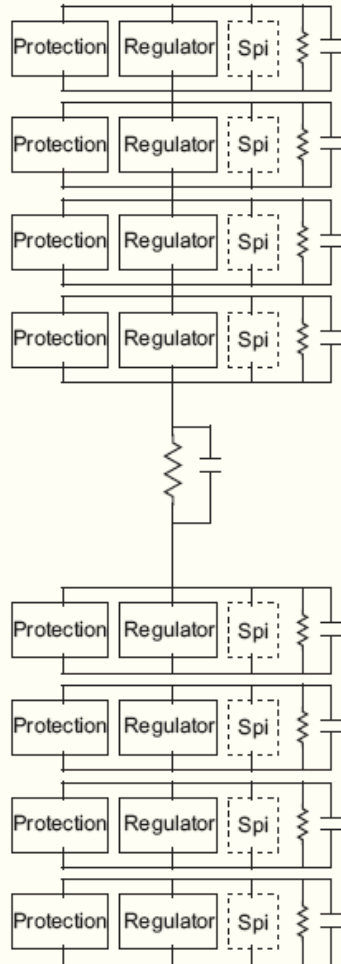 

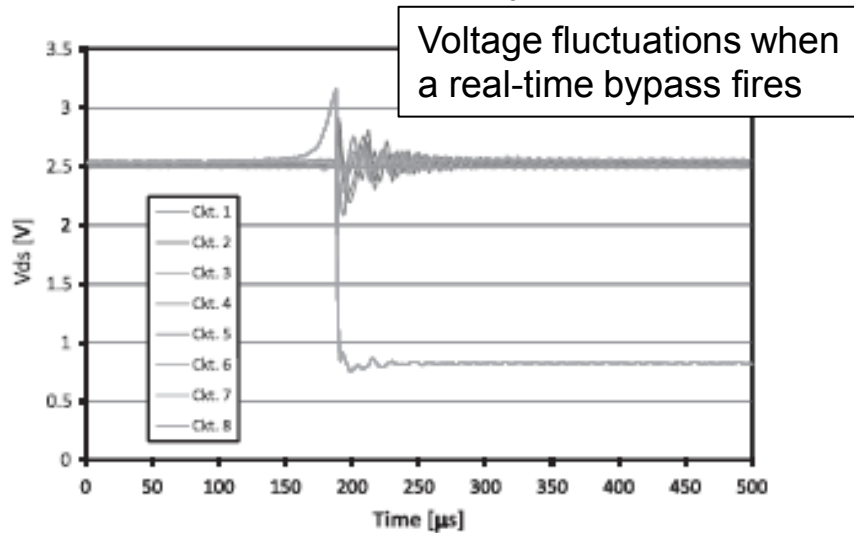- Mimics 8 hybrids + protection + regulators
  - Mimics clock dependent current loads
  - Studies power-up issues
- Tests real-time circuits; can induce controlled “open circuits”
- Tests 1-wire bypass circuits





M-shunt board



SPi board

“Serial power protection for ATLAS silicon strip staves”, D. Lynn, et al., Nucl. Instr. and Meth. A 633 (2011) 51-60

# Serial Powering Protection on Stavelet

  


0.5 W



- Hybrid bypassing works as expected

- $P=VI=100\text{ mV}\cdot 5\text{ A}=0.5\text{ W}$
- Noise slightly lower with neighbour's bypassed

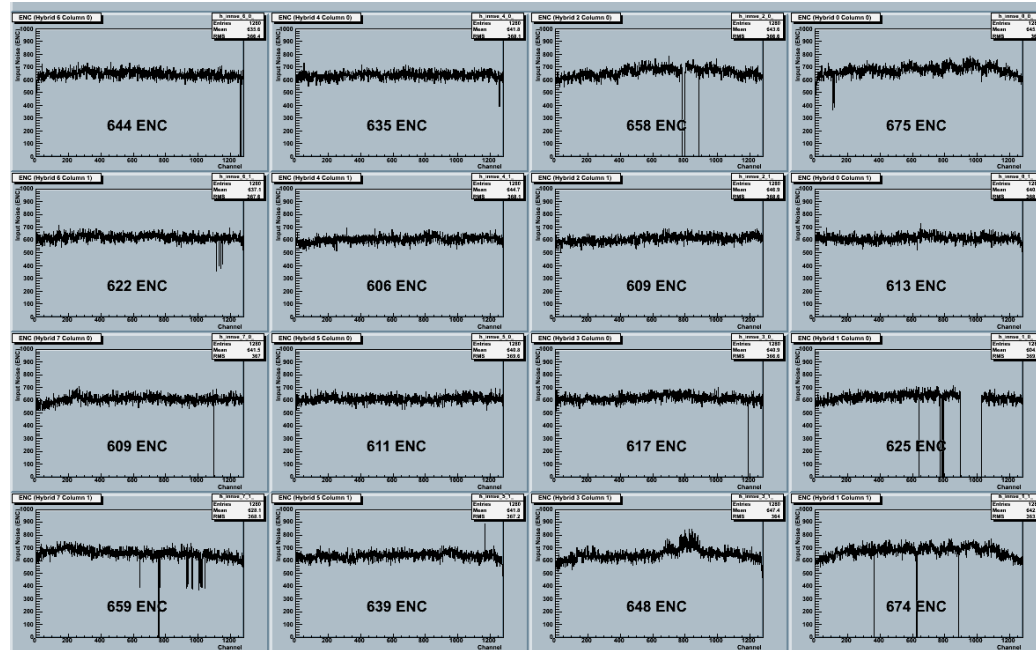Constant Current Source at 5A, ODDS AND EVENS, Composite





# Serial Power Protection ASIC


**Custom serial power protection ASIC (130 nm) is in design.  
Analogue only section prototyped in MPW under test**

**“Serial Power & Protection (SPP) ASIC for 1 to 2.5V Hybrid Operation”**

<http://indico.cern.ch/getFile.py/access?contribId=11&resId=0&materialId=slides&confId=85278>




- Designed for use with 250 nm and 130 nm ABCNext

- One wire control circuit supplies power to the SPP and controlled programmable shut down control
  - SPP chip has internal shunt regulator to set its voltage to 2.3V.
- On chip band gap forms reference for SPP 2.3V and for hybrid voltage.
- Hybrid voltage may be set from 1V to 2.5V
- SCR for autonomous shut down for over voltage.
  - ~100 mV across hybrid with autonomous shutoff
- On board shunt transistor available to guarantee hybrid switch off.
  - ~60 mV across hybrid with controlled shutoff

 

   
# Full-scale LVDS Test

- Need to determine “maximal” chain for clock/command using AC-coupled multi-drop LVDS
- Designed/manufactured the Buffer Controller Chip (BCC) in 250 nm IBM to allow multi-module testing in a serial power chain
  - Developed by SLAC/UCL/Cambridge/LBNL
  - Generates 80 MHz data clock and multiplexes data lines
  - Replaced in final chip set by Hybrid Controller Chip (HCC)
- Chain of 24 BCC operated as a system on the full length bus
  - Sufficient amplitudes and short enough rise time for all positions for BCC to regenerate clocks correctly


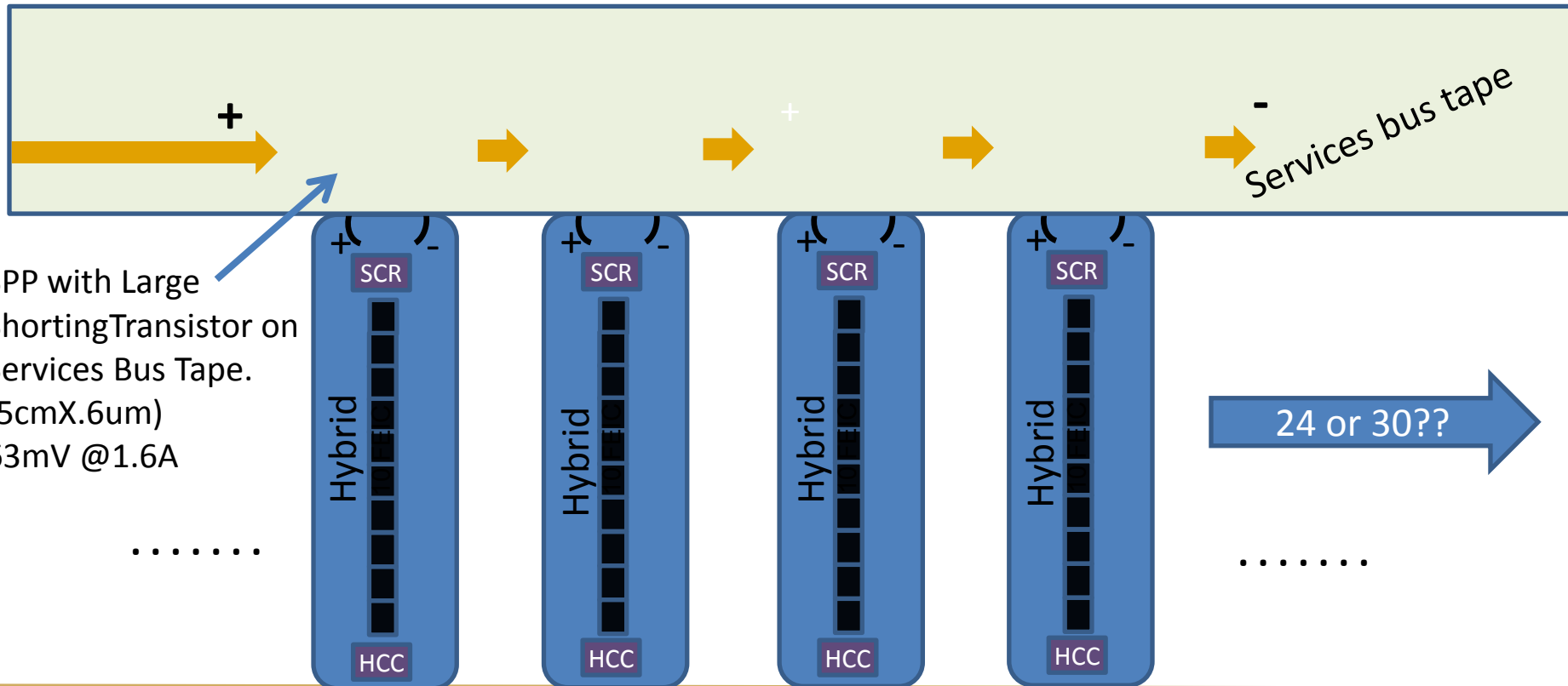
# One “Final” Envisioned Serial Power Architecture

- **SPP directly attached to stave bus**
  - Single Global power line supplies each SPP with independent power
  - SPP is addressable to turn “on” and “off” a hybrid.
  - Built in Transistor capable of shunting hybrid current independent of ASIC based shunt transistors
  - Includes serial power regulator and SCR circuit for overvoltage protection
- **Extra SCR on each hybrid in case of SPP failure**
- **Shunt with LDOs in each ABCn to generate analogue/digital voltages**




# Material Estimate for Serial Power

Using currently understanding, the radiation length of material needed to service power has been estimated

- Excludes extra bus tape traces, support, traces

Goal of less than 2% for a stave's radiation length

 - Serial Power: 1 shunt per ABCN, 1 control and 1 protection ASIC per hybrid
  - Estimate 0.03% of a radiation length to stave from serial power
    - Mostly from extra needed hybrid area and AC-coupling capacitors




24 mm

BCC replaced by bare die hybrid control chip (HCC) on each hybrid. 10 extra 0402 capacitors need for AC coupling clock/command/trigger

Discrete serial power protection will be replaced with custom ASIC (3 mm<sup>2</sup>), 1 1206 resistor, and 4 0402 capacitors



~35 mm

 

Discrete shunt control on current hybrid will be replaced with custom ASIC (9 mm<sup>2</sup>), 2 0805 resistors, 2 0402 capacitors





# Strip Serial Powering Conclusions

- All technology needed for SP has been prototyped and shown to work (and compatible with 130 nm CMOS)
  - Remaining concerns are locations of devices and number of units in a SP chain (concerned with both common mode build-up and failures)
- Largest continuous current channelled through any one ASIC will be less than 200 mA
- Largest power dissipation in SP control/protection ASICs is less than 50 mW
- Hybrid voltage regulation will have several amps of reserve current handling
  - Have shown up to 10 A in a hybrid
  - Allows flexibility for set voltages/currents
- Minimal impact on material budget
- Last bit for ultimate noise performance still under study
  - But measured noise would yield 15:1 S/N at end of life

 
 
# ATLAS Pixels SP Shunt-LDO

- **Combination of a LDO and a shunt transistor**
  - Shunt transistor is part of the LDO load
  - LDO power transistor works as an input series resistor for the shunt
- **Advantages for Serial Power**
  - Removed input series resistor for shunt improves power efficiency
  - Shunt-LDO regulators can be placed in parallel without problems regarding mismatch & shunt current distribution
  - Shunt-LDO having different output voltages can be placed in parallel
  - Shunt-LDO can cope with an increased supply current if one FE-I4 does not contribute to the regulation
  - Failed regulator loses one ASIC instead of one hybrid
- Working principle and good performance demonstrated with 2 prototypes already
  - 130 nm MPW
- Nominal Power Efficiency of 2 Shunt-LDO in parallel with different  $V_{out} = 75\%$



  
# FEI4 Pixel ASIC

Voltage drop between chip and board ground







 - Prototype FEI4 ASICs and packages undergoing first testing now
- So far, Shunt-LDOs working as expected



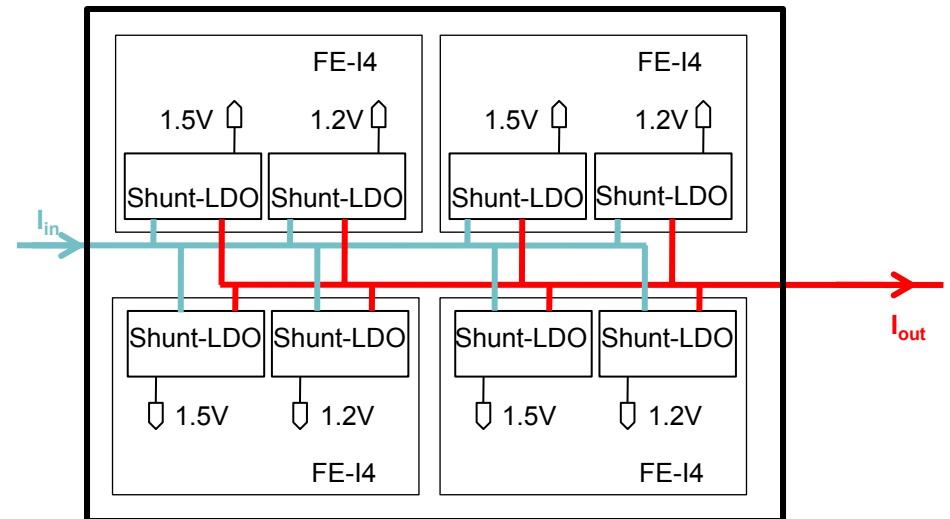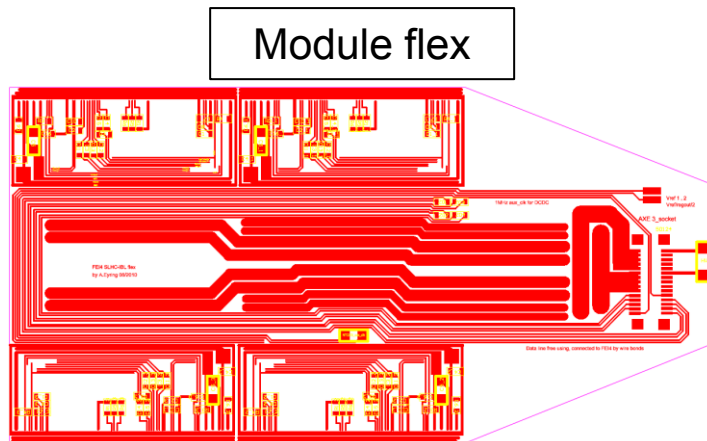  
# Phase II FEI4 Serial Powered Pixel Modules

- Cable prototype for serial power has made
  - 8 modules in chain on a stave
- At module level, the current is routed in parallel to the 4 FE-I4s
  - Prototype module flex in production
  - $I = I_{mod} = 2.4A$  (max)
- 2 Shunt-LDO/FE to generate  $VDDA = 1.5V$  and  $VDDD = 1.2V$  per ASIC
- 8 Shunt-LDO regulators per module in parallel


 
# Pixel Module Protection Chip


- Chip ASIC in design
  - 130nm IBM
  - Bypass transistor
- Independent slow ctrl line & OV protection
  - OV protection = Silicon controlled rectifier
- Preliminary simulations:




Slow ctrl

Bypass


Fast response

 

 DGNMOS  
 $W = 48\mu\text{m}$   
 $L = 0.24\mu\text{m}$



 $C1 = 100\text{nf}$   
 $C2 = C_{gs} = 33\text{pf}$   
 $D1, D2 = \text{PMOS}$



# Conclusions

- Modification of power schemes necessary for SLHC Silicon Systems
  - Much high segmentations and larger areas
- Serial powering has been shown to be a viable option
  - Low mass, higher power efficiency, simple, flexible
- Two different systems are under test for ATLAS pixels and strip detector systems
  - So far, all results are positive
  - Still in serious consideration for final system

**BACKUP MATERIAL**




# SPP – 12 Hybrid HSPICE simulations (Monte=10)


Hybrid voltage  
(1.2v)  
80mv when shorted

Decode  
0:unshort hybrid


Decode 1: short  
hybrid

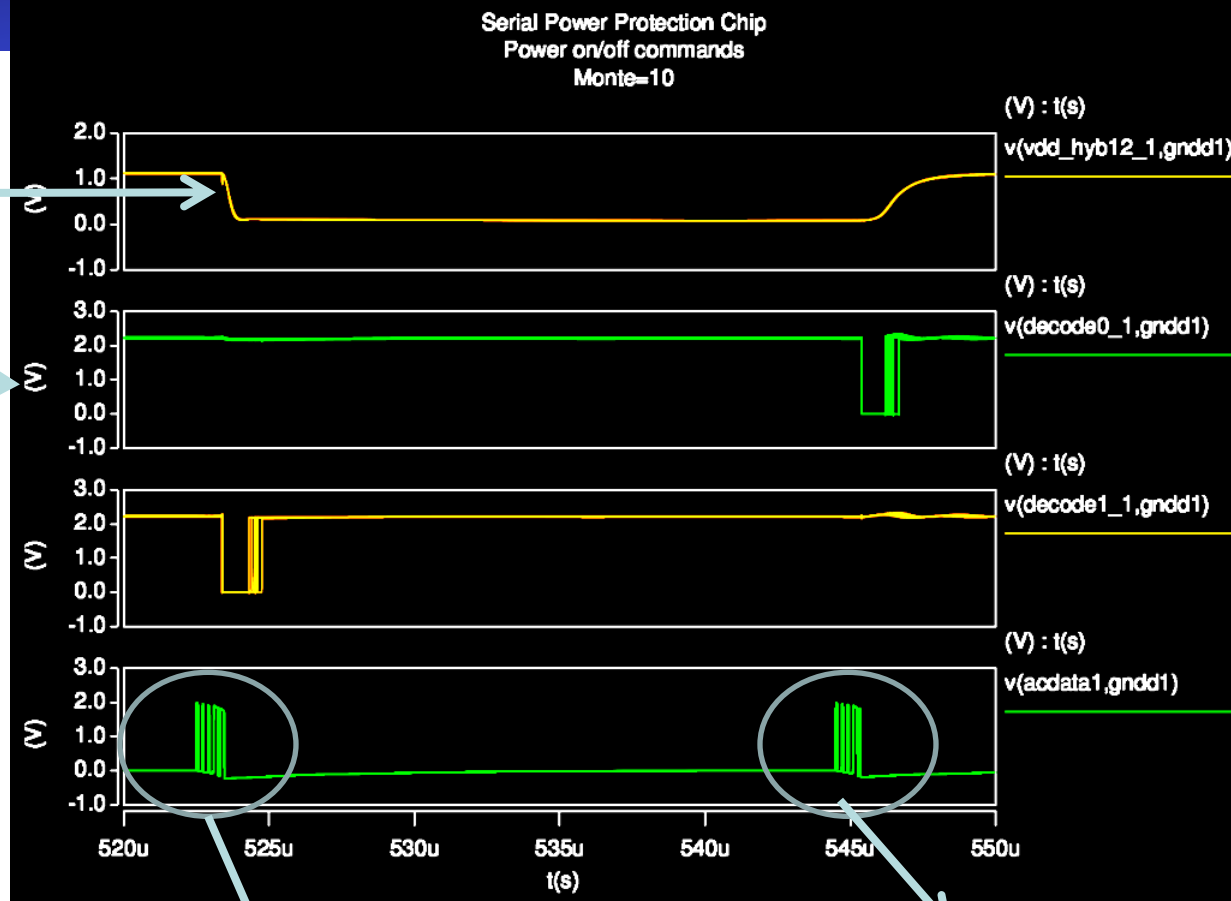

Decode 1: short hybrid

 

Decode 0:  
unshort hybrid

 

# SPP – 12 hybrid HSPICE simulations (Monte=10)

Vglobal (25v) SPP pwr


Load Current in one FE IC

Hybrid voltage (1.2v)  
80mv when shorted

Decode 0: unshort hybrid

Decode 1: short hybrid

AC coupled pulse-width modulated signal

 

# Scaling up the Serial Powered System


The length of the SP chain and its reference connections needs careful examination under dynamic conditions as we begin to scale up from one module towards a full stave

## Simulation results



Common Mode for Hybrid to EOS Signals

The plot on the left shows a simulation result for a 12 hybrid SP loop when L1's are being issued (modeled as a 20% increase in digital current for all ABC chips.) The plot shows the local hybrid reference vs EOS ground. This represents one source of common mode noise in the digital signaling between the EOS and Hybrid.

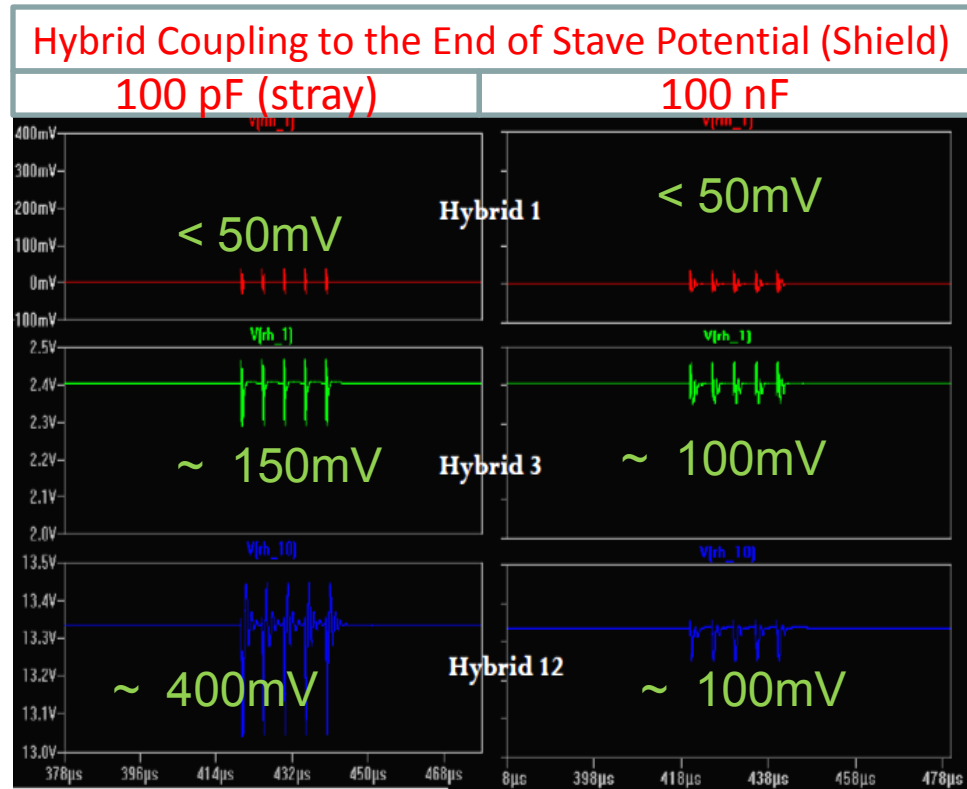These simulations show a significant the potential for a growing common mode signal as the length of the SP chain is increased.




# Shunt Regulator (FE-I3 approach)

 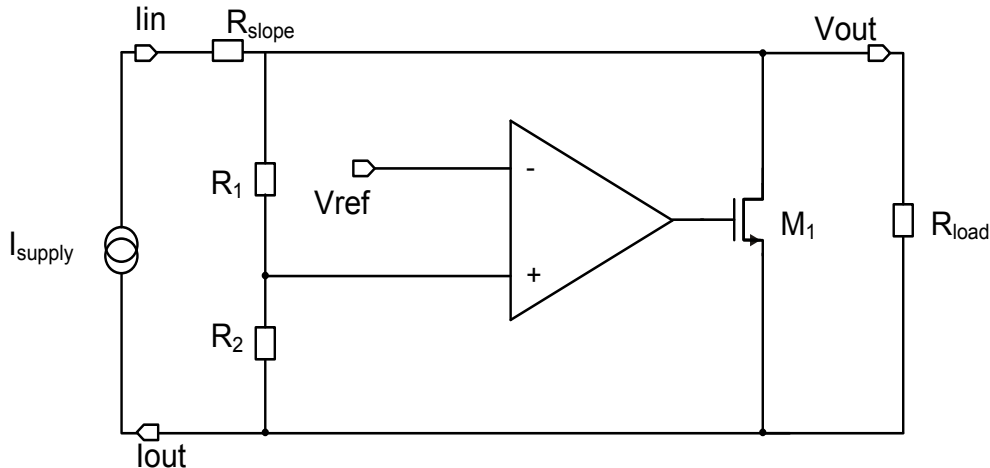

- Shunt regulator generates a constant output voltage out of the current supply
- current that is not drawn by the load is shunted by transistor M1
- Very steep voltage to current characteristic
- Mismatch & process variation will lead to different  $V_{ref}$  and  $V_{out}$  potentials
- Most of the shunt current will flow to the regulator with lowest  $V_{out}$  potential
- **Potential risk of device break down at turn on**
- Using an input series resistor reduces the slope of the voltage to current characteristic

# LDO Regulator (FE-I3 approach)

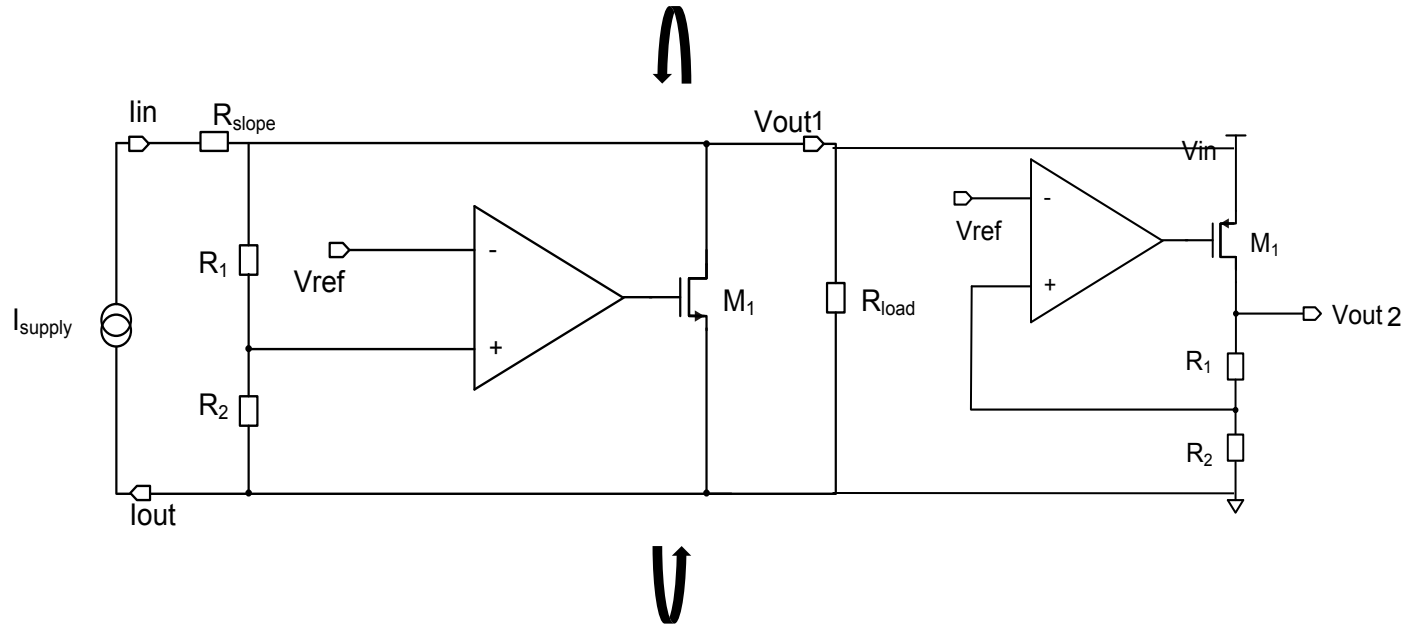

- Second supply voltage of lower potential is generated by a LDO regulator powered by the shunt regulator
- The LDO power transistor operates like a regulated series resistor which controls the voltage drop between input output voltage to have a constant output voltage
- Change order of regulation chain
- $R_{SLOPE}$  replaced by the LDO power transistor
- Shunt transistor connected to the LDO output

# Shunt Regulator Architectures

- **Hybrid with Shunt “M”**


- Use one external shunt regulator
- Use each ABCN's integrated shunt transistor(s)
  - Two (redundant) shunt transistors, 140mA each

Each option has its merits. All now available in silicon:  
final choice to be based upon test results.




 
# Stave+Petal Programme



- Collaboration of more than 25 institutes from 5 countries
- Designed to minimise material
  - Early electrical systems tests needed to determine which mass-saving changes possible
- Requirements of automated assembly built in from the start- *Simplify build as much as possible!!*
- Minimize material in thermal management by shorting cooling path- Gluing module to a stave core with embedded pipes
- Design aims to be low cost- *Minimize specialist components!*



Petal Hybrid

  

Stave Module

  

~ 1.2 meter

