



Cavity Field Control

- RF Signal Detection and Actuation

LLRF Lecture Part 3.4

S. Simrock, Z. Geng

ITER / SLAC




Outline

- Requirements to RF field detector
- RF field detection methodology
- Reduce the noises and compensate the drifts in RF field detection
- RF actuation
- Appendix
 - Typical hardware for RF field detection
 - Mixer
 - Analog to Digital Converter (ADC)



Requirements to RF Field Detector



Context of the RF Field Detector

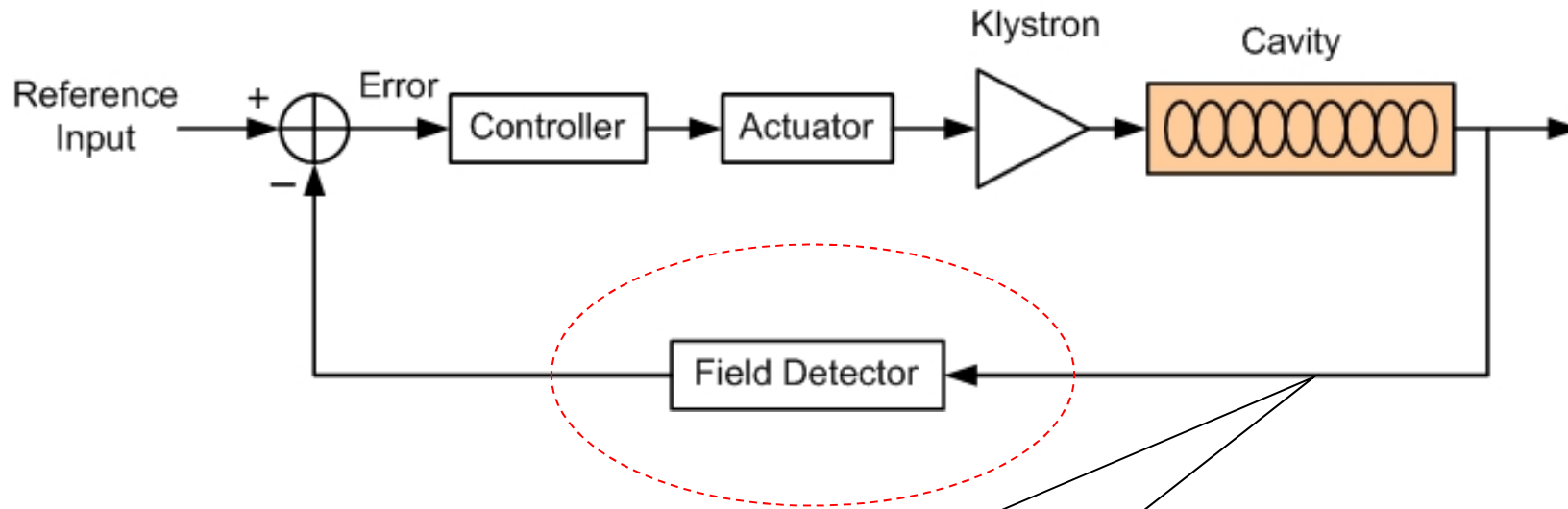

$$\begin{aligned}
 V_c(t) &= A(t) \cdot \cos[\omega t + \varphi(t)] \\
 &= I(t) \cdot \cos(\omega t) + Q(t) \cdot \sin(\omega t)
 \end{aligned}$$



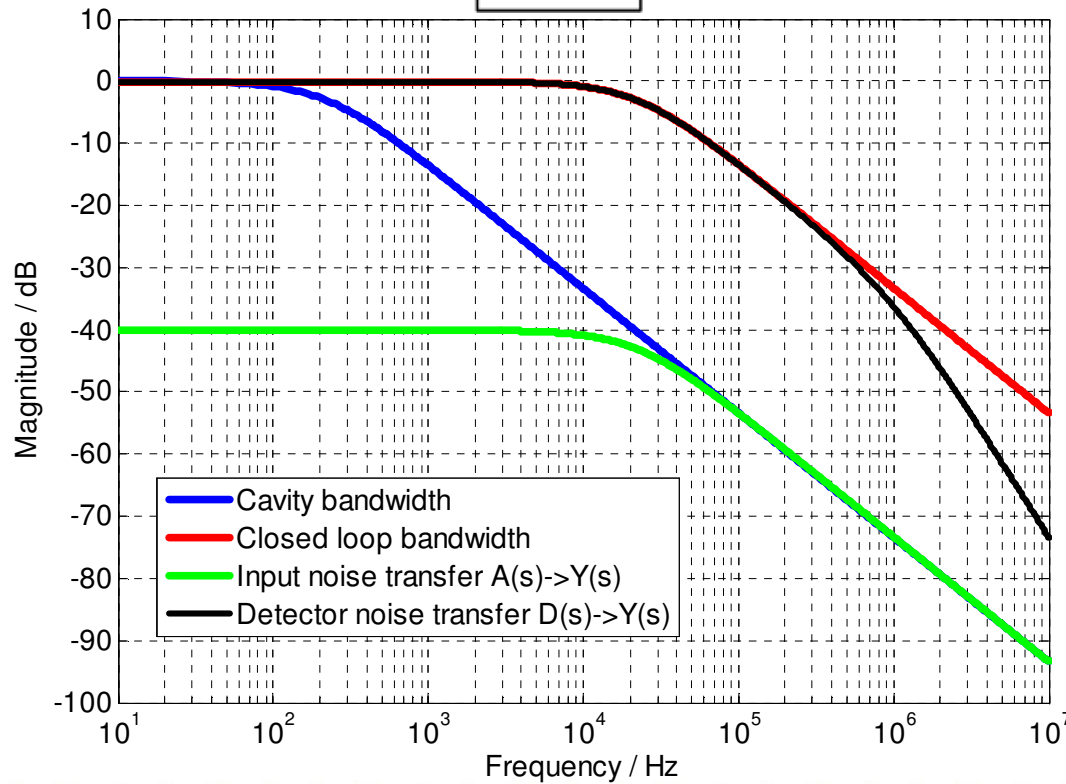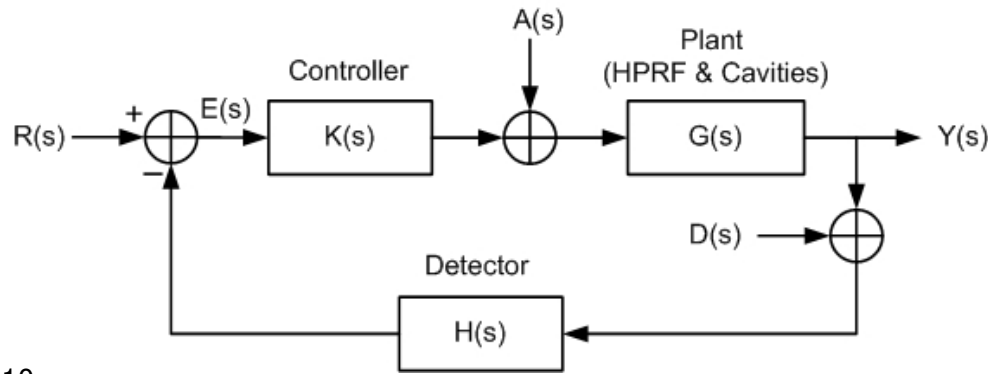Recall: Transfer Function from Detector Noise to Cavity Field



- Low frequency noise of detector is transferred directly to the cavity output; high frequency noise is filtered by closed loop bandwidth and detector bandwidth
- Reducing the detector noise will be essential to get highly stable cavity field!



Requirements to the RF Field Detector

- The requirements of the RF field detector should be derived from the overall requirements to LLRF system
- **Functional requirements:** detect the amplitude and phase of RF field for each cavity in real time
- **Quality requirements:**
 - Field detection bandwidth
 - Amplitude and phase error
 - Non-linearity

Example for FLASH:


- Field detection bandwidth: 10 MHz
- Amplitude and phase error: $< 10^{-4}$
- Non-linearity: at full scale of the measurement, the amplitude compression should be less than 1% and phase shift should be less than 0.5 degree



RF Field Detection Methodology



Direct Amplitude and Phase Detection

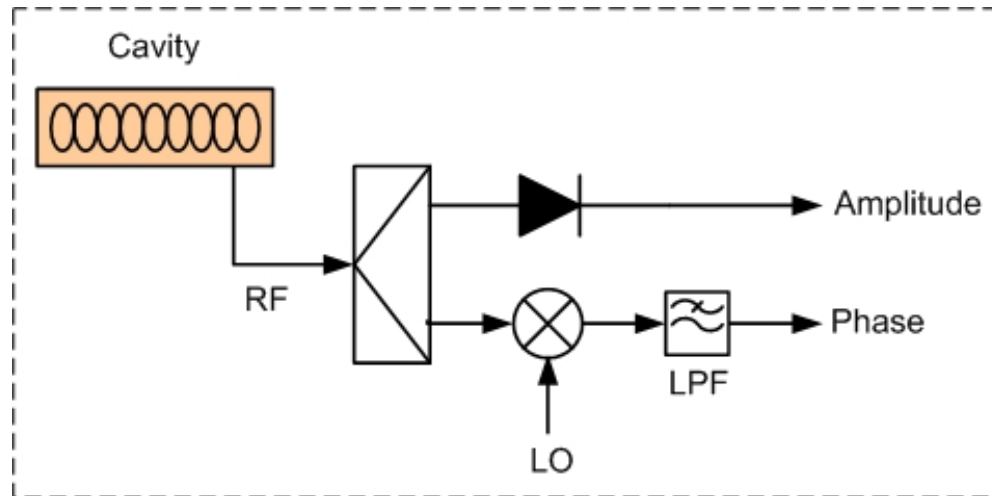

Mixer input:

$$V_{RF}(t) = A_{RF} \sin(\omega t + \varphi_0)$$

$$V_{LO}(t) = A_{LO} \cos(\omega t)$$

Mixer output:

$$V_{mixer} = A_{RF} \sin(\omega t + \varphi_0) \cdot A_{LO} \cos(\omega t) = \frac{A_{RF} A_{LO}}{2} [\sin \varphi_0 + \sin(2\omega t + \varphi_0)]$$

$$LPF\{V_{mixer}\} = \frac{A_{RF} A_{LO}}{2} \sin \varphi_0 \approx \frac{A_{RF} A_{LO}}{2} \varphi_0 \quad (\text{for small } \varphi_0)$$

- Simple system structure
- Linear for small phase errors
- Phase measurement is influenced by the amplitude error of the RF or LO signal



Analog I/Q Detection

Inputs:

$$V_{RF}(t) = A_{RF} \cos(\omega t + \varphi_0)$$



$$V_{LO}(t) = A_{LO} \cos(\omega t)$$

Outputs:

$$I = LPF \left\{ \frac{A_{RF}}{\sqrt{2}} \cos(\omega t + \varphi_0) \cdot \frac{A_{LO}}{\sqrt{2}} \cos(\omega t) \right\} = \frac{A_{RF} A_{LO}}{4} \cos \varphi_0$$



$$Q = LPF \left\{ -\frac{A_{RF}}{\sqrt{2}} \cos(\omega t + \varphi_0) \cdot \frac{A_{LO}}{\sqrt{2}} \sin(\omega t) \right\} = \frac{A_{RF} A_{LO}}{4} \sin \varphi_0$$
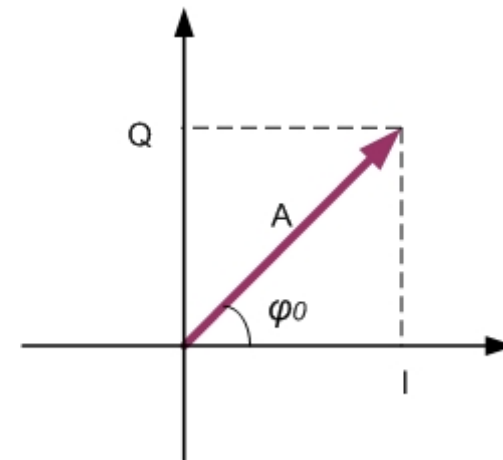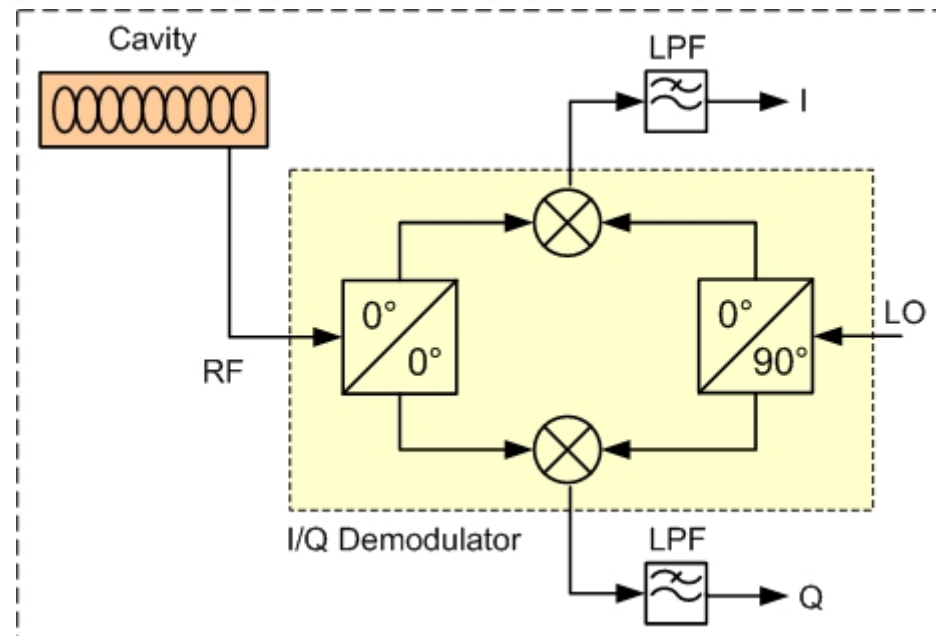
$$\varphi_0 = \tan^{-1} \left(\frac{Q}{I} \right) \quad A = \sqrt{I^2 + Q^2}$$




Analog I/Q Detection

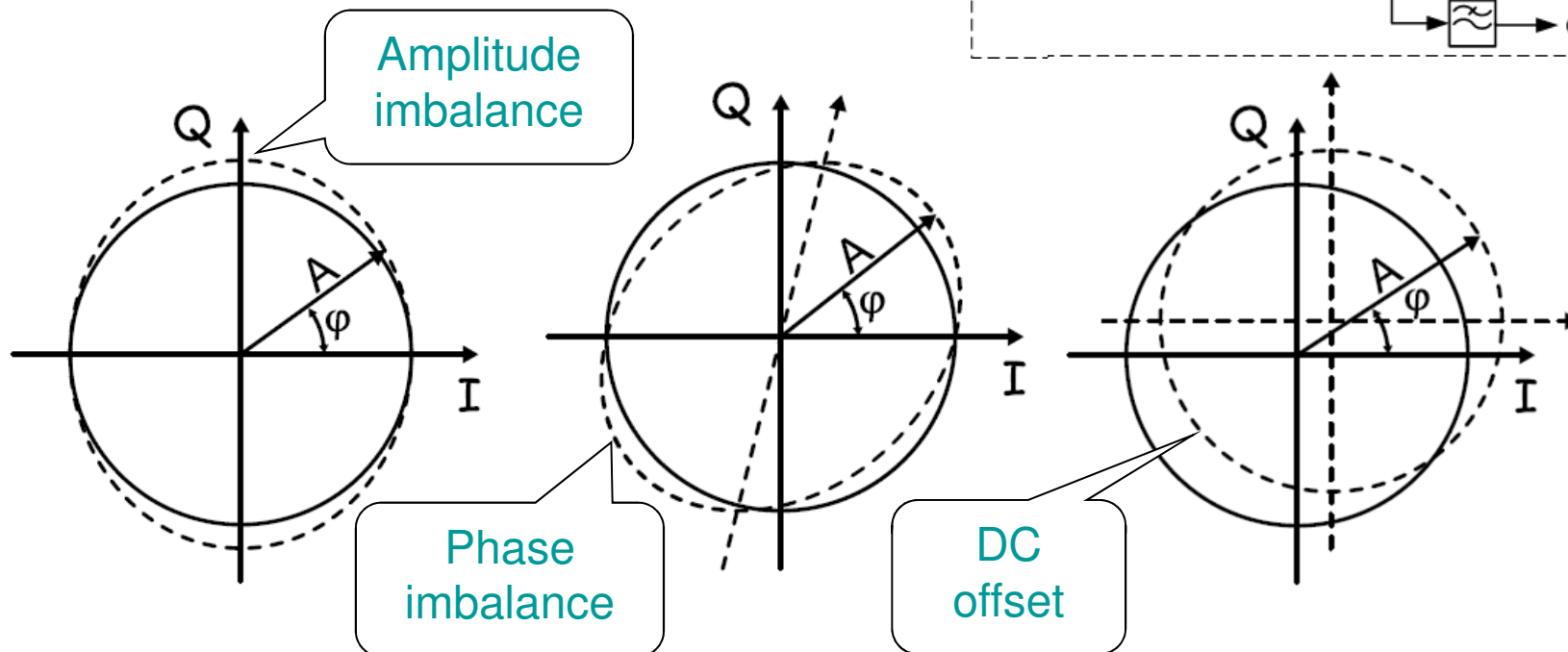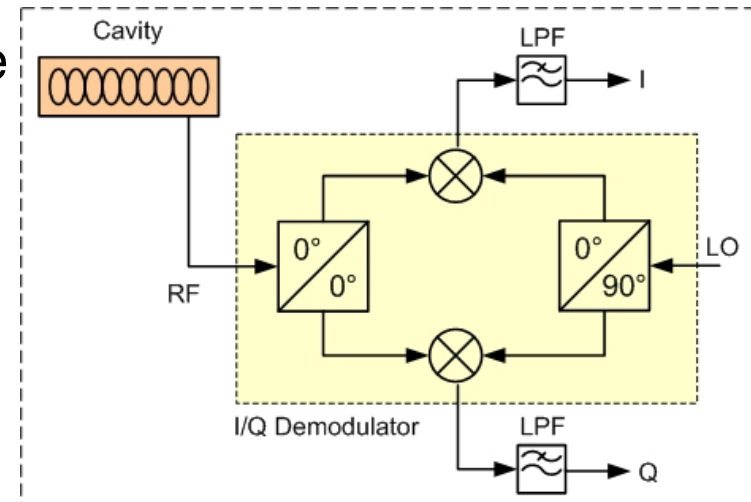
- Phase measurement is linear for the whole range of 360°
- Low efforts of digital processing
- Disadvantages:
 - Phase and amplitude imbalance
 - DC offset




IQ Sampling

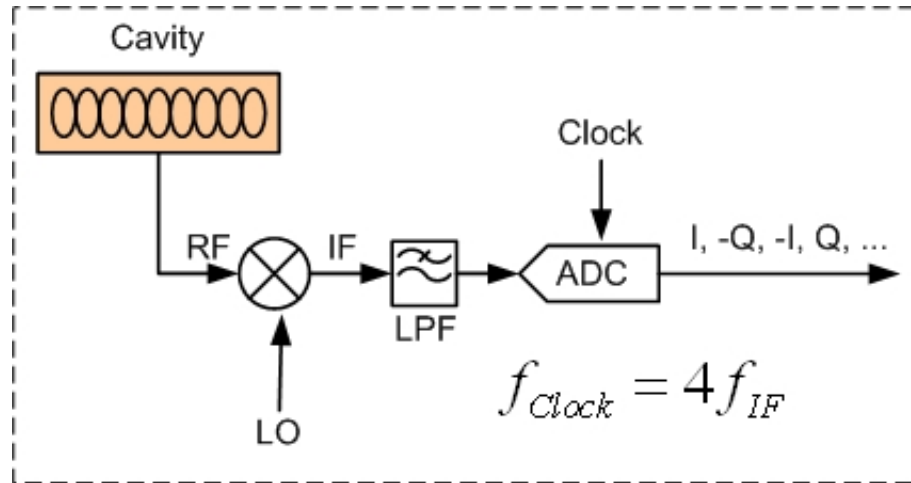

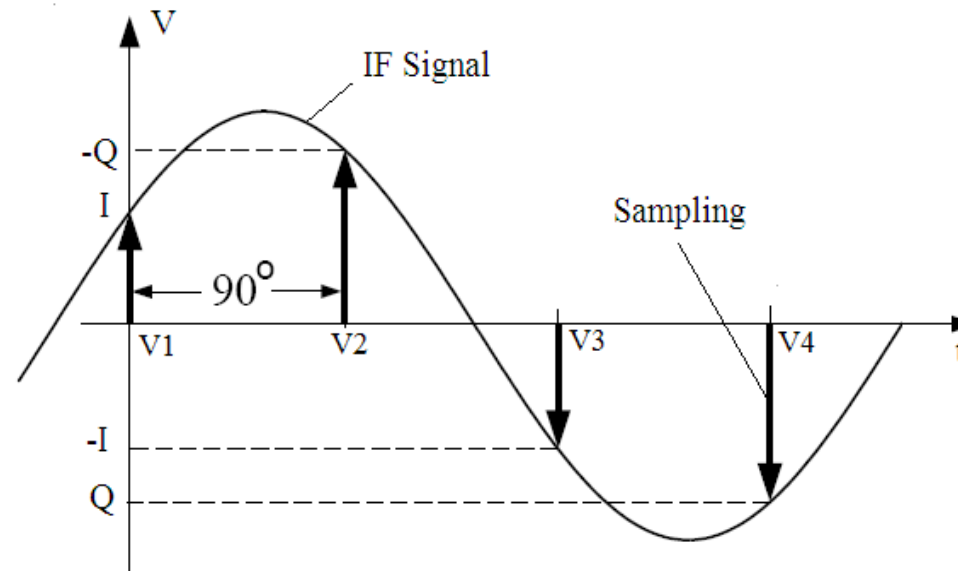
- Digital I/Q detection
- IF and clock signal should be synchronized
- Alternating samples give I and Q components of the cavity field



IQ Sampling at FLASH

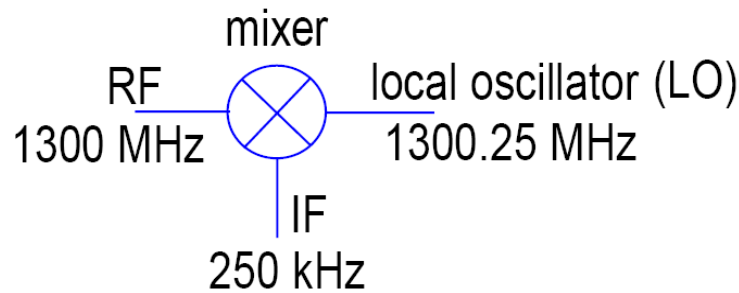

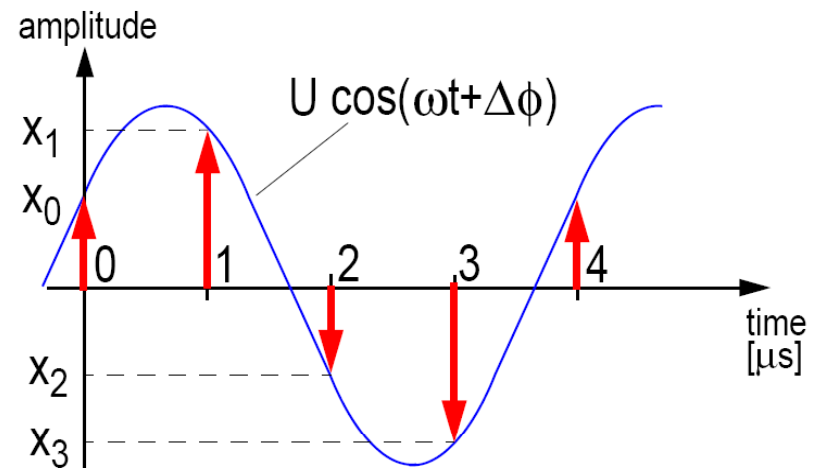- downconversion of cavity field to IF frequency at 250 kHz
- complete phase and amplitude information of the accelerating field is preserved.








- sample IF signal at 1MHz rate
- subsequent samples describe real and imaginary component of the cavity field.



IQ Sampling

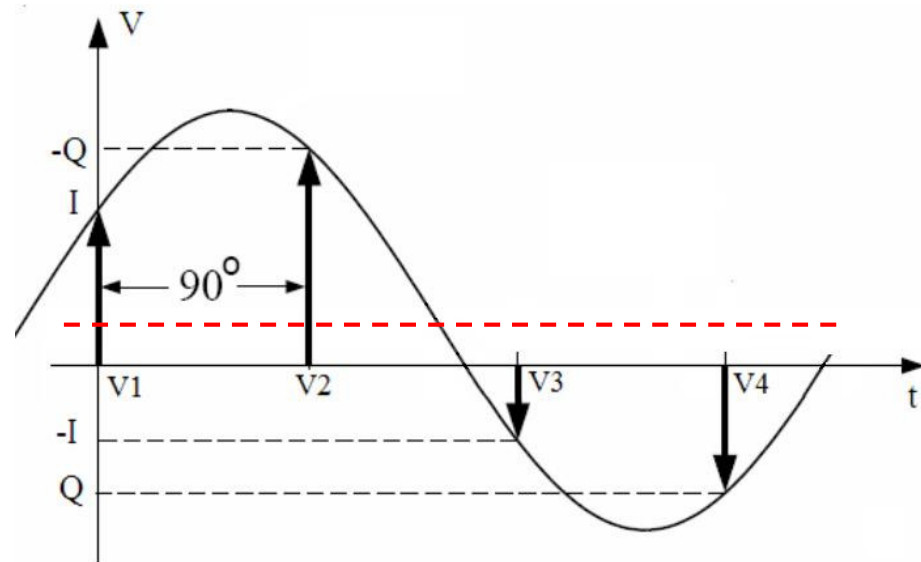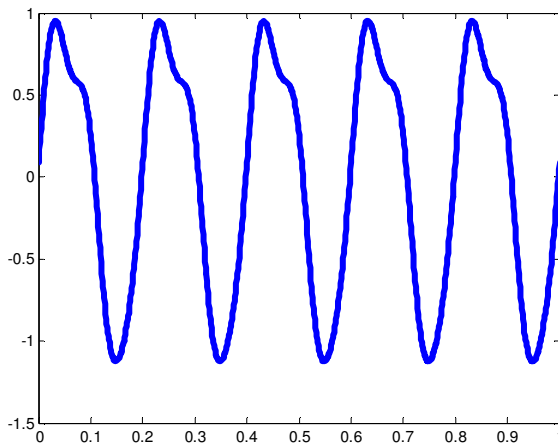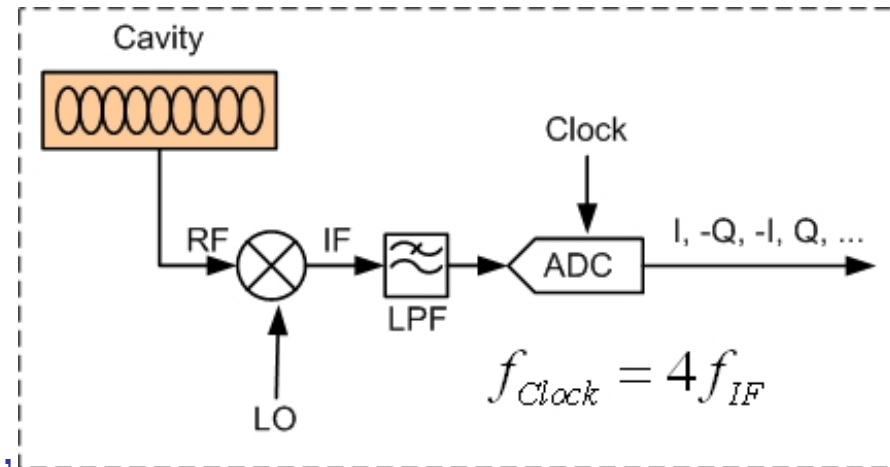- Advantages
 - Get rid of the imbalance effect compared with the analog I/Q demodulator
- Problems
 - DC offset caused by the mixer
 - Nonlinearities in the analog front-end or the ADC generate harmonics, which will be aliased to the IF frequency




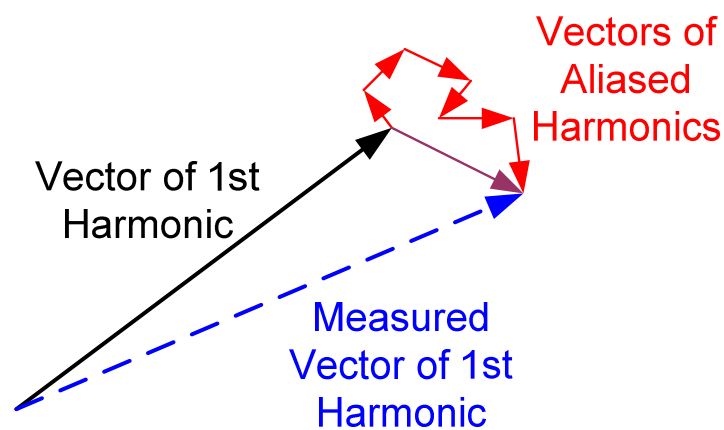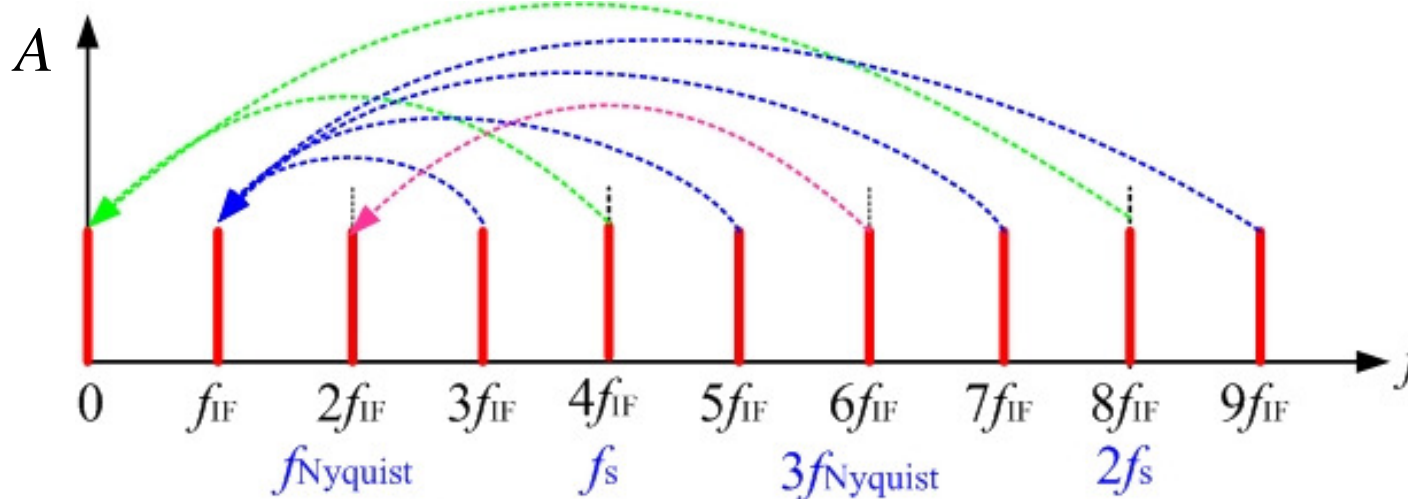

- The phase of n th harmonic changes n times faster than the fundamental phase
- Phase shifts in the cavity due to microphonics and Lorenz force detuning will lead to a time dependent error


Non-IQ Sampling

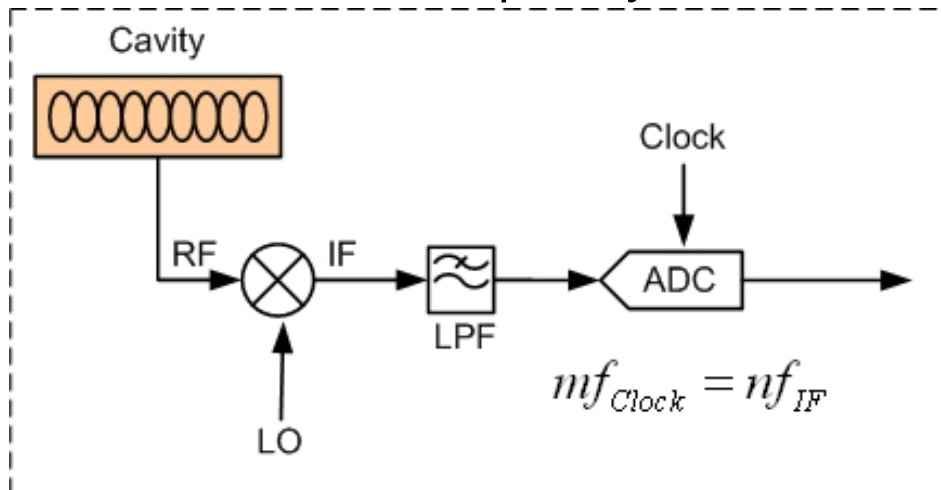- Compared with IQ sampling, non-IQ sampling is aimed to avoid the harmonics aliasing by shifting the sampling frequency slightly from 4 times of the IF frequency



$$\Delta\varphi = \frac{m}{n} \cdot 2\pi$$

Example: $m=4, n=15$

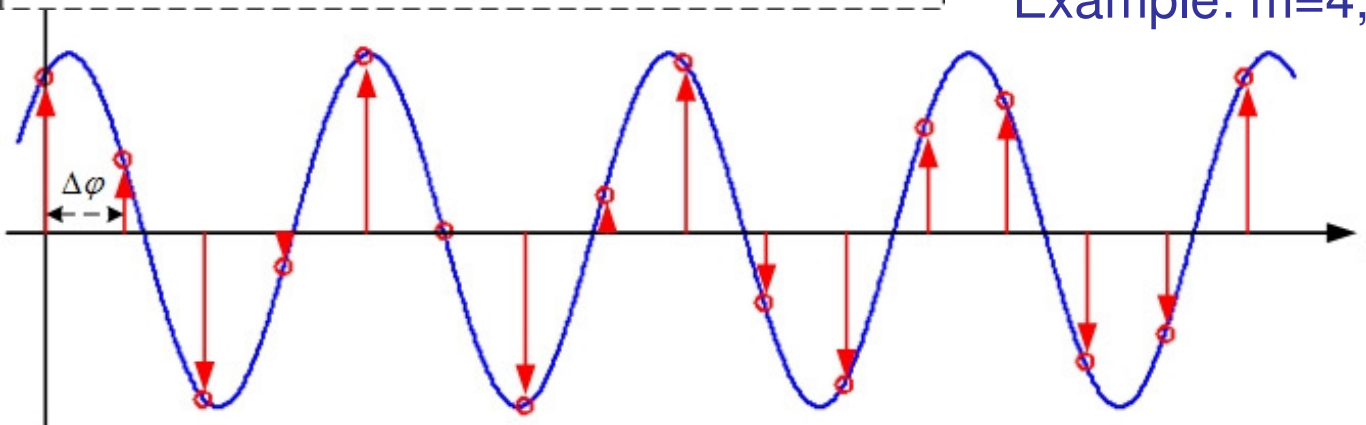



Non-IQ Sampling

- Fourier series decomposition of the RF signal

$$s(t) = A \sin(2\pi f_{IF} t + \varphi) = I \cos(2\pi f_{IF} t) + Q \sin(2\pi f_{IF} t)$$

$$s(t) = \frac{a_0}{2} + \sum_{k=1}^{\infty} [a_k \cos(k 2\pi f_{IF} t) + b_k \sin(k 2\pi f_{IF} t)]$$

$$\begin{cases} a_k = \frac{2}{T} \int_0^T s(t) \cos(k 2\pi f_{IF} t) dt \\ b_k = \frac{2}{T} \int_0^T s(t) \sin(k 2\pi f_{IF} t) dt \end{cases}, \quad k = 1, 2, \dots$$


- Demodulation algorithm:

$$I = \frac{2}{n} \sum_{i=0}^{n-1} x_i \cos(i\Delta\varphi), \quad Q = \frac{2}{n} \sum_{i=0}^{n-1} x_i \sin(i\Delta\varphi)$$




Non-IQ Sampling

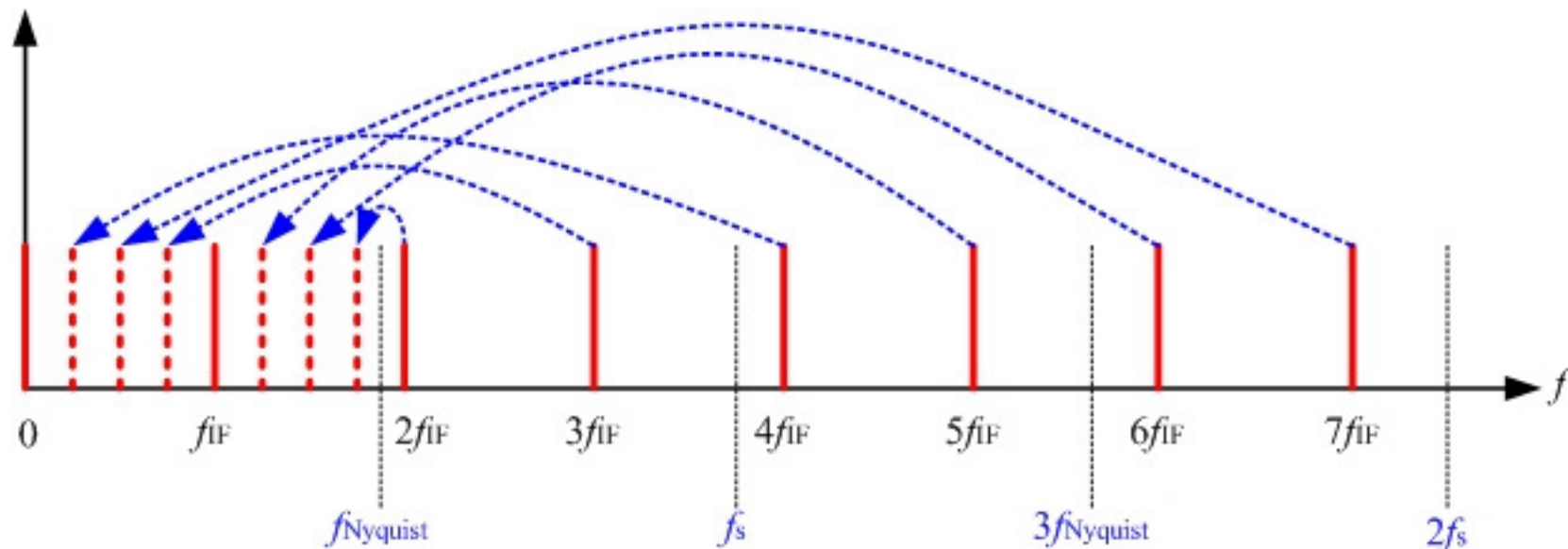- Most harmonics no longer line up with IF frequency. Influence due to the higher order harmonics and DC offset can be reduced with band pass filter.
- The algorithm for demodulation need more computation power and will cause larger latency



Direct Sampling

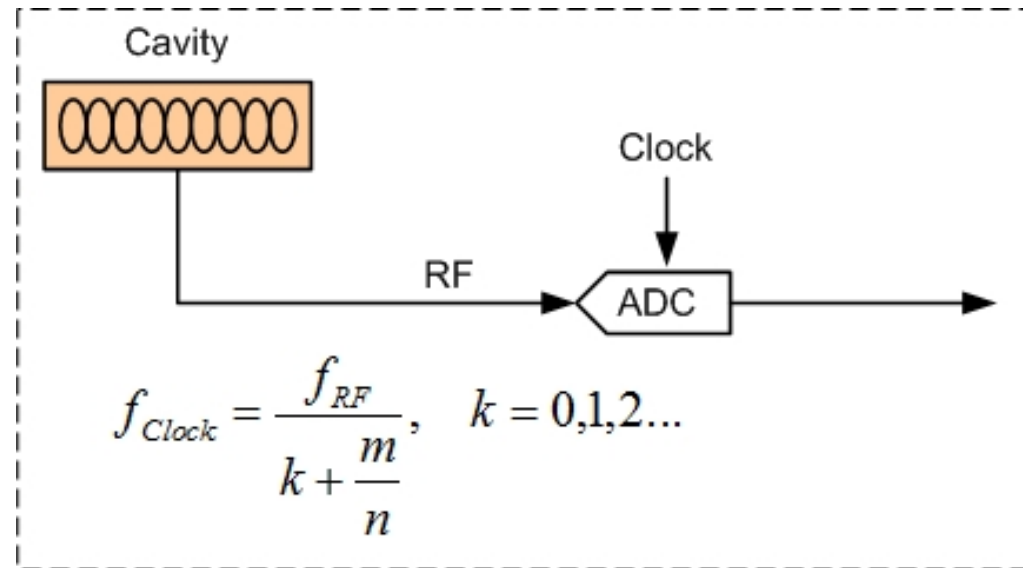



- Example for available ADC: ADS5474, 14 bits, 400MSPS, 1.4GHz bandwidth
- Under-sampling
- Non-IQ sampling (m,n have the same meaning as the discussion of non-IQ sampling)



Direct Sampling


- Advantage: no down converter needed
- **Essential problems:** ADC measurement noise is sensitive to the clock jitter due to the high input RF frequency
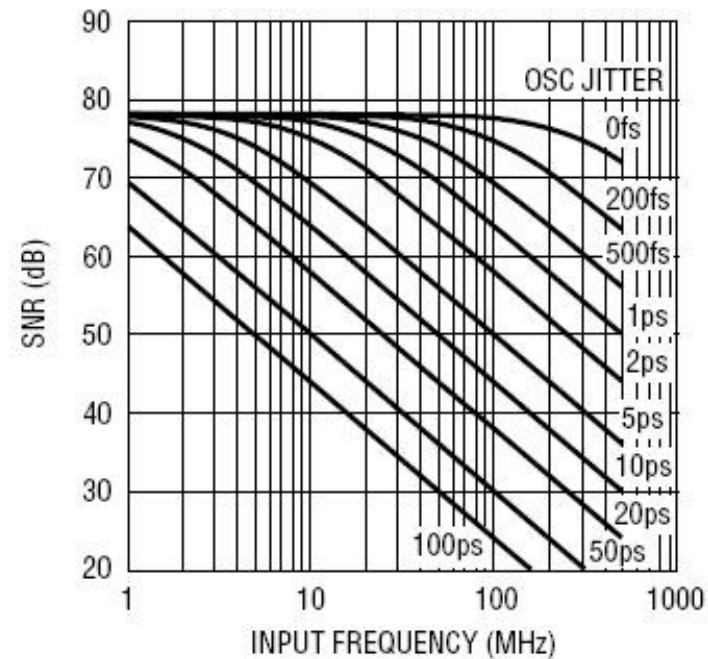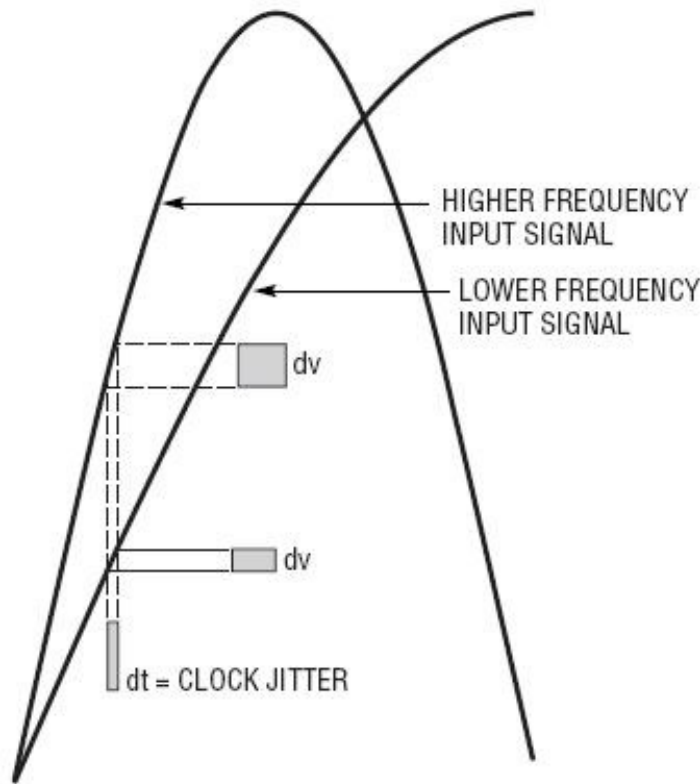
$$SNR_{jitter} = -20 \log_{10} (2\pi f_{RF} t_{jitter_rms})$$






Digital Down Conversion

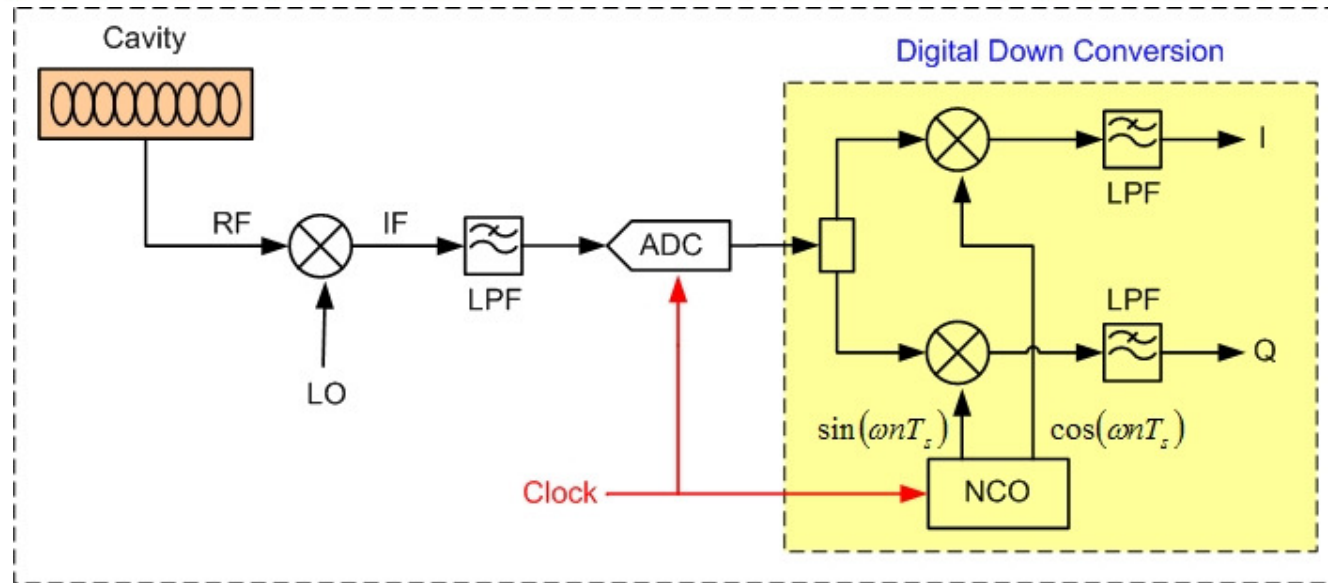

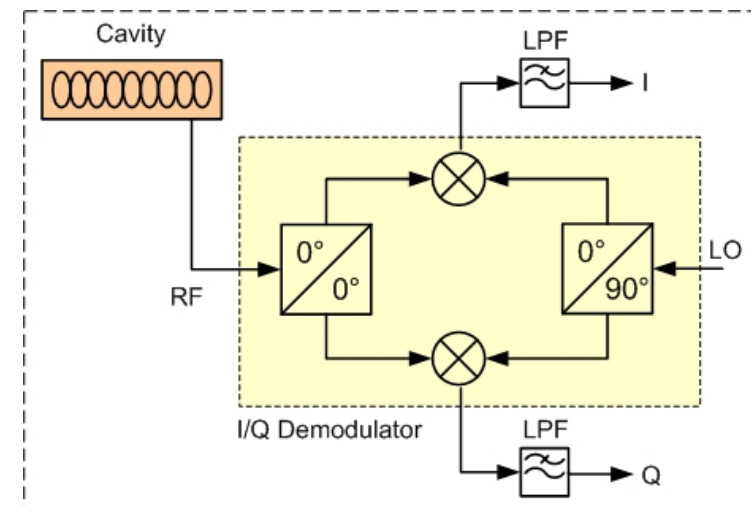- Principle same as analog I/Q demodulator
- NCO: Numerical Controlled Oscillator
- Digital mixer: multiplication operation in processors (in FPGA can be multiplier cores)
- Digital low pass filter, can be IIR, FIR or CIC filter






Reduce the Noises and Compensate the Drifts in RF Field Detection



Noise and Drift Sources for RF Detection

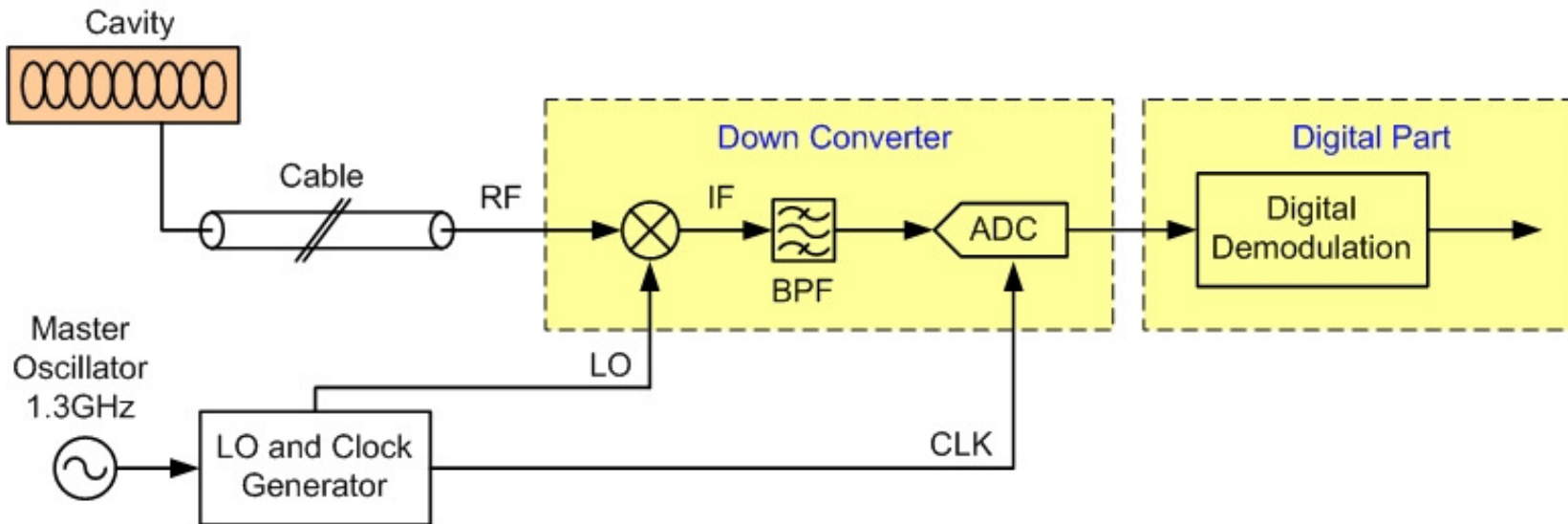


- Slow phase and amplitude drifts:
 - Cavity pick up cables
 - Down converter
 - LO low frequency phase noise
- Fast phase and amplitude jitters:
 - Thermal noise
 - LO high frequency phase noise
 - ADC noise



Reduce the High Frequency Noise

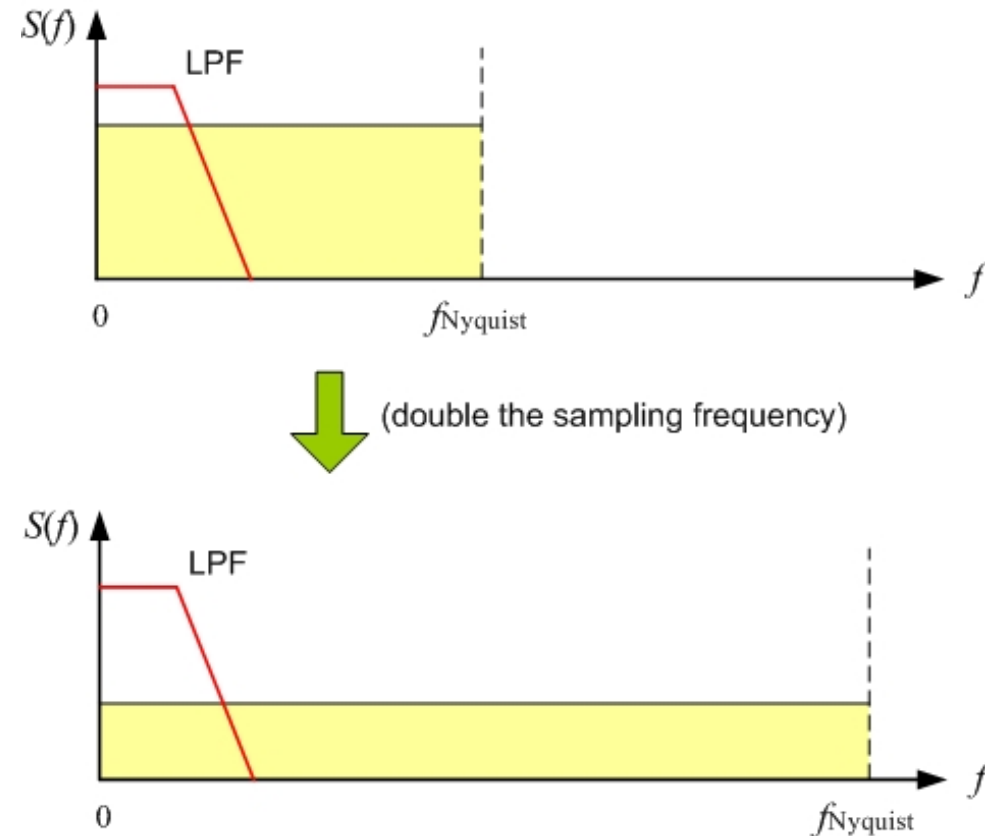
- Select components of down converter with low noise level
- Filtering in RF side
- ADC oversampling





Drift and Fluctuation Correction


Reference tracking

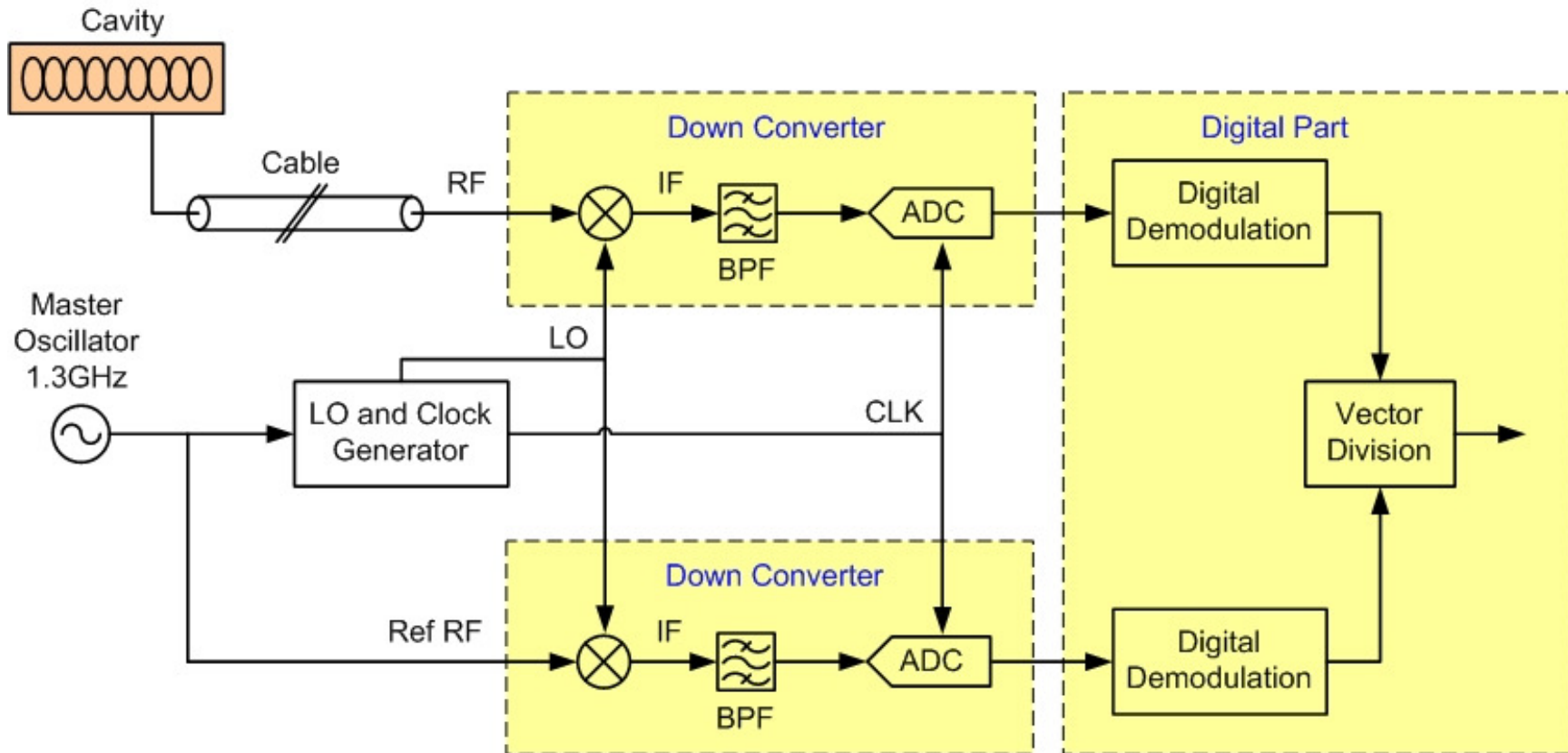



Drift and Fluctuation Correction

Measurement chain drift calibration

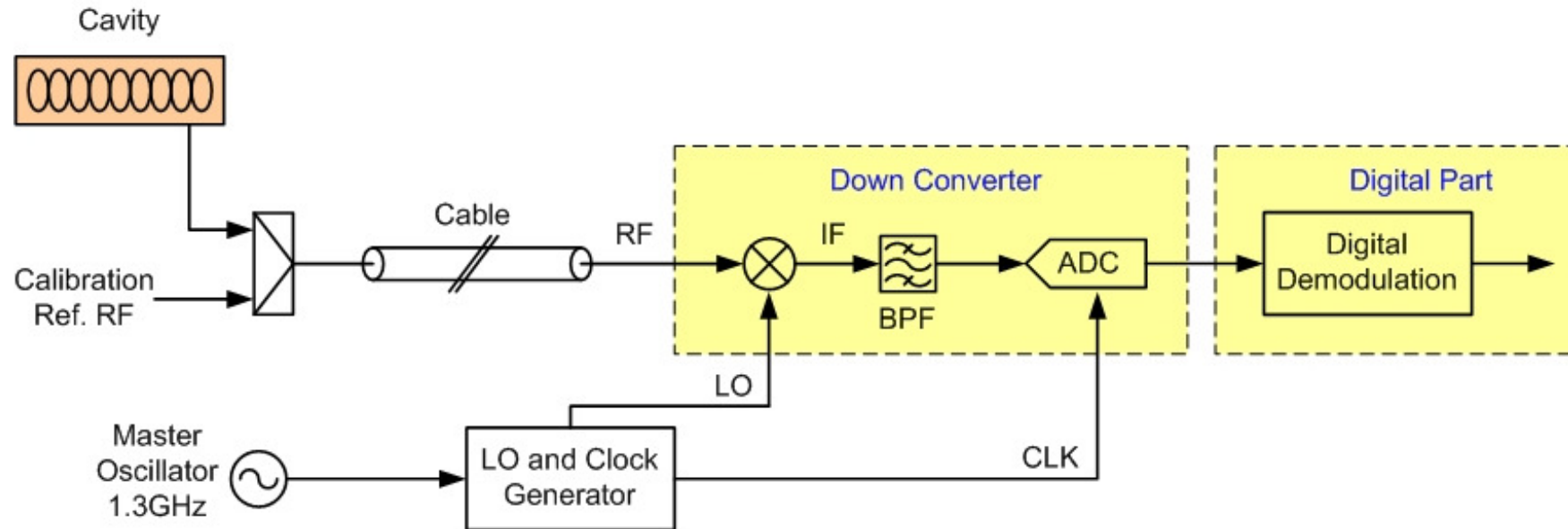




RF Actuation



RF Actuator

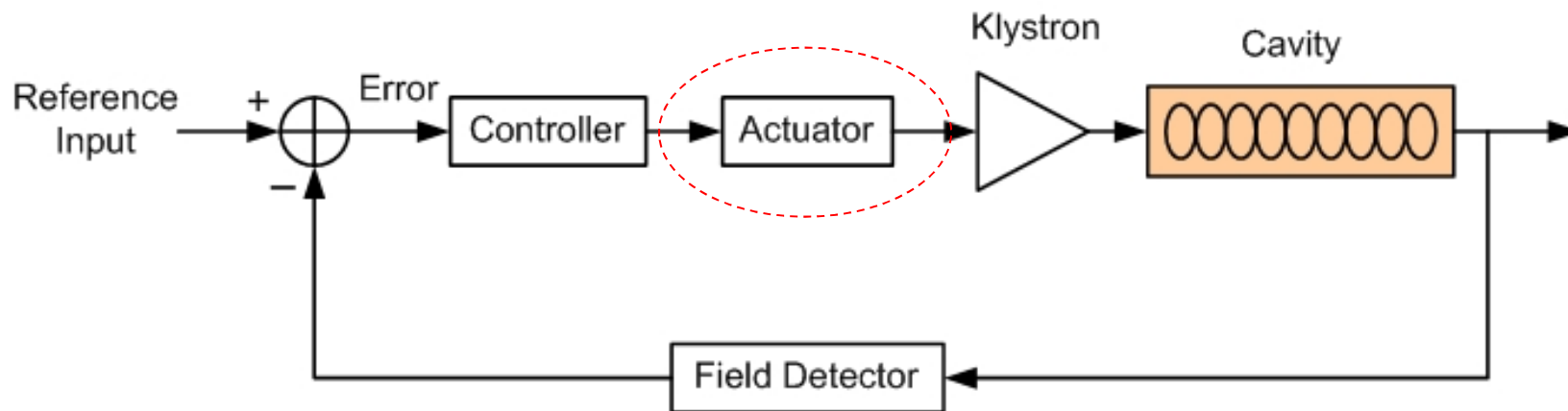- Change the amplitude and phase of RF driving signal and perform frequency up-conversion
- Widely used solutions:
 - Direct up-conversion
 - IF up-conversion
 - Single sideband up-conversion





Direct Up-conversion

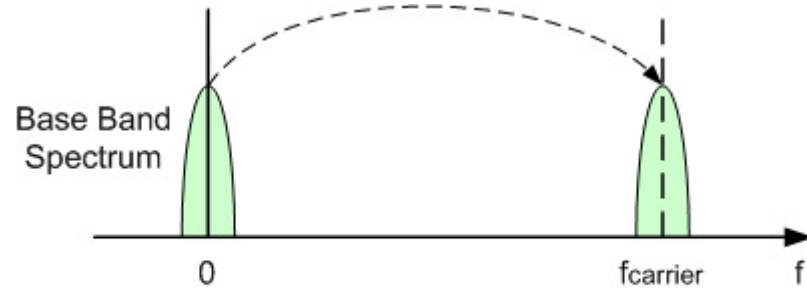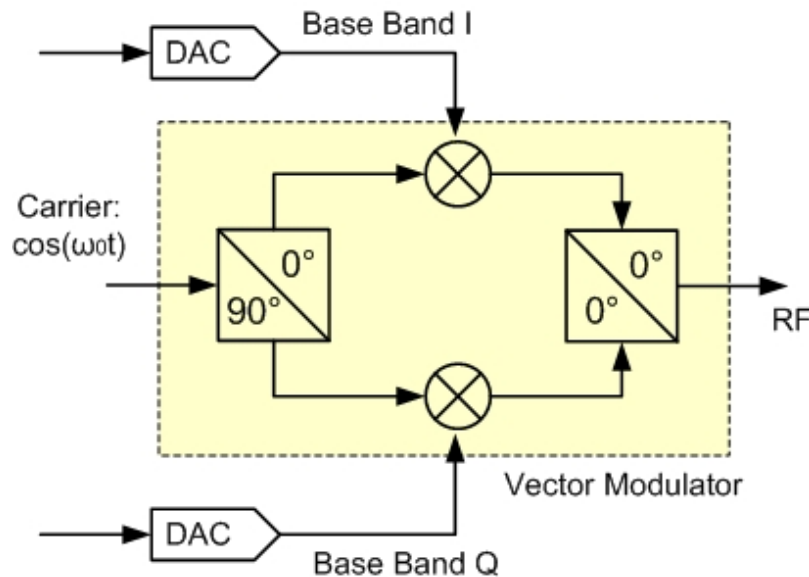


$$RF = I \cos(\omega_0 t) - Q \sin(\omega_0 t) = A \cos(\omega_0 t + \varphi)$$

$$A = \sqrt{I^2 + Q^2}, \quad \varphi = \tan^{-1}\left(\frac{Q}{I}\right)$$

- Easy to implement
- Suffer from the DC offset in I/Q base band signals and the phase and amplitude imbalance of the vector modulator




IF Up-conversion

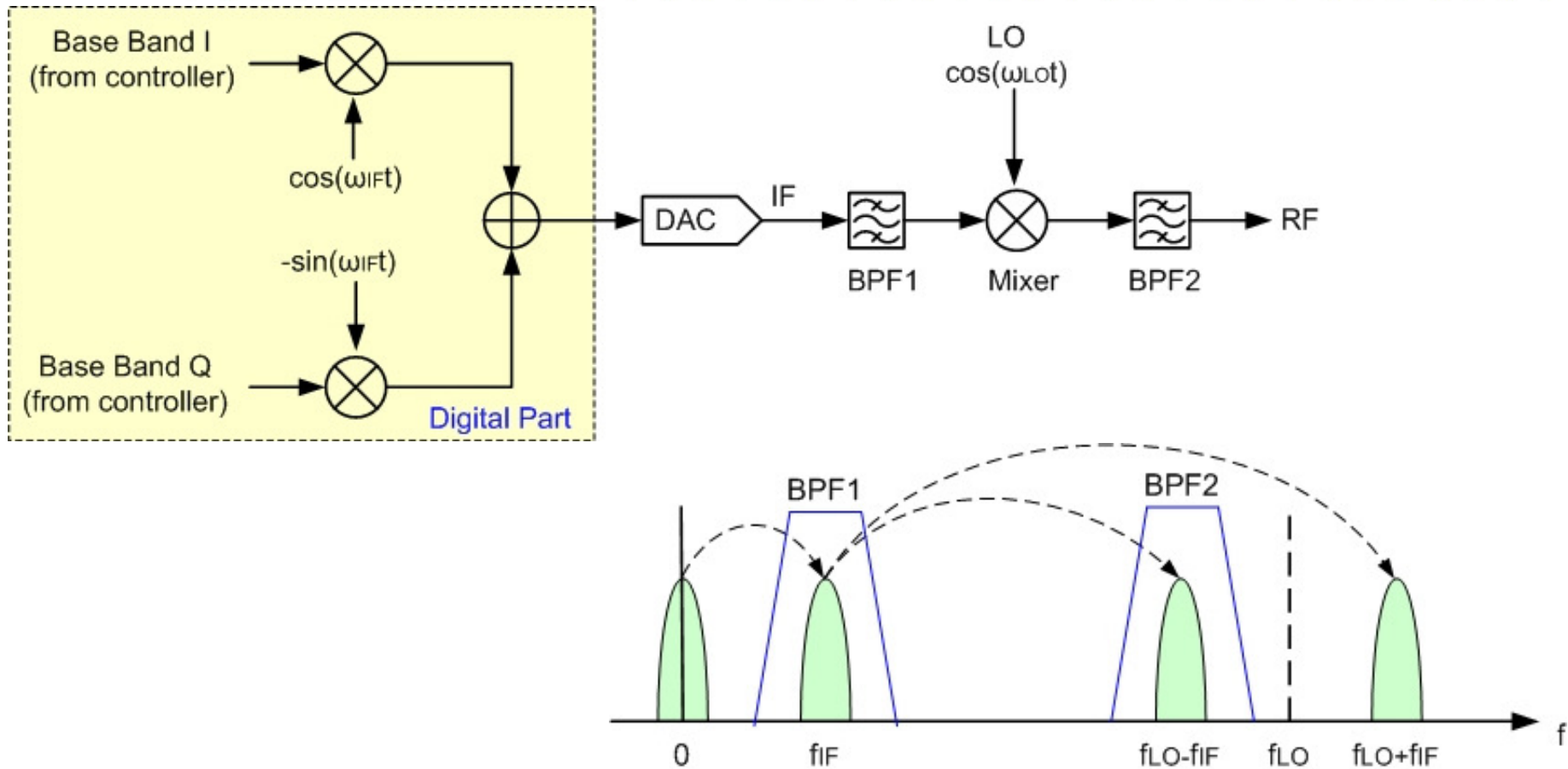

- Band pass filter after the DAC can remove the DC offset
- Band pass filter after the mixer is necessary
- If IF is small, filter design will be critical



Single Sideband Up-conversion

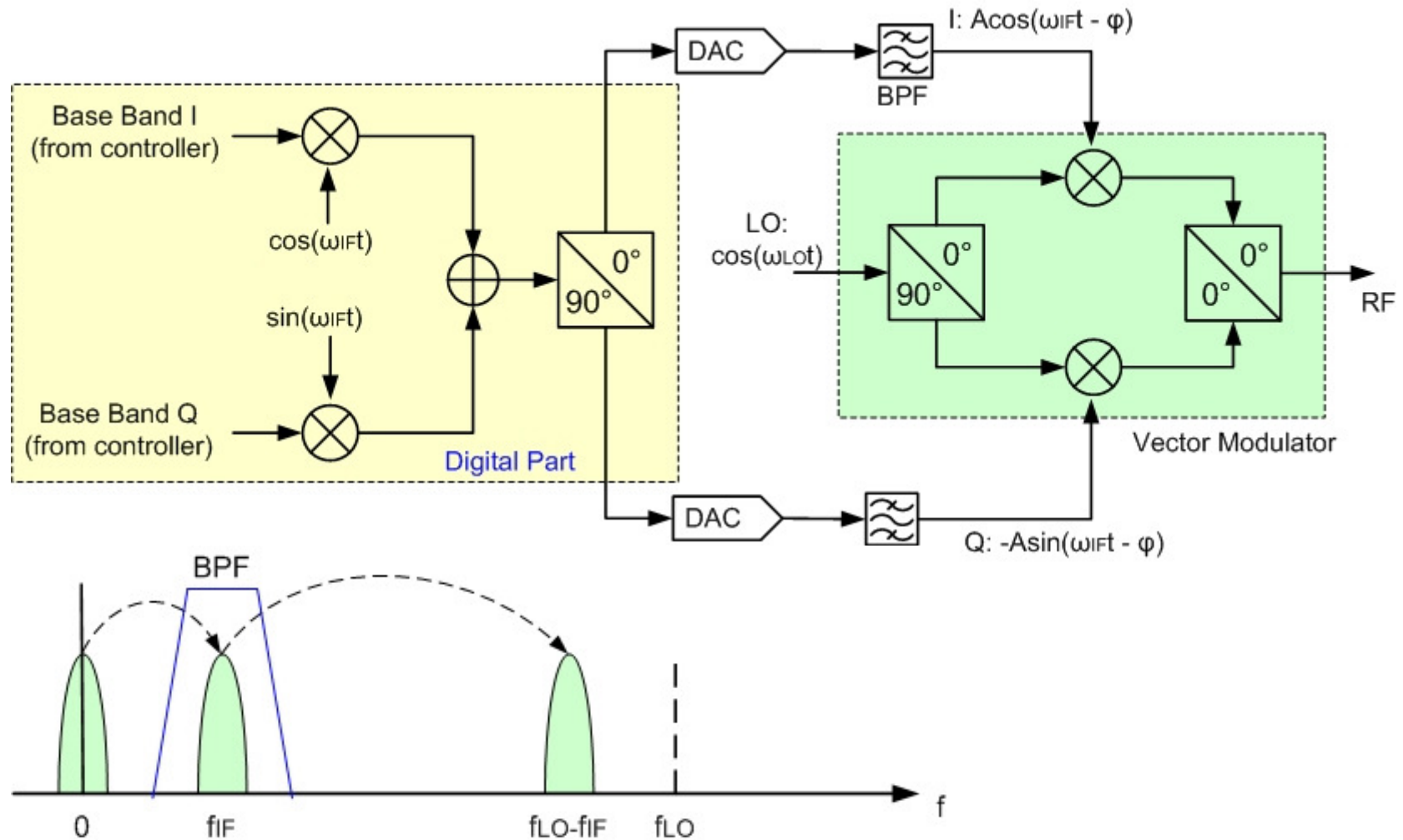

$$RF = A\cos(\omega_{LO}t)\cos(\omega_{IF}t - \varphi) + A\sin(\omega_{LO}t)\sin(\omega_{IF}t - \varphi) = A\cos[(\omega_{LO} - \omega_{IF})t + \varphi]$$



Summary

In this part, we have learnt:

- Principles and characteristics of several RF field detection methods
- Ideas to correct the noise and drift of the RF field detector
- Principles for several RF actuation (up-conversion) methods




Reference

- [1] Z. Geng. Design and Construction of the Phasing System for BEPCII Linac. Ph.D. thesis of Chinese Academy of Sciences, 2007
- [2] T. Schilcher. Vector Sum Control of Pulsed Accelerating Fields in Lorentz Force Detuned Superconducting Cavities. Ph. D. Thesis of DESY, 1998
- [3] M. Hoffmann. Development of A Multichannel RF Field Detector for the Low-Level RF Control of the Free-Electron Laser at Hamburg. Ph.D. Thesis of DESY, 2008
- [4] L. Doolittle. Digital Low-Level RF Control Using Non-IQ Sampling. LINAC2006, Knoxville, Tennessee USA
- [5] Z. Geng, S. Simrock. Evaluation of Fast ADCs for Direct Sampling RF Field Detector for the European XFEL and ILC. LINAC2008, Victoria, BC, Canada



Appendix: Typical Hardware for RF Field Detection

Mixer

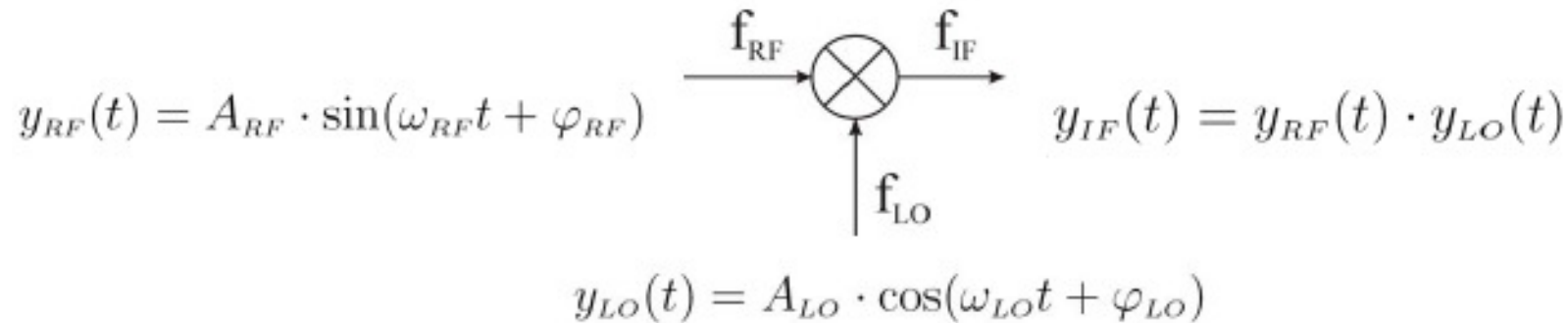

mixer: linear time varying circuit, non-linear circuit (diodes...)

$$\Rightarrow y_{IF}(t) = \frac{1}{2} A_{LO} A_{RF} \cdot \left(\begin{array}{l} \boxed{\sin[(\omega_{RF} - \omega_{LO})t + (\varphi_{RF} - \varphi_{LO})]} \\ + \boxed{\sin[(\omega_{RF} + \omega_{LO})t + (\varphi_{RF} + \varphi_{LO})]} \end{array} \right)$$

lower sideband
upper sideband

➔ even ideal mixers produce two sidebands



Mixer

➔ ideal mixer: output is the multiplication of the two input signals

➔ down conversion:



RF, LO are high frequency inputs

IF: lower intermediate frequency output

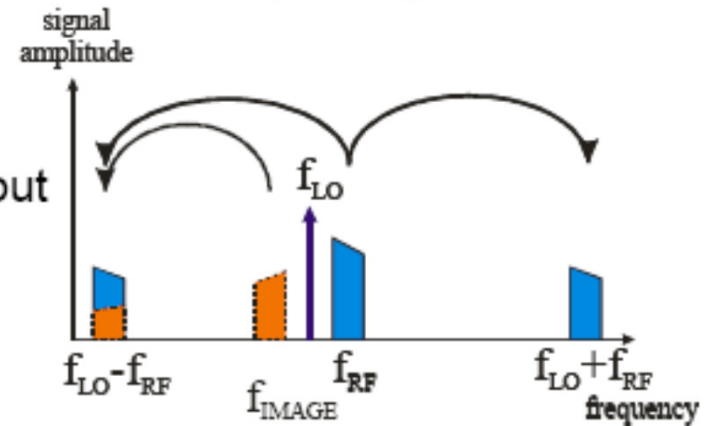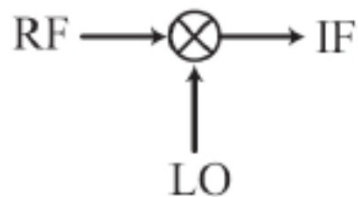

➔ up conversion:

IF is input, RF is output

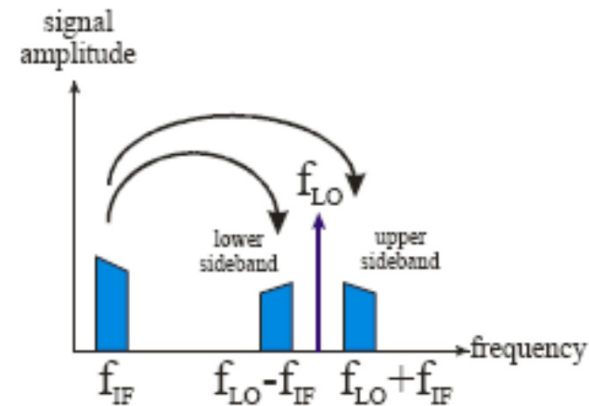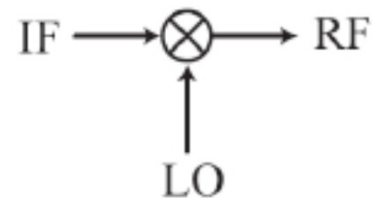

down conversion:

$$y_{IF}(t) = \frac{1}{2} A_{LO} A_{RF} \cdot \left(\sin[(\omega_{RF} - \omega_{LO})t + (\varphi_{RF} - \varphi_{LO})] + \sin[(\omega_{RF} + \omega_{LO})t + (\varphi_{RF} + \varphi_{LO})] \right)$$

low pass filtering the upper sideband:

$$\Rightarrow y_{IF}(t) = A_{IF} \cdot \sin(\omega_{IF}t + \varphi_{IF})$$

$$\omega_{IF} = \omega_{RF} - \omega_{LO}$$

$$A_{IF} = \frac{1}{2} A_{LO} A_{RF} \sim A_{RF} \quad \text{with constant } A_{LO}$$

$$\varphi_{IF} = \varphi_{RF} - \varphi_{LO} \sim \varphi_{RF} \quad \text{with constant } \varphi_{LO}$$

**basic properties of RF
signal are conserved
(ampl./phase)**


important properties:

- phase changes/jitter are conserved during down conversion,
e.g. $1^\circ @ f_{RF}=1.5 \text{ GHz} \leftrightarrow 1^\circ @ f_{IF}=50 \text{ MHz}$
- comparison: sampling IF or RF (direct sampling)?
timing jitter results in different phases!
(e.g. $10 \text{ ps} @ 500 \text{ MHz} \rightarrow 1.8^\circ$; $10 \text{ ps} @ 50 \text{ MHz} \rightarrow 0.18^\circ$)


➔ tougher requirements for direct RF sampling !

real mixers = non linear devices

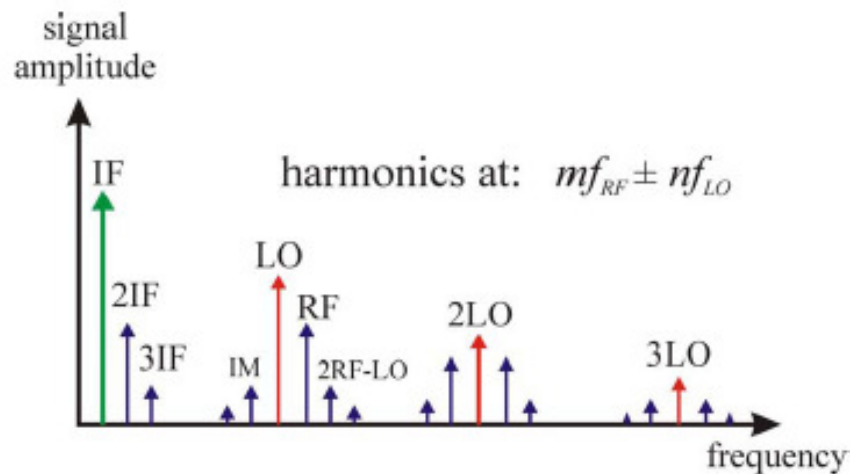- ➡ many undesired harmonics in frequency spectrum
- ➡ non-linearities in IF signal



I-V curve of a diode

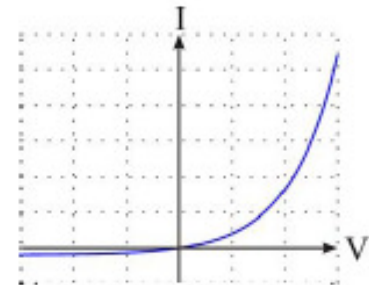


$$I = I_0(e^{V/V_T} - 1)$$

$$\Delta I = I_0 e^{V/V_T} \left(\frac{\Delta V}{V_T} + \frac{1}{2} \left(\frac{\Delta V}{V_T} \right)^2 + \frac{1}{6} \left(\frac{\Delta V}{V_T} \right)^3 + \dots \right)$$

- ➡ filtering the output of a mixer might be necessary
 - ➡ take care about the introduced group delay by the filter
- } trade off!

Analog to Digital Converter

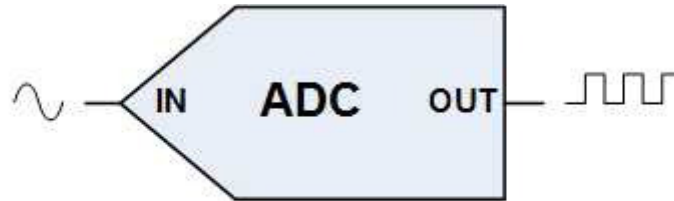

ELECTRICAL SYMBOL FOR ANALOG TO DIGITAL CONVERTER (ADC)


What is an ADC?

- **Mixed-Signal Device**
 - Analog Input
 - Digital Output
- **May be Considered to be a Divider**
 - Output says: Input is What Fraction of V_{REF} ?
- ➔ **Output = $2^n \times G \times A_{IN} / V_{REF}$**
 - n = # of Output Bits (Resolution)
 - G = Gain Factor (usually “1”)
 - A_{IN} = Analog Input Voltage (or Current)
 - V_{REF} (I_{REF}) = Reference Voltage (or Current)



Analog to Digital Converter

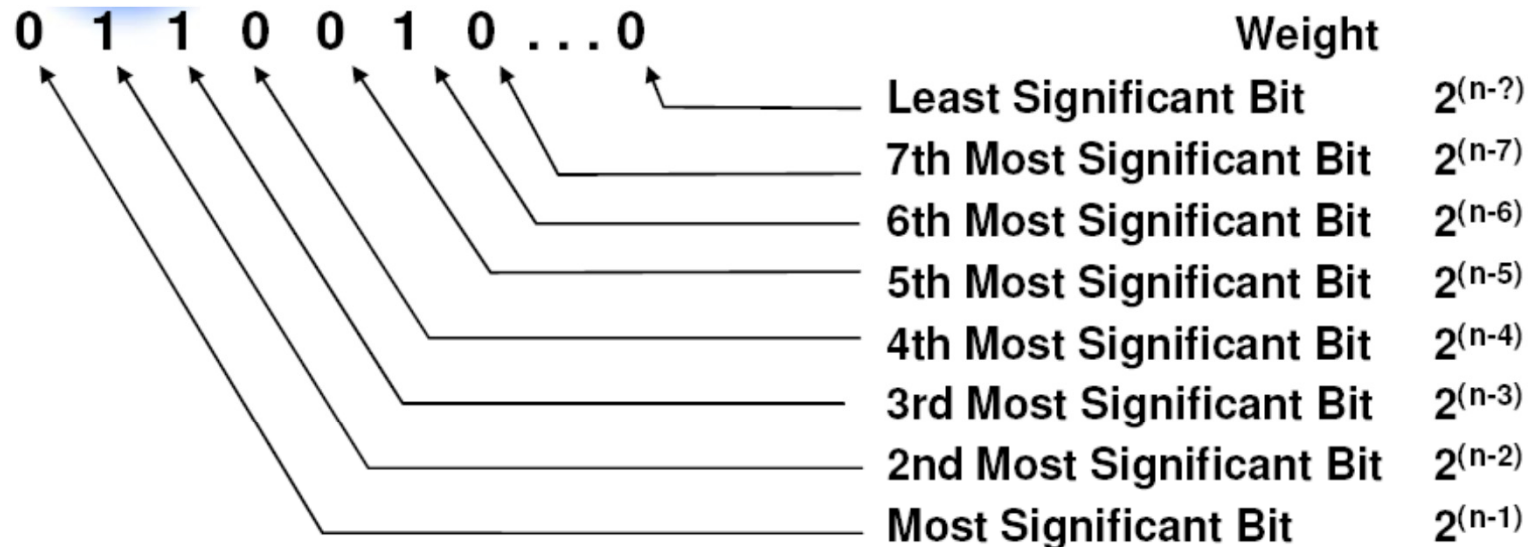
Least Significant Bit (LSB) and Most Significant Bit (MSB)



MSB								LSB
B7	B6	B5	B4	B3	B2	B1	B0	
128	64	32	16	8	4	2	1	



Analog to Digital Converter

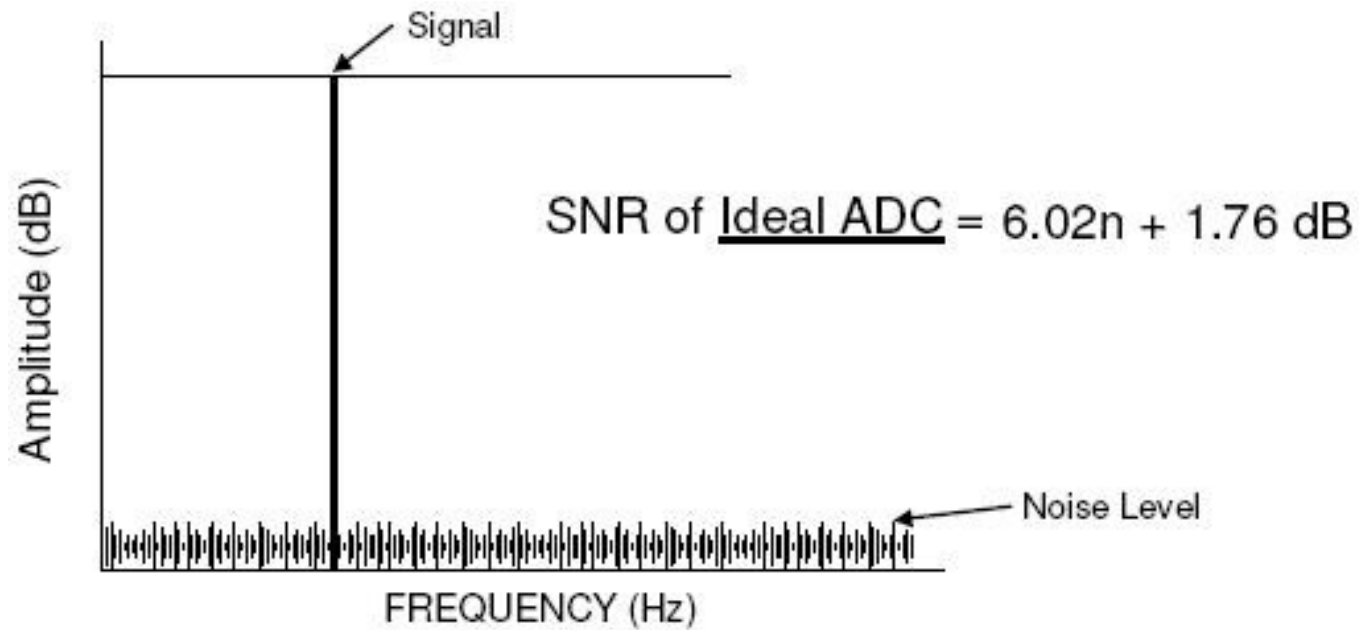




Analog to Digital Converter

ADC noise source: Quantization noise

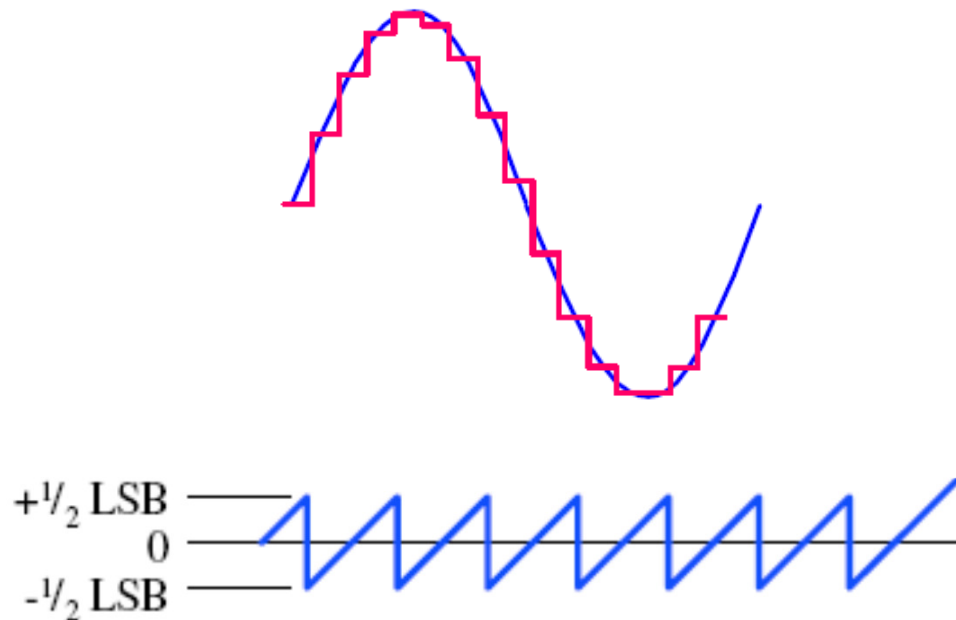- **Quantization Produces Noise**
- **Quantization Noise Is Inversely**
- **Inversely Proportional to ADC Resolution**







Analog to Digital Converter

ADC noise source: Clock jitter
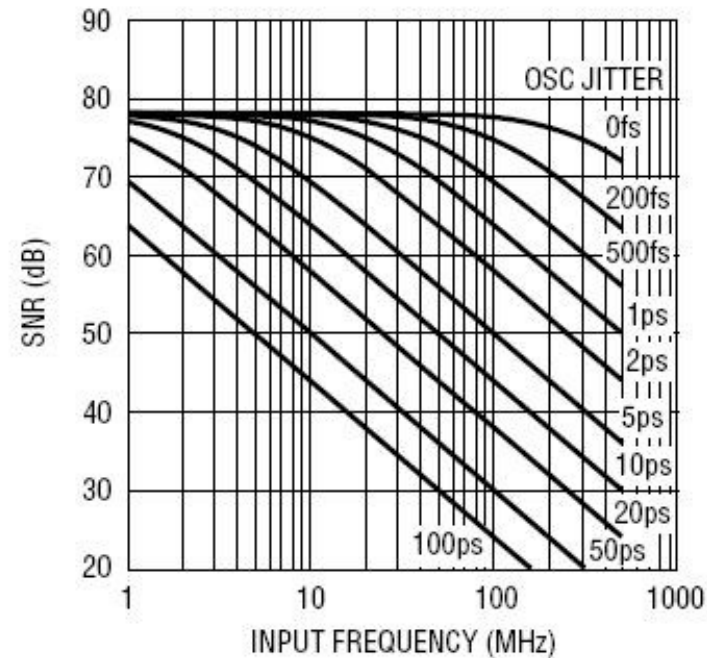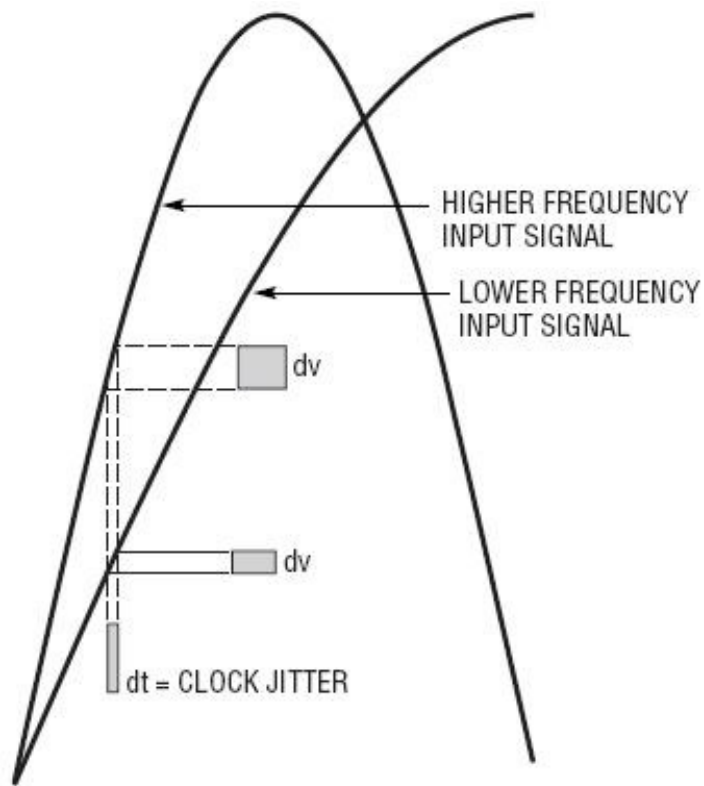
$$SNR_{jitter} = -20 \log_{10} (2\pi f_{RF} t_{jitter_rms})$$





Analog to Digital Converter

ADC noise source: Noisy components or circuitry

- **ADC Input Signal Conditioning is Common**
- **Noisy Amplifiers**
- **Resistors**
 - Noise
 - Use Low Values
- **High Frequency Coupling**
- **Resistor Packs**
 - Bandpass Characteristics
 - Oscillation
 - D.C. Offset



Analog to Digital Converter

Signal to Noise Ratio (SNR) of ADC:

$$\text{SNR}_{\text{dB}} = -20 \log_{10} \left[(2\pi f_a t_j)^2 + \frac{2}{3} \left(\frac{1 + \epsilon}{2^N} \right)^2 + \left(\frac{2\sqrt{2}V_n}{2^N} \right)^2 \right]^{\frac{1}{2}}$$

f_a : input frequency [Hz]

t_j : rms clock timing jitter [s]

ϵ : differential nonlinearity, DNL [LSB]


N : number of bits

V_n : equivalent input noise [LSB].



Analog to Digital Converter

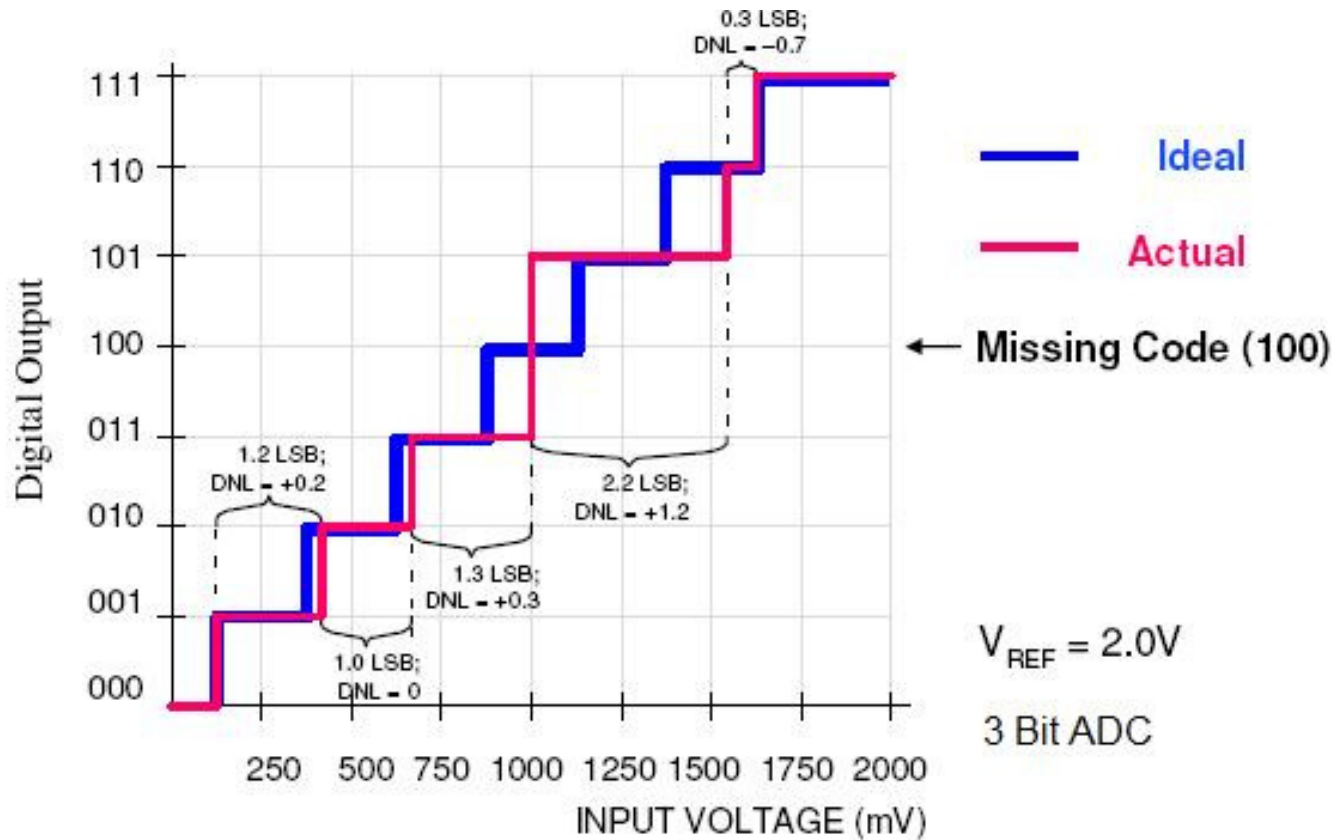
Differential Non-Linearity (DNL): “small scale” code to code errors






Analog to Digital Converter

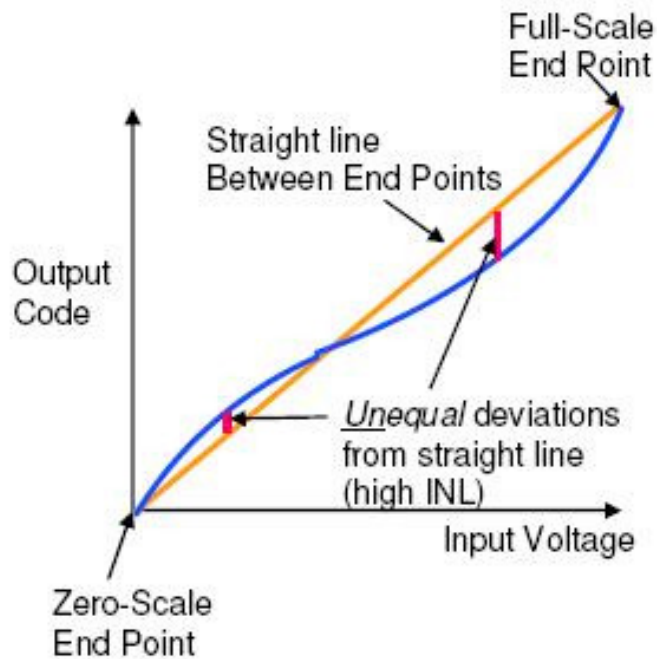Integral Non-Linearity (INL): “large scale” overall transfer function error



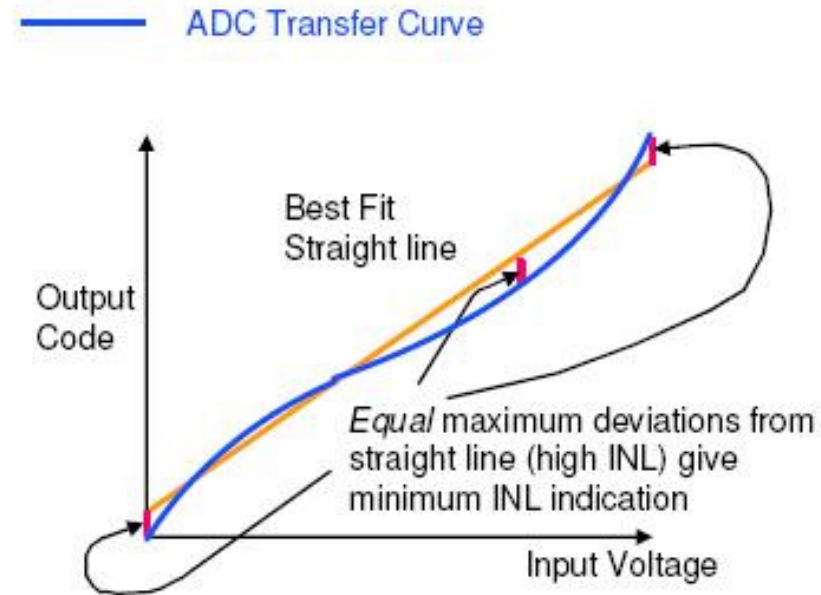“End-Point” INL Measurement Indicates Worst Case INL



“Best-Fit” INL Measurement Provides Best Possible INL Specification