 


Peak Sensing ADC for SiPM readout

Wei Shen



*Kirchhoff Institut für Physik
Ruprecht-Karls Universität Heidelberg*



10.12.2013 DESY

Outline



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386

- ✓ *Motivation & Requirements of the ADC*
- ✓ *Analog to Digital Converter structure*
 - *Peak holder*
 - *SAR capacitor array*
 - *Switches*
 - *Comparator*
 - *Residue amplification*
 - *Power estimation*
- ✓ *Status & Time Plan*


Motivation and Requirements



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386

- ✓ **Quantization (one ADC per channel):**
 - charge integration for SiPM output*
 - low power $< 1\text{mW}$*
- ✓ **Charge collection is a time dependent process**
 - peaking time is rather sensitive to the signal shape*
- ✓ **Resolution - 12 bits is needed in a small range**
 - 3 different types of signal to quantize:*
 - ☆ **SiPM calibration signal**
 - $12 \text{ bits, } \sigma = 260\mu\text{V} < \sigma_e$
 - ☆ **physical MIP-like signal**
 - ramp voltage**
 - $10 \text{ bits, } \sigma = 1.04\text{mV} \sim \sigma_e \ll S_{\text{pixel}}$

ADC structure

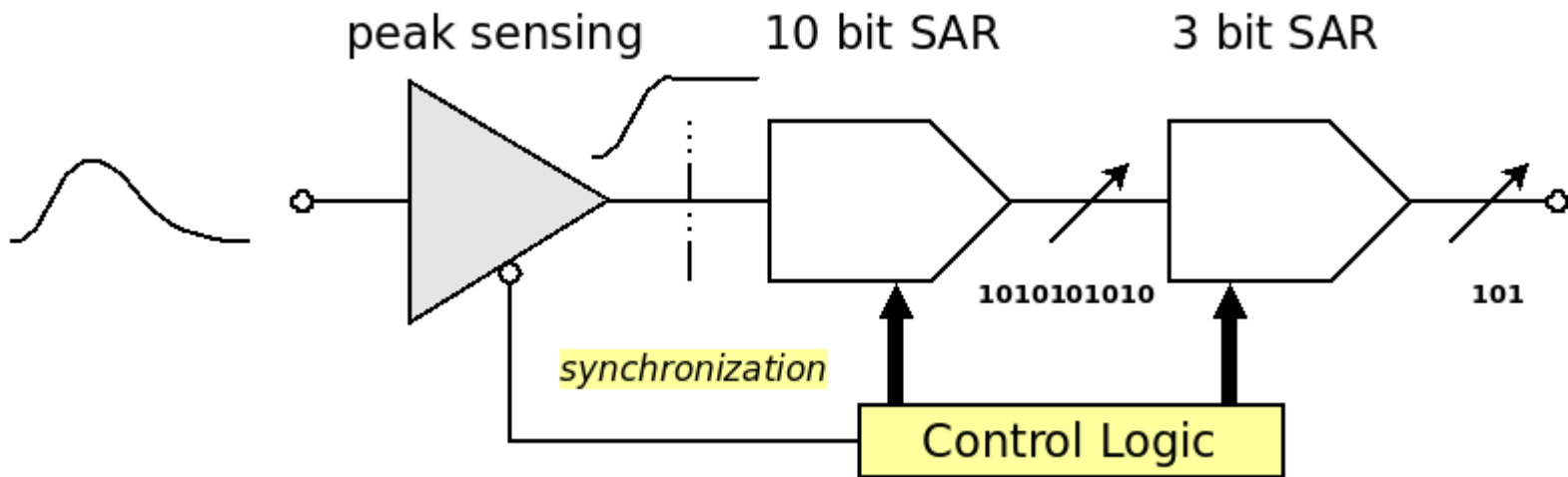

- *Random signal peak tracking >1.2V
peaking time > 50ns*
- *Peak identification is provided for synchronization*
- *SAR sampling rate 5MS/s , but not limited
max 50MS/s*

ADC structure




- The total processing time consists of

peaking time : $t_{peaking}$

synchronization time : t_{syn}

conversion time : t_{conv}

reset time : t_{reset}

 

shaping time $\tau = 50ns$, sampling rate = 5Ms/s

$t_{peaking} = 100ns$, $t_{conv} = 200ns$

$t_{syn} = 20ns$, $t_{reset} = 150ns$ (5%)

$t_{total} = 470ns$, $< 10 \tau$

direct signal processing + conversion

The data taken is only dependent on the FIFO size

✓ $\tau = 25ns$, 10Ms/s , $t_{total} < 350ns$

Circuit units - umc 0.18 μ



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386

Peak holder




3 functional phases

*tracking (sampling switch)
peaking
reset (fast recovery needed)*

capacitor is shared by the SAR array

 *bootstrape switch is needed
non-linearity should not be affected by
signal amplitude.
Only a constant part*



Peak holder - simulation




UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386

*Offset is expected, but differential
operation might rescue
Pedestal tracking beforehand*

*Residue smaller than $\pm 1\text{mV}$ in
all signal range*

 *nevertheless, only the small signal
part needs 12 bit resolution*



SAR capa array



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386

- *Largest Error comes from switch of the MSB*

$$DNL = (2^k - 1)dC/C \text{ LSBs}$$

k=10 , DNL < 1 LSB, dC/C must be better than 0.1%

According to the UMC datasheet, for Cpoly W=L > 7um, 10um will be taken


- *The total size of the C-array*

*32um * 100um, differential 64um * 100um*

KT/C noise, (thermal noise comes from the switch channel resistance) will be around 0.2 mV

Setting time < 10ns


SAR capa array

 

SAR capa simulation



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386

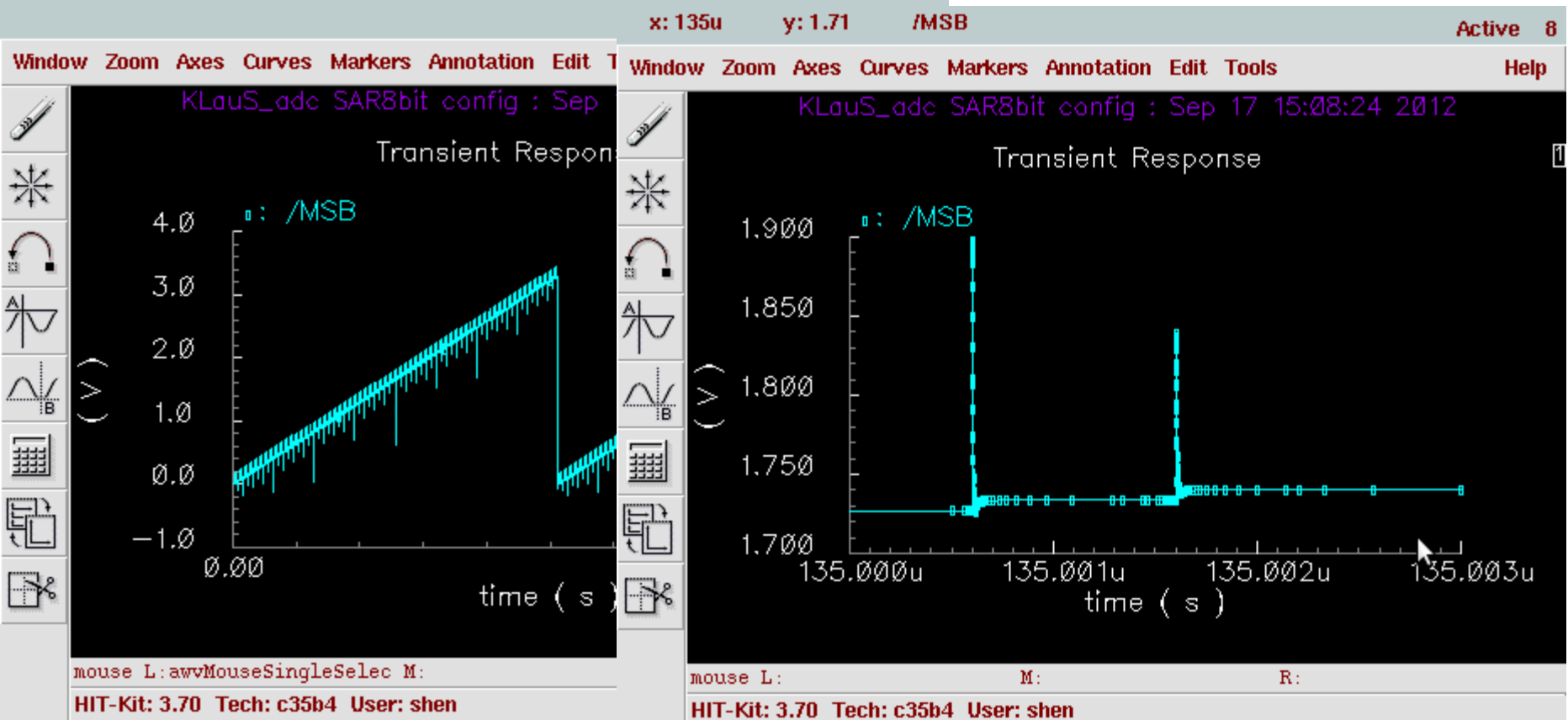

$DNL/INL < 0.5 \text{ LSB}$



response fast enough

switch design



- *There are 3 types of signal to switch*
- *vcc, gnd, signal, 3 different switches need*

*gnd
switch*

  

No complete cancellation

*At all corners, error about
1-2mV in MC connected to
Cmin,*


*Max error **+/-125uV** at
comparator*

switch design



- For signal, range range from 0 to 1.8V, switch with P/N mos is necessary, but the channel charge / clock feedthrough is dependent on input signal:

Bootstrap Switch

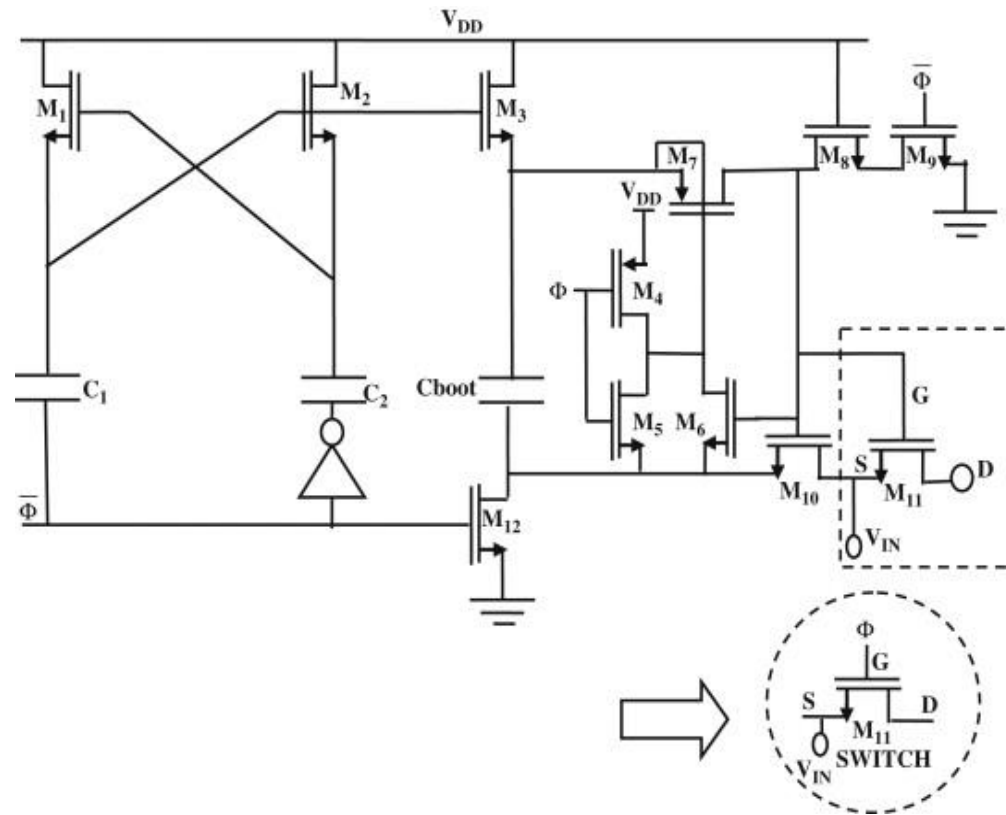

Residue Amplification




- Only functional in the calibration mode 12 bits
- Residue is amplified by

$C_{array}/C_{feedback}$

Detailed
switch control

Is necessary

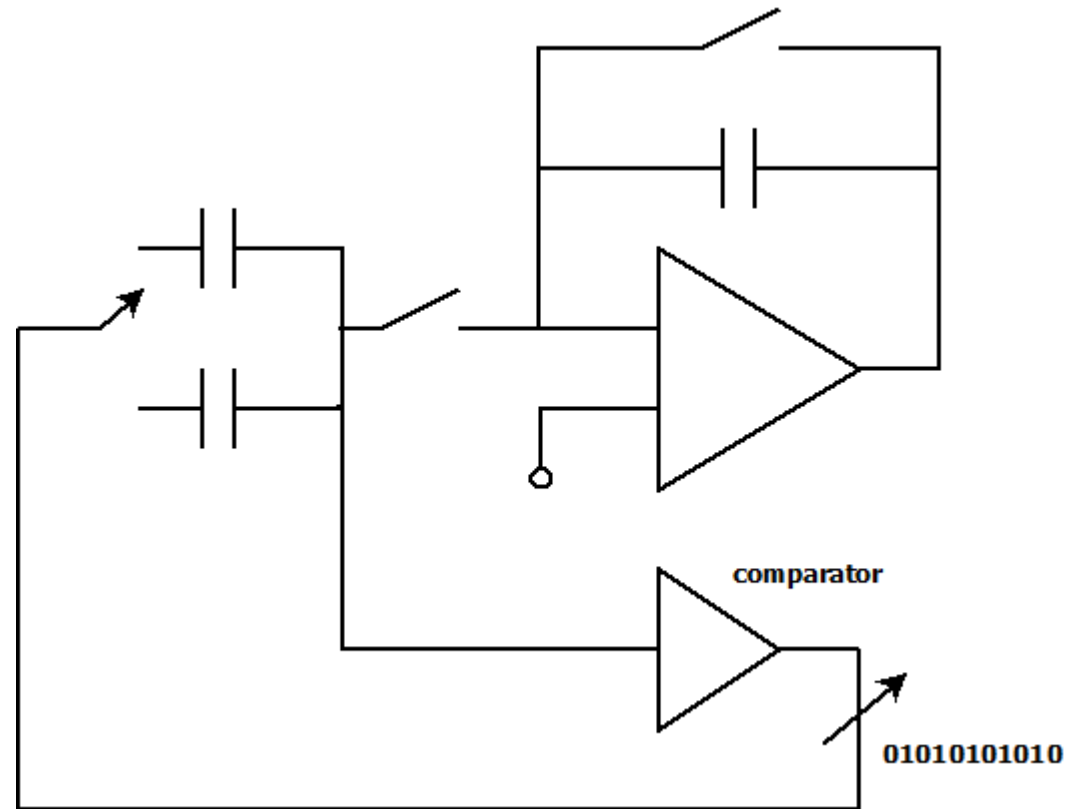

Power estimation



- The power consists of **5** components
 - peak sensing (amp, additional comparator)
amp = 350 μ W , additional comparator = 50 μ W
 - capacitor track power
1 μ W (1% occupancy)
 - SAR switching power
80 μ W (max)
 - dynamic comparator
5 μ W
 - control logic *100 μ W*

In total < 600 μ W (aggressively, 400 μ W)

Status & summary



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386

- *SAR ADC structure chosen*
- *12 bits = 10 + 3 with 1 bit redundancy*
- *SAR part*

peak sensing , switches, comparators finished

control logic and fine tuning

residue part not finished yet

Tape out , spring 2014, UMC 0.18 μ CMOS