



DAQ Hardware Status

Valeria Bartsch

Veronique Boisvert Maurice Goodrick, Barry Green, Bart Hommels, Marc Kelly, Andrzej Misiejuk, Vishal Panchal, Martin Postranecky, Matthew Warren, Matthew Wing, Tao Wu



DAQ architecture


DAQ software

Off Detector Receiver (ODR)

Link Data Aggregator (LDA)

Detector Interface (DIF)

Detector Unit

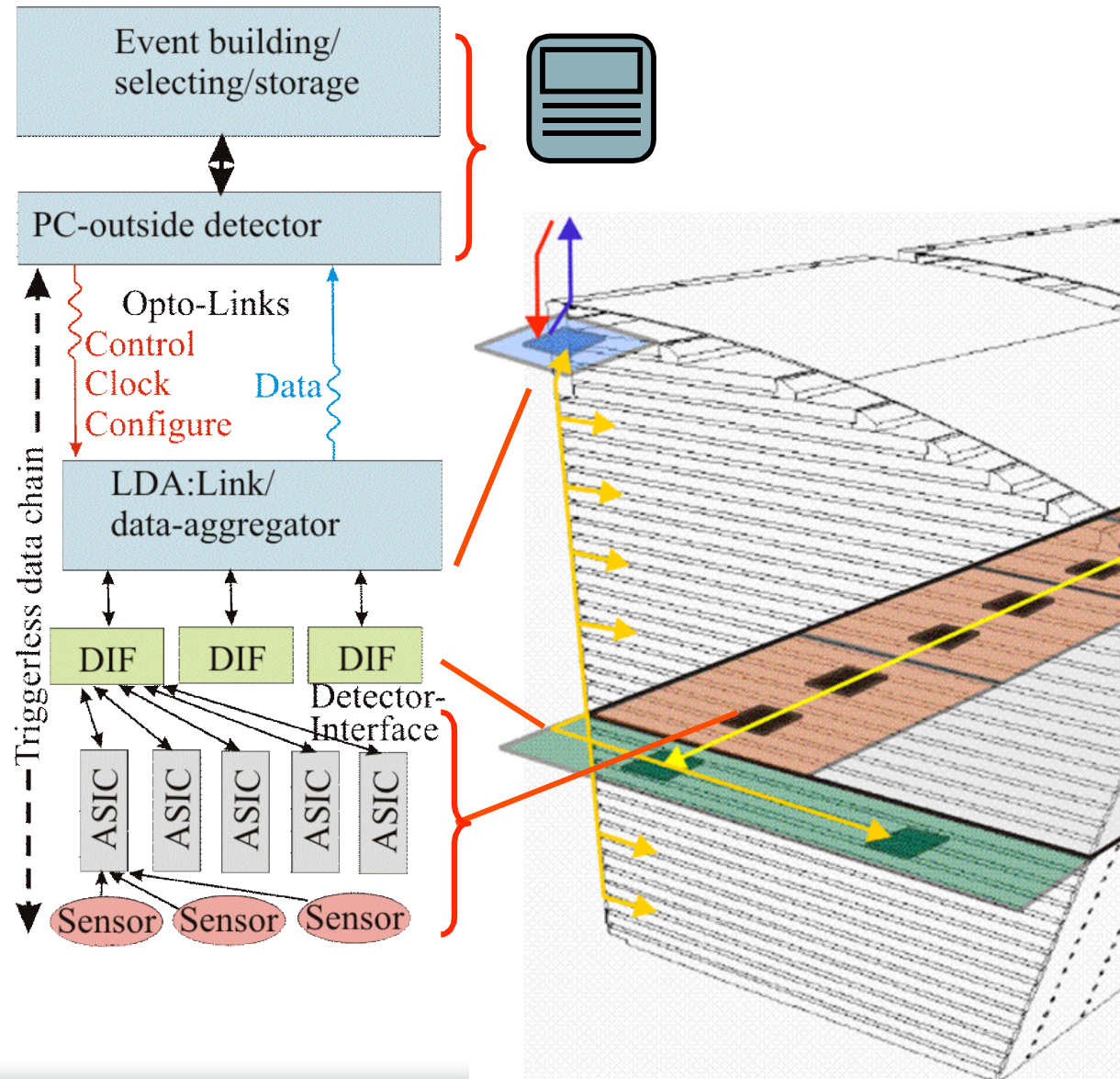

DAQ architecture

Detector Unit: ASICs


ODR: Off Detector Receiver – PC interface for system.

DIF: Detector InterFace connects Generic DAQ and services

NEW! CCC: Clock & Control Card: Fanout to ODRs (or LDAs)

LDA: Link/Data Aggregator – fanout/in DIFs and drives link to ODR



NEW! CONTROL PC: DOOCS GUI (run-control)

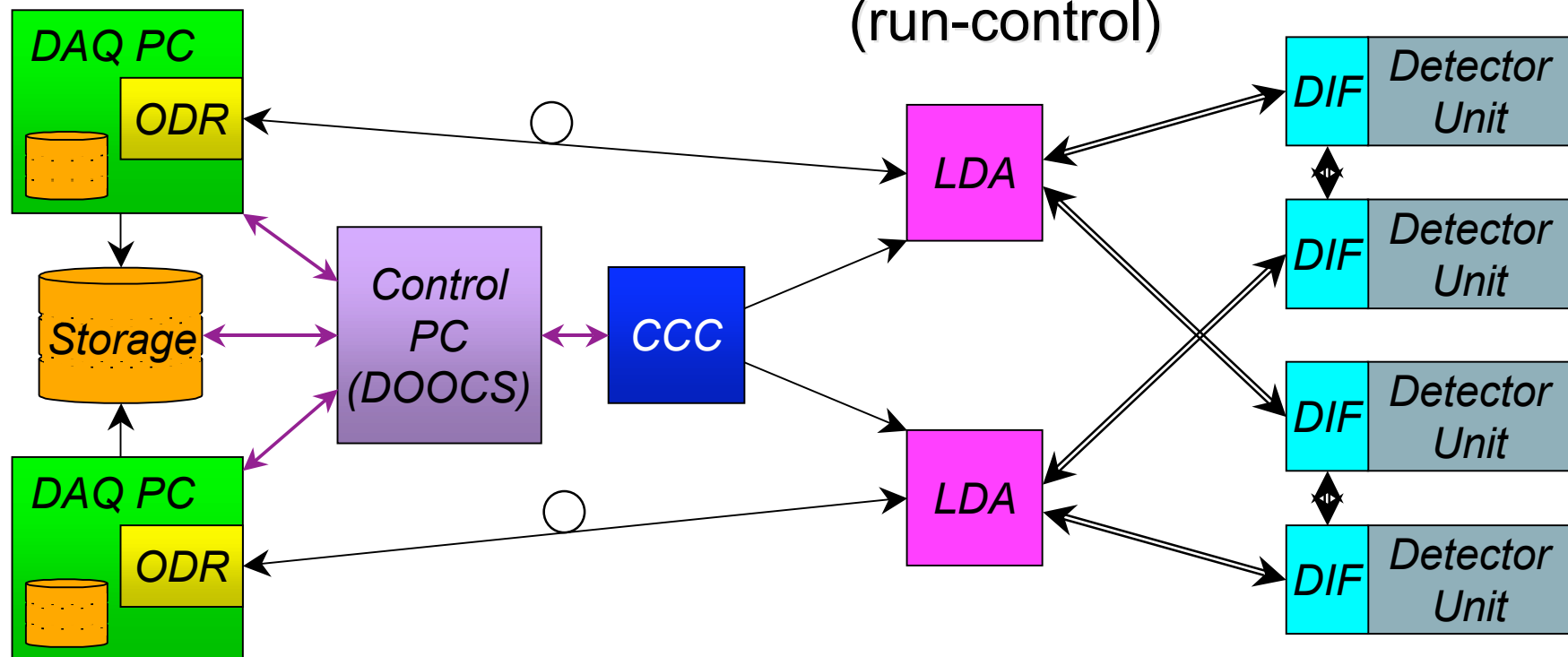

Clock: Detailed Overview Schematic


CLOCK

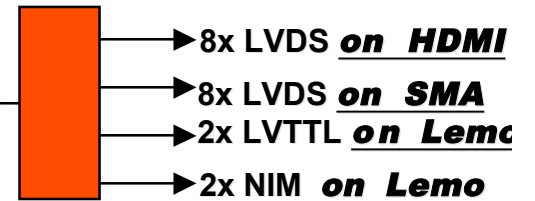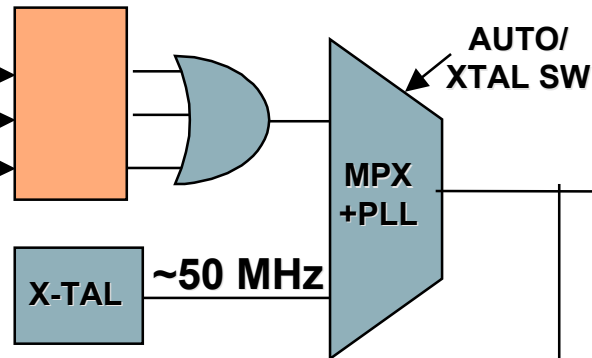LVDS on SMA
LVTTTL on Lemo
NIM/TTL on Lemo





ASync

LVDS on SMA
ECL on 2pin Lemo

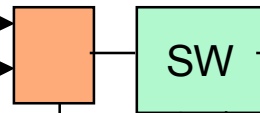



Controls (SYNCCMD, BUSY-IN etc)

4x LVDS on SMA
4x NIM on Lemo

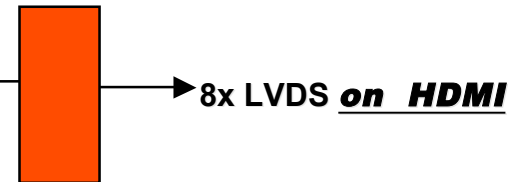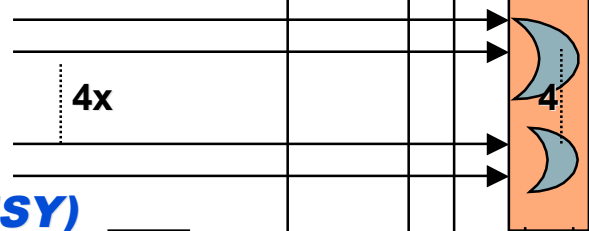





GEN (was BUSY)

LVDS on SMA
NIM on Lemo
o/c TTL on Lemo

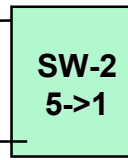 

SPARE (DATA, D2L)

LVTTTL on Lemo

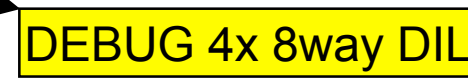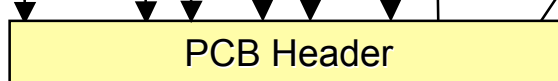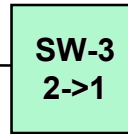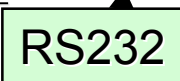

CCC Link Signals

Uses same HDMI cable and signal types/direction

CCC HDMI Signals		
<i>CLink Signal</i>	<i>CCC Signal</i>	<i>Function</i>
CLOCK_L2D	CLOCK_OUT	Clock
DATA_L2D	TRAINSINC_OUT	Trainsync signal output
DATA_D2L	Unused	Unused
ASYNC_L2D	FAST_OUT	Asynchronous signal
GEN_D2L	FAST_IN	Busy

- **CLOCK**

- Machine clock (50-100MHz)

- **TRAINSINC_OUT**

- Synchronisation of all the front-end slow clocks.
 - An external signal will be synchronized with/to CLOCK, phase adjusted and transmitted as a single clock-period wide pulse to the LDA.
 - To allow communicating with a stand-alone DIF, the CCC board can be configured to send the LDA 8b/10b serialised command for train-sync.

- **FAST_OUT**


- Transfer asynchronous triggers as fast as possible.
 - In AUTO mode, used to Transfer BUSY to detector (toggle = level)


- **FAST_IN**

- Used by DIFs (via LDA) signal to “stop acquisition” when needed.
 - Due to AC coupling the busy must asserted by constantly toggling this line.

Clock: Timing Overview

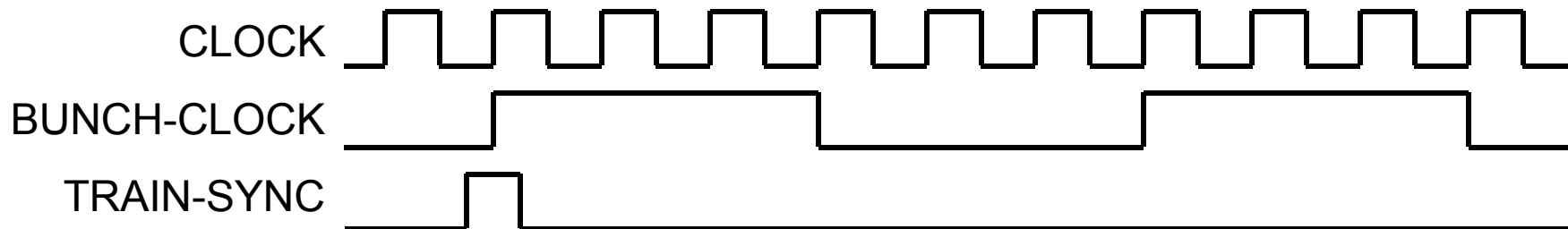- Presume machine CLOCK period $<$ bunch-period
 - Expected to be 50-100MHz, local or machine.
 - Common fanned-out to the detector
- BUNCH-CLOCK (slow clock) derived as $CLOCK/n$
 - Re-produced locally on DIF (with TRAINSYNC & counter)
- Start of train signal (TRAINSYNC) synchronises bunch-clocks on all DIFs.
 - Requires fixed-latency signal – a SYNC CMD.
 - TRAINSYNC “qualifies” CLOCK edge





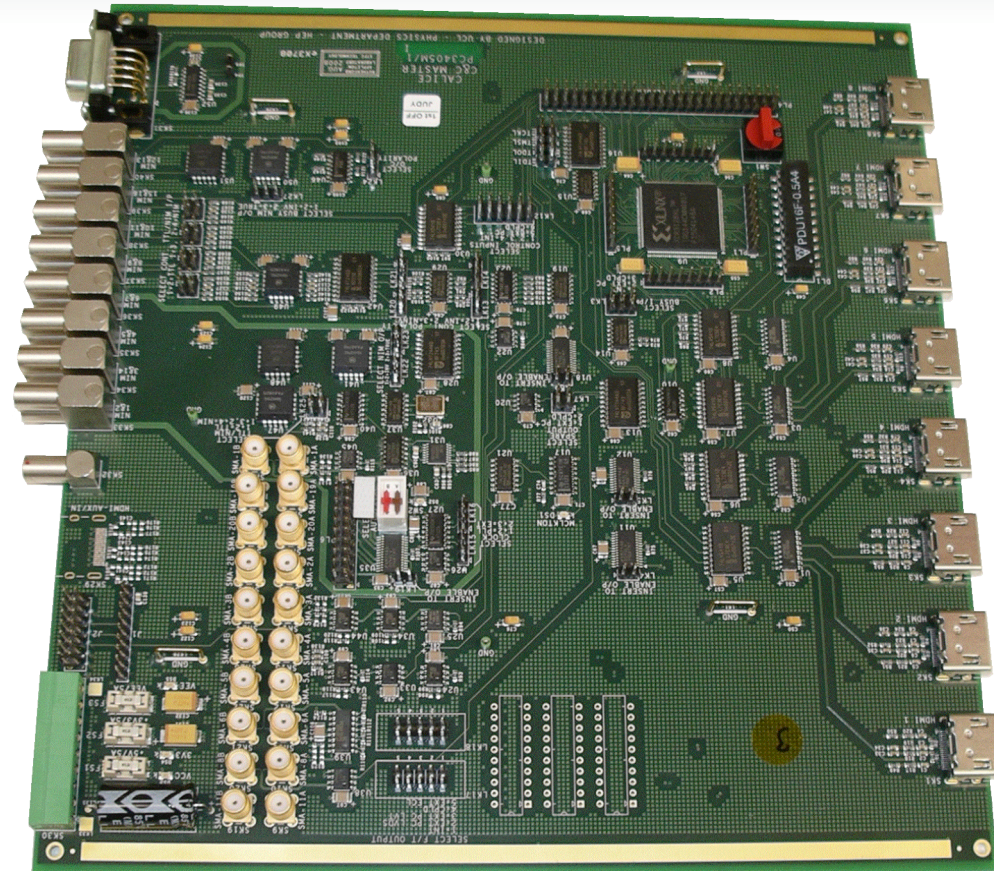

- Schematic **DONE**
- Layout **DONE**
- Manufacture **DONE**
 - Testing to be started
 - Run of 2 with 8 more when satisfied working
- Firmware development: **TO BE STARTED**

DIF -LDA link testing

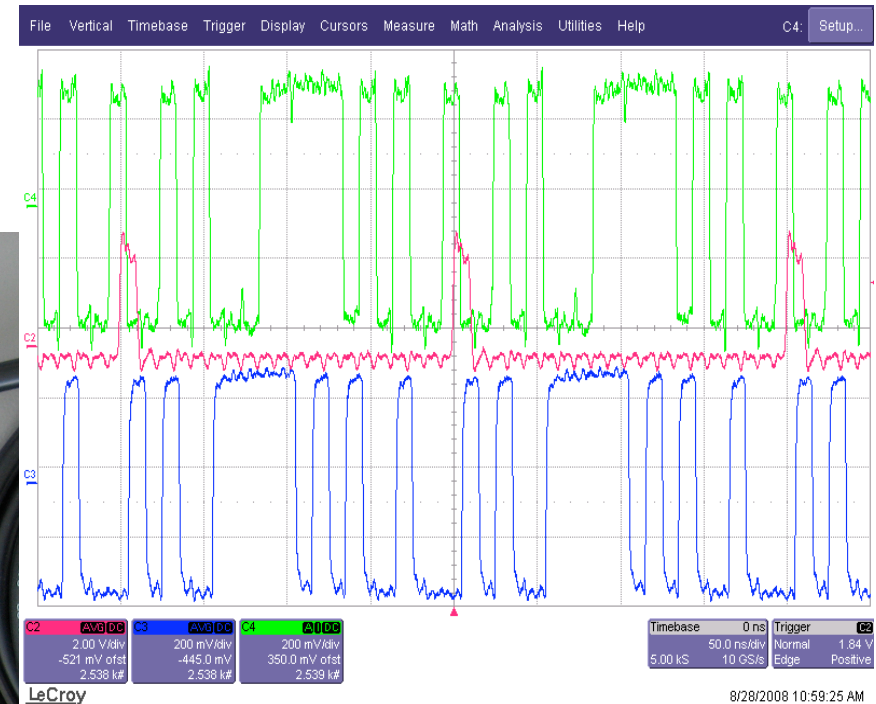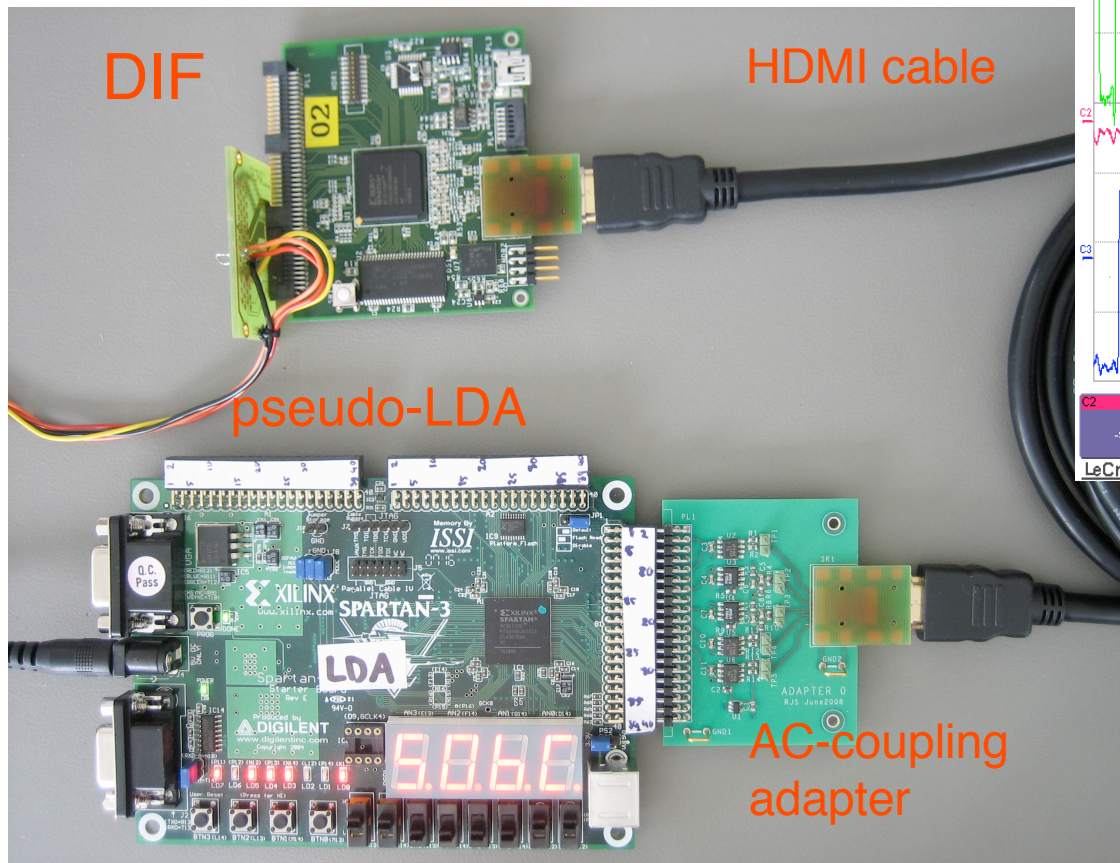- Link shows signs of life.
 - pseudo-LDA sends CLK & 8B/10B data @ 100MHz over AC-coupled LVDS on HDMI cables



data loop-back in firmware
stable


DIF: Status (generic) and Plans

e.g: ECAL DIF

- Test hardware: **DONE**
- Firmware development: **STARTED**
 - LDA Link integration

ECAL DIF prototype: 65x72mm, 8 layers

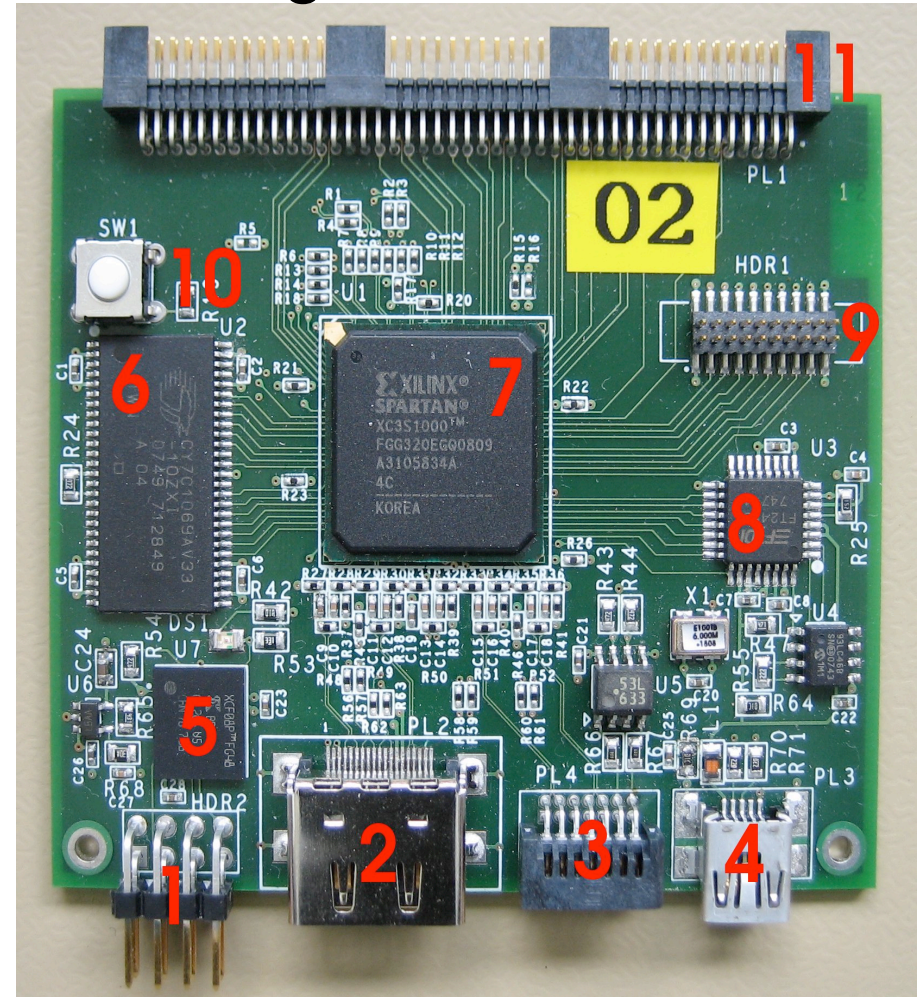
1. JTAG programming header
2. LDA link HDMI connector
3. DIF link connector
4. mini-USB connector
5. Xilinx PROM
6. Cypress 2MB 10ns SRAM
7. Xilinx Spartan3-1000 FPGA
8. FDTI FT245R USB controller
9. 20p user header connector
10. reset pushbutton
11. 90pin SAMTEC IB connector



- 2 DIFs produced, parts available for 10 more.
- DIF hardware is (at least partly) functional


LDA-ODR Connectivity

- Prototype LDA has hardware problems
 - Mainly incorrect signals routed on PCB to Eth add-on
 - LDA has been modified to attempt fix (see pic!)
 - Ethernet RX OK, auto-negotiation starts OK. BUT ..
- Ethernet TX appears corrupt
- random glitches and/or clock recovery problems
- PHY in loop-back OK, so looks like the SERDES
 - Investigating ...
- **SOME GOOD NEWS:**
ODR-LDA protocol almost finalised

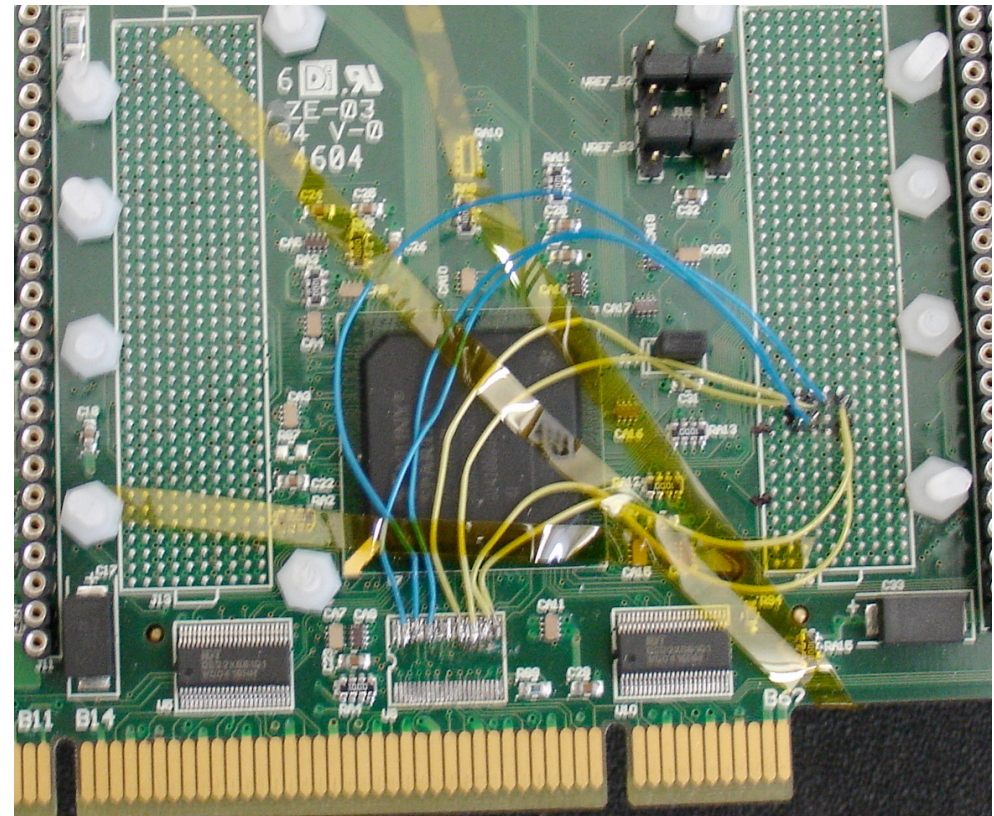

LDA-DIF Connectivity

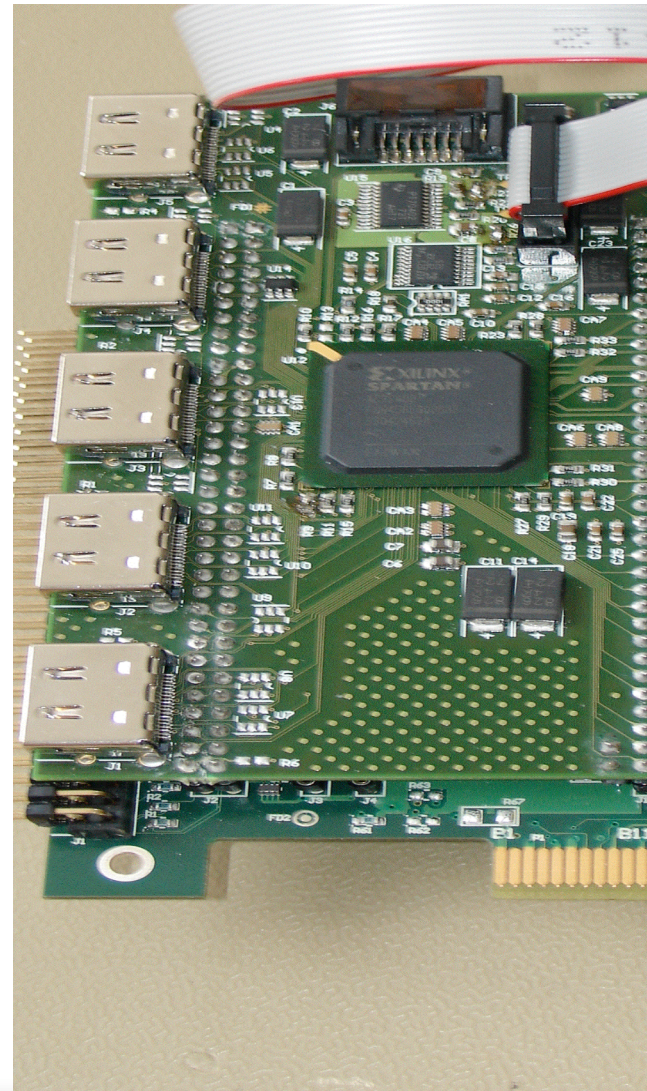
- Current boards have 8 working HDMI links
 - Option for 10 on future boards with simple change of FPGA
- FPGA is basically used as an LVDS transceiver and clock fanout, although it will probably also handle the separate prompt/fast signals to/from the DIF
- Link documentation is proceeding, large amounts have been already done



New LDA Base Board

- Enterpoint is designing a replacement board for the BroadDown2 known as the Mulldonoch2
 - Extra I/O capabilities
 - EBX format board
 - PCI connector is replaced by a PC104 connector
 - SDRAM onboard
 - SPI flash ram
 - Better power system
- **Prototype production is expected sometime this month.**
- Is not designed for us especially, but rather is a generic board Enterpoint had planned already. Design time table got shifted when we found the error in the existing BD2 design
- A corrected BroadDown2 design is also going to be available in roughly the same time frame

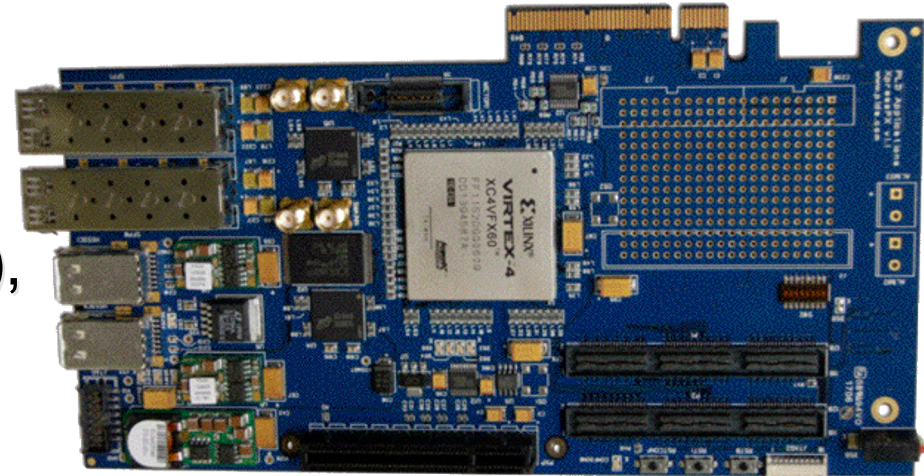- ODR: **WORKING**
 - Receive data on 4x fibre (RX),
 - Write to disk FAST (250MB)
 - Send data up fibre (TX)
 - Controlled from Linux driver
- Future upgrade: Decode event header from LDA
 - Provides on-line info
 - Can deal with control messages from LDA
 - Allows host to write to disk without processing




ODR: Rate performance optimization

(from ODR to disk)

Several factors to optimize:

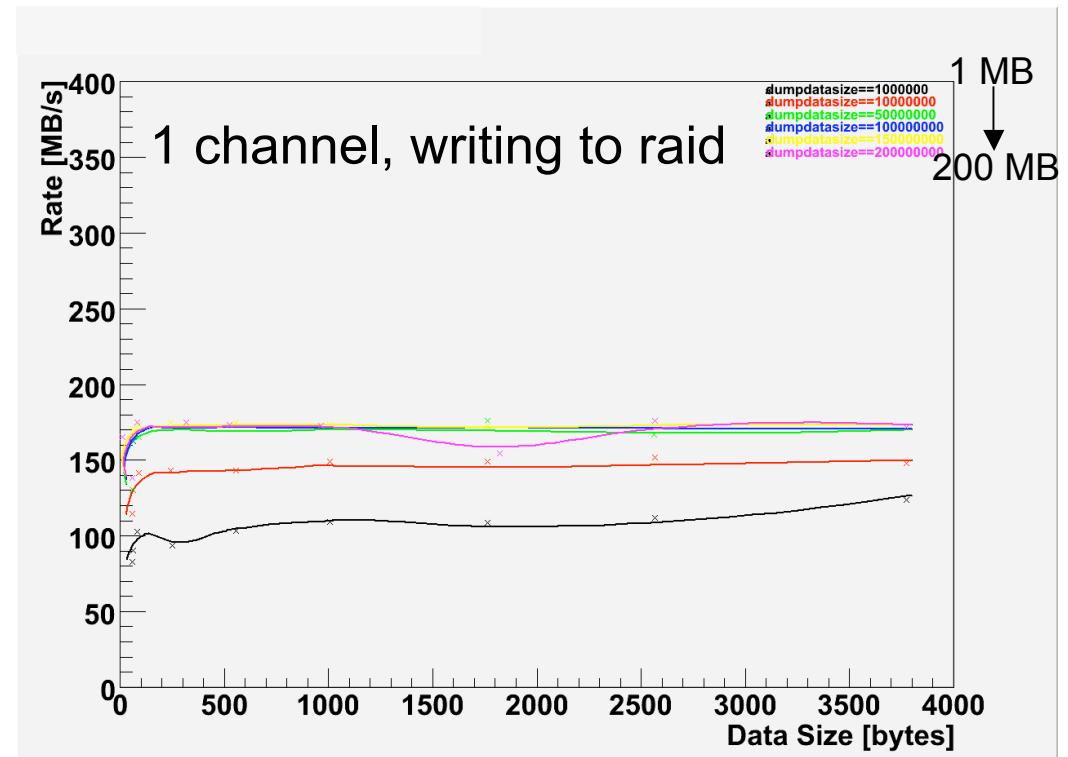- Architecture of the host (hyper-threading, raid array disks, kernel version, etc)
- Number of DMA buffers
 - currently using 950
- Number of buffers to fill before dumping the data to disk
 - best to have about N DMA buffers - 200 (so 750 for 950 DMA buffers)
- **Size of files to write** (grouping of data files)
 - Called dumpdatasize on plot
 - Dominant factor
 - chose 100 MB



DAQ status

- Overall status: all components exist, firmware needs to be developed
- LDA needs a respin, new board to arrive Mid-October (holds up integration of all other components to a testbench)
- CCC board has been delivered and will be tested soon

